



# **ANALOG ELECTRONICS**


**PREPARED BY**

**RAMYA K**

# BJT FREQUENCY ANALYSIS

- **Frequency response of RC Coupled amplifier:**
- Fig. (1) shows the frequency response of RC coupled amplifier. The horizontal scale is a logarithmic scale to permit a plot extending from low to high frequency regions. The frequency range is divided into 3 regions.
- (i) Low frequency region.
- (ii) Mid frequency region.
- (iii) High frequency region.
- The drop in the gain at low frequencies

○ FIG 1

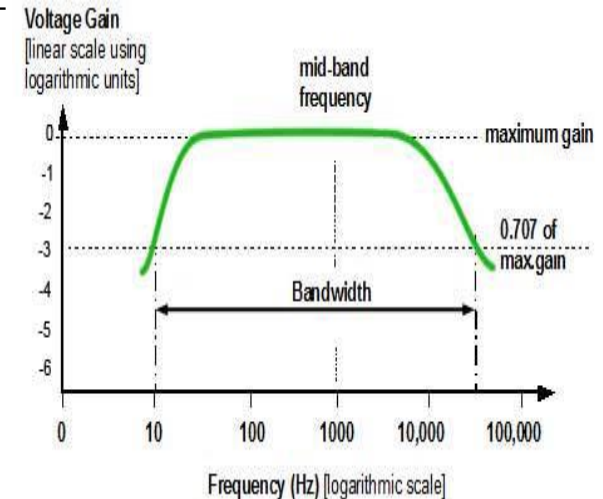



- **Frequency response of transformer coupled amplifier:**

- Fig.(2) shows frequency response of transformer coupled amplifier. The magnetizing inductive reactance of the transformer winding is  $X_L = 2\pi fL$ . At low frequencies the gain drops due to small value of  $X_L$ .

- At  $f=0$  (DC) there is no change in flux in the core. As a result the secondary induced voltage or output voltage is zero and hence the gain. At high frequencies the gain drops due to stray capacitance between the turns of primary and secondary windings.



### ○ FIG 3

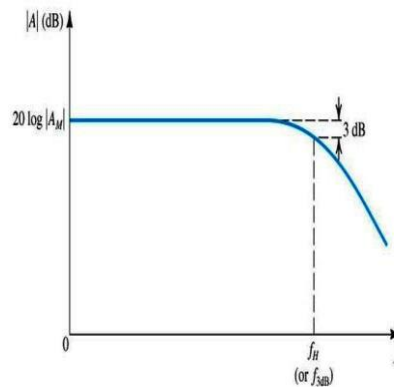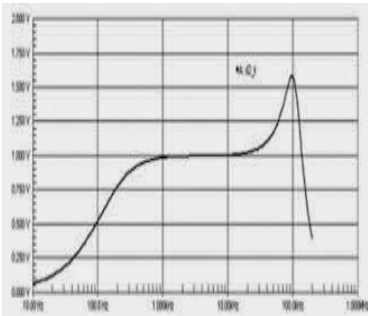

- **Frequency response of direct coupled amplifier:**
- Fig. (3) shows frequency response of direct coupled amplifier. Since there are no coupling or bypass capacitors, there is no drop in gain at low frequencies. It has a flat response to the upper cut-off frequency. Gain drops at high frequencies due to device internal capacitances and the stray wiring capacitance



- **Half power frequencies and bandwidth:**
- The frequencies  $f_1$  and  $f_2$  at which the gain is  $0.707 A_{v\text{mid}}$  are called cut-off frequencies or corner frequencies or break frequencies.  $f_1$  is called the lower cut-off frequency and  $f_2$  is called the upper cut-off frequency.
- Bandwidth or pass band of the amplifier is



- $BW = f_2 - f_1$  ----- (1)
- The output voltage in the mid band is  $|V_O| = |A_{v_{mid}}| |V_i|$
- Output power in the mid band is

$$P_{O(\text{mid})} = \frac{|V_O|^2}{R_O}$$
$$= \frac{|A_{v_{mid}}|^2 |V_i|^2}{R_O} \text{ ----- (2)}$$



The output voltage at cut-off frequencies is

$$|V_O| = |0.707 A_{v_{mid}}| |V_i|$$

The output power at cut-off frequencies is

$$\begin{aligned} P_{O(\text{cut-off})} &= \frac{|0.707 A_{v_{mid}}|^2 |V_i|^2}{R_O} \\ &= \frac{0.5 |A_{v_{mid}}|^2 |V_i|^2}{R_O} \\ &= 0.5 P_{O(\text{mid})} \text{ ----- (3)} \end{aligned}$$



## NORMALIZED GAIN V/S FREQUENCY PLOT:

- The normalized gain is obtained by dividing the gain at each frequency by the mid band gain  $A_{v_{mid}}$ .
- Therefore normalized gain

$$= \frac{A_v}{A_{v_{mid}}} \text{ ----- (4)}$$





Fig. (4) shows the normalized gain V/s frequency plot for an RC coup

The normalized mid band gain is  $\frac{Av_{mid}}{Av_{mid}} = 1$

The normalized gain at cut-off frequencies is  $\frac{0.707Av_{mid}}{Av_{mid}} = 0.707$

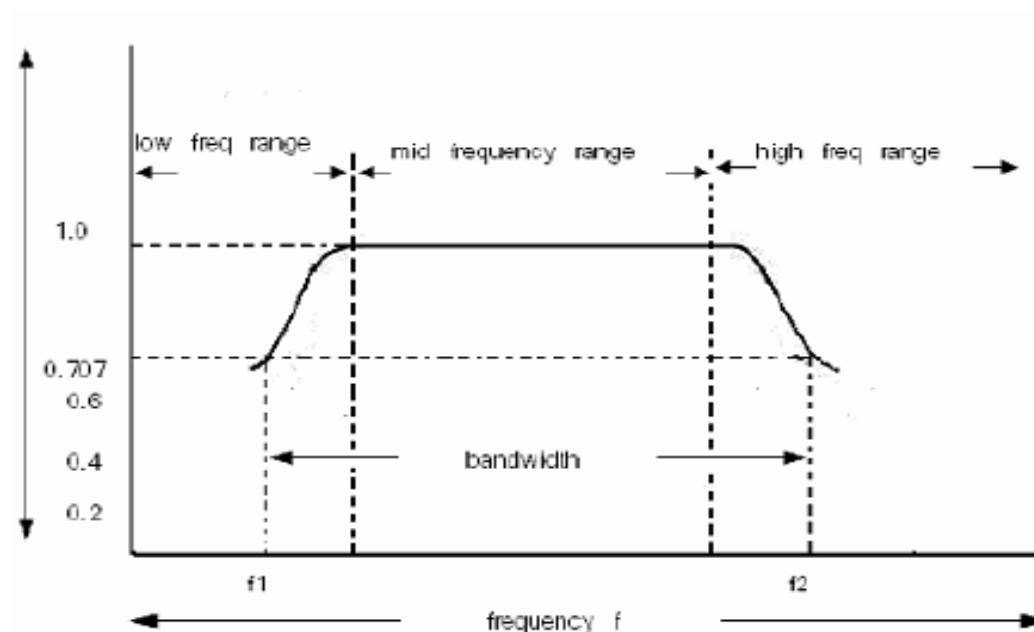


Fig. (4) Normalized gain V/s frequency plot

Normalized decibel gain is  $\frac{Av}{Av_{mid}} \Big|_{dB} = 20 \log_{10} \left[ \frac{Av}{Av_{mid}} \right]$  -----(5)



Normalized decibel voltage gain at cut-off frequencies is

$$20 \log_{10} \left[ \frac{0.707 A_v}{A_{v_{mid}}} \right] = -3 \text{ dB}$$

Since normalized decibel voltage gain at cut-off frequencies is 3dB less than the normalized decibel mid band voltage gain.  $f_1$  and  $f_2$  are also called corner frequencies.

$f_1 \rightarrow$  lower 3dB frequency

$f_2 \rightarrow$  upper 3dB frequency

Fig. (5) shows the plot of normalized dB voltage gain V/s frequency for a coupled amplifier.

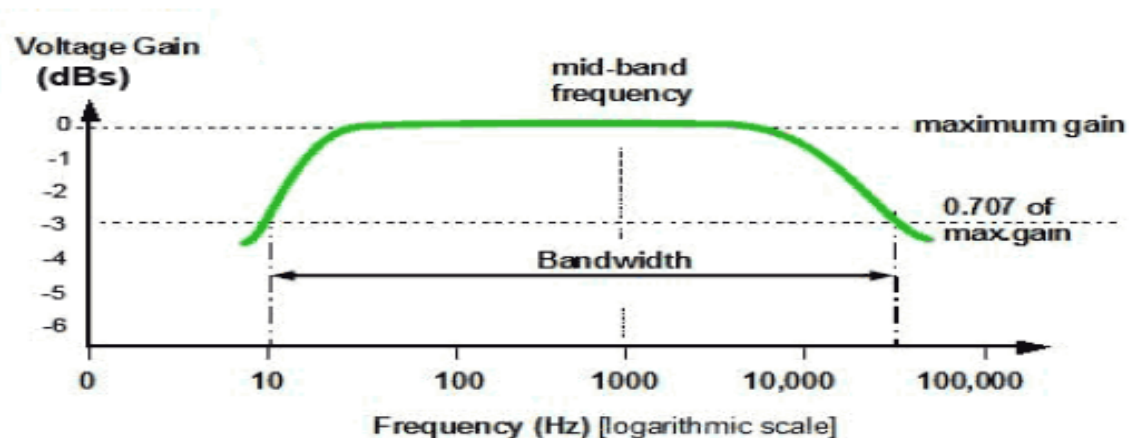


Fig. (5) Plot of normalized decibel voltage gain V/s frequency.



## Low frequency Response of BJT amplifier:

Fig. (13) shows the circuit of single stage BJT amplifier. The coupling capacitors  $C_S$  and  $C_C$  and bypass capacitor  $C_E$  determines the low frequency response.

### Effect of $C_S$ on low frequency response:

The input coupling capacitor  $C_S$  couples the source signal to BJT. First, we will neglect the effects of  $C_C$  and  $C_E$  i.e. they are treated as short circuits.

The AC equivalent circuit is obtained by reducing  $V_{CC}$  to zero and  $C_C$  and  $C_E$  by their short circuit equivalent as shown in Fig. (14).

- The resistance of the transistor between base-emitter is  $h_{ie}$


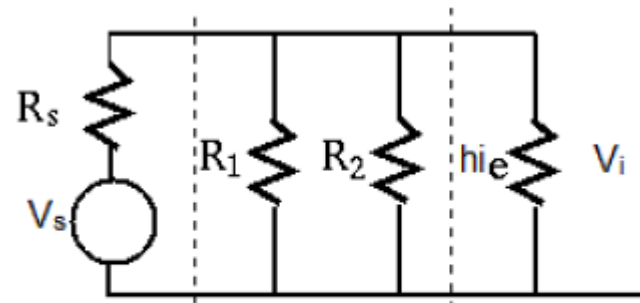


Fig. (15) Input AC equivalent

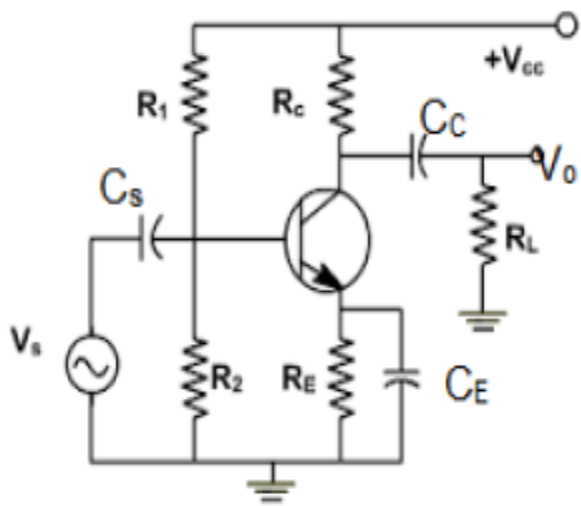

Let  $R_i = R_1 \parallel R_2 \parallel h_{ie}$

Where  $h_{ie} = \beta r_e$

Using voltage division rule in the circuit of the voltage applied to the amplifier is

$$V_i = \frac{V_S R_i}{(R_S + R_i) - f X_{C_S}}$$



Where  $X_{C_S} = \frac{1}{2\pi f C_S}$

$$V_i = \frac{V_S \left[ \frac{R_i}{R_S + R_i} \right]}{1 - j \left[ \frac{X_{C_S}}{R_i + R_S} \right]}$$

$$V_i = \frac{|V_S| \left[ \frac{R_i}{R_S + R_i} \right]}{\sqrt{1 + j \left[ \frac{X_{C_S}}{R_i + R_S} \right]^2}} \dots$$



- In the mid frequency band,  $f$  is large. As a result

$$, X_{C_S} \rightarrow 0.$$

$$|V_i|_{\text{mid}} = \frac{|V_S|R_i}{(R_S+R_i)}$$

$$|V_i| = \frac{|V_i|_{\text{mid}}}{\sqrt{1 + \left[ \frac{X_{C_S}}{R_i + R_S} \right]^2}}$$

The lower 3dB cut-off occurs when  $|V_i| = \frac{|V_i|_{\text{mid}}}{\sqrt{2}} = 0.707 |V_i|_{\text{mid}}$



$$0.707 |V_i|_{\text{mid}} = \frac{|V_i|_{\text{mid}}}{\sqrt{1 + \left[ \frac{X_{C_S}}{R_i + R_S} \right]^2}}$$

This condition is satisfied

$$\text{if } \frac{X_{C_S}}{R_i + R_S} = 1 \text{ or } X_{C_S} = R_i + R_S$$

$$\frac{1}{2\pi f C_S} = R_i + R_S$$


$$\text{Therefore } f = \frac{1}{2\pi(R_S + R_i)C_S}$$





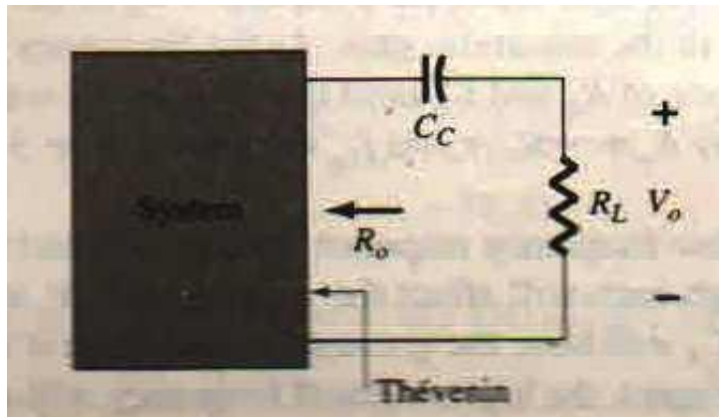- $f_{Ls} = \frac{1}{2\pi(R_S + R_i)C_S}$  coupling capacitor CC on low frequency response :
- The output coupling capacitor CC couples the output of the BJT to the load. The equivalent circuit on the output side by neglecting the effect of CS and CE by treating them as short circuits is as shown in Figure






Let  $R_o = r_o \parallel R_C$

$V_C$  = output voltage of BJT

$V_o$  = load voltage

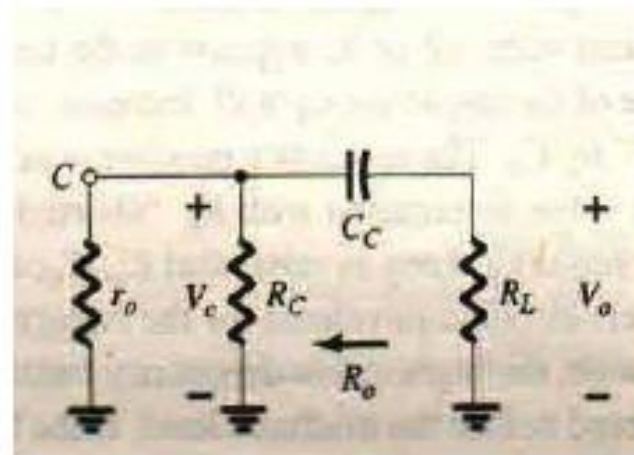

$$V_O = \frac{V_C R_L}{(R_O + R_L) - jX_{CC}}$$

$$\text{Where } X_{CC} = \frac{1}{2\pi f C_C}$$

$$V_O = \frac{V_C \left[ \frac{R_L}{R_O + R_L} \right]}{1 - j \left[ \frac{X_{CC}}{R_O + R_L} \right]}$$

$$|V_O| = \frac{|V_C| \left[ \frac{R_L}{R_O + R_L} \right]}{\sqrt{1 + \left[ \frac{X_{CC}}{R_O + R_L} \right]^2}}$$

In the mid frequency band,  $X_{CC} \rightarrow 0$



Therefore  $|V_O|_{\text{mid}} = \frac{|V_C|R_L}{(R_O+R_L)}$

$$|V_O| = \frac{|V_O|_{\text{mid}}}{\sqrt{1 + \left[ \frac{X_{CC}}{R_O+R_L} \right]^2}}$$

The lower 3dB cut-off occurs when  $|V_O| = \frac{|V_O|_{\text{mid}}}{\sqrt{2}} = 0.707 |V_O|_{\text{mid}}$

This is possible iff,


$$\frac{X_{CC}}{R_O+R_L} = 1 \text{ or } X_{CC} = R_O + R_L$$




$$f = \frac{1}{2\pi(R_O + R_L)C_C}$$

$$f_{LC} = \frac{1}{2\pi(R_O + R_L)C_C}$$

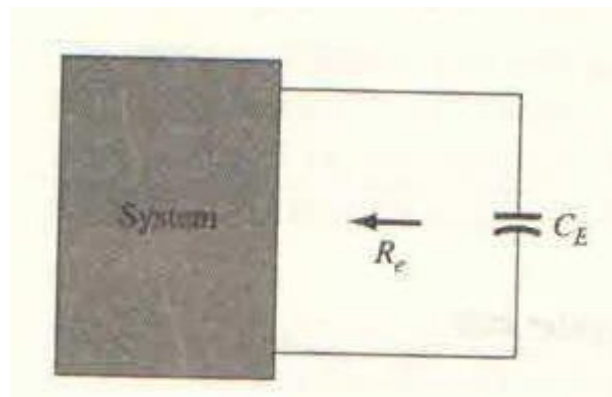**Effect of Emitter bypass capacitor CE on low frequency response :** The equivalent circuit considering the effect of CE is as shown in Fig. Hence the effect of CS and CC are neglected.



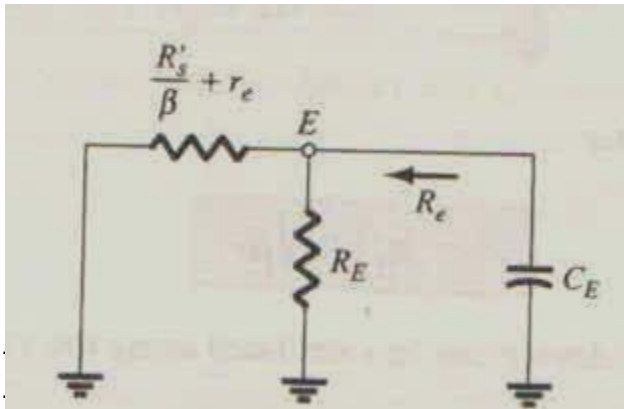- AC equivalent circuit using hybrid model



- To find the equivalent resistance seen by  $C_E$ . To find  $R_e$ ,  $V_S$  is reduced to 0.



- Let  $Z' = R_S \parallel R_1 \parallel R_2$  .

$\hat{R}_S = \beta r_e$  is in base circuit. When it is transformed to emitter circuit, it is divided by  $\beta$ . Therefore  $I_E \approx I_C = \beta I_B$ .

$$R_e = R_E \parallel \frac{\hat{R}_S}{\beta} + r_e$$

$$f_{L_E} = \frac{1}{2\pi R_e C_E}$$



### Effect of $C_E$ on voltage gain:

The mid band voltage gain of amplifier of Fig. (13) without  $C_E$  is given by,

$$A_{V_{mid}} = -\frac{R_O || R_L}{r_e + R_E} \text{ ----- (38)}$$

Where  $R_O = R_C || r_o$

If  $C_E$  is connected in parallel with  $R_E$ , then voltage gain becomes a function of frequency. The voltage gain at any frequency is





$$A_V = -\frac{R_O \parallel R_L}{r_e + R_E \parallel X_{C_E}} \text{ ----- (39)}$$

$$\text{Where } X_{C_E} = \frac{1}{2\pi f C_E} \text{ ----- (40)}$$

As the frequency increases:

- (i)  $X_{C_E}$  decreases.
- (ii)  $R_E \parallel X_{C_E}$  decreases.
- (iii)  $A_V$  increases in magnitude.


As the frequency approaches the mid band value

- (i)  $X_{C_E}$  approaches zero.
- (ii)  $R_E \parallel X_{C_E}$  approaches zero. (i.e.  $R_E$  is shorted out)
- (iii)  $A_V$  approaches maximum value or mid band value.

$$A_{V_{mid}} = -\frac{R_O \parallel R_L}{r_e} \text{ ----- (41)}$$

## Miller Effect Capacitance:

Fig. (19) shows an inverting amplifier with a capacitance  $C_f$  between the input and output nodes. WKT,  $A_V$  is  $-Ve$  for inverting amplifier since  $V_O$  and  $V_i$  are  $180^\circ$  out of phase. Using Millers theorem we can find the loading effect of  $C_f$  on the input and output circuits of the amplifier.

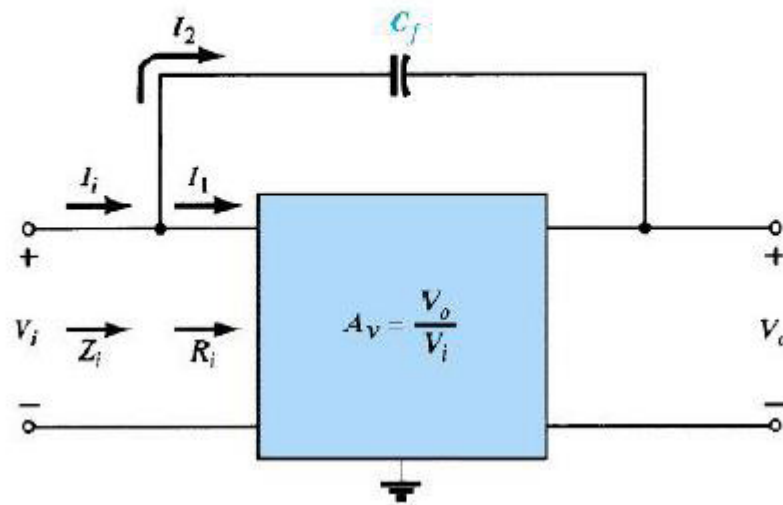

## To find Miller-Input Capacitance ( $C_{mi}$ ) :

From Fig. (19),

$$R_i = \frac{V_i}{I_1} \rightarrow I_1 = \frac{V_i}{R_i}$$

$$Z_i = \frac{V_i}{I_i} \rightarrow I_i = \frac{V_i}{Z_i}$$

Apply KCL at input node A,

$$I_i = I_1 + I_2 \text{ ----- (42)}$$

From Fig. (23),

$$I_2 = \frac{V_i - V_o}{X_{C_f}}$$

But  $V_o = A_V V_i$

$$\text{Therefore } I_2 = \frac{V_i - A_V V_i}{X_{C_f}} = \frac{V_i [1 - A_V]}{X_{C_f}}$$

Substitute for  $I_i$ ,  $I_1$  and  $I_2$  in Eq. (42), we get

$$\frac{V_i}{Z_i} = \frac{V_i}{R_i} + \frac{V_i[1-A_V]}{X_{C_f}}$$

Eliminating  $V_i$  through,

$$\frac{1}{Z_i} = \frac{1}{R_i} + \frac{[1-A_V]}{X_{C_f}} = \frac{1}{R_i} + \frac{1}{\frac{X_{C_f}}{1-A_V}}$$

$$\text{Let } X_{C_{mi}} = \frac{X_{C_f}}{1-A_V} \text{ ----- (43)}$$

$$\frac{1}{Z_i} = \frac{1}{R_i} + \frac{1}{X_{C_{mi}}} \text{ ----- (44)}$$

$$\text{But } X_{C_f} = \frac{1}{2\pi f C_f}$$

$$X_{C_{mi}} = \frac{1}{[1-A_V]2\pi f C_f} \text{ ----- (45)}$$



Where  $C_{mi} = [1 - A_V]C_f =$  miller input capacitance

**To find Miller output capacitance ( $C_{mo}$ ) :**

From Fig. (19),

$$R_O = \frac{V_o}{V_i} \rightarrow I_1 = \frac{V_o}{R_O}$$

$$Z_O = \frac{V_o}{I_o} \rightarrow I_o = \frac{V_o}{Z_O}$$

Apply KCL at node B,

$$I_o = I_1 + I_2 \text{ ----- (47)}$$



### Statement of Millar's theorem:

A capacitance  $C_f$  connected between the input and output nodes of an inverting amplifier can be replaced by

- (i) Miller input capacitance,  $C_{m_i} = [1 - A_V]C_f$  connected between input node and ground.
- (ii) Miller output capacitance,  $C_{m_o} = \left[1 - \frac{1}{A_V}\right]C_f$  connected between output node and ground.

For an non-inverting amplifier  $A_V$  is positive. In order to obtain positive values for  $C_{m_i}$  and  $C_{m_o}$ . Eq. (46) and Eq. (49) should be modified as follows


$$C_{m_i} = [1 + A_V]C_f \text{ ----- (50)}$$

$$C_{m_o} = \left[1 + \frac{1}{A_V}\right]C_f \text{ ----- (51)}$$





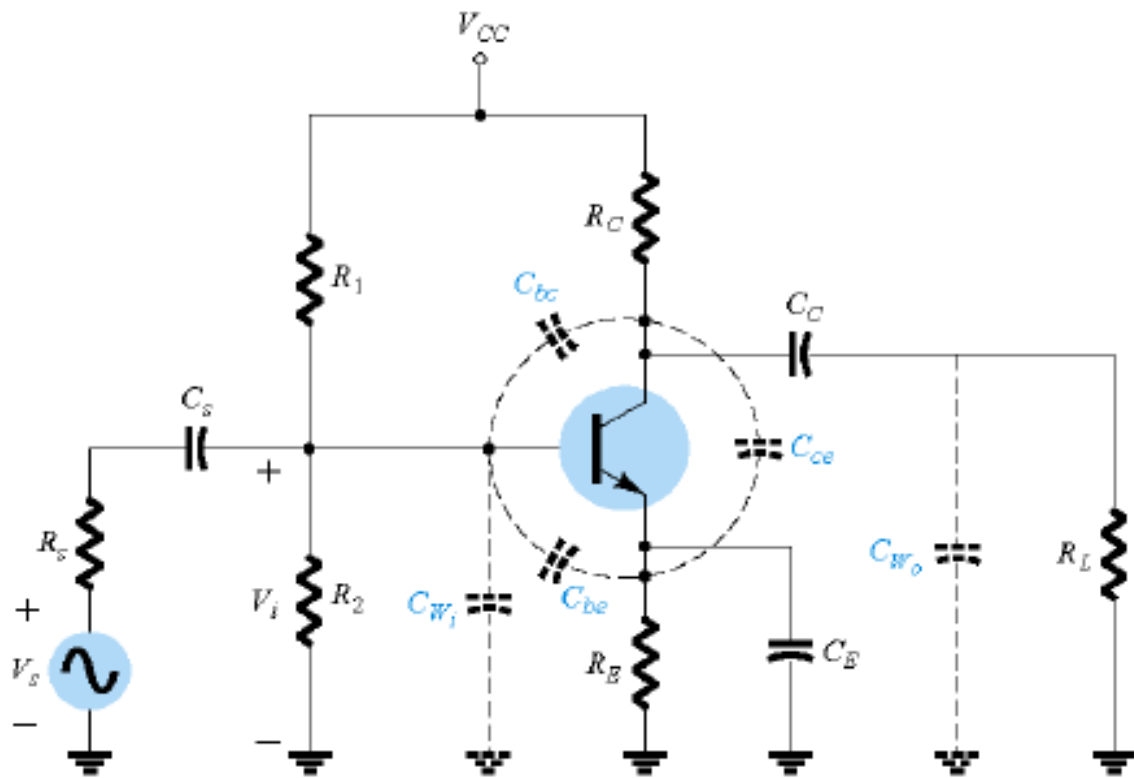- **High Frequency Response of BJT amplifier:**
- In the high frequency response of BJT amplifier, the upper 3dB cut-off point is defined by the following factors.
- (i) The network capacitance which includes the parasitic capacitances of the transistor and the wiring capacitances.
- (ii) The frequency dependence of short circuit current gain








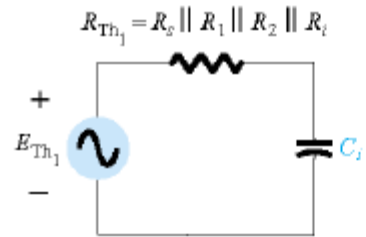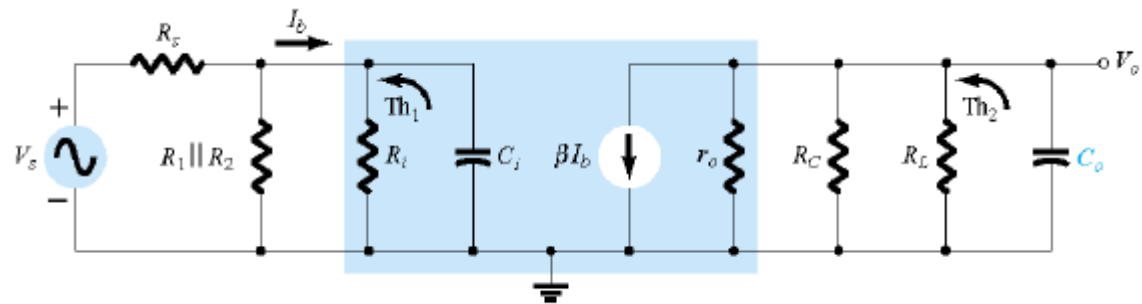

(a)

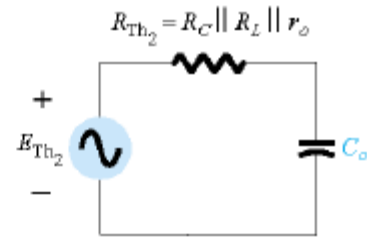

(b)



Using Miller's theorem, the transit capacitance,  $C_{bc}$  can be replaced by two capacitances;  $C_{mi}$  at the input and  $C_{mo}$  at output.

The total capacitance  $C_i$  is the sum of  $C_{mi}$ ,  $C_{be}$  and  $C_{wi}$ .

$$\text{i.e. } C_i = C_{mi} + C_{be} + C_{wi} \text{ ----- (52)}$$

$$\text{where } C_{mi} = [1 - A_V] C_{bc} \text{ ----- (53)}$$

The total output capacitance is the sum of  $C_{mo}$ ,  $C_{ce}$  and  $C_{wo}$ .

$$\text{i.e. } C_o = C_{wo} + C_{ce} + C_{mo} \text{ ----- (54)}$$

$$\text{where } C_{mo} = \left[ 1 + \frac{1}{A_V} \right] C_f$$



### Upper cut-off frequency due to $C_i$ :

Apply voltage division rule to circuit of Fig. (22),

$$E_{Thi} = V_s \left[ \frac{R_1 \parallel R_2 \parallel \hat{R}_i}{R_S + R_1 \parallel R_2 \parallel \hat{R}_i} \right] \text{----- (56)}$$

From circuit in Fig. (21);

$$R_{Thi} = R_S + R_1 \parallel R_2 \parallel \hat{R}_i \text{----- (57)}$$

Where  $\hat{R}_i = \beta r_e$

From Fig. (29) (b), Apply  $V_g$  division rule,

$$|V_i| = |E_{Thi}| \left[ \frac{X_{Ci}}{\sqrt{(R_{Thi})^2 + (X_{Ci})^2}} \right]$$
$$|V_i| = |E_{Thi}| \frac{|E_{Thi}|}{\sqrt{1 + \left(\frac{R_{Thi}}{X_{Ci}}\right)^2}} \text{----- (58)}$$

$$\text{Where } X_{Ci} = \frac{1}{2\pi f C_i} \text{----- (59)}$$

In the mid band, the effect of  $C_i$  is negligible. As a result,  $X_{Ci}$  can be treated as open circuit i.e.  $X_{Ci} = \infty$ .

Therefore  $|V_i|_{\text{mid}} \approx |E_{Thi}|$

At high frequencies,  $C_i$  cannot be neglected with increase in  $f$ ,  $X_{Ci}$  decreases,  $\frac{R_{Thi}}{X_{Ci}}$  increases,  $|V_i|$  decreases and hence the voltage gain decreases.

3dB cut-off occurs at a frequency at which

$$|V_i| = \frac{|V_i|_{\text{mid}}}{\sqrt{2}} = \frac{|E_{Thi}|}{\sqrt{2}}$$

From (58), this condition occurs, when

$$R_{Thi} = X_{Ci}$$

$$R_{Thi} = \frac{1}{2\pi f C_i}$$

$$\text{Or } f = f_{Hi} = \frac{1}{2\pi R_{Thi} C_i}$$

$$= \left[ \frac{f}{f_{Hi}} \right]$$

Therefore Eq. (58) becomes,

$$|V_i| = \frac{|E_{Thi}|}{\sqrt{1 + \left(\frac{f}{f_{Hi}}\right)^2}} \text{ ----- (62)}$$

Thus, due to  $C_i$ ,  $V_g$  gain decreases at the rate of 20dB/decade.

### Upper cut-off frequency due to output capacitance $C_o$ :

Consider the output circuit of Fig.(22) which is shown in Fig. (23).

$\beta I_b$ ,  $r_o$  and  $R_C || R_L$  is connected to voltage source as shown in Fig. (22).

$$R_{Tho} = r_o || R_C || R_L \text{ ----- (63)}$$

$$E_{Tho} = [-\beta I_b] [r_o || R_C || R_L] \text{ ----- (64)}$$

Using the same procedure as listed above, we have

$$|V_o| = \frac{|E_{Tho}|}{\sqrt{1 + \left(\frac{R_{Tho}}{X_{Co}}\right)^2}} \text{ ----- (65)}$$

$$\text{Where } X_{Co} = \frac{1}{2\pi f C_o} \text{ ----- (66)}$$



### Combined effect of $C_i$ and $C_o$ on high frequency response:

- (i) The input capacitance  $C_i$ , defines upper cut-off frequency  $f_{Hi}$ .
- (ii) The output capacitance  $C_o$ , defines another upper cut-off frequency  $f_{Ho}$ .
- (iii) The lowest of these 2 frequencies will be taken as overall upper cut-off frequency.
- (iv) If the variation of  $h_{fe}$  with frequency is considered then the actual cut-off frequency may be lower than  $f_{Hi}$  or  $f_{Ho}$ .

