

**Third Semester B.E. Degree Examination, June/July 2018**  
**Analog Electronics Circuits**

Time: 3 hrs.

Max. Marks: 100

*Note: Answer FIVE full questions, selecting atleast TWO questions from each part.*

**PART - A**

- 1 a. Assuming an ideal diode, sketch  $v_i$ ,  $v_d$  and  $i_d$  for half-wave rectifier of Fig.1(a). The input is a sinusoid with frequency 50 Hz. (08 Marks)

 


Fig.Q1(a)

- b. Determine  $v_o$  for the network shown in Fig.Q1(b). (06 Marks)

 


Fig.Q1(b)

- c. Sketch  $v_o$  for the network shown in Fig.Q1(c). (06 Marks)

 


Fig.Q1(c)

- 2 a. Using exact analysis, obtain the Q-point values for the voltage-divider bias circuit. (08 Marks)
- b. Obtain the expression for  $S(I_{CQ})$  for an emitter-bias circuit and determine its value for the circuit with  $R_B = 470 \text{ k}\Omega$ ,  $R_E = 2.2 \text{ k}\Omega$ ,  $R_C = 3.3 \text{ k}\Omega$ ,  $V_{CC} = 12 \text{ V}$  and  $\beta = 100$ . (06 Marks)
- c. For the circuit shown in Fig.Q2(c), determine the values for  $R_1$  and  $R_C$ . (06 Marks)

 


Fig.Q2(c)

- 3 a. Derive the equations for  $Z_i$ ,  $Z_o$  and  $A_V$  for fully bypassed common emitter RC-coupled amplifier. (08 Marks)
- b. Compare  $Z_i$ ,  $Z_o$  and  $A_V$  of a RC coupled amplifier with emitter follower and explain why emitter follower is called as impedance matching network. (06 Marks)
- c. For the circuit shown in Fig.Q3(c), find  $Z_i$ ,  $Z_o$  and  $A_V$ . (06 Marks)

 


Fig.Q3(c)

- 4 a. Draw the frequency response of RC coupled amplifier and explain high-pass action at low frequencies and low-pass action at high frequencies with relevant equations and Bode plots. (08 Marks)
- b. Draw the high frequency equivalent circuit for RC coupled amplifier and obtain expressions for  $f_{HI}$  and  $f_{HO}$ . (06 Marks)
- c. Determine  $f_{CS}$  and  $f_{CC}$  for circuit with,  
 $C_S = 10\mu F$ ,  $C_E = 20\mu F$ ,  $C_C = 1\mu F$ ,  $R_S = 1k\Omega$ ,  $R_1 = 40k\Omega$ ,  $R_2 = 10k\Omega$ ,  $R_E = 2k\Omega$ ,  
 $R_C = 4k\Omega$ ,  $R_L = 2.2k\Omega$ ,  $\beta = 100$ ,  $r_o = \infty$ ,  $V_{CC} = 20V$ . (06 Marks)

**PART - B**

- 5 a. Explain the advantages of employing negative feedback in an amplifier. (06 Marks)
- b. Derive an equation for  $Z_i$  and  $A_V$  for a Darlington emitter follower. (08 Marks)
- c. For cascaded stages shown in Fig.Q5(c), determine :  
 i) Loaded gain for each stage  
 ii) Total gain for the system  $A_V$  and  $A_{VS}$ . (06 Marks)

 


Fig.Q5(c)

- 6 a. Derive the expression for maximum percentage efficiency for a seriesfed class-A power amplifier. (08 Marks)
- b. Calculate the second harmonic distortion for an output waveform with  $V_{CEQ} = 10V$ ,  $V_{CE_{min}} = 1V$ ,  $V_{CE_{max}} = 18V$ . (06 Marks)
- c. Draw the circuit of a class-B push-pull amplifier and explain the working. Explain why cross-over distortion occurs in class-B and how it is overcome. (06 Marks)
- 7 a. With a neat circuit diagram, explain the principle of operation of RC phase-shift oscillator with necessary equations. (08 Marks)
- b. Explain the working of transistor crystal oscillator in series resonant mode. (06 Marks)
- c. Design a Weinbridge oscillator for a frequency of 4KHz. (06 Marks)
- 8 a. Derive equations for  $Z_i$ ,  $Z_o$  and  $A_v$  for JFET fixed bias configuration, with source resistor bypassed. (08 Marks)
- b. For JFET amplifier shown in Fig.Q8(b), find  $Z_i$ ,  $Z_o$  and  $A_v$  (08 Marks)

 


Fig.Q8(b)

- c. Explain the graphical determination of  $g_m$ . (04 Marks)

**Third Semester B.E. Degree Examination, June/July 2019**  
**Analog Electronic Circuits**

Time: 3 hrs.

Max. Marks: 100

*Note: Answer any FIVE full questions, choosing ONE full question from each module.*

**Module-1**

- 1 a. With a neat circuit diagram, explain Emitter stabilized bias circuit, write the necessary equation. (08 Marks)
- b. Determine output voltage for the following circuit in Fig.Q.(b). Assume  $f = 1000\text{Hz}$  and ideal diode. (06 Marks)

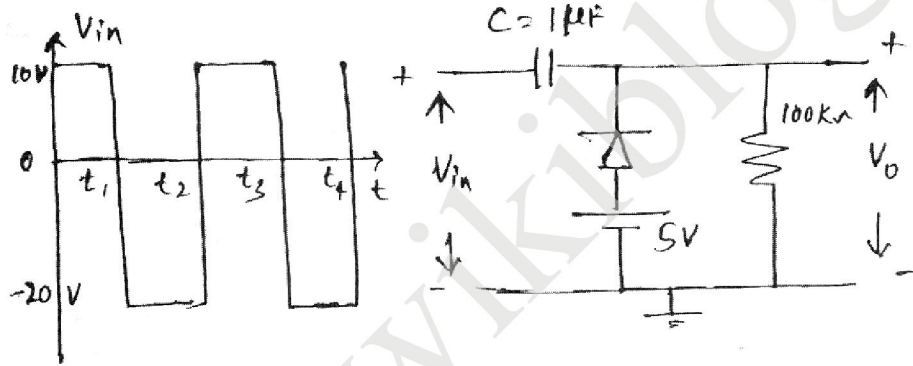


Fig.Q.1(b)

- c. Derive the expression for stability factors of fixed bias circuit with respect to  $I_{CO}$ ,  $V_{BE}$ ,  $\beta$  and draw the circuit diagram. (06 Marks)
- OR**
- 2 a. Explain the circuit of a transistor switch being used as an inverter. (06 Marks)
  - b. Determine the voltage  $V_{CE}$  and the current  $I_C$  for the voltage divider configuration Given:  $R_1 = 39\text{K}\Omega$ ,  $R_2 = 3.9\text{K}\Omega$ ,  $R_C = 10\text{K}\Omega$ ,  $R_E = 1.5\text{K}\Omega$ ,  $C_E = 50\mu\text{F}$ ,  $B = 100$ ,  $V_{BE} = 0.7$ . (08 Marks)
  - c. Sketch the output waveform for the network shown in Fig.Q.2(c). If the peak value of the a.c input is 15V and draw the transfer characteristics. (06 Marks)

 


Fig.Q.2(c)



**Module-2**

- 3 a. With a neat circuit diagram, derive an expression for  $Z_i$ ,  $Z_o$  and  $A_v$  of fixed bias circuit using  $r_c$  - model. (08 Marks)
- b. For the Emitter follower network shown in Fig.Q.3(b). Determine  $r_c$ ,  $Z_i$ ,  $Z_o$  and  $A_v$ . (06 Marks)

 


Fig.Q.3(b)

- c. Prove that Miller effect of input capacitance  $C_{Mi} = (1-A_v)C_f$  and output capacitance  $C_{Mo} = \left(1 - \frac{1}{A_v}\right)C_f$ . (06 Marks)

**OR**

- 4 a. For the following circuit determine  $Z_i$ ,  $Z_o$ ,  $A_v$ ,  $A_i$   $h_{fb} = -0.99$ ,  $h_{ib} = 14.3\Omega$ . (08 Marks)

 


Fig.Q.4(a)

- b. What are the advantages of h-parameters? (06 Marks)
- c. Define h-parameters and obtain h-parameter equivalent circuit of CE configuration. (06 Marks)

**Module-3**

- 5 a. Obtain expression for voltage gain, current gain, input and output impedance of a Darlington Emitter follower circuit. Draw necessary equivalent circuit. (12 Marks)
- b. With a neat block diagram, obtain expression for  $Z_{if}$  and  $Z_{of}$  for voltage series feedback amplifier. (08 Marks)

**OR**

- 6 a. Explain the general characteristics of negative feedback amplifier. (08 Marks)
- b. Explain the need of cascading amplifier. A given amplifier arrangement has the following gains.  $A_{v1} = 10$ ,  $A_{v2} = 20$  and  $A_{v3} = 40$ . Calculate overall voltage gain and total voltage gain in dB. (06 Marks)
- c. With a simple block diagram, explain the concept of feedback amplifier. (06 Marks)

**Module-4**

- 7 a. With a neat circuit diagram, explain the operation of a class B push pull power amplifier and maximum conversion efficiency is 78.5%. (08 Marks)
- b. With a neat circuit diagram, explain the operation of RC-phase shift oscillator using BJT and write  $f_{osc}$  equation. (06 Marks)
- c. A series fed class A amplifier as shown in Fig.Q.7(c). Operates from a DC source and applied sinusoidal input signal generates peak base current 9mA. Calculate  $I_{CQ}$ ,  $V_{CEQ}$ ,  $P_{dc}$ ,  $P_{ac}$  and efficiency. (06 Marks)

 


Fig.Q.7(c)

OR

- 8 a. The frequency selective circuit arms of wein bridge oscillator uses  $C_1 = C_2 = 0.001\mu F$ ,  $R_1 = 10K\Omega$  while  $R_2$  is kept variable. The frequency is to be varied from 10Hz to 50kHz by varying  $R_2$ . Find the range of  $R_2$ . (06 Marks)
- b. With a neat circuit diagram, explain the operation of a transformer coupled class A power amplifier and prove that conversion efficiency is 50%. (08 Marks)
- c. With a neat circuit diagram, explain the working principle of crystal oscillator in series resonant mode. (06 Marks)

**Module-5**

- 9 a. Explain the operation of JFET amplifier using fixed bias. Draw the JFET small signal model and derive the expression for  $Z_i$ ,  $Z_o$  and  $A_v$ . (06 Marks)
- b. Explain the construction, working and characteristics of n-channel enhancement type MOSFET. (08 Marks)
- c. Determine the following for network shown in Fig.Q.9(c)  $V_{GSQ}$ ,  $V_{DS}$ ,  $V_S$ ,  $V_G$ ,  $V_D$ . (06 Marks)

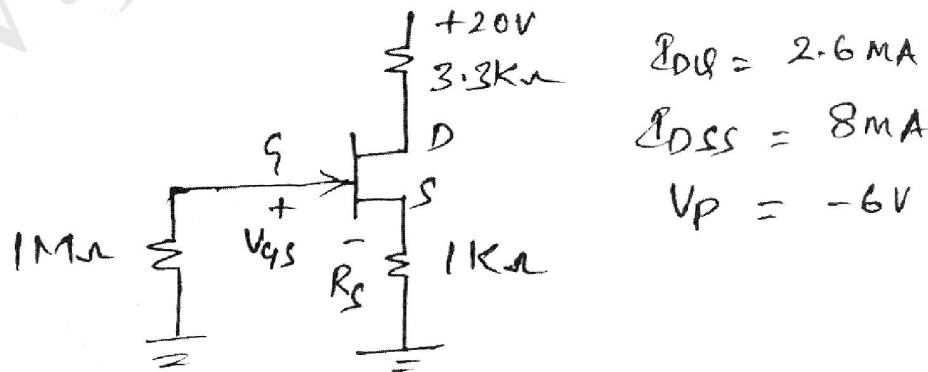


Fig.Q.9(c)

OR

- 10 a. Compare FET over BJT. (06 Marks)
- b. With neat diagrams, Explain the construction, working and characteristics of n-JFET's. (08 Marks)
- c. Design the fixed bias network as shown in Fig.Q.10(c) having an a.c. gain of 10. Determine the value of  $R_D$ . (06 Marks)

 


Fig.Q.10(c)

**Third Semester BE Degree Examination March 2021  
(CBCS Scheme)**

Time: 3 Hours

Max Marks: 100 marks

**Sub: Analog Electronics****Q P Code: 62302****Instructions:** 1. Answer **five full** questions.

2. Choose one full question from each module.

3. Your answer should be specific to the questions asked.

4. write the same question numbers as they appear in this question paper.

5. Write Legibly

**Module – 1**

- 1 a Compare the characteristics of CB,CC and CE configuration with necessary circuits and represent them in re model. 10 marks
- b What is transistor biasing? Explain the fixed bias circuit with relevant equations and circuit 10 marks

**Or**


- 2 a Derive an expression for  $A_v, Z_i, Z_o$  for emitter follower circuit using re model. 10 marks
- b Determine the values of  $R_1$  and  $R_c$  for voltage divider bias circuit with  $V_{cc}=20V, R_2=22 K\Omega, R_E=1 K\Omega$  and  $I_C=2.5mA$  10 marks

**Module – 2**

- 3 a Explain low frequency response of FET amplifier and derive an expression for cut off frequencies defined by input and output circuits. 10 marks
- b Determine the lower cut off frequency for the FET amplifier using the following parameters  $C_G=0.01\mu F, C_C=0.5\mu F, C_S=2\mu F, R_{sig}=10K\Omega, R_G=1M\Omega, R_D=4.7K\Omega, R_S=1K\Omega, R_L=2.2K\Omega, I_{DSS}=8mA, V_p=-4V, r_d=\infty\Omega, V_{DD}=20V, V_{GSQ}=-2V, I_{DQ}=2mA$  10 marks

 **Or**

- 4 a Derive an expression for  $Z_i$  and  $Z_o, A_v$  for common gate configuration for JFET. 10 marks
- b For JFET voltage divider bias calculate  $Z_i, Z_o$  and  $A_v$  and also find  $V_o$  if  $V_i=25mV(rms)$  10 marks



### Module – 3

- 5 a Consider common drain amplifier circuit with  $g_m=1\text{m A/V}$  and  $r_o=150\text{ K}\Omega$  let  $R_{sig}=1\text{ M}\Omega$  and  $R_L=15\text{ K}\Omega$  find  $R_{in}$ ,  $R_{out}$ ,  $A_v$  and  $G_v$  10 marks
- b From small signal operation of an amplifier derive an expression for DC bias point, signal current in Drain terminal ( $i_D$ ), voltage gain and trans conductance 10 marks

**Or**

- 6 a Explain CS amplifier with necessary circuit and equations with and without source resistance 10 marks
- b Explain the different types of internal capacitances in MOSFET and explain the gate capacitive effect. 10 marks

### Module – 4

- 7 a For a voltage series feedback amplifier topology. Obtain an expression for  $A_v$ ,  $R_{if}$  and  $R_{of}$ . 10 marks
- b A crystal oscillator has  $L=0.334\text{H}$ ,  $C=0.065\text{pF}$ ,  $C_M=1\text{pF}$ ,  $R=5.5\text{K}\Omega$  calculate its series and parallel resonating frequency and find Q of the crystal 10 marks

**Or**

- 8 a Briefly explain Barkhausen criterion for oscillations and explain RC phase shift oscillator with necessary circuit and equations 10 marks
- b With neat circuit diagram explain the operation of BJT colpitts oscillator. 10 marks

### Module – 5

- 9 a With neat circuit diagram, explain the operation of a transformer coupled class A power amplifier. 10 marks
- b Derive an expression for second harmonic distortion in power amplifier using 3-point method. 10 marks

**Or**

- 10 a With neat circuit diagram explain the operation of a class B push pull power amplifier and derive its conversion efficiency.. 10 marks
- b Briefly explain series voltage regulator and shunt voltage regulator with necessary block diagrams. 10 marks

\*\*\*\*\*



**Third Semester B.E. Degree Examination, Dec.2019/Jan.2020**  
**Analog Electronic Circuits**

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

**Module-1**

- 1 a. Derive an expression for  $S_{I_{CO}}$  and  $S_{V_B}$  of collector to base bias circuit. (08 Marks)  
 b. Design a suitable Clipper circuit to the output shown in Fig Q1(b). Assume silicon diode.

 


Fig Q1(b)

(05 Marks)

- c. Find  $I_C$ ,  $V_E$ ,  $V_B$ ,  $V_C$  and  $V_{CE}$  for the circuit shown in Fig 1(c). Assume silicon transistor with  $\beta = 60$ .

 


Fig Q1(c)

(07 Marks)

**OR**

- 2 a. Explain how a transistor can be used as a switch. (07 Marks)  
 b. Determine  $I_E$ ,  $I_B$ ,  $V_{CE}$ ,  $V_{CB}$ ,  $V_C$ , and  $V_E$  for the network shown in Fig Q2(b). Assume silicon transistor with  $\beta = 60$ .

 


Fig Q2(b)

(07 Marks)

- c. Determine  $V_o$  for the network shown in Fig Q2(c) the frequency of i/p signal is 1KHz. Assume ideal diode.

 


Fig Q2(c)

(06 Marks)

**Module-2**

- 3 a. For the network shown in Fig Q3(a) determine  $z_i$ ,  $z_o$ ,  $A_v$  and  $A_i$

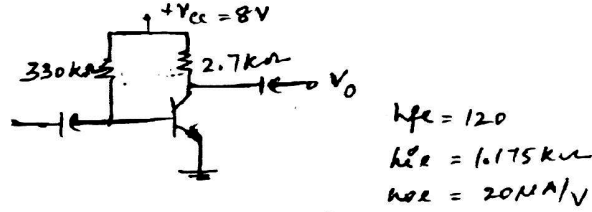


Fig Q3(a)

(08 Marks)

- b. Derive an expression for  $z_i$ ,  $z_o$ ,  $A_v$  for emitter follower configuration using approximate hybrid model. (08 Marks)  
 c. Obtain the expression for Miller i/p capacitance. (04 Marks)

**OR**

- 4 a. Draw the complete hybrid equivalent model of a transistor. Derive an expression for  $z_i$ ,  $z_o$ ,  $A_i$  and  $A_v$ . (10 Marks)  
 b. For the common base amplifier shown in Fig Q4(b), determine: i)  $z_i$  ii)  $A_i$  iii)  $A_v$ . Give  $h_{ie} = 1.6k\Omega$ ,  $h_{fe} = 110$ ,  $h_{re} = 2 \times 10^{-4}$ ,  $h_{oe} = 20\mu A/v$ .

 


Fig Q4(b)

(10 Marks)

**Module-3**

- 5 a. For the Darlington emitter, follower shown in Fig Q5(a)  
 i) Calculate the dc bias voltages  $V_B$ ,  $V_E$ ,  $V_C$  and currents  $I_B$  and  $I_C$   
 ii) Calculate the i/p and o/p impedances  
 iii) Determine the voltage and current gains  
 iv) The ac o/p voltage for  $V_i = 120mV$ .

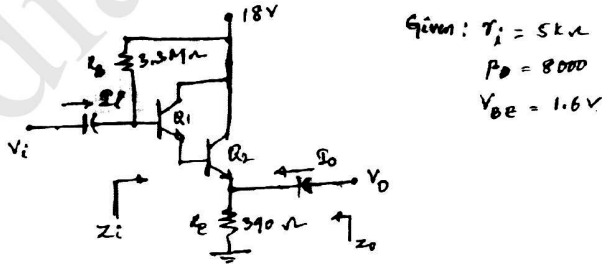


Fig Q5(a)

(10 Marks)

- b. For the cascaded arrangement shown in Fig Q5(b), calculate :  
 i) The loaded voltage gain of each stage  
 ii) The total gain of the system  $A_v$  and  $A_{v1}$   
 iii) The loaded current gain of each stage  
 iv) The total current gain of the system.

 


Fig Q5(b)

(10 Marks)

OR

- 6 a. List the advantages of negative feedback. (10 Marks)  
 b. Derive an expression for input resistance of current series and current shunt feedback amplifier. (04 Marks)  
 c. Negative feedback to be used to reduce noise from an amplifier by 90% i) what must the percentage negative feedback to accomplish this, if the initial voltage gain is 50?  
 ii) What will be the voltage gain with feedback. (06 Marks)

**Module-4**

- 7 a. Derive an expression for frequency of oscillation of RC phase shift oscillator. (10 Marks)  
 b. With a neat circuit diagram, explain the working of complementary class B power amplifier. (06 Marks)  
 c. The following distortion readings are available for a power amplifier.  $D_2 = 0.2$ ,  $D_3 = 0.02$ ,  $D_4 = 0.06$  with  $I_1 = 3.3$  A and  $R_C = 4\Omega$ .  
 i) Calculate THD ii) Determine the fundamental power iii) calculate the total power (04 Marks)

OR

- 8 a. With a neat circuit diagram, explain the working of Hartley oscillator. (06 Marks)  
 b. For a class B amplifier providing a 20V peak signal to a  $16\Omega$  load and a power supply of  $V_{CC} = 30V$ , determine the i/p power, o/p power and efficiency. (06 Marks)  
 c. Explain the classification of power amplifier based on Q- point. (08 Marks)

**Module-5**

- 9 a. Draw the circuit a fixed bias JFET amplifier and its equivalent circuit. Hence obtain the expression  $Z_{in}$ ,  $Z_o$  and  $A_v$ . (10 Marks)  
 b. A JFET has device parameter of  $g_{m0} = 10mS$  and  $I_{DSS} = 12mA$ . When the device is suitably biased, the drain current was found to be 8mA. Determine : i)  $V_p$  ii)  $g_m$  iii)  $V_{GS}$  (06 Marks)  
 c. Give the comparison of FET over BJT. (04 Marks)

OR

- 10 a. With a neat sketch, explain the construction and working principle of N-channel enhancement type MOSFET and also explain its static drain characteristics. (10 Marks)  
 b. Obtain the expression for trans conductance  $g_m$  of JFET. (04 Marks)  
 c. For the voltage divider bias configuration shown in Fig Q10(c). Determine the value of  $R_s$ , if  $V_D = 12V$  and  $V_{GSQ} = -2V$ .

 


Fig Q10(c)

(06 Marks)



**Third Semester B.E. Degree Examination, Dec.2019/Jan.2020**  
**Analog Electronics Circuits**

Time: 3 hrs.

Max. Marks: 100

*Note: Answer any FIVE full questions, choosing ONE full question from each module.*

**Module-1**

- 1 a. Draw a double ended clipper circuit and explain the working principle with transfer characteristics. (10 Marks)
- b. Draw and explain the working of clamper circuit which clamps the positive peak of a signal to zero. (10 Marks)

**OR**

- 2 a. Derive the expression for stability factors  $S'$  and  $S''$  for fixed bias circuit. (08 Marks)
- b. A voltage divider biased circuit has  $R_1 = 39K\Omega$ ,  $R_2 = 82K\Omega$ ,  $R_C = 3.3K\Omega$ ,  $R_E = 1K\Omega$  and  $V_{CC} = 18V$ . The silicon transistor used has  $\beta = 120$ . Find Q-point and stability factor. (07 Marks)
- c. Explain the operation of transistor as switch with suitable circuit and necessary waveforms. (05 Marks)

**Module-2**

- 3 a. State and prove Millers theorem. (06 Marks)
- b. Compare the characteristics of CB, CE and CC configurations. (06 Marks)
- c. For the collector feedback configuration having  $R_F = 180K\Omega$ ,  $R_C = 2.7K\Omega$ ,  $C_1 = 10\mu F$ ,  $C_2 = 10\mu F$ ,  $\beta = 200$ ,  $r_0 = \infty\Omega$  and  $V_{CC} = 9\text{volts}$ . Determine the following parameters:  
i)  $r_e$     ii)  $z_i$     iii)  $z_o$     iv)  $A_v$  (08 Marks)

**OR**

- 4 a. Derive suitable expression to explain the effect of cascading of amplifiers on lower and upper cut off frequencies. (08 Marks)
- b. Derive equations for miller input capacitance and miller output capacitance. (08 Marks)
- c. A transistor in CE mode has h-parameters  $h_{ie} = 1.1K\Omega$ ,  $h_{re} = 2 \times 10^{-4}$ ,  $h_{fe} = 100$  and  $h_{oc} = 25\mu A/V$ . Determine the equivalent CB parameters. (04 Marks)

**Module-3**

- 5 a. Derive expression for  $Z_i$  and  $A_i$  for a Darlington Emitter follower circuit. (10 Marks)
- b. Explain the need of a cascading amplifier. Draw and explain the block diagram of two stage cascade amplifier. (06 Marks)
- c. Write a note on cascade amplifier. (04 Marks)

**OR**

- 6 a. List the general characteristics of negative feedback amplifier. (04 Marks)  
b. A given amplifier arrangement has the following voltage gain  $AV_1 = 10$ ,  $AV_2 = 20$  and  $AV_3 = 40$ . Calculate the overall voltage gain and determine the total voltage gain in dBS. (08 Marks)  
c. For the voltage series feedback amplifier. Derive an expression for output impedance (Resistance). (08 Marks)

**Module-4**

- 7 a. Show that maximum efficiency of class-B push pull amplifier (power amplifier) circuit is 78.54%. (08 Marks)  
b. Explain the classification of power amplifier with a neat circuit diagram and waveforms. (07 Marks)  
c. A class-B push pull amplifier operating with  $V_{CC} = 25V$  provides a 22V peak signal to  $8\Omega$  load. Calculate the circuit efficiency and power dissipated per transistor. (05 Marks)

**OR**

- 8 a. Draw the circuit of wein bridge oscillator and explain its operation. (10 Marks)  
b. With a neat circuit diagram and waveform, explain the working principal of crystal oscillator operating in series resonant mode. A crystal has the following parameters  $L = 0.334H$ ,  $C = 0.065pF$  and  $R = 5.5K\Omega$ . Calculate its resonant frequency. (10 Marks)

**Module-5**

- 9 a. With the help of neat diagram, explain the working and characteristics of N-channel JFET. (10 Marks)  
b. For a self bias JFET circuit,  $V_{DD} = +12V$ ,  $R_D = 2.2K\Omega$ ,  $R_G = 1M\Omega$ ,  $R_S = 1K\Omega$ ,  $I_{DSS} = 8mA$ ,  $V_P = -4$  Volts. Determine the following parameters: i)  $V_{GS}$  ii)  $I_D$  iii)  $V_{DS}$  iv)  $V_S$  v)  $V_G$  vi)  $V_D$  (10 Marks)

**OR**

- 10 a. With neat sketches, explain the operation and characteristics of n-channel depletion type MOSFET. (10 Marks)  
b. Derive expression for  $V_{GS}$ ,  $I_D$ ,  $V_{DS}$ ,  $V_D$  and  $V_S$  for a voltage divider bias circuit using FET. (10 Marks)



## Third Semester BE Degree Examination January 2020

(CBCS Scheme)

Time: 3 Hours

Max Marks: 100 Marks

## Sub: ANALOG ELECTRONICS

- Instructions:**
1. Answer five full questions
  2. Choose one full question from each module
  3. Your answer should be specific to the questions asked
  4. Write the same question numbers as they appear in this question paper
  5. Write Legibly.

## Module -1


- |    |   |   |    |   |
|----|---|---|----|---|
| 1  | a | Define h-parameter. Draw the h-parameter model of a CE configuration.   | 10 | M |
|    | b | Derive an expression for $I_B$ , $I_C$ and $V_{CE}$ for voltage divider bias using exact analysis.  | 10 | M |
| Or |   |   |    |   |
| 2  | a | Derive an expression for $A_v$ , $Z_i$ , $Z_o$ for Emitter follower using re model  | 10 | M |
|    | b | A voltage divider biased circuit has $R_C=4K\Omega$ , $R_E=1.5K\Omega$ , $R_1=39K\Omega$ , $R_2=3.9K\Omega$ $V_{CC}=18V$ and $\beta=70$ . Find $I_C$ , $V_{CE}$ . | 10 | M |

## Module -2

- |   |   |   |    |   |
|---|---|---|----|---|
| 3 | a | Explain high frequency response of FET amplifier and derive an expression for cut off frequencies defined by input and output circuits.   | 10 | M |
|   | b | Determine the lower cut off frequency for the FET amplifier using the following parameters $C_G=0.01\mu F$ , $C_C=0.5\mu F$ , $C_S=2\mu F$ $R_{sig}=10K\Omega$ , $R_G=1M\Omega$ , $R_D=4.7K\Omega$ , $R_S=1K\Omega$ , $R_L=2.2K\Omega$ , $I_{DSS}=8mA$ , $V_P=-4V$ $r_d=\infty\Omega$ , $V_{DD}=20V$ , $V_{GSQ}=-2V$ , $I_{DQ}=2mA$ | 10 | M |

Or

- |   |   |   |    |   |
|---|---|---|----|---|
| 4 | a | Derive an expression for $Z_i$ and $Z_o$ , $A_v$ for self-bias configuration for JFET.  | 10 | M |
|   | b | The fixed-bias configuration of FET amplifier had an operating point defined by $V_{GSQ} = -2 V$ and $I_{DQ} = 5.625 mA$ , with $I_{DSS} = 10 mA$ and $V_P = -8 V$ . The network is shown below with an applied signal $V_i$ $Y_{os}=40\mu S$ . | 10 | M |

 

**Module -3**

- 5 a Explain CS amplifier with necessary circuit and equations with and without source resistance 12 M
- b From small signal operation of an amplifier derive an expression for DC bias point, signal current in Drain terminal ( $i_D$ ), voltage gain and trans conductance 08 M

Or

- 6 a With neat diagram and small signal model of common drain amplifier prove that  $A_{vo}=1, G_v=1$  10 M
- b Explain the different types of internal capacitances in MOSFET and explain the gate capacitive effect. 10 M

**Module -4**

- 7 a For a voltage series feedback amplifier topology. obtain an expression for  $A_v, R_{if}$  and  $R_{of}$  also explain the practical feedback circuit using voltage series feedback. 10 M
- b with neat circuit diagram explain the working of series resonant crystal oscillator. A crystal oscillator has  $L=0.334H, C=0.065pF, C_M=1pF, R=5.5K\Omega$  calculate its series and parallel resonating frequency. 10 M

Or

- 8 a What are tuned oscillators? Explain the two types of tuned oscillators. 10 M
- b Briefly explain Barkhausen criterion for oscillations and explain RC phase shift oscillator with necessary circuit and equations. 10 M

**Module -5**

- 9 a Explain the working of class B push pull power amplifier. Derive an expression for its efficiency  $\eta=78.4\%$  10 M
- b Derive an expression for second harmonic distortion in power amplifier using 3-point method. 10 M

Or

- 10 a With neat circuit diagram explain the operation of a series-fed class A power amplifier and prove that  $\eta=25\%$ . 10 M
- b Briefly explain the series voltage regulator. Calculate the output voltage and the Zener current in the regulator circuit of Figure shown below for  $R_L = 1K\Omega$  10 M

