

**Third Semester B.E. Degree Examination, Dec.2018/Jan.2019**  
**Digital Electronics**

Time: 3 hrs.

Max. Marks: 80

**Note: Answer any FIVE full questions, choosing  
ONE full question from each module.**

**Module-1**

- 1 a. Define combinational logic. Design a combinational circuit which takes two, 2 bit binary numbers as its input and generates an output equal to 1, when the sum of the two numbers is even. (10 Marks)
- b. Simplify using Karnaugh map. Write the Boolean equation and realize using NAND gates.  
 $D = f(w, x, y, z) = \sum m(0, 2, 4, 6, 8) + \sum d(10, 11, 12, 13, 14, 15)$ . (06 Marks)

**OR**

- 2 a. Define canonical SOP and canonical POS. Expand  $f = (\bar{a} + b + c)(a + c + \bar{d})$  into canonical POS. (04 Marks)
- b. Solve using Quine-McCluskey tabulation method,  
 $f(a, b, c, d) = \sum m(0, 1, 4, 5, 9, 10, 12, 14, 15) + \sum \phi(2, 8, 13)$   
 Obtain the minimal form of the given function. Verify the result using k-map. (12 Marks)

**Module-2**

- 3 a. Define decoder. Implement full subtractor using a decodes. Write the truth table. (08 Marks)
- b. Compare ripple carry adder and look ahead carry adder. Explain the circuit and operation of a 4 bit binary adder with look ahead carry. (08 Marks)

**OR**

- 4 a. Design and implement one bit comparator. (04 Marks)
- b. Implement the multiple functions :  
 $f_1(a, b, c, d) = \sum(0, 4, 8, 10, 14, 15)$  and  
 $f_2(a, b, c, d) = \sum(3, 7, 9, 13)$   
 using two 3 to 8 decoders, i.e. 74138 ICs. (06 Marks)
- c. Implement full adder circuit using 8 : 1 multiplexer. (06 Marks)

**Module-3**

- 5 a. What is gated SR Latch? Explain the operation of gated SR Latch, with a logic diagram, truth table and logic symbol. (08 Marks)
- b. Derive the characteristic equation of SR, JK, D and T flip-flops with the help of function tables. (08 Marks)

**OR**

- 6 a. Explain the operation of a switch debouncer built using SR Latch. Draw the supporting waveforms. (04 Marks)
- b. Explain 0s and 1s catching problem of Master Slave JK flip flop with waveform. Suggest the solution for this problem. (04 Marks)
- c. What is edge triggered flip flop? With a neat circuit diagram, explain the operation of positive edge triggered D flip flop, using NAND gates. (08 Marks)

**Module-4**

- 7 a. With the help of neat diagram, explain PISO and PIPO operation of unidirectional shift registers. (08 Marks)  
 b. Design a 4 bit binary ripple 'UP' counter using negative edge triggered JK flip flop. Show the up counter execution with the help of timing diagram. (08 Marks)

**OR**

- 8 a. Implement a Mod 8 twisted ring counter using D flip flops. Give the counting sequence and decoding gate inputs. (06 Marks)  
 b. Design a synchronous MOD-6 counter using JK flip flop for the following count sequence 0, 2, 3, 6, 5, 1 and repeat. Write the transition table, logic equations and the counter implementation diagram. (10 Marks)

**Module-5**

- 9 a. Compare Mealy and Moore sequential circuit models with suitable example. (04 Marks)  
 b. For the logic diagram shown in Fig.Q9(b), write the state and output equations. Give the transition table and the state diagram. (12 Marks)

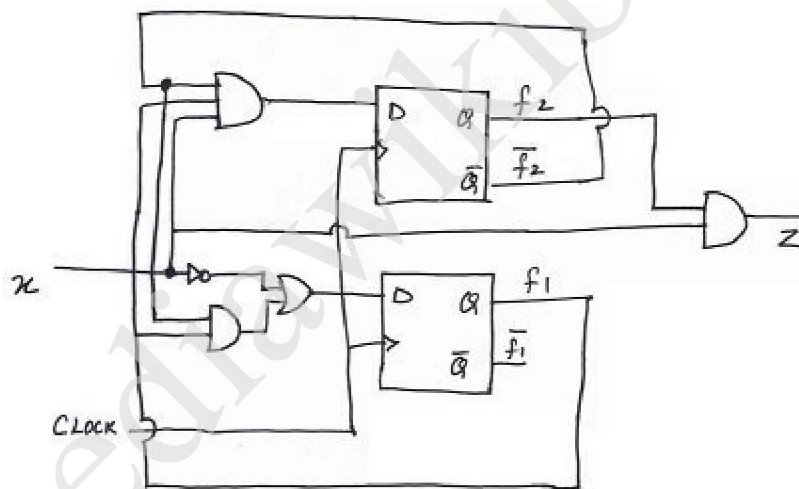


Fig.Q9(b)

**OR**

- 10 a. Write the basic recommended steps for the design of a clocked synchronous sequential circuit. (06 Marks)  
 b. How to convert a Mealy machine to a Moore machine? (02 Marks)  
 c. A sequential circuit has one input and one output. The state diagram is shown in Fig.Q10(c). Design a sequential circuit using D flip flop. (08 Marks)

 


Fig.Q10(c)

**Third Semester B.E. Degree Examination, Dec.2019/Jan.2020**  
**Digital Electronics**

Time: 3 hrs.

Max. Marks: 100

*Note: Answer any FIVE full questions, choosing ONE full question from each module.*

**Module-1**

- 1 a. Express the following functions into a canonical form:  
i)  $f_1 = a + bc + bcd$   
ii)  $f_2 = a(b + c)(b + c + d)$  (08 Marks)  
b. Represent the number of days in a month for a non-leap year by a truth table, indicating the output of a invalid inputs if any by '0'. (06 Marks)  
c. Simplify the given function using K-map method  
 $f(abcd) = \sum m(1, 2, 4, 11, 13, 14, 15) + d(0, 5, 7, 8, 10)$ . (06 Marks)

**OR**

- 2 a. Find all prime implicants of the function using Quine-industry method and verify the same by K-map method.  $f(abcd) = \sum m(0, 2, 3, 4, 8, 10, 12, 13, 14)$  (10 Marks)  
b. Find minimal sum and minimal product for the incomplete Boolean function using K-map  
 $f(abcd) = \sum m(6, 7, 9, 10, 13) + d \sum(1, 4, 5, 11, 15)$ . (10 Marks)

**Module-2**

- 3 a. Design two bit magnitude comparator. (10 Marks)  
b. Design 4:2 priority encoder with a valid output where highest priority is given to the highest bit position. (10 Marks)

**OR**

- 4 a. Design and realize the Boolean function using IC-74139.  
 $f_1(ab) = \sum(0, 2)$ ,  $f_2(abc) = \sum(1, 3, 5, 7)$ . (05 Marks)  
b. Explain how look ahead carry adder circuit will reduce the propagation delay with the help of carry propagate and carry generate function. (08 Marks)  
c. Implement the Boolean function  $f(abcd) = \sum(0, 2, 4, 5, 7, 9, 10, 14)$  using multiplexers with two 4:1 MUX with variable 'a' and 'b' are connected to their select lines in first level and one 2:1 MUX with variable 'c' connected to its select line in second level. (07 Marks)

**Module-3**

- 5 a. With the help of logic circuit and waveforms. Explain switch bouncing applications using SR latch. (06 Marks)  
b. Write the characteristics equation for SR, JK flip flop. (06 Marks)  
c. With neat logic diagram, and waveform. Explain the operation of master-slave J-K flip-flop. (08 Marks)

OR

- 6 a. List the difference between combinational and sequential circuit. (06 Marks)  
b. Explain the operation of clocked SR flip-flop using NAND-gate. s (06 Marks)  
c. What is the significance of Edge triggering? Explain the working of positive edge triggered D flip-flop with their function table. (08 Marks)

**Module-4**

- 7 a. With neat diagram, explain the operation of universal shift register. (08 Marks)  
b. Design 3 bit binary synchronous down counter using JK Flip Flop. Write excitation table, transition table, and logic diagram. (12 Marks)

OR

- 8 a. What is register? With neat circuit diagram, explain the operation of 4-bit ring counter. (07 Marks)  
b. With logic diagram, sequence table, decoding logic. Explain the operation of mod-7 twisted ring counter. (07 Marks)  
c. Explain the working of 4 bit binary ripple counter using positive edge triggered T-flip-flop also draw timing diagram, truth table. (06 Marks)

**Module-5**

- 9 a. Write the difference between Moore and Mealy model with necessary block diagram. (08 Marks)  
b. Design asynchronous circuit using positive edge triggered J-K flip-flop with minimal combinational gating to generate the following sequence. 0-1-2-0: if input X = 0 and 0 - 2 - 1 - 0; if input X = 1, provide an output which goes high to indicate the non-zero state in the 0-1-2-0 sequence. Is this a mealy machine? (12 Marks)

OR

- 10 a. Design a cyclic mod-8 synchronous binary counter using JK flip-flop. (10 Marks)  
b. Analyze the given sequential circuit show in Fig.Q.10(b) and obtain.  
i) Flip-flop Input and Output Equation  
ii) Transition Equation  
iii) Transition Table (N)  
iv) State Table  
v) State Diagram.

 


Fig.Q.10(b)

(10 Marks)

## CBCS Scheme

USN

--	--	--	--	--	--	--	--	--	--

15EC33

Third Semester B.E. Degree Examination, Dec.2016/Jan.2017

## Digital Electronics

Time: 3 hrs.

Max. Marks: 80

Note: Answer FIVE full questions, choosing one full question from each module.

Module-1

- 1 a. Define the following: i) TVUM Table; ii) Combinational circuit; iii) Canonical SOP; iv) Canonical POS. (04 Marks)
- b. Obtain minimal expression using k-map for the following incompletely specified function:  
 $F(a, b, c, d) = \sum_m (0,1,4,6,7,9,15) + \sum_d (3,5,11,13)$  and draw the circuit diagram using gates. (06 Marks)
- c. Write the truth table and design a circuit to generate o/p using K-map for the problem statement given: o/p of a combinational circuit having 4 inputs and an o/p, becomes logical '1' when two or more inputs goto logic level '1'. (06 Marks)

OR

- 2 a. Define K-map, incompletely specified function, essential prime implicants and grey code. (04 Marks)
- b. Obtain minimal logical expression for the given maxterm expression using K-map.  
 $f(a, b, c, d) = \pi_M (0,1,4,5,6,7,9,14) \cdot \pi_d (13,15)$ . (04 Marks)
- c. Use Quine McCluskey's method of minimization to obtain essential prime implicants and minimal expression for the following minterm expression:  
 $f(a, b, c, d) = \sum_m (0, 1, 4, 5, 7, 8, 13, 15) + \sum_d (2)$ . (08 Marks)

Module-2

- 3 a. Define encoder, decoder, priority encoder and multiplexer. (04 Marks)
- b. Write block diagram representation of a full adder using 3:8 decoders. (04 Marks)
- c. Design full adder using i) 8:1 MUX and ii) 4:1 MUX. (08 Marks)

OR

- 4 a. Explain Carry look ahead adder with neat diagram and relevant expressions. (08 Marks)
- b. Design 2-bit comparator and briefly explain. (08 Marks)

Module-3

- 5 a. Define bistable element, latch, flip-flop and function table. (04 Marks)
- b. Sketch timing diagrams for JK flipflop and D-flip-flop. (06 Marks)
- c. Explain M/S JK flip-flop with the help of circuit diagram and waveforms. (06 Marks)

OR

- 6 a. Find characteristic equations for T and SR-flip-flops with the help of function tables. (06 Marks)
- b. Write circuit diagram for the edge triggered D-flip-flop and provide explanation for different input condition. (06 Marks)
- c. Explain the operation of a switch debouncer built using SR-latch with the help of waveforms. (04 Marks)

1 of 2

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
 2. Any revealing of identification, appeal to evaluator and/or equations written eg, 42+8 = 50, will be treated as malpractice.

15EC33

**Module-4**

- 7 a. Define register, asynchronous ripple counter synchronous counter and ring counter. (04 Marks)  
 b. Design mod-8 counter using right shift register. Use D-flip-flop to build register circuit. Explain the operation using function table. (06 Marks)  
 c. Write timing diagrams, counting sequence and the logic diagram for 4-bit ripple counter and briefly explain. (06 Marks)

**OR**

- 8 a. Explain PIPO and SIPO operations using single diagram. (06 Marks)  
 b. Design Mod-6 synchronous counter using JK flip-flop. The sequence is 000, 001, 011, 100, 101, 111...000. (07 Marks)  
 c. Write state diagram for Mod-5 self correcting counter and briefly explain. The sequence is 000, 001, 101, 110, 111, 000. (03 Marks)

**Module-5**

- 9 a. What are Melay and Moore models of a sequential circuit? Briefly explain with diagrams. (04 Marks)  
 b. Write characteristic/excitation table for JK flip-flop and explain. (03 Marks)  
 c. Analyze the following sequential circuit. Writ excitation equations K-maps and state diagrams to analyze. (09 Marks)

 


Fig.Q.9(c)

**OR**

- 10 a. Write state diagrams for a four state machine using Melay and Moore models and briefly explain. (04 Marks)  
 b. What is a state table? Give an example. (02 Marks)  
 c. Design a counter circuit for the following state table. Follow the standard steps for design. (10 Marks)

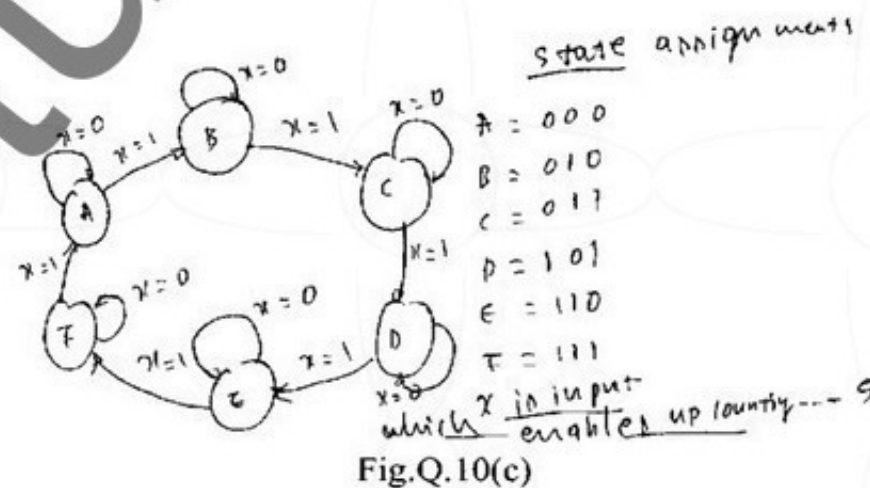


Fig.Q.10(c)

\*\*\*\*\*  
 2 of 2

## CBCS Scheme

USN

--	--	--	--	--	--	--	--	--	--

ISEC33

**Third Semester B.E. Degree Examination, Dec.2017/Jan.2018**  
**Digital Electronics**

Time: 3 hrs.

Max. Marks: 80

**Note: Answer any FIVE full questions, choosing  
 ONE full question from each module.**

Module-1

- 1 a. Identify all prime implicants and essential prime implicants of following function using k-map.  
 $f(a, b, c, d) = \sum m(6, 7, 9, 10, 13) + d.c(1, 4, 5, 11, 15)$   
 $f(a, b, c, d) = \pi m(1, 2, 3, 4, 9, 10) + d.c(0, 14, 15)$  (08 Marks)
- b. Find minimal sum for following Boolean function using Quine-McClusky method:  
 $f(a, b, c, d) = \sum m(7, 9, 12, 13, 14, 15) + d.c(4, 11)$ . (08 Marks)

OR

- 2 a. Transform each of following canonical expression into other canonical form in decimal notation.  
 $f(x, y, z) = \sum m(0, 1, 3, 4, 6, 7)$   
 $f(w, x, y, z) = \pi M(0, 1, 2, 3, 4, 6, 12)$ . (04 Marks)
- b. Find a minimal sum for following Boolean function using decimal QM method and PI table reduction.  
 $f(a, b, c, d) = \sum m(1, 3, 6, 8, 9, 10, 12, 14) + d.c(7, 13)$ . (12 Marks)

Module-2

- 3 a. Implement following functions using single 3:8 decoder  
 $f_1(a, b, c) = \pi M(2, 3, 4, 5, 7)$   
 $f_2(a, b, c) = \sum m(1, 3, 5)$ . (04 Marks)
- b. What is magnitude comparator? Design a two bit digital comparator by writing TT, relevant expression and logic diagram. (12 Marks)

OR

- 4 a. Implement  $f(a, b, c, d) = \sum m(0, 1, 5, 6, 7, 10, 15)$  using  
 i) 8:1 MUX with a, b, c as select lines  
 ii) 4:1 MUX with a, b as select lines. (08 Marks)
- b. What are the problems associated with basic encoder? Explain how can these problems be overcome by priority encoder considering 8 input lines. (08 Marks)

Module-3

- 5 a. What is flip-flop. Discuss working principle of SR flip-flop with its TT. Also highlight role of SR f/f in switch debouncer circuit. (08 Marks)
- b. What is significance of edge triggering? Explain working of +ve edge triggered D flip-flop with their functional table. (08 Marks)

1 of 2

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
 2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.

15EC33

OR

- 6 a. Explain the working of M/S JK flip-flop with functional table and timing diagram. Show how race condition is overcome. (10 Marks)  
b. Obtain characteristic equation for following flip-flops. i) JK ii) SR. (06 Marks)

**Module-4**

- 7 a. Realize a 3 bit binary synchronous up counter using JK flip-flop. Write excitation table, transition table and logic diagram. (10 Marks)  
b. Explain SIPO and PISO shift registers with relevant logic diagrams. (06 Marks)

OR

- 8 a. Explain the working principle of 4bit binary ripple counter configured using +ve edge triggered T – F/F. Also draw timing diagram. (08 Marks)  
b. Explain the operation of universal shift register with a neat diagram. (08 Marks)

**Module-5**

- 9 a. Distinguish between Moore and Mealy model with necessary block diagram. (06 Marks)  
b. Construct mealy state diagram that will detect input sequence 10110, when input pattern is detected, z is asserted high. Give state diagram for each state. (10 Marks)

OR

- 10 a. Design a cyclic mod 8 synchronous binary counter using JK flip-flop. Give state diagram, transition table and excitation table. (08 Marks)  
b. Analyse the following sequential circuit shown in figure and obtain :  
i) Flip-flop input and output equation  
ii) Transition equation (ch.equ)  
iii) Transition table  
iv) State table  
v) Draw state diagram. (08 Marks)

\*\*\*\*\*



## CBCS SCHEME

USN 

--	--	--	--	--	--	--	--	--	--

17EC34

Third Semester B.E. Degree Examination, Dec.2018/Jan.2019

## Digital Electronics

Time: 3 hrs.

Max. Marks: 100

*Note: Answer any FIVE full questions, choosing one full question from each module.*Module-1

- 1 a. Convert  $x = \bar{a}b + bc$  to canonical SOP form. (02 Marks)  
 b. Simplify  $G = f(w, x, y, z) = \pi M(1,3,8,10,12,13,14,15)$  in POS form and implement using NOR gates. (08 Marks)  
 c. Simplify the following using Quine-McClusky's minimization technique.  
 $V = f(a, b, c, d) = \sum m(1, 3, 4, 5, 6, 9, 11, 12, 13, 14)$  (10 Marks)

OR

- 2 a. Convert  $P = (\bar{w} + x)(y + \bar{z})$  to canonical POS form. (03 Marks)  
 b. Simplify  $P = f(a, b, c, d) = \sum m(2, 3, 4, 5, 13, 15) + \sum d(8, 9, 10, 11)$  in SOP form and implement using NAND gates. (07 Marks)  
 c. Simplify using Quine-McClusky's minimization technique.  
 $V = f(a, b, c, d) = \sum m(1, 5, 7, 9, 13, 15) + \sum d(8, 10, 11, 14)$  (10 Marks)

Module-2

- 3 a. Implement  $f_1(a, b, c) = \sum m(1, 3, 5)$ ,  $f_2(a, b, c) = \sum m(0, 1, 6)$  using 74138, 3:8 decoder. (06 Marks)  
 b. With a neat circuit diagram explain the carry look ahead adder with relevant expressions. (10 Marks)  
 c. Design a one-bit comparator, implement using suitable gates. (04 Marks)

OR

- 4 a. Using 74151, 8:1 Mux, realize the Boolean function  $F(a, b, c, d) = \sum m(0, 1, 5, 6, 7, 10, 15)$  with b, c, d as select lines. (04 Marks)  
 b. With neat circuit diagram, explain the keypad interface using 74147, 10 line to BCD encoder. (10 Marks)  
 c. Design a full subtractor and implement using logic gates. (06 Marks)

Module-3

- 5 a. Discuss the working principle of Gated SR latch with its truth Table. (06 Marks)  
 b. Explain the operation of Switch debouncer built using SR latch with the help of circuit and waveforms. (08 Marks)  
 c. Obtain the characteristic equations of JK flip flop and SR flip flop. (06 Marks)

OR

- 6 a. What is race around condition? How it can be overcome? (02 Marks)  
 b. Explain the working of MS-JK flip flop with logic symbol and timing diagram. (10 Marks)  
 c. Explain the working of +ve edge triggered D flip flop with the functional table. (08 Marks)

1 of 2

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
 2. Any revealing of identification, appeal to evaluator and/or equations written eg. 42+8 = 50, will be treated as malpractice.

17EC34

**Module-4**

- 7 a. Explain the working of four bit ripple counter using +ve edge triggered T flip-flops with the counting sequence table and timing diagram. (10 Marks)
- b. Explain the SIPO and SISO operation of shift register with relevant logic diagram and the truth table. (06 Marks)
- c. Explain the operation of ring counter using logic diagram and truth table. (04 Marks)

**OR**

- 8 a. Explain Universal Shift Register with the help of logic diagram and mode control table. (10 Marks)
- b. Realize a three-bit binary synchronous up counter using JK flip flops. (10 Marks)

**Module-5**

- 9 a. Construct a Mealy state diagram that will detect input sequence 10110, when input pattern is detected Z is asserted high. Write the state diagram. (10 Marks)
- b. Design a synchronous counter using T flip flops to count the sequence 0, 2, 3, 6, 5, 1, 0, 2, ... Write the excitation table and state diagram and logic diagram. (10 Marks)

**OR**

- 10 a. Explain Mealy and Moore model of clocked synchronous sequential circuit with the block diagram. (08 Marks)
- b. For the logic diagram given in Fig.Q10(b):
  - i) Derive the excitation and output equations
  - ii) Write the state equations
  - iii) Construct transition table and state table
  - iv) Draw the state diagram

 


Fig.Q10(b)

(12 Marks)

\*\*\*\*\*

**Third Semester B.E. Degree Examination, June/July 2019**  
**Digital Electronics**

Time: 3 hrs.

Max. Marks: 80

**Note: Answer any FIVE full questions, choosing ONE full question from each module.**

**Module-1**

- 1 a. Write the switching equation for a digital circuit with four inputs and whose output is '1' if majority of its inputs are '1'. (04 Marks)
- b. Place the following equations into proper canonical forms and write its decimal notations also :
- i)  $P = f(a, b, c) = a\bar{b} + a\bar{c} + bc$
- ii)  $Q = f(x, y, z) = (x + \bar{y})(\bar{y} + z)$ . (06 Marks)
- c. Solve using k – map and implement using only NAND gates  
 $B = f(w, x, y, z) = \Sigma(1, 2, 3, 4, 9) + \Sigma d(10, 11, 12, 13, 14, 15)$ . (06 Marks)

**OR**

- 2 a. Solve using K Map  
 $A = f(w, x, y, z) = \pi(1, 2, 3, 4, 8, 9, 10, 11, 12, 13, 14, 15)$   
 and implement using NOR gates only. (06 Marks)
- b. Simplify using Quine Me Clusky method :  
 $D = f(a, b, c, d) = \Sigma(0, 1, 2, 3, 6, 7, 8, 9, 14, 15)$   
 Show the prime implicant table to determine the EPIs. (10 Marks)

**Module-2**

- 3 a. Design a combinational circuit that multiplies two 2bit binary values, and produces 4-bit product. Get the minterms for  $P_0, P_1, P_2$  and  $P_3$ . Simplify only for  $P_2$ . (08 Marks)
- b. Design a 4 to 16 decoder using 3 to 8 decoders (74LS138) only and realize the function :
- $P = f(w, x, y, z) = \Sigma(1, 4, 8, 13)$
- $Q = f(w, x, y, z) = \Sigma(2, 7, 13, 14)$ . (08 Marks)

**OR**

- 4 a. Design a 2 bit magnitude comparator and get an expression for  $A < B$  only, which is the minimal expression. (08 Marks)
- b. Explain a carry look ahead adder with a neat diagram and relevant expressions. (08 Marks)

**Module-3**

- 5 a. Explain an SR latch using NOR gates with circuit diagram function table and timing diagram. (06 Marks)
- b. Explain a positive edge triggered D flip flop with circuit diagram, function table and timing diagram. (10 Marks)

OR

- 6 a. What is race around? How is it overcome in master slave JK F/F. Explain MS JK with relevant circuit diagram, function table. (10 Marks)
- b. Derive the characteristics equation for : (06 Marks)
- i) SR F/F ii) JK F/F iii) D F/F iv) T F/F.

**Module-4**

- 7 a. Given an universal shift register, sketch its diagram only for left shift operates and explain its working. (08 Marks)
- b. What is a twisted ring counter? Sketch its diagram and explain its counting sequence and also give the bits that determine a state uniquely. (08 Marks)

OR

- 8 a. Design a model synchronous counter for the sequence, using a D flip-flop [Refer Fig.Q8(a)].



Fig.Q8(a)

(08 Marks)

- b. Explain with net diagram, the counting sequence and timing diagram, the working of a 4 bit binary ripple counter, using positive edge triggered T flip flop. (08 Marks)

**Module-5**

- 9 a. Draw and explain the Mealy and Moore sequential circuit models. (06 Marks)
- b. Analyze the following sequential circuit and draw its state diagram.[Refer Fig.Q9(b)]. (10 Marks)

 


Fig.Q9(b)

OR

- 10 a. Represent a Moore circuit notation of a JK flip-flop through state diagram and explain. (06 Marks)
- b. Design a modulo 8 synchronous counter with : (10 Marks)
- i) state diagram ii) state table iii) transition table iv) excitation table, kmap and logic diagram

**Third Semester B.E. Degree Examination, June/July 2019**  
**Digital Electronics**

Time: 3 hrs.

Max. Marks: 100

**Note: Answer any FIVE full questions, choosing  
ONE full question from each module.**

**Module-1**

- 1 a. Construct a truth table and write a Boolean expression for the problem statement. An output variable Y is to be true when the value of inputs exceeds 4. The weights for each input variable is  $a = 4$ ,  $b = 3$ ,  $c = -1$ , and  $d = 1$ . Design the logic circuit for the obtained expression. (10 Marks)
- b. Place the equation  $P = f(a, b, c) = ab + \bar{a}c + b\bar{c}$  into proper canonical form and write the minterms. (05 Marks)
- c. What do you mean by canonical SOP and canonical POS? Explain with example? (05 Marks)

**OR**

- 2 a. Simplify  $K = f(w, x, y, z) = \sum m(0, 1, 5, 13, 15) + \sum d(2, 7, 10, 14)$  using K-map method. Draw the logic diagram for obtained expression. (10 Marks)
- b. Simplify  $D = f(a, b, c, d) = \sum m(0, 1, 2, 3, 6, 7, 8, 9, 12, 15)$  using QM – method, verify the same using K–map. Draw the logic diagram for simplified expression. (10 Marks)

**Module-2**

- 3 a. What is an encoder? Design 4 to 2 priority encoder? (08 Marks)
- b. Realize the function  $X = f(a, b, c, d) = \sum m(0, 3, 7, 10, 13)$  using 74LS138 ICs. (08 Marks)
- c. Design 4 : 1 Mux and draw the logic diagram using basic gates. (04 Marks)

**OR**

- 4 a. Implement  $f(a, b, c, d) = \sum m(0, 1, 5, 6, 7, 10, 15)$  using 8 : 1 Mux with a, b, c as select lines. (08 Marks)
- b. Design a binary full subtractor using NAND gates only. (06 Marks)
- c. Explain about carry look ahead adder. (06 Marks)

**Module-3**

- 5 a. Obtain the characteristic equations for D and T flip-flops. (08 Marks)
- b. Explain the operation of SR–Flip-Flop with the help of logic diagram. Draw functional table. (08 Marks)
- c. What is race around condition? Explain with diagram. (04 Marks)

**OR**

- 6 a. Explain the working of master slave J-K flip flop with the help of logic diagram. Draw the timing diagrams of the same. (10 Marks)
- b. Explain D-flip-flop operation using positive edge triggered clock. (06 Marks)
- c. Write two-two difference between :  
 i) Combinational and sequential logic  
 ii) Latch and flip-flop. (04 Marks)

**Module-4**

- 7 a. What is register? Explain with diagram of 4-bit serial-in parallel-out shift register. (10 Marks)  
 b. Explain 3-bit asynchronous up and down binary counters. (10 Marks)

**OR**

- 8 a. Design mod-5 ripple counter using T-flip-flops. (08 Marks)  
 b. Design 3-bit synchronous up counter. (08 Marks)  
 c. Compare asynchronous and synchronous counters. (04 Marks)

**Module-5**

- 9 a. Design a Mealy type sequence detector to detect a serial input sequence of 101. (10 Marks)  
 b. Design 2-bit synchronous up counter. (10 Marks)

**OR**

- 10 a. Analyze the following sequential circuit, by writing input and output equations, state table and state diagram. (12 Marks)

 


Fig.Q10(a)

- b. What are Mealy and Moore models? Explain briefly with diagram. (04 Marks)  
 c. Draw a state table and state diagram with an example. (04 Marks)

## CBCS Scheme

USN

--	--	--	--	--	--	--	--	--	--

15EC33

**Third Semester B.E. Degree Examination, June/July 2017**  
**Digital Electronics**

Time: 3 hrs.

Max. Marks: 80

**Note: Answer any FIVE full questions, choosing one full question from each module.**

Module-1

- 1 a. Convert the given Boolean function into
- $Y = f(a, b, c) = (a + b)(a + c)$  minterm canonical form (04 Marks)
  - $P = f(a, b, c) = (a + b)(b + c)(\bar{c} + a)$  maxterm canonical form. (04 Marks)
- b. Using K-map determine the minimal sum of product expression and realize the simplified expression using only NAND gates. (08 Marks)
- $M = f(W, X, Y, Z) = \sum (1, 4, 5, 6, 11, 12, 13, 14, 15)$ .

OR

- 2 a. Simplify the given Boolean function using Quine – McCluskey method :  
 $Y = f(a, b, c, d) = \sum (0, 2, 3, 5, 8, 10, 11)$ . Verify the result using k-map. (12 Marks)
- b. Distinguish between prime implicant and Essential prime implicant. (04 Marks)

Module-2

- 3 a. Define Decoder. Implement the following multiple output function using IC 74138 and external gates. Also write the truth table.  
 $P = f_1(X, Y, Z) = \sum (1, 2, 5, 6)$   
 $Q = f_2(X, Y, Z) = \pi (3, 5, 6, 7)$ . (06 Marks)
- b. Implement the following Boolean function using 8:1 multiplexer :  
 $Y = f(A, B, C, D) = \bar{A}\bar{B}D + ACD + \bar{B}CD + \bar{A}CD$  (10 Marks)

OR

- 4 a. Design and implement 4-bit look ahead carry adder. (08 Marks)
- b. Design and implement BCD to Excess-3 code converter. (08 Marks)

Module-3

- 5 a. Explain the working principle of gated SR latch. (06 Marks)
- b. Explain the working of master slave JK flip-flop with the help of a logic diagram, function table, logic symbol and timing diagram. (10 Marks)

OR

- 6 a. With a neat logic diagram, explain the working of positive edge triggered D flip-flop. Also draw the timing diagram. (08 Marks)
- b. Derive the characteristic equation for JK and T flip-flop. (08 Marks)

Module-4

- 7 a. Describe the working principle of universal shift register with the help of logic diagram and mode control table. (08 Marks)
- b. Illustrate the operation of 4-bit binary ripple counter using logic diagram and timing diagram. (08 Marks)

1 of 2

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
 2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.

15EC33

OR

- 8 a. Design a synchronous Mod-6 counter using clocked T flip-flop.
- b. Explain Mod-4 ring counter using D flip-flop.

(10 Marks)  
(06 Marks)

**Module-5**

- 9 a. Explain Mealy and Moore sequential circuit models.
- b. For the logic diagram shown in Fig Q 9(b).
  - i) Write input and output equations
  - ii) Construct transition table
  - iii) Draw state diagram.

(04 Marks)

(12 Marks)

 


Fig Q9(b)

OR

- 10 a. Define the terms as applied to sequential circuit :  
Input variable, output variable, Excitation variable and state variable.
- b. Design a sequential circuit for a state diagram shown in Fig Q 10(b).

(04 Marks)

(12 Marks)

 


Fig Q10(b)



## CBCS Scheme

USN

--	--	--	--	--	--	--	--	--	--

15EC33

**Third Semester B.E. Degree Examination, June/July 2018**  
**Digital Electronics**

Time: 3 hrs.

Max. Marks: 80

**Note: Answer any FIVE full questions, choosing  
 ONE full question from each module.**

Module-1

- 1 a. Given,  $F = A(B + C) + D$ , obtain : i) minimal SOP ii) minimal POS iii) canonical SOP  
 iv) canonical POS. (08 Marks)
- b. Realize a circuit for Ex-NOR using only four NOR gates. (02 Marks)
- c. Simplify the function using K-map. :  
 $Y = f(a, b, c, d) = \sum_m(0,1,2,3,5,6,8,10,15)$ .  
 Write the simplified SOP expression. (06 Marks)

OR

- 2 a. Simplify the following function using Quine – McClusky method :  
 $P = f(a, b, c, d) = \sum_m(0, 2, 3, 5, 8, 10, 11, 13)$ . (06 Marks)
- b. Reduce the following Boolean function using K-map and realize the simplified expression  
 using NOR gates.  
 $T = f(a, b, c, d) = \sum_m(0, 2, 3, 5, 6, 7, 8, 9) + \sum_d(10, 11, 12, 13, 14, 15)$ . (06 Marks)
- c. Prove that,  $ABC + \overline{A}BC + A\overline{B}C + \overline{A}\overline{B}C = \overline{A}B + BC + CA$  (04 Marks)

Module-2

- 3 a. Design a binary full subtractor using logic gates. Write a truth table Implement the logic  
 circuit using basic gates. (06 Marks)
- b. Define magnitude comparator. Design a two bit binary comparator and implement with  
 suitable logic gates. (10 Marks)

OR

- 4 a. Implement full adder using 4 : 1 multiplexer (MUX). (08 Marks)
- b. With a neat logic diagram, explain carry look ahead adder. (08 Marks)

Module-3

- 5 a. Obtain the characteristic equation for D and T flip-flop. (04 Marks)
- b. Explain the working of a master–slave SR flip-flop with the help of a logic diagram,  
 function table, logic symbol and timing diagram. (08 Marks)
- c. Differentiate sequential logic circuit and combinational logic circuit. (04 Marks)

OR

- 6 a. Explain the working of master slave JK flip-flops with functional table and timing diagram.  
 Show how race around condition is over come. (08 Marks)
- b. Discuss the difference between a flip-flop and latch. (04 Marks)
- c. Derive the characteristic equations of SR and JK flip-flops. (04 Marks)

1 of 2

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
 2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.

15EC33

**Module-4**

- 7 a. Design a synchronous mod-5 counter using JK flip-flops and implement it. (08 Marks)  
b. Design synchronous mod-6 counter using D flip-flop to generate the count sequence, (0, 2, 3, 6, 5, 1, 0). (08 Marks)

OR

- 8 a. Design divide by 6 synchronous counter using T – flip-flops. Write state table and reduce the expression using K-map. (06 Marks)  
b. Compare synchronous and asynchronous counters. (04 Marks)  
c. Design mod-6 ripple counter using T flip-flops. (06 Marks)

**Module-5**

- 9 a. Design a Moore type sequence detector to detect a serial input sequence of 101. (08 Marks)  
b. Design a synchronous counter using JK – flip-flops to count the sequence 0, 1, 2, 4, 5, 6, 0, 1, 2. Use state diagram and state table. (08 Marks)

OR

- 10 a. Explain the Mealy model and Moore model of a clocked synchronous sequential network. (08 Marks)  
b. Design a Mealy type sequence detector to detect a serial input sequence of 101. (08 Marks)

\*\*\*\*\*

## CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

15EC33

**Third Semester B.E. Degree Examination, June/July 2019**  
**Digital Electronics**

Time: 3 hrs.

Max. Marks: 80

*Note: Answer any FIVE full questions, choosing  
 ONE full question from each module.*

Module-1

- 1 a. Write the switching equation for a digital circuit with four inputs and whose output is '1' if majority of its inputs are '1'. (04 Marks)
- b. Place the following equations into proper canonical forms and write its decimal notations also :
- i)  $P = f(a, b, c) = a\bar{b} + a\bar{c} + bc$
- ii)  $Q = f(x, y, z) = (x + \bar{y})(\bar{y} + z)$ . (06 Marks)
- c. Solve using k – map and implement using only NAND gates  
 $B = f(w, x, y, z) = \Sigma(1, 2, 3, 4, 9) + \Sigma d(10, 11, 12, 13, 14, 15)$ . (06 Marks)

OR

- 2 a. Solve using K Map  
 $A = f(w, x, y, z) = \pi(1, 2, 3, 4, 8, 9, 10, 11, 12, 13, 14, 15)$   
 and implement using NOR gates only. (06 Marks)
- b. Simplify using Quine Mc Clusky method :  
 $D = f(a, b, c, d) = \Sigma(0, 1, 2, 3, 6, 7, 8, 9, 14, 15)$   
 Show the prime implicant table to determine the EPIs. (10 Marks)

Module-2

- 3 a. Design a combinational circuit that multiplies two 2bit binary values, and produces 4-bit product. Get the minterms for  $P_0, P_1, P_2$  and  $P_3$ . Simplify only for  $P_2$ . (08 Marks)
- b. Design a 4 to 16 decoder using 3 to 8 decoders (74LS138) only and realize the function :
- $P = f(w, x, y, z) = \Sigma(1, 4, 8, 13)$
- $Q = f(w, x, y, z) = \Sigma(2, 7, 13, 14)$ . (08 Marks)

OR

- 4 a. Design a 2 bit magnitude comparator and get an expression for  $A < B$  only, which is the minimal expression. (08 Marks)
- b. Explain a carry look ahead adder with a neat diagram and relevant expressions. (08 Marks)

Module-3

- 5 a. Explain an SR latch using NOR gates with circuit diagram function table and timing diagram. (06 Marks)
- b. Explain a positive edge triggered D flip flop with circuit diagram, function table and timing diagram. (10 Marks)

1 of 2

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
 2. Any revealing of identification, appeal to evaluator and/or equations written eg, 42+8 = 50, will be treated as malpractice.

15EC33

OR

- 6 a. What is race around? How is it overcome in master slave JK F/F. Explain MS JK with relevant circuit diagram, function table. (10 Marks)  
 b. Derive the characteristics equation for :  
 i) SR F/F ii) JK F/F iii) D F/F iv) T F/F. (06 Marks)

**Module-4**

- 7 a. Given an universal shift register, sketch its diagram only for left shift operates and explain its working. (08 Marks)  
 b. What is a twisted ring counter? Sketch its diagram and explain its counting sequence and also give the bits that determine a state uniquely. (08 Marks)

OR

- 8 a. Design a model synchronous counter for the sequence, using a D flip-flop [Refer Fig.Q8(a)].

 


Fig.Q8(a)

- b. Explain with net diagram, the counting sequence and timing diagram, the working of a 4 bit binary ripple counter, using positive edge triggered T flip flop. (08 Marks)

**Module-5**

- 9 a. Draw and explain the Mealy and Moore sequential circuit models (06 Marks)  
 b. Analyze the following sequential circuit and draw its state diagram.[Refer Fig.Q9(b)]. (10 Marks)

 


Fig.Q9(b)

OR

- 10 a. Represent a Moore circuit notation of a JK flip-flop through state diagram and explain. (06 Marks)  
 b. Design a modulo 8 synchronous counter with :  
 i) state diagram ii) state table iii) transition table iv) excitation table, kmap and logic diagram (10 Marks)

\*\*\*\*\*