

---

## SYLLABUS

### Module -1

**Basic Concepts:** Practical sources, Source transformations, Network reduction using Star – Delta transformation, Loop and node analysis With linearly dependent and independent sources for DC and AC networks, Concepts of super node and super mesh.

### Module -2

**Network Theorems:** Superposition, Reciprocity, Millman's theorems, Thevenin's and Norton's theorems and Maximum Power transfer theorem.

### Module -3

**Transient behavior and initial conditions:** Behavior of circuit elements under switching condition and their Representation, evaluation of initial and final conditions in RL, RC and RLC circuits for AC and DC excitations.

**Laplace Transformation & Applications:** Solution of networks, step, ramp and impulse responses, waveform Synthesis.

### Module -4

**Resonant Circuits:** Series and parallel resonance, frequency- response of series and Parallel circuits, Q-Factor, Bandwidth.

### Module -5

**Two port network parameters:** Definition of z, y, h and transmission parameters, modeling with these parameters, relationship between parameters sets.

### Text Books:

1. M.E. Van Valkenberg (2000), "Network analysis", Prentice Hall of India, 3<sup>rd</sup> edition, 2000, ISBN: 9780136110958.
2. Roy Choudhury, "Networks and systems", 2nd edition, New Age International Publications, 2006, ISBN: 9788122427677.

### Reference Books:

1. Hayt, Kemmerly and Durbin "Engineering Circuit Analysis", TMH 7th Edition, 2010.
2. J. David Irwin /R. Mark Nelms, "Basic Engineering Circuit Analysis", John Wiley, 8th edition, 2006.
3. Charles K Alexander and Mathew N O Sadiku, "Fundamentals of Electric Circuits", Tata McGraw-Hill, 3rdEd, 2009.

## Module 1: Basic Circuit Concepts

### Circuit Elements:

Any two terminal circuit components are called circuit elements.

### Types:

1) **Active elements:** Deliver the energy to the network

Examples: Voltage Source, Current Source

2) **Passive elements:** Absorb the energy from the network

Examples: Resistors, Capacitors, Inductors


### Network:

Interconnection of two or more circuit elements is called network



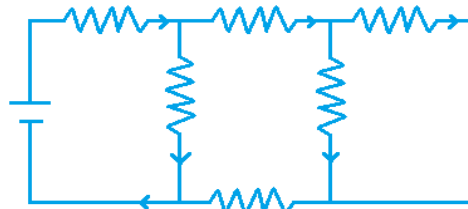
### Circuit:

Network with at least one closed path is called circuit



**Note:** Every circuit is a network but all networks are not circuits

### Network Terminology

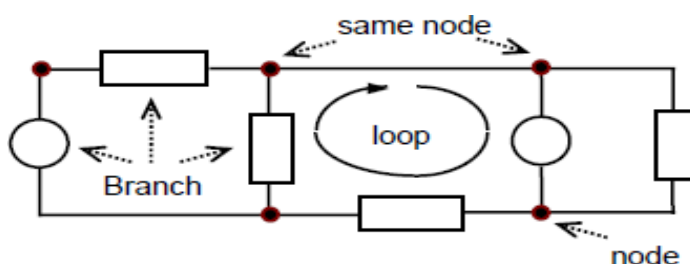

- **Branch**

A branch represents a single element, such as a resistor or a battery



- **Node**

A node is the point or junction in a circuit connecting two or more branches or circuit elements. The node is usually indicated by a dot (.) in a circuit


- **Loop**

A loop is any closed path in a circuit

- **Mesh**


It is a loop that contains no other loop within it.

### Energy sources:

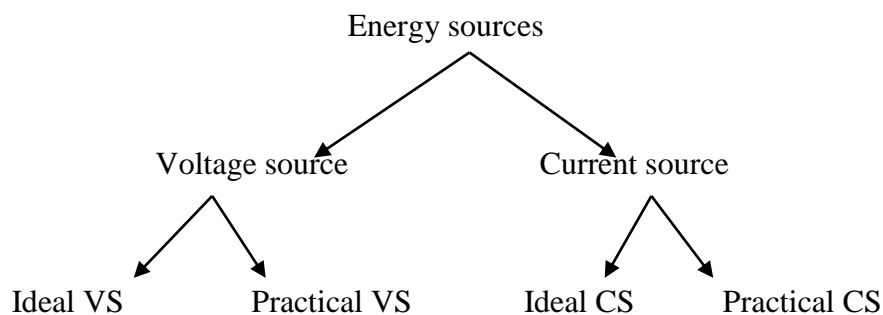

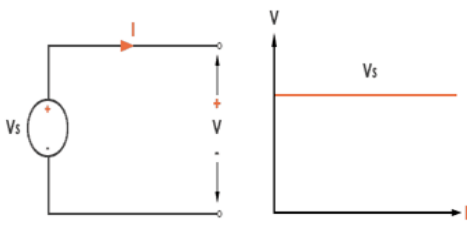
### Ideal VS:

- Whose internal resistance is zero
- Irrespective of the load current, terminal voltage is constant



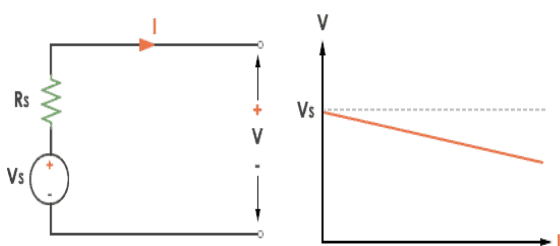
### Practical VS:

- Which has finite internal resistance and connected in series with the source
- Terminal voltage decreases with increase in load current



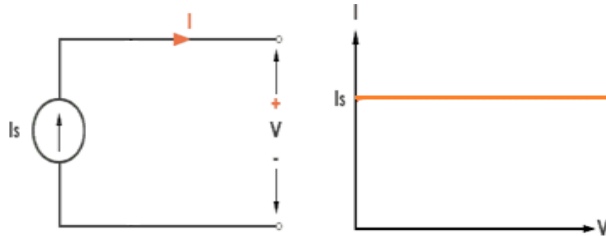
**Ideal CS:**

- Has infinite internal resistance
- Irrespective of the load voltage, terminal current is constant



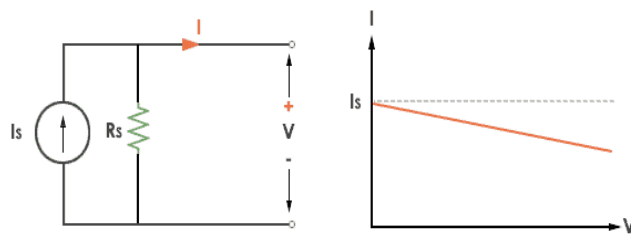
**Practical CS:**

- Has finite internal resistance
- Terminal current decreases with increase in load current



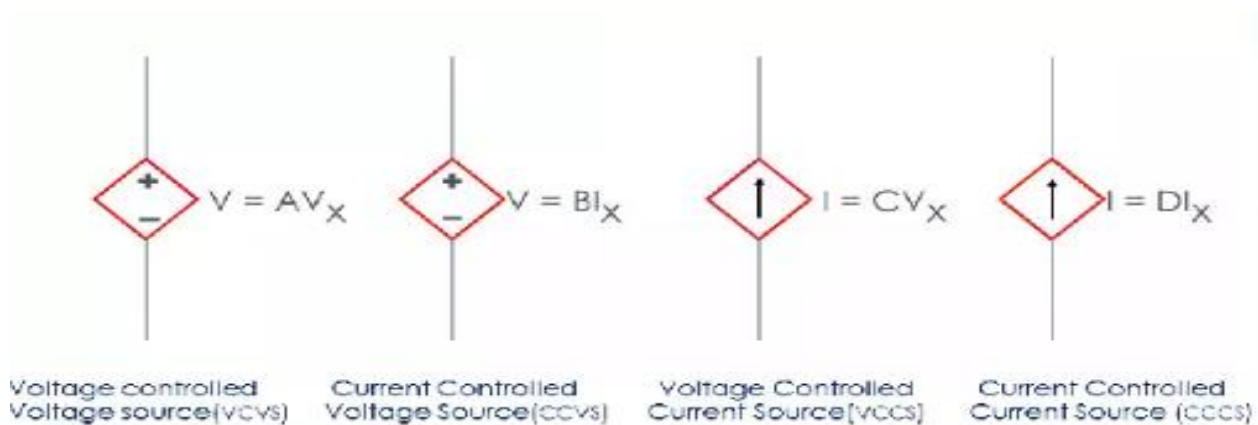**Dependent sources/ Controlled sources:**

- Sources whose voltage/current depends on voltage/current that appears at some other location of the network.
- Represented by diamond symbol
- 4 types



## Classification of Networks:

### 1) Linear and Non linear networks

A *Linear circuit* is one whose parameters are constant i.e., they do not change with voltage or current.

Examples: Network consisting of R, L and C

A *Non linear circuit* is one whose parameters change with voltage or current.

Examples: Network consisting of diode and transistor

### 2) Unilateral and Bilateral networks

The circuit whose properties or characteristics change with the direction of its operation is said to be *Unilateral*.

Examples: A diode rectifier is a unilateral, because it cannot perform rectification in both directions.

A *Bilateral circuit* is one whose properties or characteristics are the same in either direction.

Examples: R, L & C.

### 3) Active and Passive network

Network consisting of only passive elements is called **Passive** network

Examples: Network consisting of R, L and C

Network consisting of at least one active element is called **Active** network

Examples: Network consisting of VS and CS

### 4) Lumped and Distributed network

Network in which elements are physically separable is called **Lumped** network.

Examples: R, L and C


Network in which elements cannot be physically separable is called **Distributed** network.

Examples: Transmission lines having R, L, C all along their length.


**Source Transformation**

Source Transformation involves the transformation of voltage source to its equivalent current source and vice-versa.

Consider a voltage source with series resistance R and a current source with same resistance R in parallel as shown below.

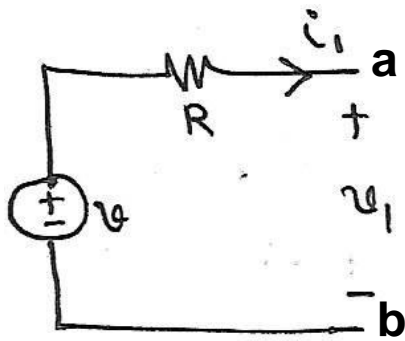

**Fig: Voltage source**

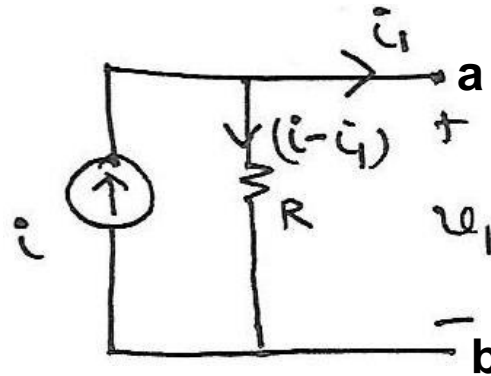

**Fig: Current source**

The terminal voltage and current relationship in the case of voltage source is;

$$v_1 = v - i_1 R \dots\dots (1)$$

The terminal voltage and current relationship in the case of current source is;

$$i_1 = i - v_1 / R$$

$$v_1 = i R - i_1 R \dots\dots (2)$$

If the voltage source above has to be equivalently transformed to or represented by a current source then the terminal voltages and currents have to be same in both cases.

This means eqn. (1) should be equal to eqn. (2).


This implies,

$$v = i R$$

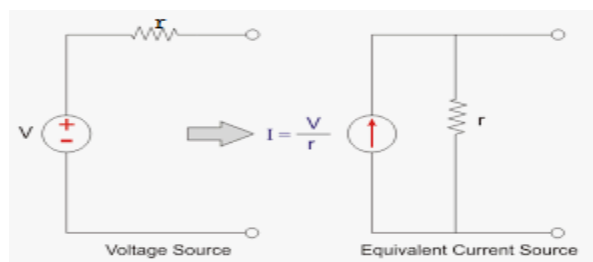
**or**

$$i = v / R \dots(3)$$

If eqn.(3) holds good, then the voltage source above can be equivalently transformed to or represented by, the current source shown above and vice-versa.




**Examples:**

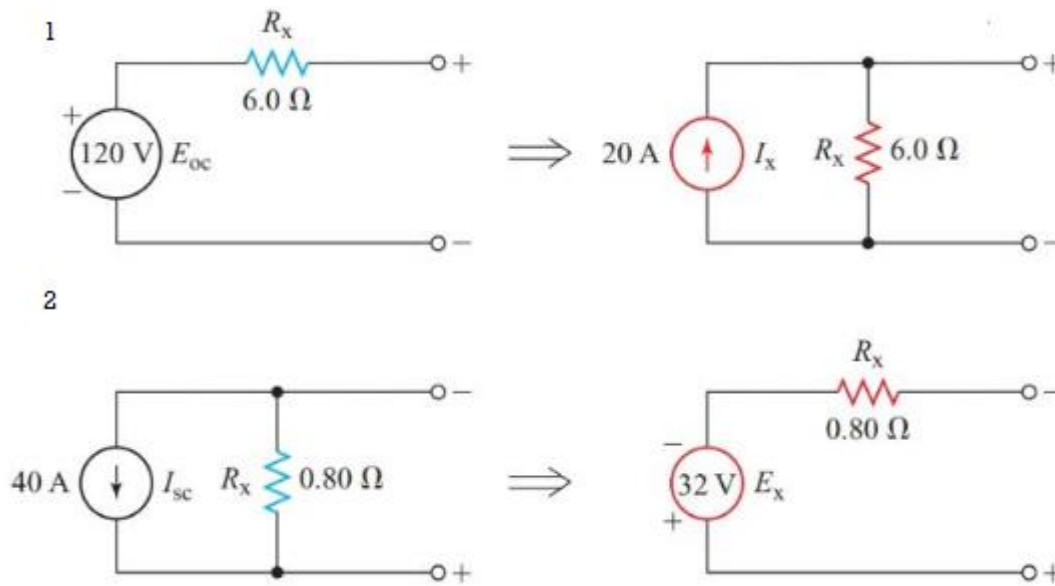


**Combination of sources:**


1. Two ideal voltage sources in series

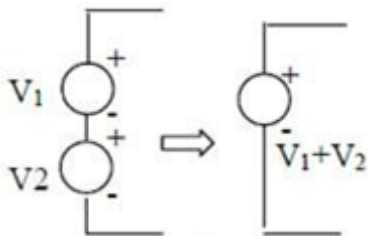


2. Two ideal voltage sources in parallel

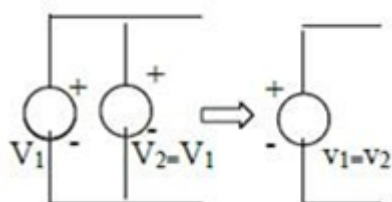


3. Two ideal current sources in parallel

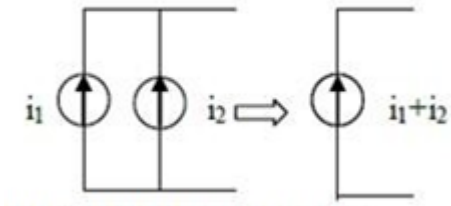


4. Two ideal current sources in series

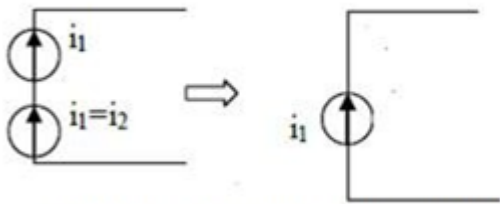

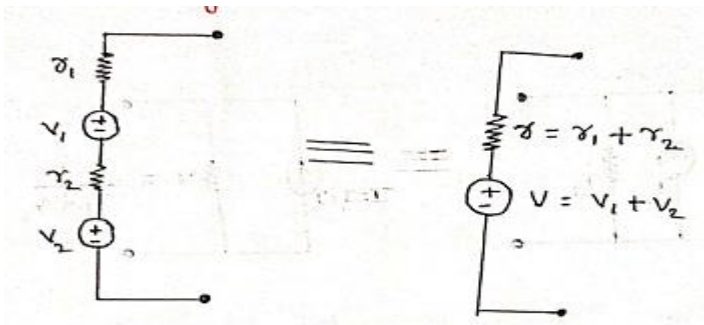
5. Two practical voltage sources in series



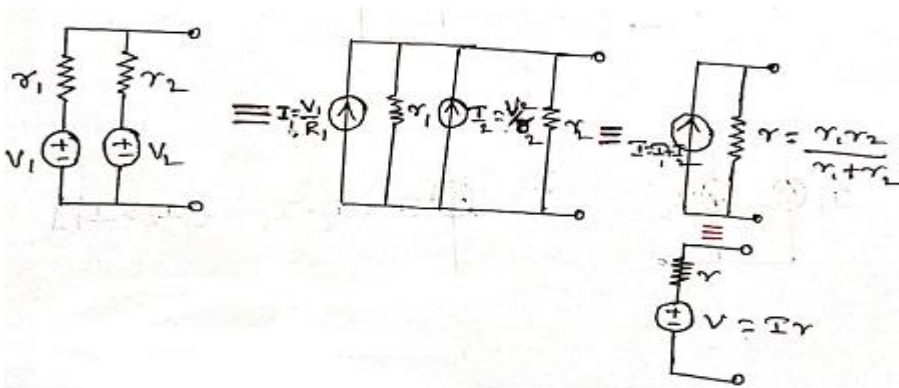
6. Two practical voltage sources in parallel



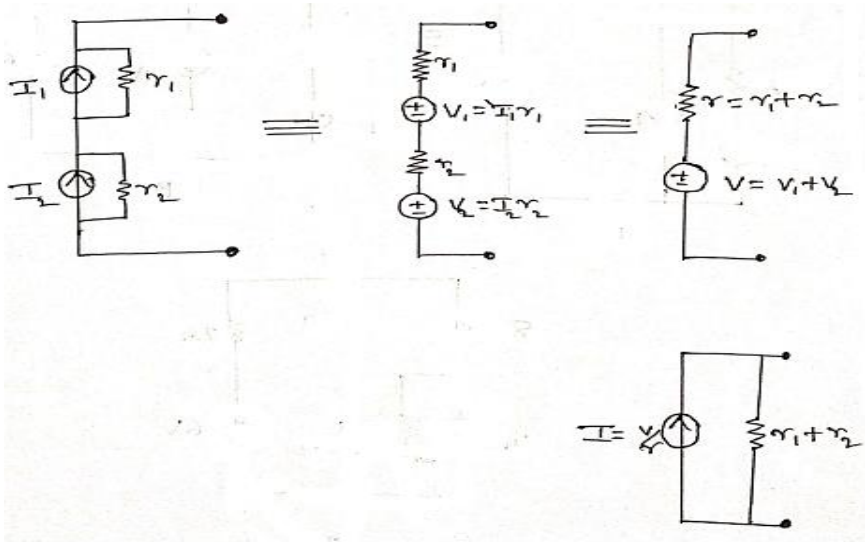
7. Two practical current sources in series



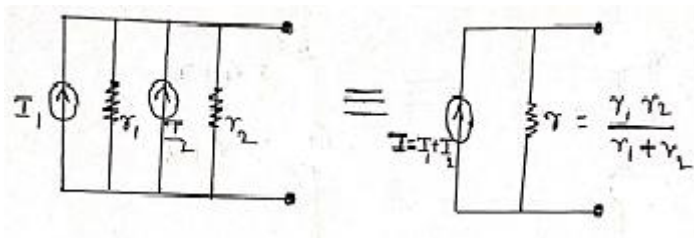
8. Two practical current sources in parallel


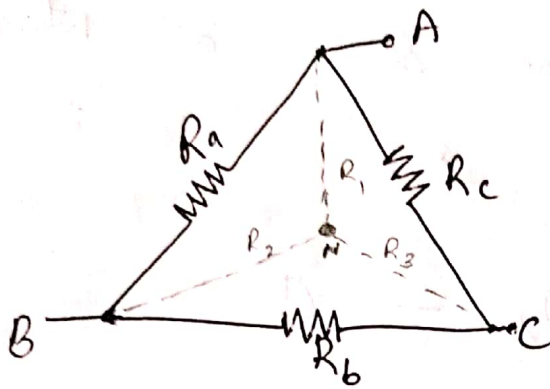
# Star-Delta transformation ( $\Delta$ - $Y$ ) :-



$\equiv$

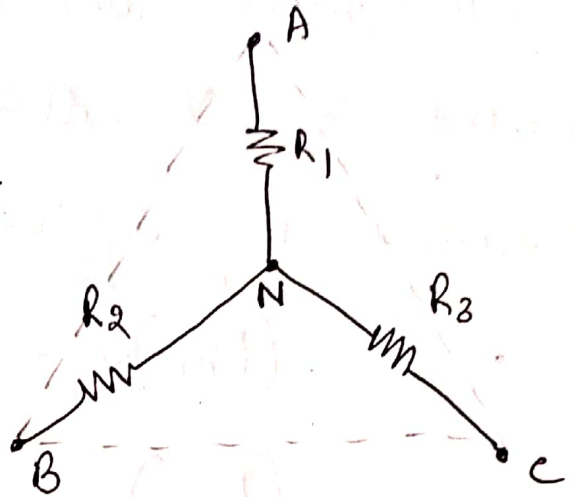

Let  $R_a$ ,  $R_b$  &  $R_c$  be the elements connected in  $\Delta$  n/w b/w the terminals A, B & C.  
 Let the n/w consisting of  $R_1$ ,  $R_2$  &  $R_3$  be the equivalent  $Y$  n/w across the same terminals A, B & C.

For converting the given  $\Delta$  n/w into equivalent  $Y$  n/w, it is necessary to derive the relations for  $R_1$ ,  $R_2$  &  $R_3$  in terms of  $R_a$ ,  $R_b$  &  $R_c$ .

Why to convert the known  $Y$  into equivalent  $\Delta$  n/w, it is necessary to derive the relations for  $R_a$ ,  $R_b$  &  $R_c$  in terms of  $R_1$ ,  $R_2$  &  $R_3$ .



## i) Delta to Star transformation :-

The resistance b/w A & B when connected in  $\gamma$  should be same as when connected in equivalent  $\Delta$ .

$$\text{i.e., } (R_{AB})_{\gamma} = (R_{AB})_{\Delta} \quad \text{--- ①}$$

$$(R_{BC})_{\gamma} = (R_{BC})_{\Delta} \quad \text{--- ②}$$

$$(R_{CA})_{\gamma} = (R_{CA})_{\Delta} \quad \text{--- ③}$$

$$\therefore (R_{AB})_{\gamma} = R_1 + R_2$$

$$(R_{AB})_{\Delta} = \frac{R_a (R_b + R_c)}{R_a + R_b + R_c}$$

from ①

$$R_1 + R_2 = \frac{R_a (R_b + R_c)}{R_a + R_b + R_c} \quad \text{--- ④}$$

$$\text{uly } R_2 + R_3 = \frac{R_b (R_c + R_a)}{R_a + R_b + R_c} \quad \text{--- ⑤}$$

$$R_3 + R_1 = \frac{R_c (R_a + R_b)}{R_a + R_b + R_c} \quad \text{--- ⑥}$$

→ ④ - ⑤ gives.

$$R_1 + \cancel{R_2} - \cancel{R_2} - R_3 = \frac{R_a (R_b + R_c) - R_b (R_c + R_a)}{R_a + R_b + R_c}$$

$$R_1 - R_3 = \frac{\cancel{R_a R_b} + R_a R_c - R_b R_c - \cancel{R_b R_a}}{R_a + R_b + R_c}$$

$$R_1 - R_3 = \frac{R_a R_c - R_b R_c}{R_a + R_b + R_c} \quad \text{--- ⑦}$$

→ ⑥ + ⑦ gives.

$$\cancel{R_3} + R_1 + \cancel{R_1} - \cancel{R_3} = \frac{R_c R_a + \cancel{R_c R_b} + R_a R_c - \cancel{R_b R_c}}{R_a + R_b + R_c}$$

$$\cancel{2R_1} = \frac{\cancel{2} R_a R_c}{R_a + R_b + R_c}$$

$$R_1 = \frac{R_a R_c}{R_a + R_b + R_c} \quad \text{--- ⑧}$$

$$\text{wly } R_2 = \frac{R_b R_a}{R_a + R_b + R_c} \quad \text{--- (9)} \quad \& \quad R_3 = \frac{R_c R_b}{R_a + R_b + R_c} \quad \text{--- (10)}$$

ii) Star to delta transformation :-

To get the expressions for  $R_a$ ,  $R_b$  &  $R_c$  in terms of  $R_1$ ,  $R_2$  &  $R_3$ , eqns (8), (9) & (10) are used.

$$\text{(8) } \times \text{(9) gives } R_1 \times R_2 = \frac{R_a^2 R_b R_c}{(R_a + R_b + R_c)^2} \quad \text{--- (11)}$$

$$\text{(9) } \times \text{(10) gives } R_2 \times R_3 = \frac{R_a R_b^2 R_c}{(R_a + R_b + R_c)^2} \quad \text{--- (12)}$$

$$\text{(10) } \times \text{(8) gives } R_3 \times R_1 = \frac{R_a R_b R_c^2}{(R_a + R_b + R_c)^2} \quad \text{--- (13)}$$

→ (11) + (12) + (13) gives

$$R_1 R_2 + R_2 R_3 + R_3 R_1 = \frac{R_a^2 R_b R_c + R_a R_b^2 R_c + R_a R_b R_c^2}{(R_a + R_b + R_c)^2}$$



$$R_1 R_2 + R_2 R_3 + R_3 R_1 = \frac{R_a R_b R_c [R_a + R_b + R_c]}{(R_a + R_b + R_c)^2}$$

$$\rightarrow = \frac{R_a R_b R_c}{(R_a + R_b + R_c)}$$

from eqn (10)  $R_3 = \frac{R_b R_c}{R_a + R_b + R_c}$


$$\therefore R_1 R_2 + R_2 R_3 + R_3 R_1 = R_a R_3$$

$$\Rightarrow R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

Similarly  $R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

1)

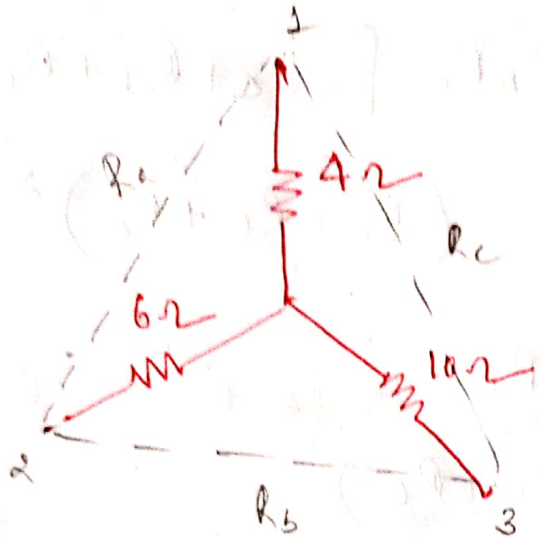

$$R_a = \frac{4 \times 6 + 6 \times 10 + 10 \times 4}{10}$$


$$R_a = 12.4 \Omega$$

$$R_b = \frac{4 \times 6 + 6 \times 10 + 10 \times 4}{4}$$

$$R_b = 31 \Omega$$

$$R_c = \frac{124}{6} = 20.66 \Omega$$

2)

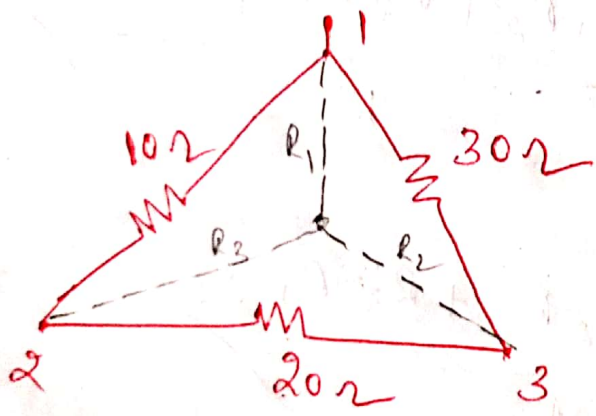

$$R_1 = \frac{10 \times 30}{10 + 30 + 20}$$

$$R_1 = 5 \Omega$$



$$R_2 = \frac{30 \times 20}{10 + 30 + 20}$$

$$R_2 = 10 \Omega$$

$$R_3 = \frac{10 \times 20}{10 + 20 + 30} = 3.33 \Omega$$

1) Determine  $R_{in}$  Using Star Delta transform



in the circuit shown below

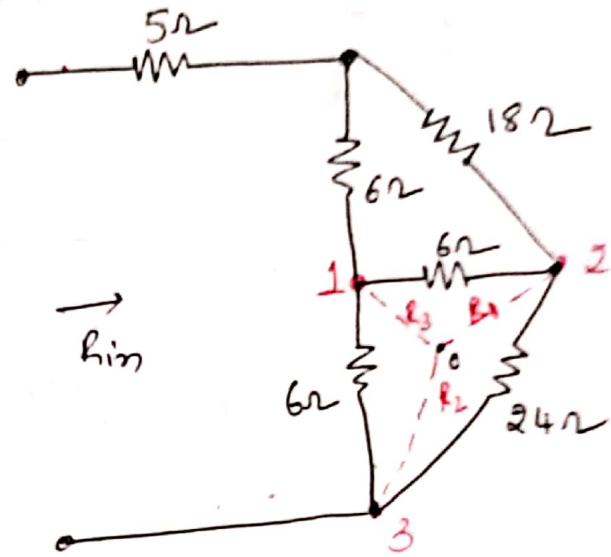
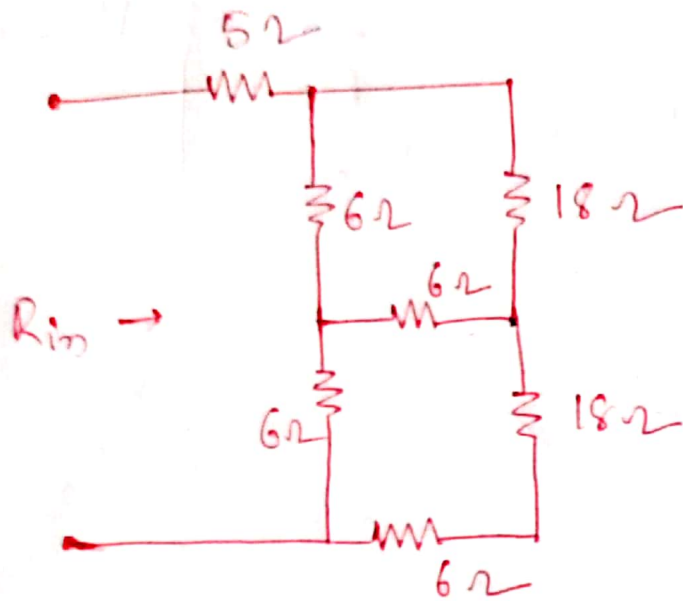


$$R_1 = \frac{24 \times 6}{6 + 6 + 24} = 4 \Omega$$

$$R_2 = \frac{24 \times 6}{6 + 6 + 24} = 4 \Omega$$

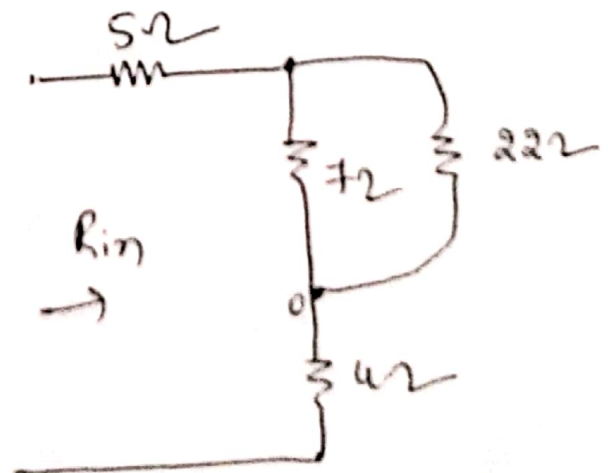
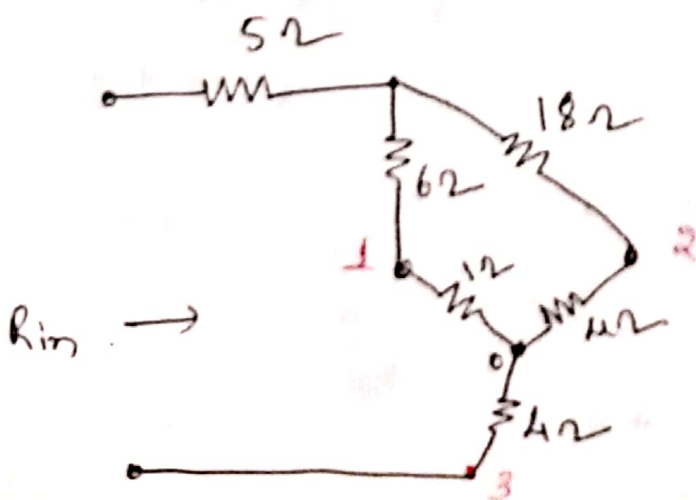
$$R_3 = \frac{6 \times 6}{6 + 6 + 24} = 1 \Omega$$



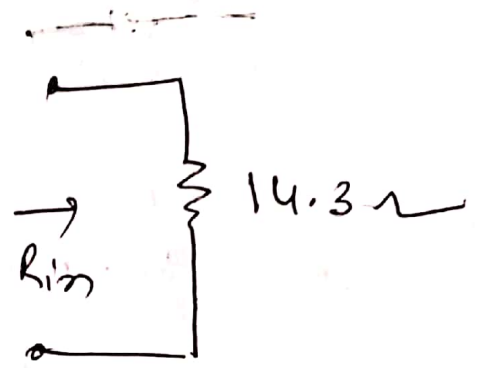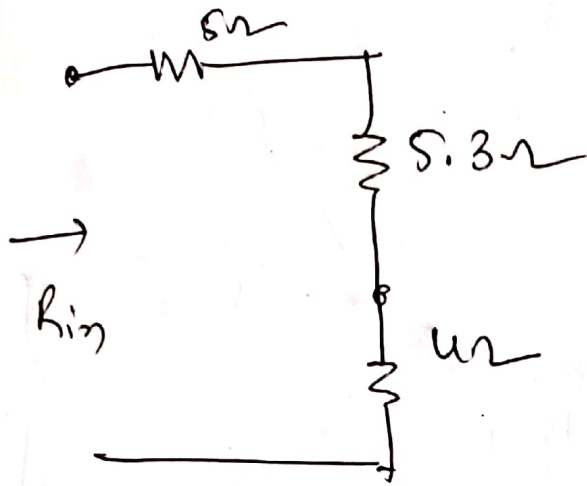

$$R_{in} = 14.3\Omega$$

(or)

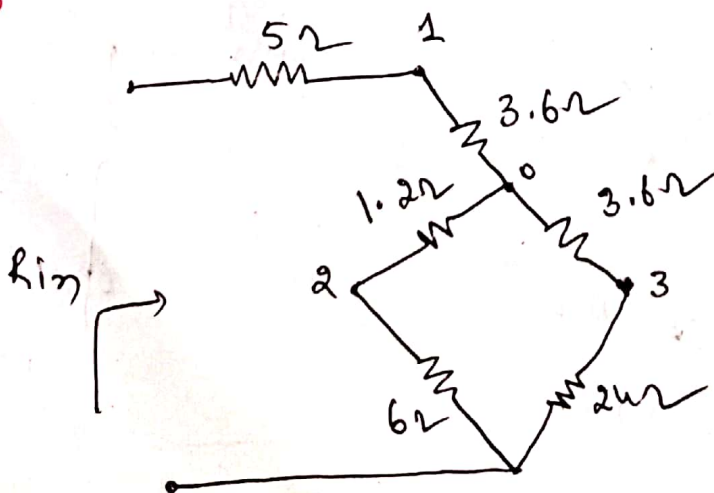
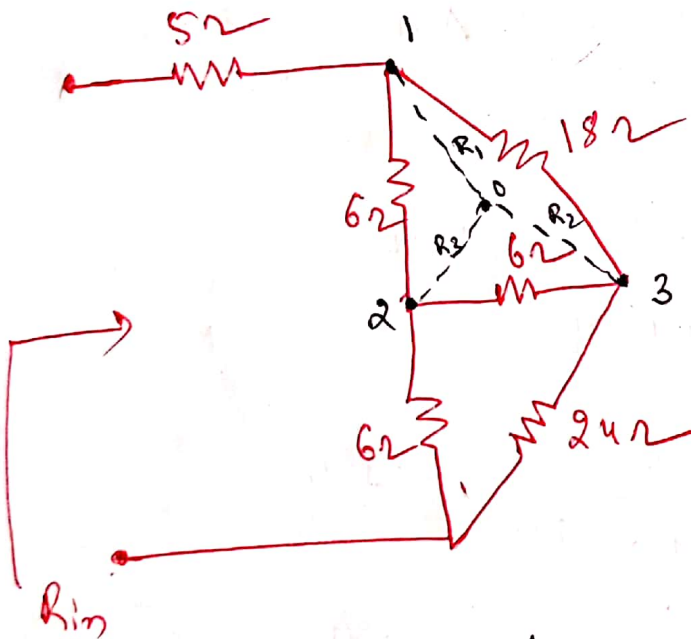


$$R_1 = \frac{6 \times 18}{6 + 18 + 6}$$


$$R_1 = 3.6\Omega$$

$$R_2 = \frac{18 \times 6}{6 + 18 + 6} = 3.6 \Omega$$

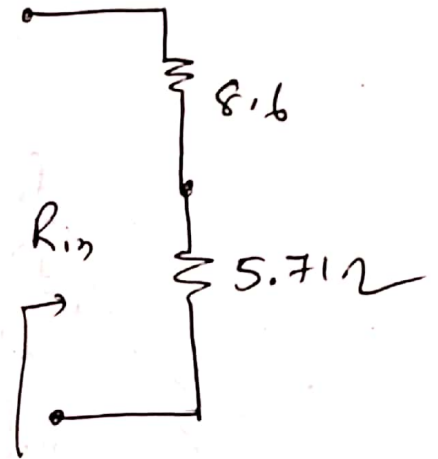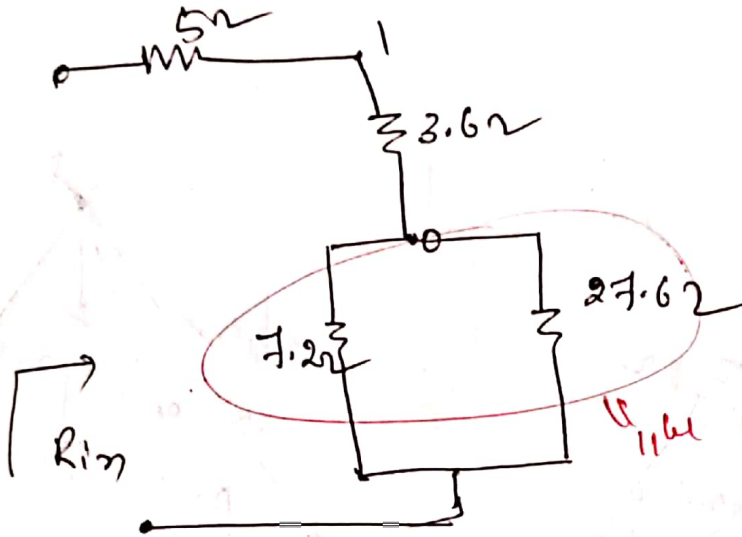
$$R_3 = \frac{6 \times 6}{6 + 18 + 6} = 1.2 \Omega$$




$$R_{in} = 14.31 \Omega$$

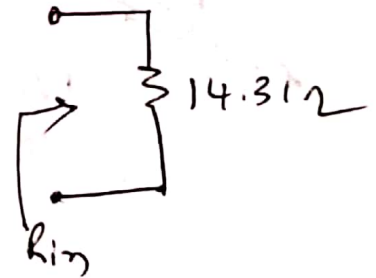

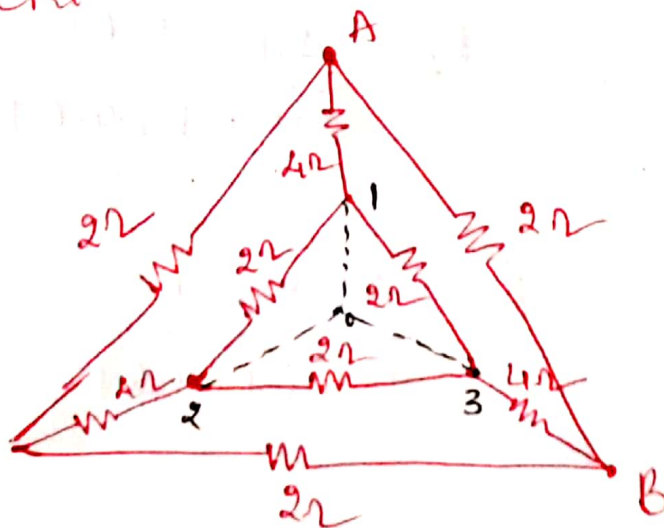2) Find the equivalent resistance b/w A & B for the ckt below.








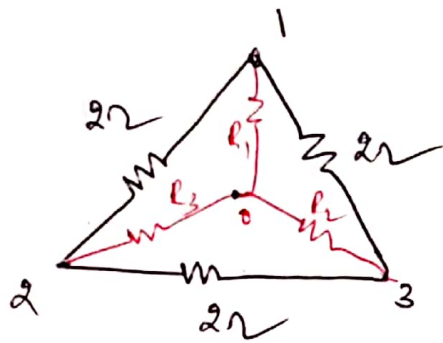

Inner delta into star

$$R_1 = \frac{2 \times 2}{2 + 2 + 2} = 0.67 \Omega$$


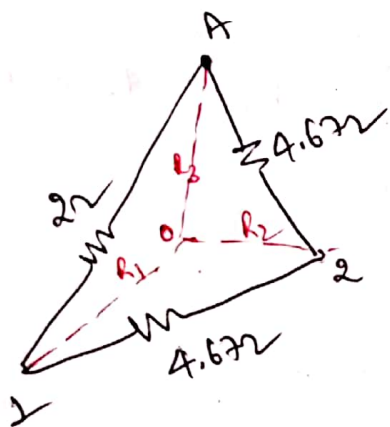
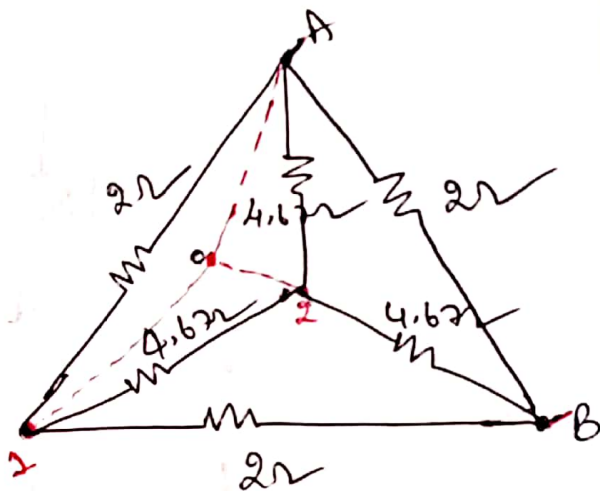
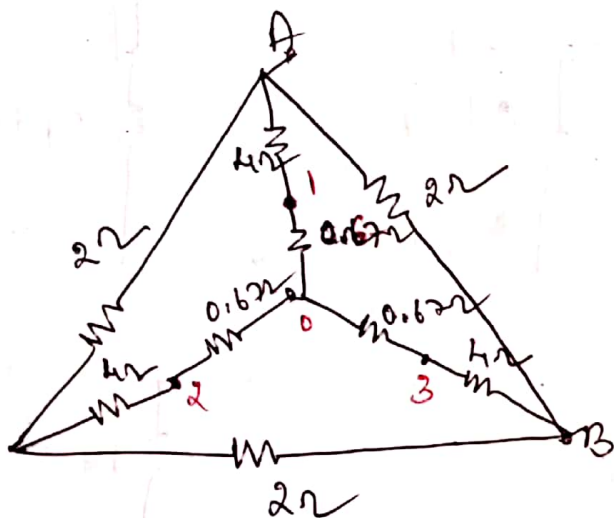
$$\text{w} \quad R_2 = R_3 = 0.67 \Omega$$



$$R_1 = \frac{2 \times 4.67}{2 + 4.67 + 4.67} = 0.8242$$




$$R_2 = \frac{4.67 \times 4.67}{2 + 4.67 + 4.67} = 1.923 \Omega$$

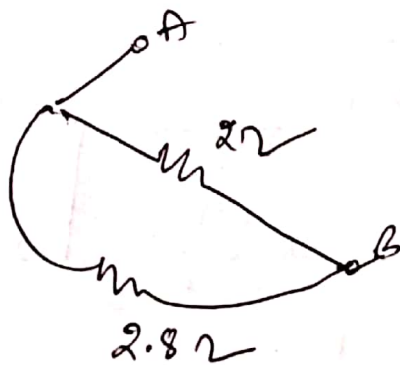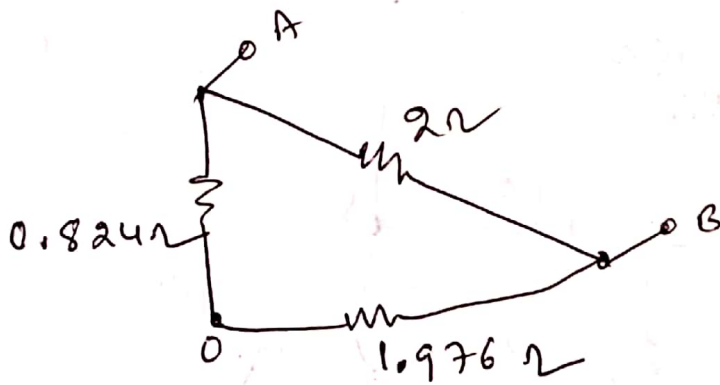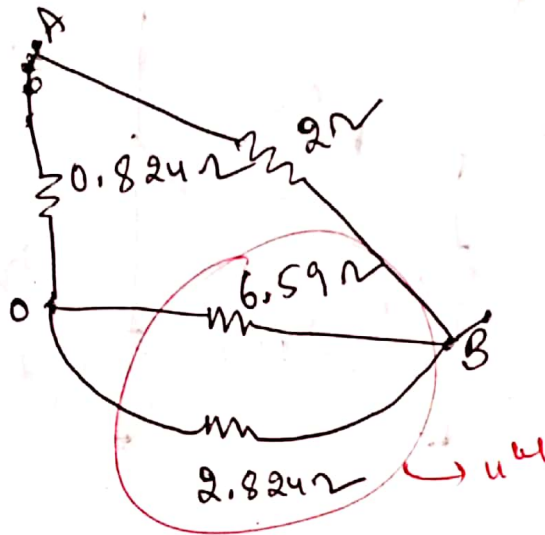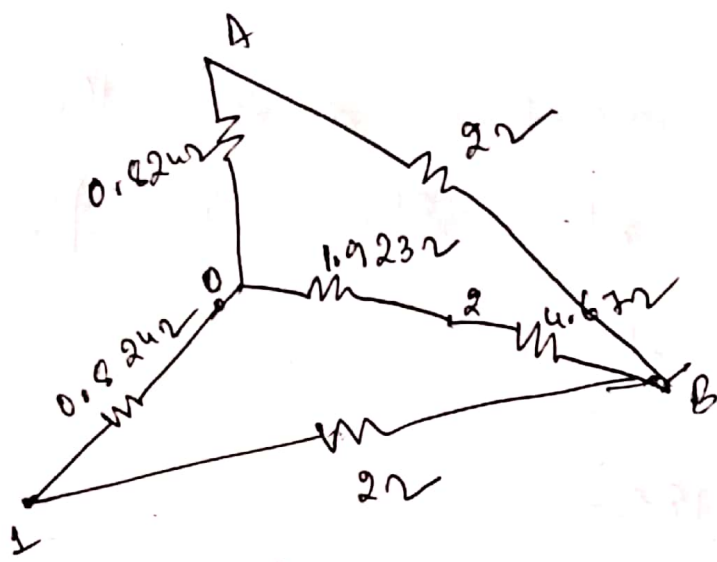
$$R_3 = \frac{2 \times 4.67}{2 + 4.67 + 4.67} = 0.8242$$



$$R_{AB} = 1.167\Omega$$

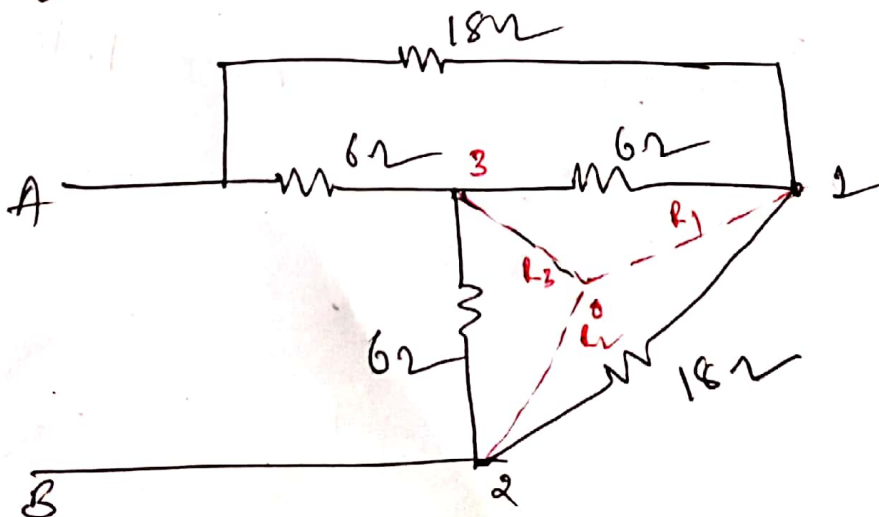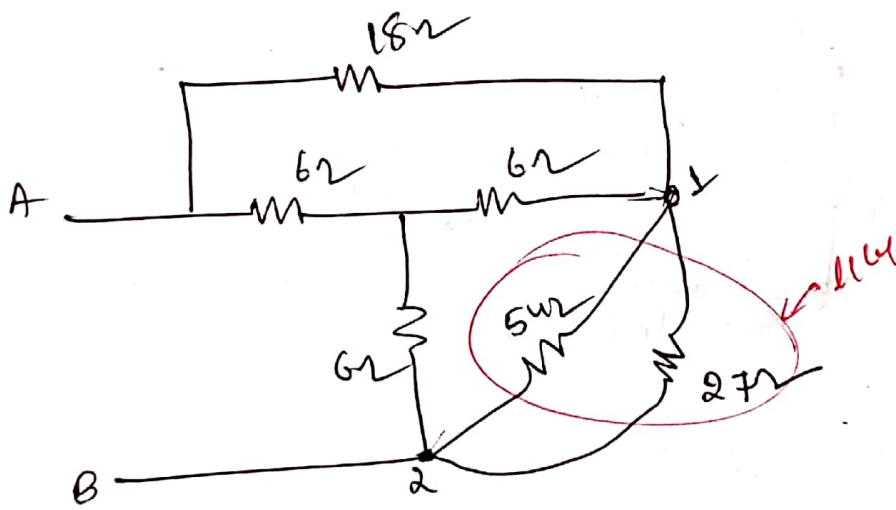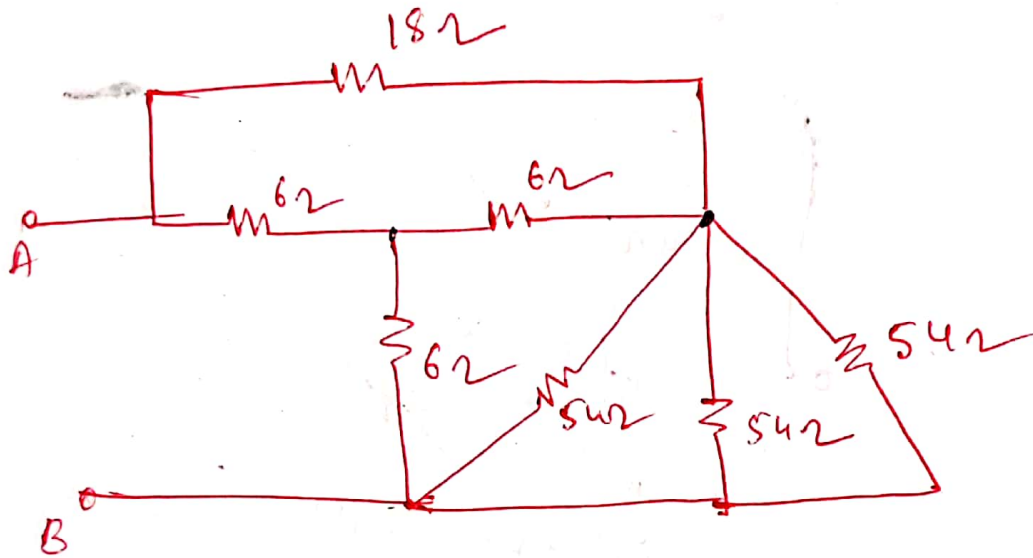3) Compute the resistance across the terminals A & B of the n/w shown in fig using  $\Delta$ - $\gamma$  transformation





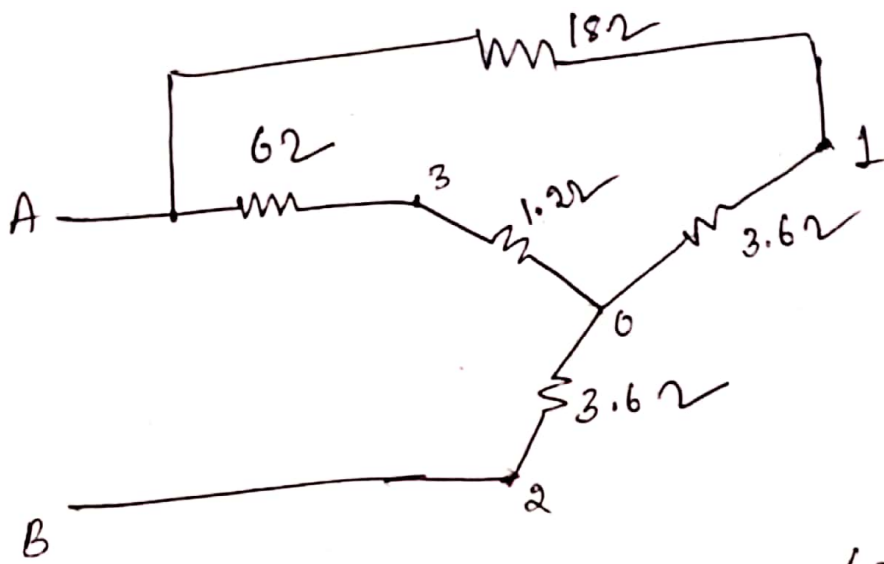

$$R_1 = \frac{6 \times 18}{6 + 18 + 6} = 3.6 \Omega$$




$$R_2 = \frac{6 \times 18}{6 + 18 + 6} = 3.6 \Omega$$
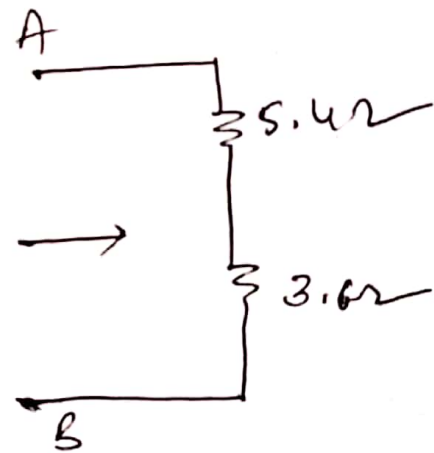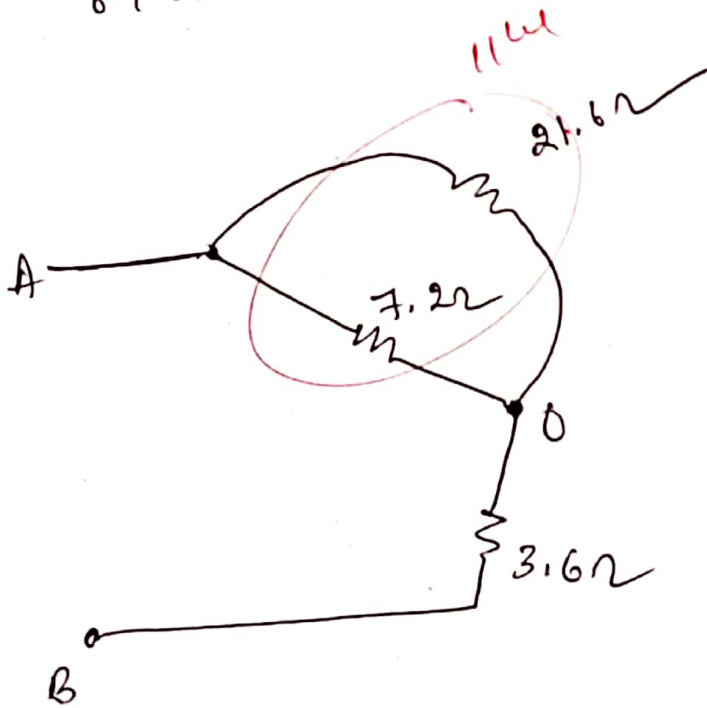
$$R_3 = \frac{6 \times 6}{6 + 18 + 6} = 1.2 \Omega$$



$$R_{AB} = 9 \Omega$$

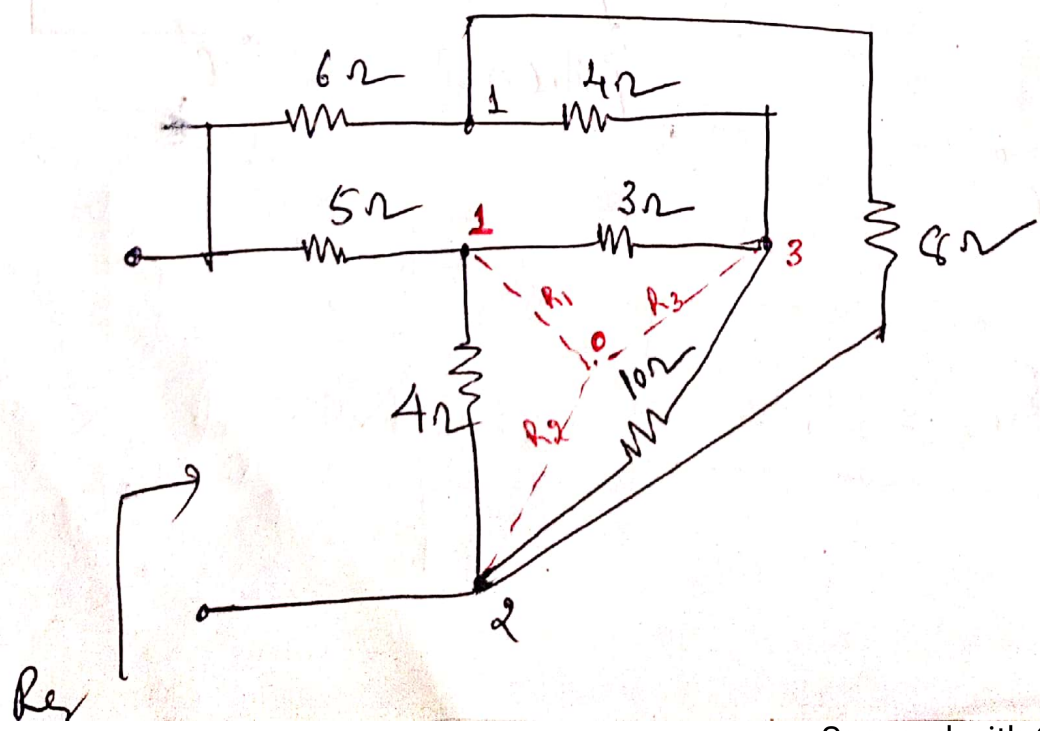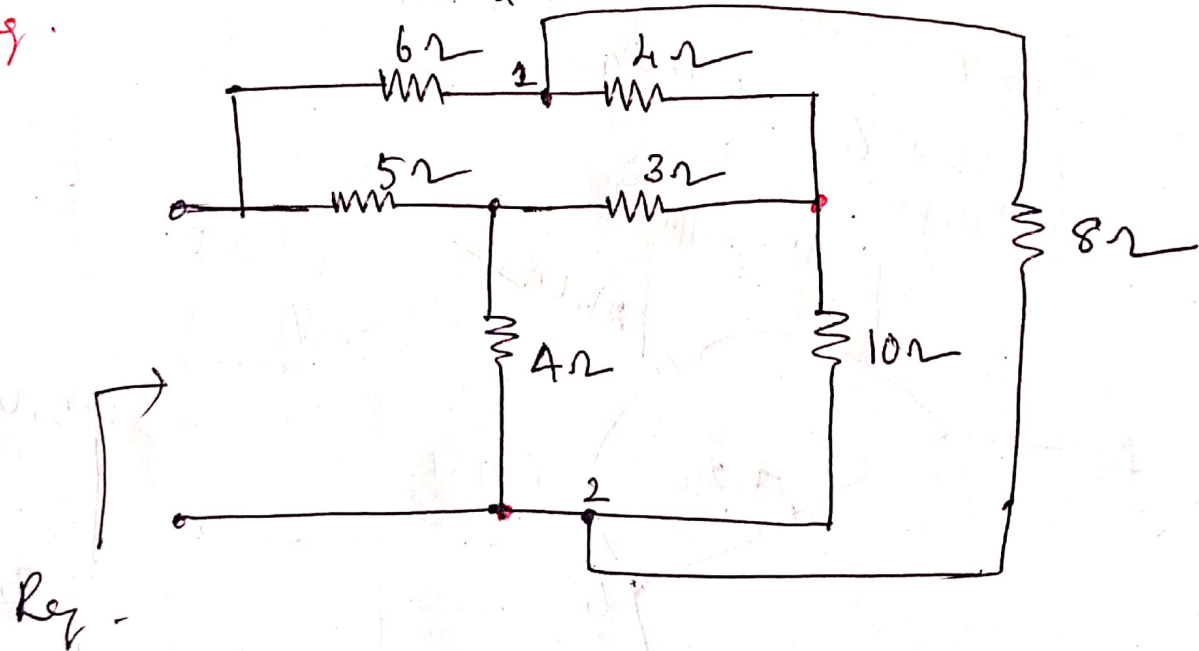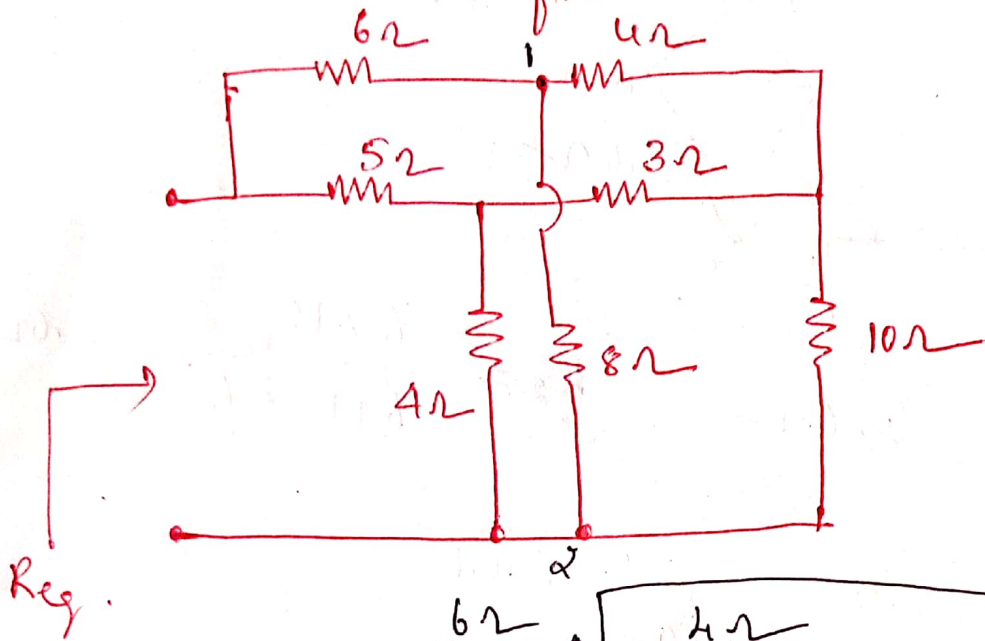4) In the n/w shown below, find  $R_{eq}$  using Star delta transformation.









$$R_1 = \frac{4 \times 3}{4 + 3 + 10} = 0.706 \Omega$$

$$R_2 = \frac{4 \times 10}{4 + 10 + 3}$$

$$R_2 = 2.353$$

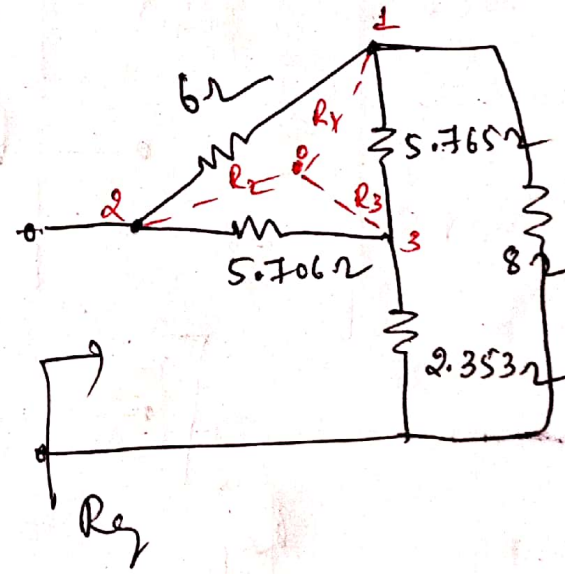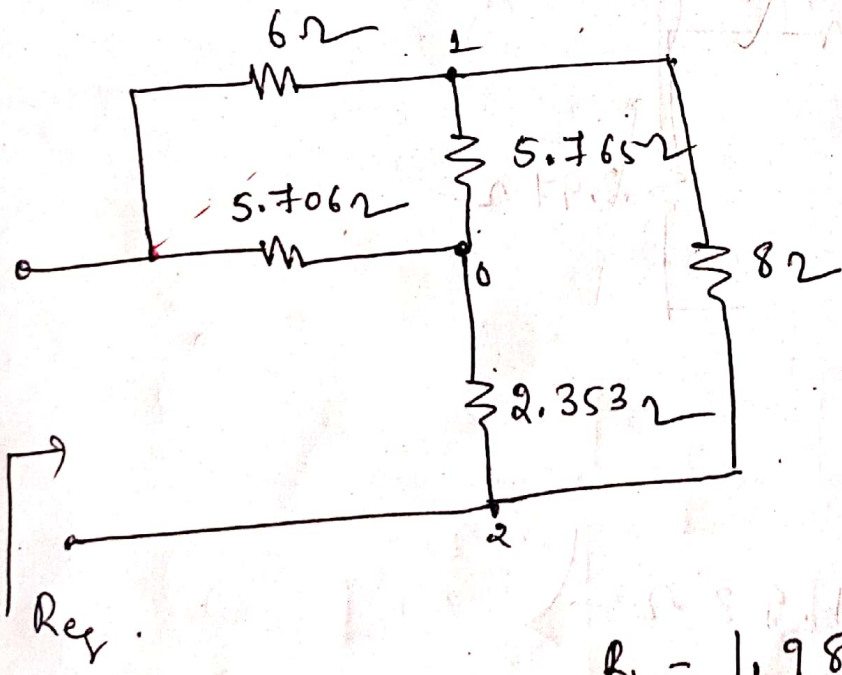
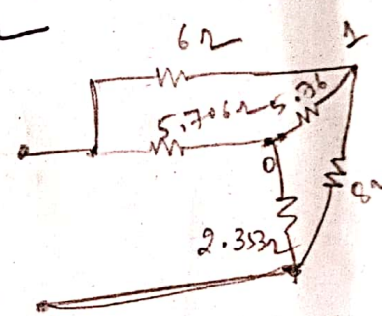
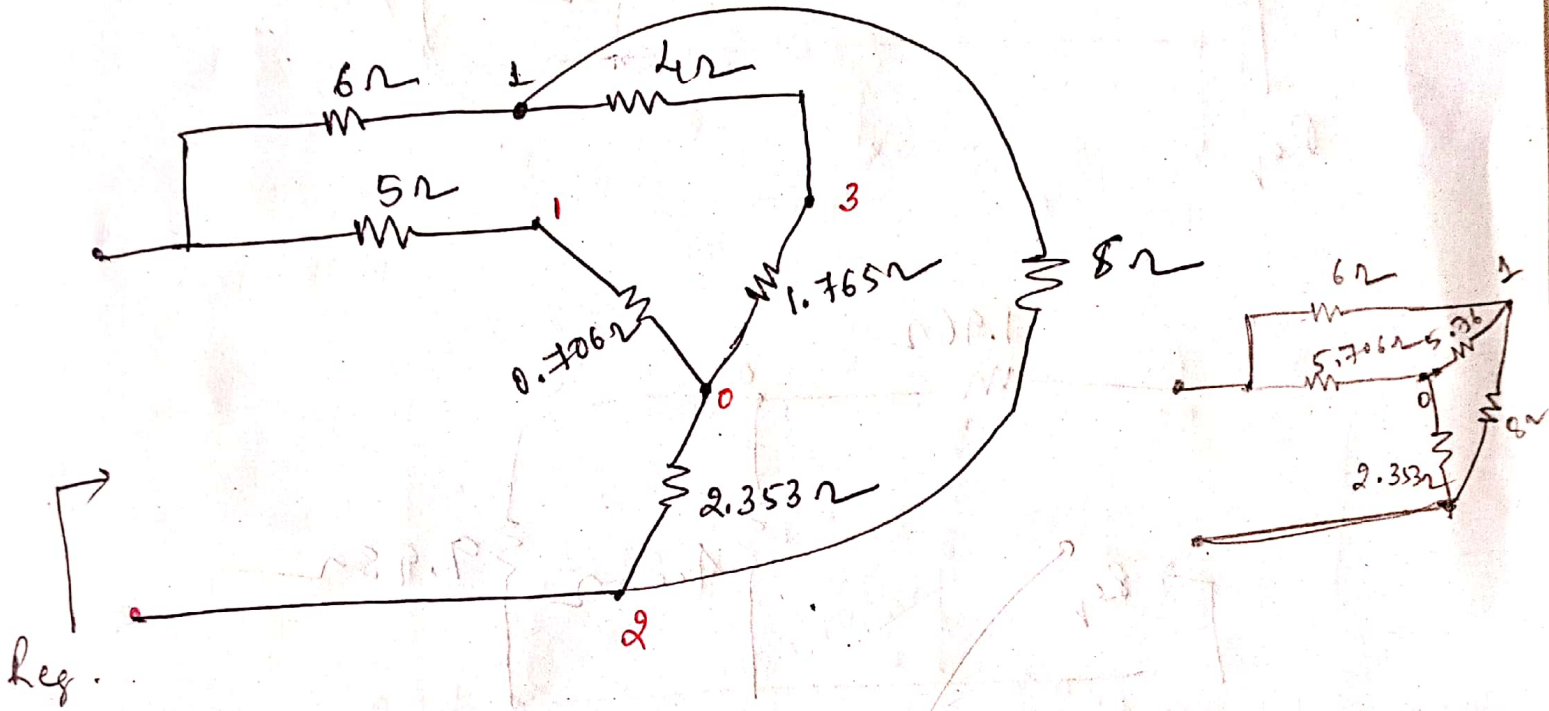
$$R_3 = \frac{3 \times 10}{3 + 4 + 10} = 1.765 \Omega$$



$$R_1 = 1.98 \Omega$$



$$R_3 = 1.88 \Omega$$

$$R_2 = 1.96 \Omega$$

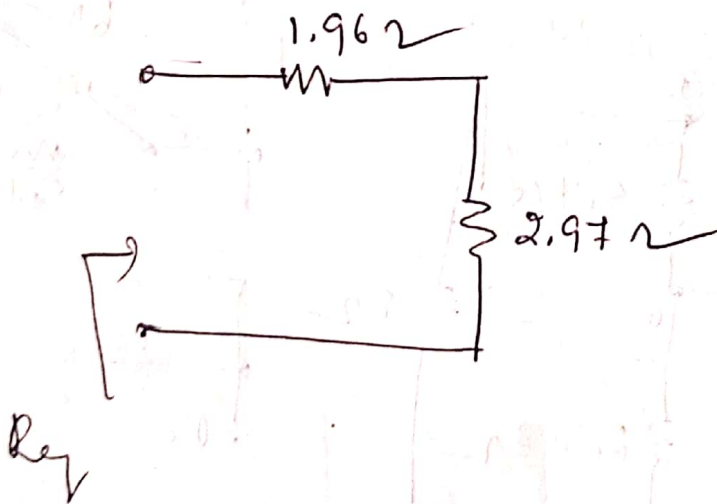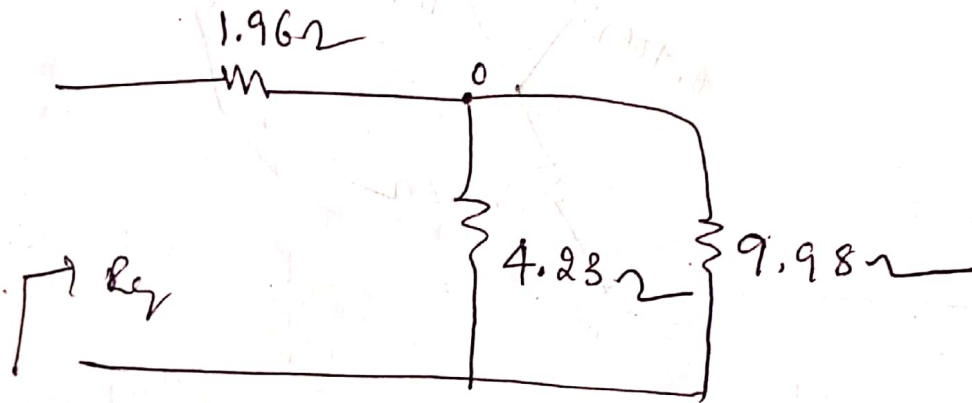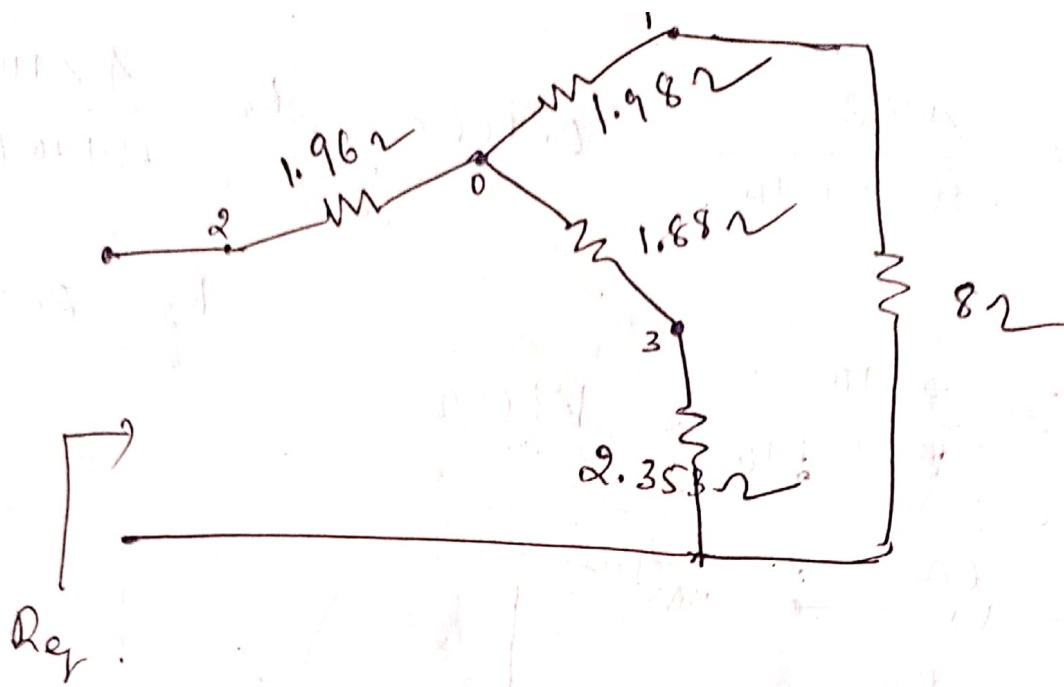

$$R_{eq} = 4.93 \Omega$$

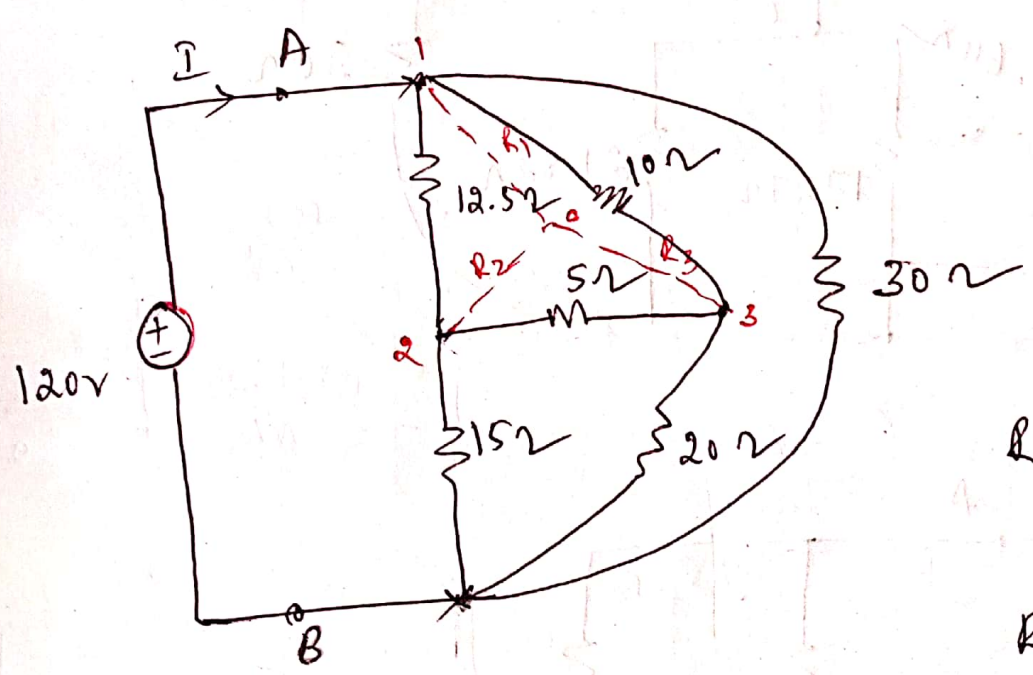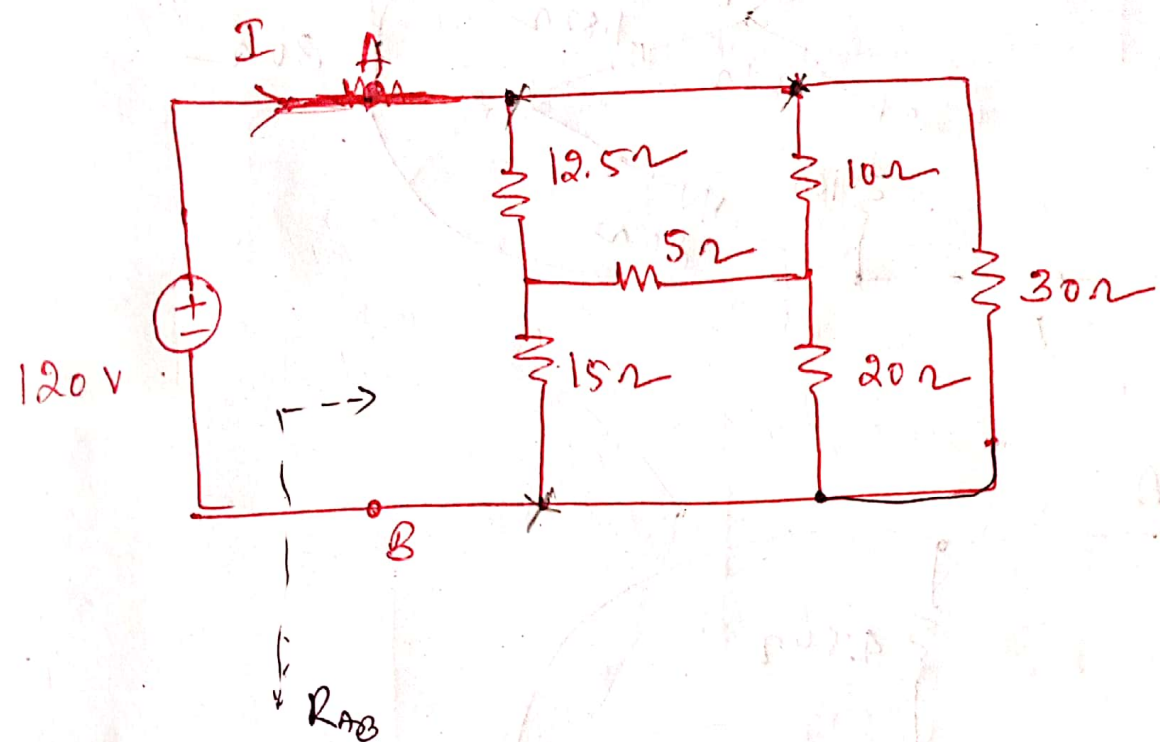5) Obtain equivalent resistance  $R_{AB}$  for the given ckt & find  $I$ .



$$R_1 = \frac{12.5 \times 10}{12.5 + 10 + 5}$$

$$R_1 = 4.54\Omega$$




$$R_2 = \frac{12.5 \times 5}{12.5 + 10 + 5}$$


$$R_2 = 2.273\Omega$$

$$R_3 = \frac{5 \times 10}{12.5 + 10 + 5}$$

$$R_3 = 1.82\Omega$$



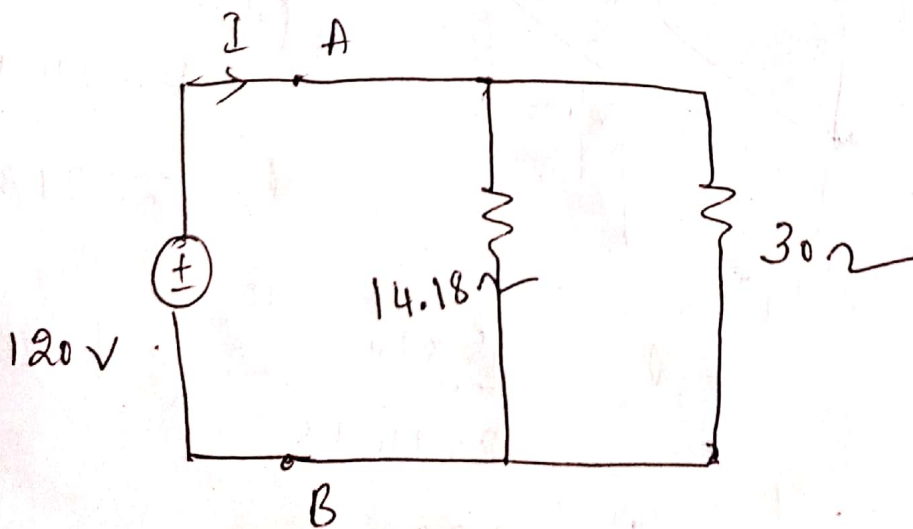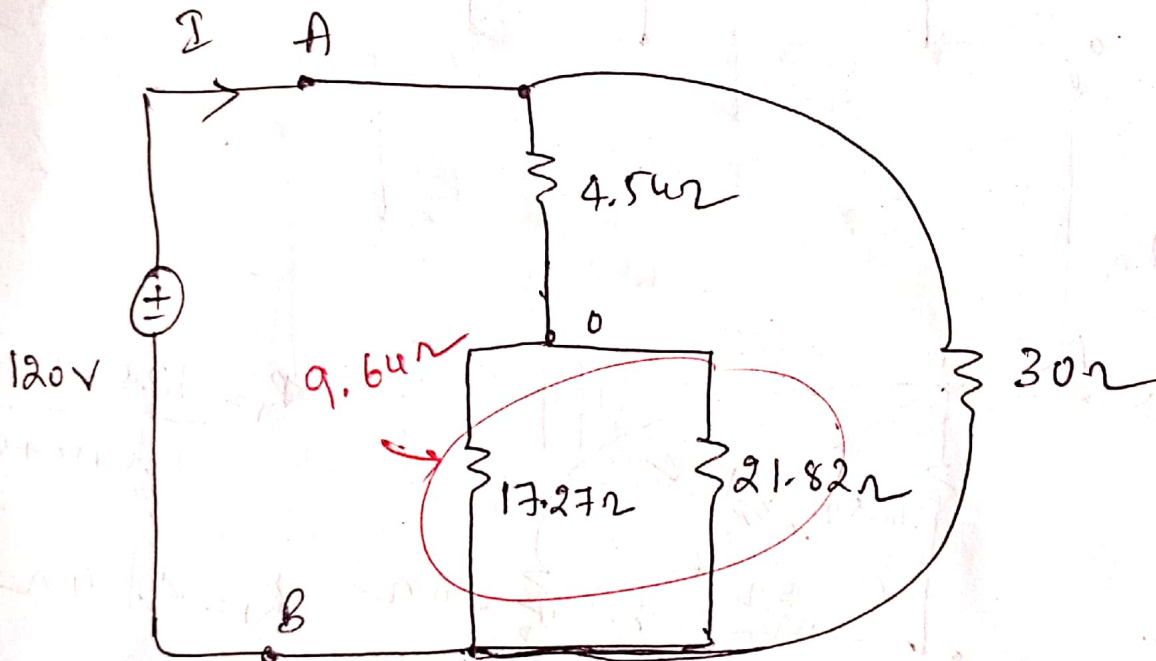
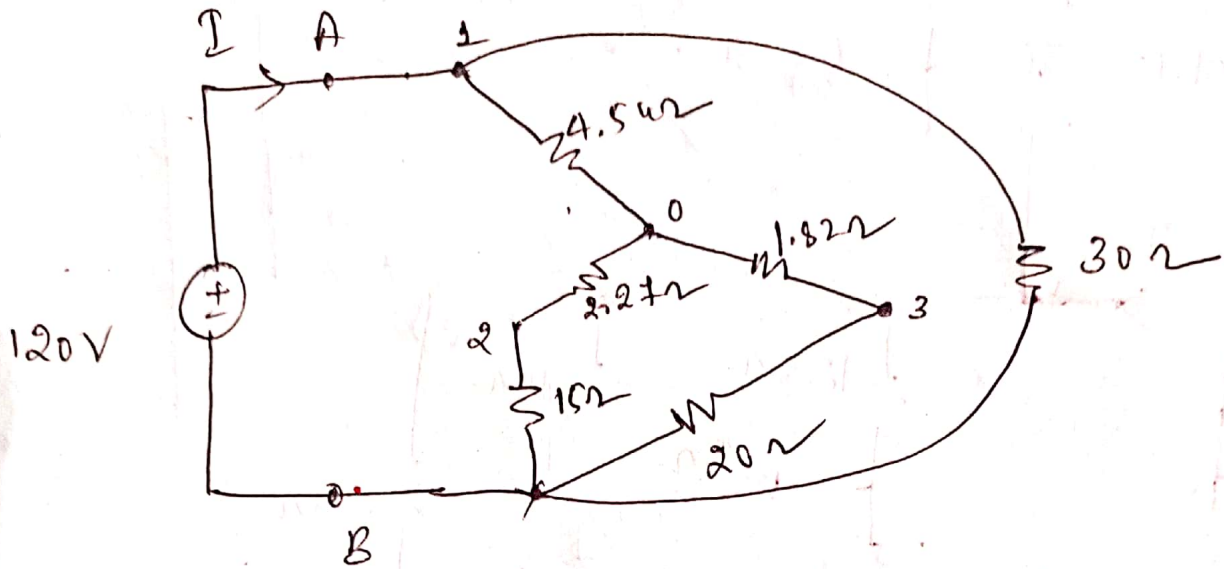




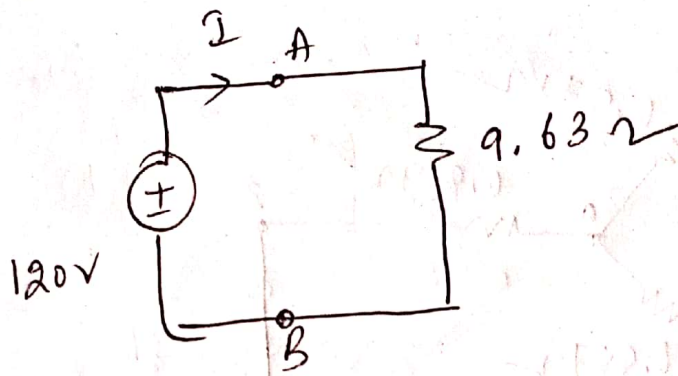


$$R_{AB} = 9.63 \Omega$$

$$I = \frac{V}{R} = \frac{120}{9.63} = 12.46 \text{ Amp.}$$

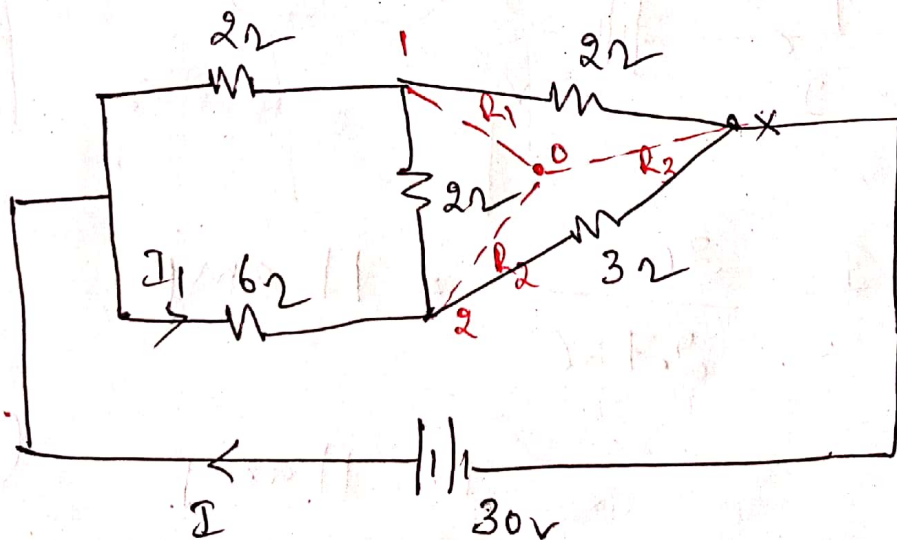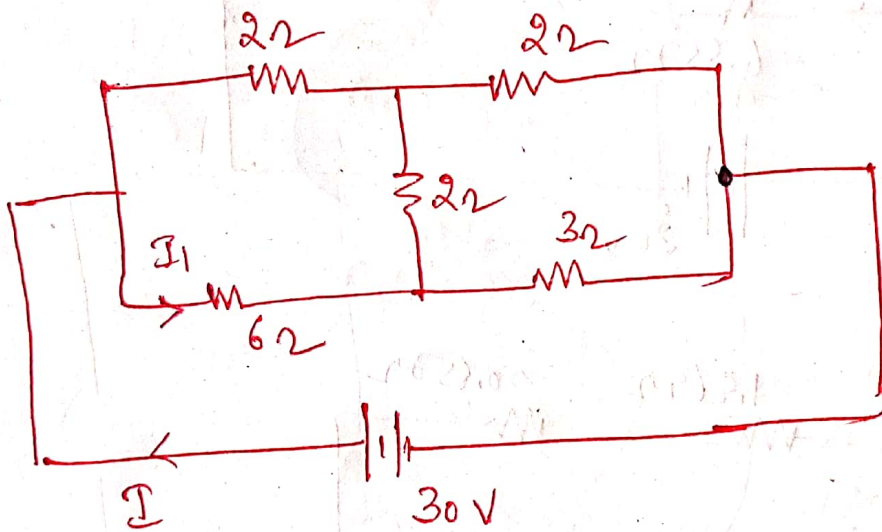6) Find  $I$  &  $I_1$  in the n/w shown using  $\Delta$ - $Y$  transformation



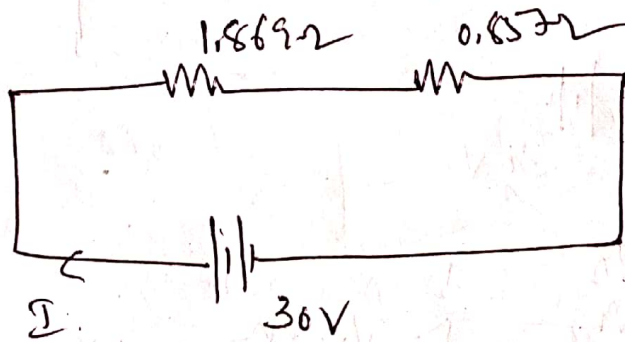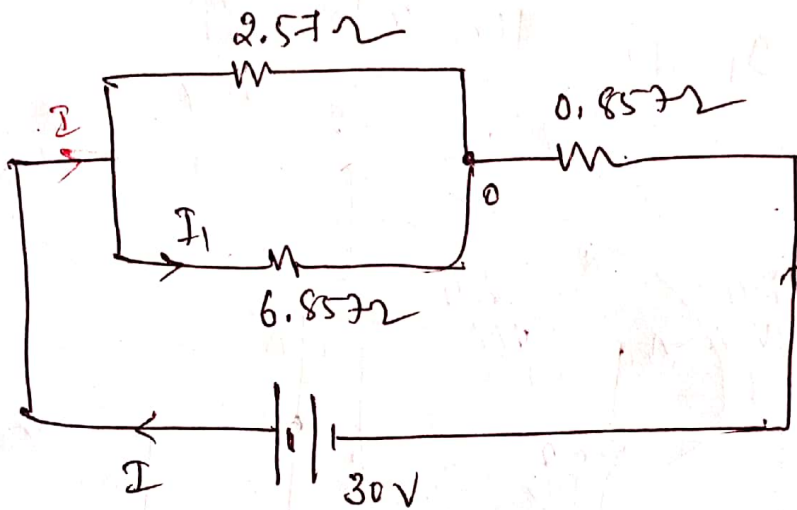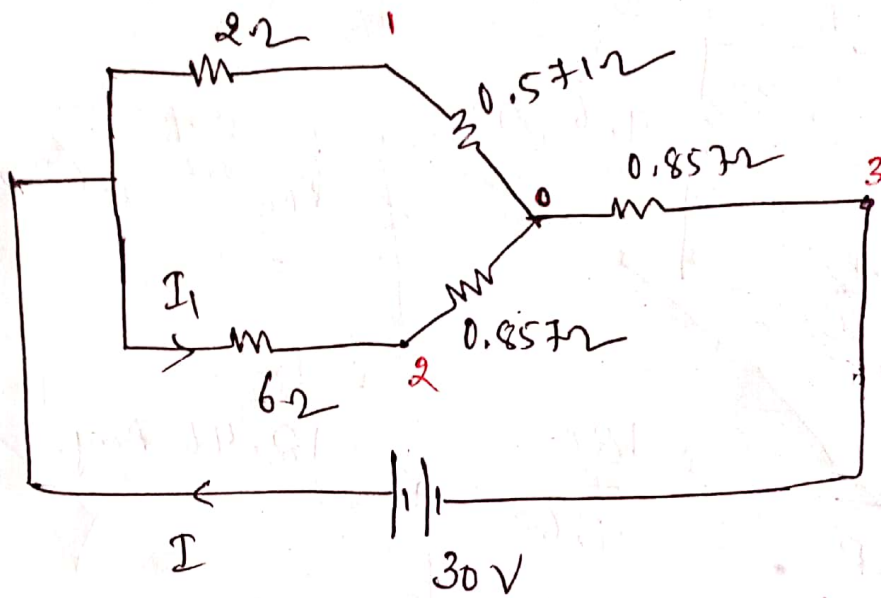

$$I = \frac{30}{2.726} = 11 \text{ amp}$$

$I = 11 \text{ amp}$








$$I_1 = \frac{I \times 2.572}{2.57 + 6.8572}$$



$$I_1 = \frac{11 \times 2.57}{2.57 + 6.87}$$

$$I_1 = 3 \text{ Amp}$$

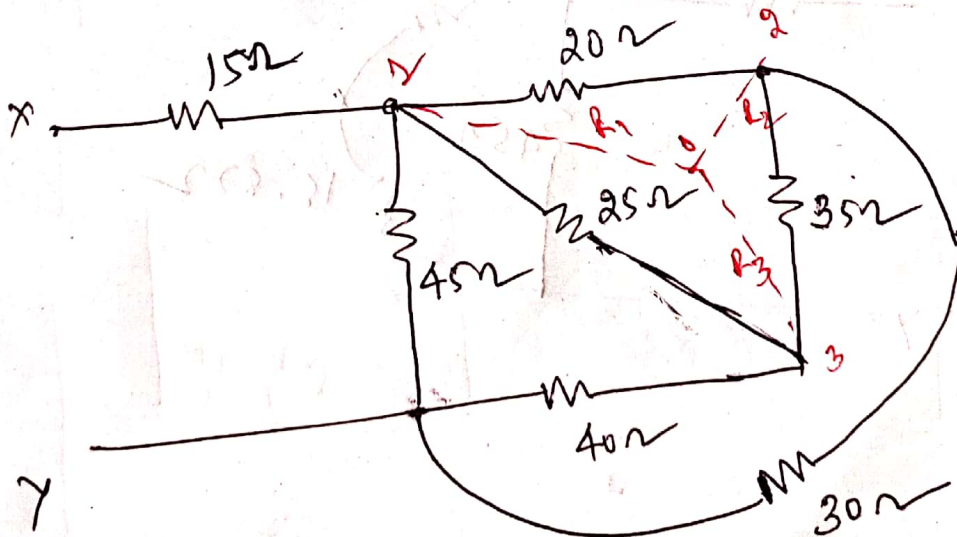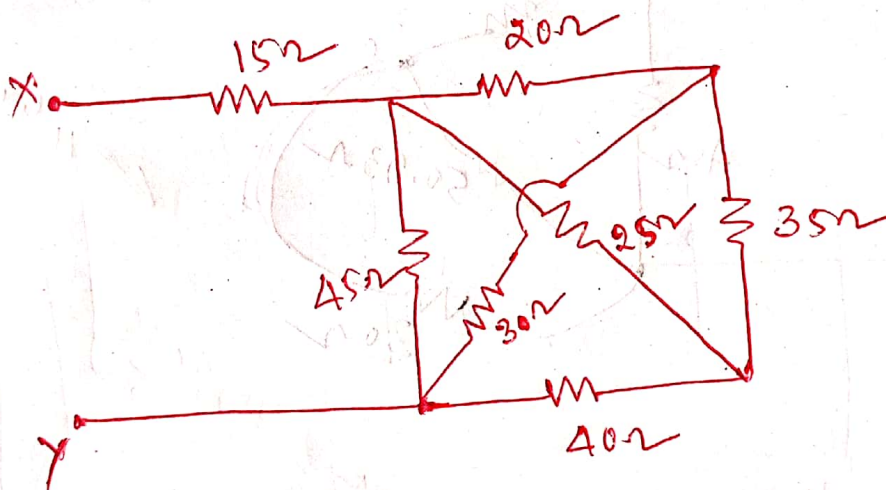
\*) Find the resistance b/w the terminals x & y



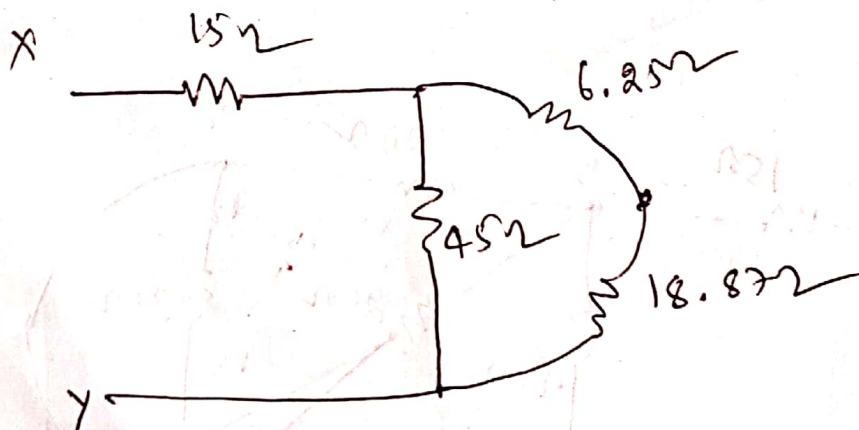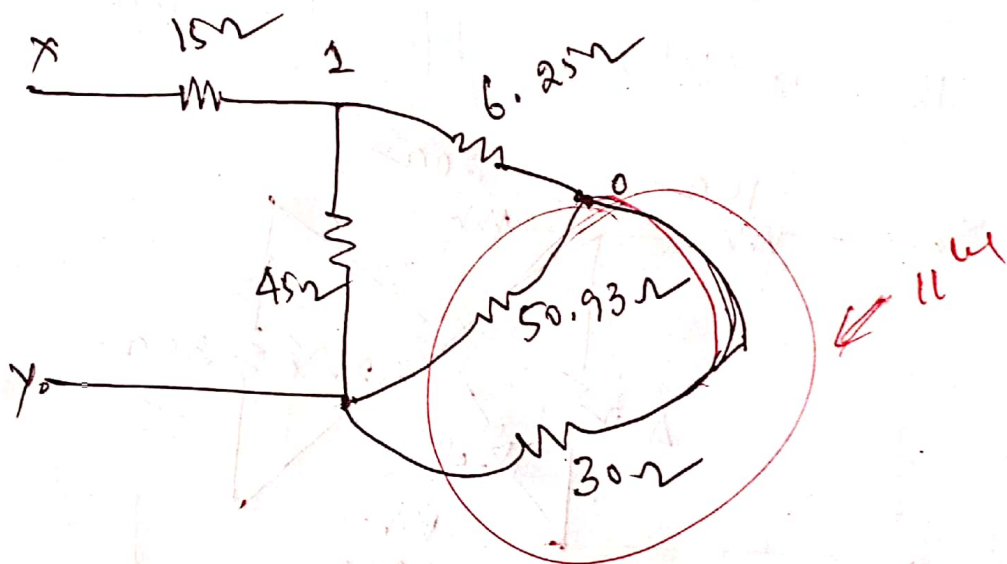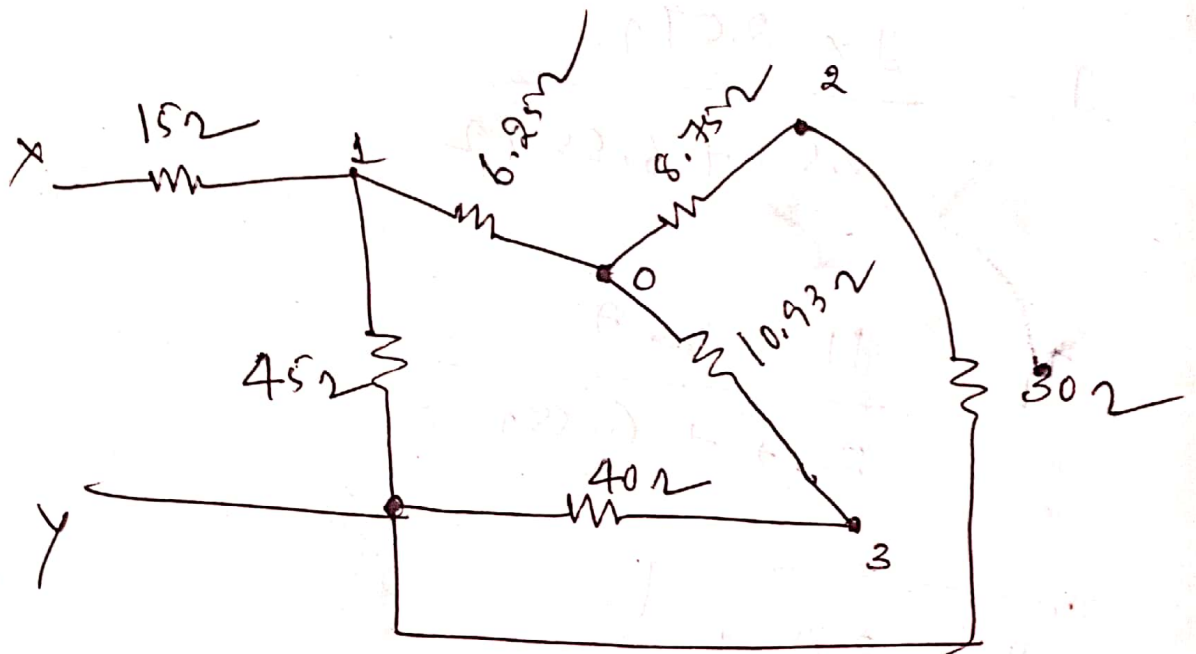

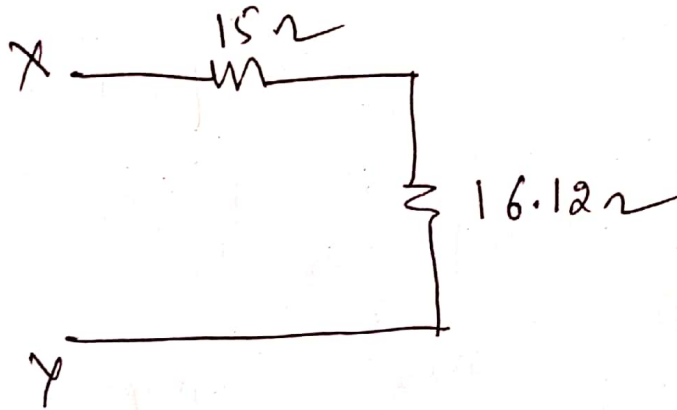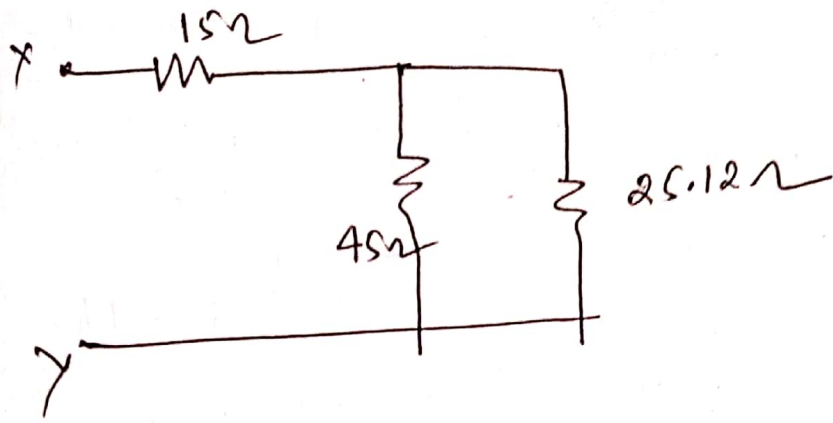


$$R_{xy} = 31.12\ \Omega$$

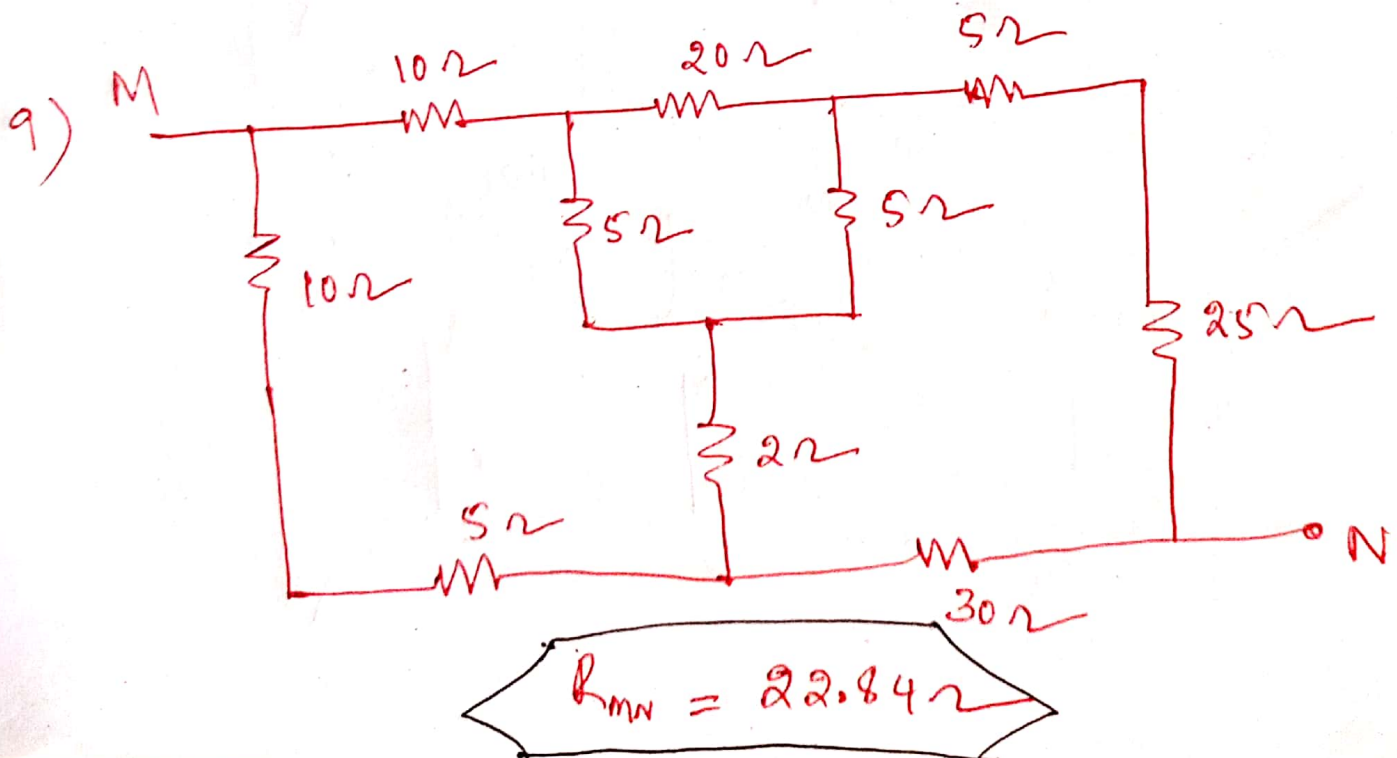

$$R_{MN} = 22.84\ \Omega$$

# Mesh Analysis :- (loop or Current Analysis)

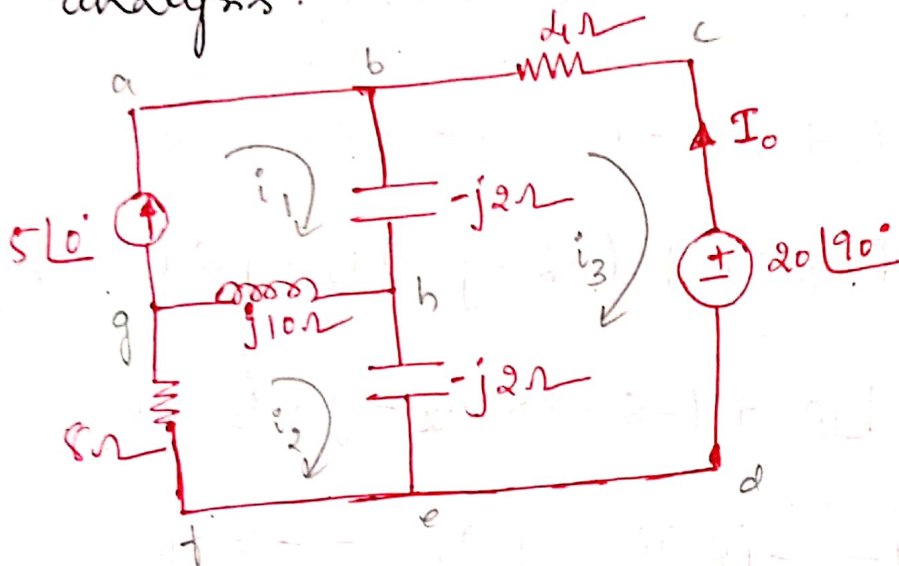1) Determine the current  $I_0$  in the circuit using mesh analysis.



$$j = 1\angle 90^\circ$$

$$-j = 1\angle -90^\circ$$

$$j2 = 2\angle 90^\circ$$

From the mesh abhga

$$i_1 = 5\angle 0^\circ \quad \text{--- ①}$$

→ KVL to the mesh bcdehb

$$-4i_3 - 20\angle 90^\circ + j2(i_3 - i_2) + j2(i_3 - i_1) = 0$$

$$-4i_3 - 20\angle 90^\circ + j2i_3 - j2i_2 + j2i_3 - j2i_1 = 0$$

$$-j2i_2 + (-4 + j4i_3) - 20\angle 90^\circ - j2(5\angle 0^\circ) = 0$$

$$-j2i_2 + (-4 + j4i_3) - 20\angle 90^\circ - 10\angle 90^\circ = 0$$

$$-j2i_2 + (-4 + j4i_3) = 30\angle 90^\circ \quad \text{--- ②}$$



→ KVL to ghefg

$$-j10(i_2 - i_1) + j2(i_2 - i_3) - 8i_2 = 0$$

$$-j10i_2 + j10i_1 + j2i_2 - j2i_3 - 8i_2 = 0$$

$$j10i_1 + (-8 - j8)i_2 - j2i_3 = 0$$

$$j10(5\angle 0^\circ) + (-8 - j8)i_2 - j2i_3 = 0$$

$$50\angle 90^\circ + (-8 - j8)i_2 - j2i_3 = 0$$

soj

$$(-8 - j8)i_2 - j2i_3 = -50j$$

$$(-8 - j8)i_2 - j2i_3 = 50\angle -90^\circ \quad \text{--- (3)}$$

matrix form

$$\begin{bmatrix} -j2 & -4+j4 \\ -8-j8 & -j2 \end{bmatrix} \begin{bmatrix} i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 30\angle 90^\circ \\ 50\angle 90^\circ \end{bmatrix}$$

$$\Delta = \begin{vmatrix} -j2 & -4+j4 \\ -8-j8 & -j2 \end{vmatrix}$$

$$\Delta = -4 - (-8-j8)(-4+j4)$$



$$\Delta = -4 - (+32 + \cancel{32j} - \cancel{32j} + 32)$$

$$\Delta = -4 - 64 = -68$$

$$\Delta = -68$$

$$\Delta_2 = \begin{vmatrix} -j2 & 30j \\ -8-j8 & -50j \end{vmatrix}$$

$$\Delta_2 = -100 - [(-8-j8)(30j)]$$

$$\Delta_2 = -100 - [-240j + 240]$$

$$\Delta_2 = -340 + j240$$

$$= \cancel{16.17}$$

$$I_3 = \frac{\Delta_2}{\Delta} = \frac{-340 + j240}{-68}$$

$$I_3 = 5 - j3.53$$


$$I_3 = 6.12 \angle -35.21^\circ \text{ Amp}$$

$$I_0 = 6.12 \angle 44.75^\circ \text{ A}$$

From the  
fig

$$I_0 = -I_3 = -6.12 \angle 35.21^\circ \text{ Amp}$$

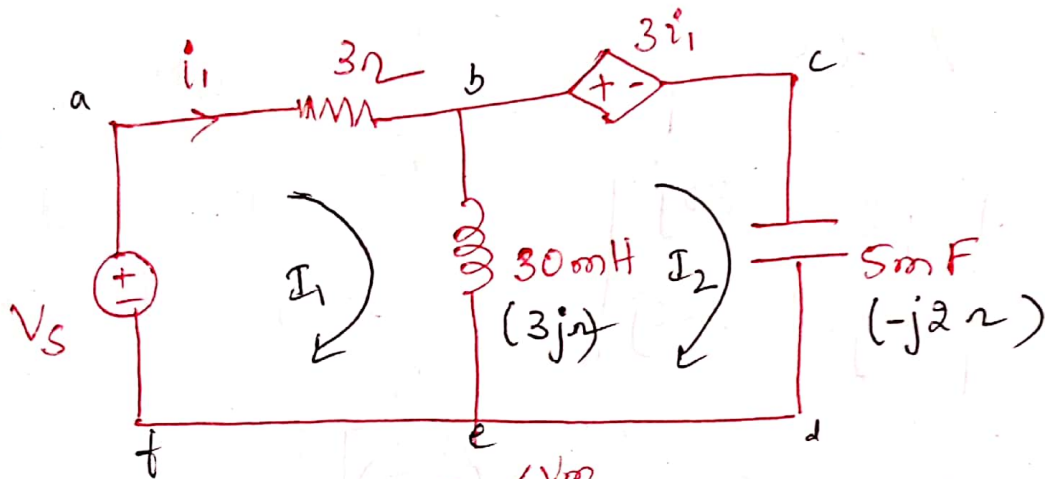2) Find the Steady State Sinusoidal current  $i_1$  for the circuit when  $V_s = 10\sqrt{2} \cos(100t + 45^\circ)$



Given  $V_s = 10\sqrt{2} \cos(100t + 45^\circ)$

$$V_s = \frac{V_m}{\sqrt{2}} \angle 45^\circ$$

$$= \frac{10\sqrt{2}}{\sqrt{2}} \angle 45^\circ = 10 \angle 45^\circ \text{ volts}$$

$$\omega t = 100t$$

$$\omega = 100$$

$$X_L = 2\pi fL$$

$$= \omega L$$

$$= 100 \times 30 \text{ mH}$$

$$= 3 \Omega$$

$$X_L = j3 \Omega$$

$$X_C = \frac{1}{2\pi fC}$$

$$= \frac{1}{\omega C}$$

$$X_C = \frac{1}{100 \times 5 \times 10^{-3}}$$

$$X_C = -j2 \Omega$$

From the figure

$$i_1 = I_1$$

→ KVL to mesh abefa

$$-3I_1 - j3(I_1 - I_2) + 10 \angle 45^\circ = 0$$

$$-3I_1 - 3jI_1 + 3jI_2 = -10 \angle 45^\circ$$

$$(-3 - 3j)I_1 + 3jI_2 = -10 \angle 45^\circ \quad \text{--- (1)}$$

→ KVL to mesh bcdeb

$$-3 \textcircled{i_1} + 2jI_2 - 3j(I_2 - I_1) = 0$$

$$-3I_1 + 2jI_2 - 3jI_2 + 3jI_1 = 0$$

$$(-3 + 3j)I_1 - jI_2 = 0 \quad \text{--- (2)}$$

WKT,

$$\begin{bmatrix} -3 - 3j & 3j \\ -3 + 3j & -j \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} -10 \angle 45^\circ \\ 0 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} -3 - 3j & 3j \\ -3 + 3j & -j \end{vmatrix}$$

$$= 3j - 3 - (3j)(-3 + 3j)$$

$$= 3j - 3 + 9j + 9 = 6 + j12$$

$$\Delta_1 = \begin{vmatrix} -10 \angle 45^\circ & 3j \\ 0 & 1 \angle -90^\circ \end{vmatrix}$$


$$\Delta_1 = -10 \angle -45^\circ$$

$$\therefore I_1 = \frac{\Delta_1}{\Delta} = \frac{-10 \angle -45^\circ}{6 + 12j} = 0.745 \angle 71.57^\circ$$

~~Aug~~ July-6  
July-07

3) In the circuit shown determine  $V_2$  which results in '0' (Zero) current through  $4\Omega$  resistor

Use mesh analysis

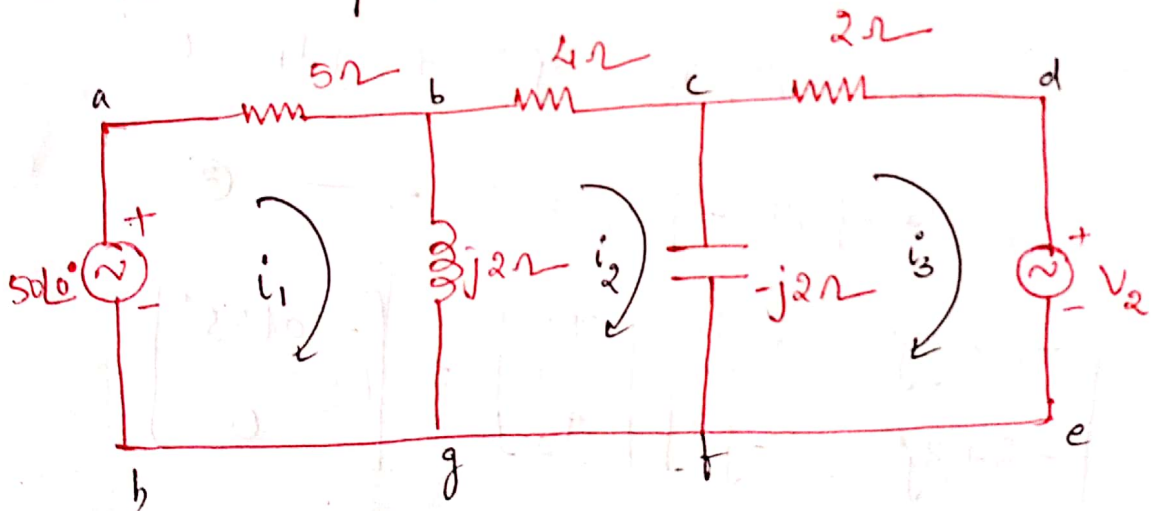

Given, current through  $4\Omega$  is zero

$$I_2 = i_2 = 0$$

→ KVL to the mesh abgha

$$-5i_1 - j2(i_1 - i_2) + 50 \angle 0^\circ = 0$$



$$-5i_1 - j2i_1 = -50 \angle 0^\circ$$

$$\neq (5 + j2)i_1 = 50 \angle 0^\circ$$

$$i_1 = \frac{50 \angle 0^\circ}{5 + j2} = \underline{\underline{9.28 \angle -21.81^\circ \text{ amp}}}$$

→ KVL to mesh b c f g b

$$-4i_2 + j2(i_2 - i_3) - j2(i_2 - i_1) = 0$$

$$-4i_2 - j2i_3 + j2i_1 = 0$$

$$j2i_1 = j2i_3$$

$$i_3 = i_1 = \underline{\underline{9.28 \angle -21.81^\circ \text{ amp}}}$$

→ KVL to mesh c d e f c

$$-2i_3 - V_2 + j2(i_3 - i_2) = 0$$

$$-2i_3 - V_2 + j2i_3 = 0$$


$$V_2 = (-2 + j2)i_3$$

$$V_2 = 2.82 \angle 35^\circ \times 9.28 \angle -21.81^\circ$$

$$\boxed{V_2 = 26.16 \angle 13.19^\circ \text{ volts}}$$

mesh analysis

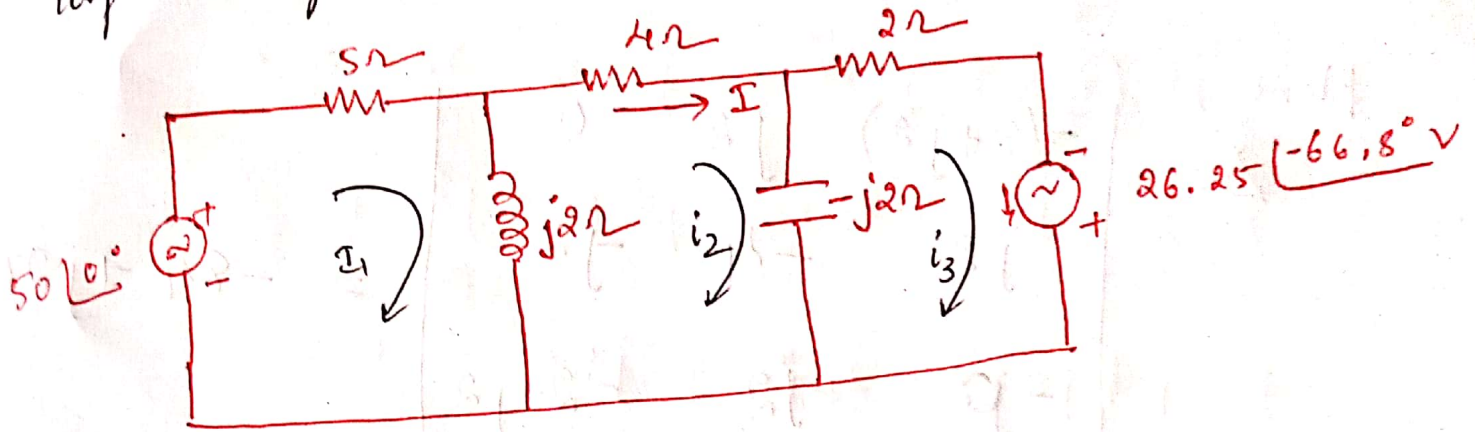4) In the circuit shown below, find  $I$  through loop analysis.



→ KVL to loop 1

$$-5i_1 - j2(i_1 - i_2) + 50\angle 0^\circ = 0$$

$$-5i_1 - j2i_1 + j2i_2 = -50\angle 0^\circ$$

$$(-5 - j2)i_1 + j2i_2 = -50\angle 0^\circ \quad \text{--- (1)}$$

→ KVL to loop 2

$$-4i_2 + j2(i_2 - i_3) - j2(i_2 - i_1) = 0$$

$$-4i_2 + \cancel{j2i_2} - j2i_3 - \cancel{j2i_2} + j2i_1 = 0$$

$$+j2i_1 - 4i_2 - j2i_3 = 0 \quad \text{--- (2)}$$

→ KVL to loop 3

$$-2i_3 + 26.25\angle -66.8^\circ + j2(i_3 - i_2) = 0$$

$$-2i_3 + 26.25\angle -66.8^\circ + j2i_3 - j2i_2 = 0$$

$$-j2i_2 + (-2 + j2)i_3 = -26.25 \angle -66.8^\circ \quad \text{--- (3)}$$

Here

$$\Delta = \begin{vmatrix} -5-j2 & j2 & 0 \\ j2 & -4 & j2 \\ 0 & -j2 & -2+j2 \end{vmatrix} = -84 + j24$$

From the figure  $I = I_2 = \frac{\Delta_2}{\Delta}$

$$\therefore \Delta_2 = \begin{vmatrix} -5-j2 & 50 \angle 0^\circ & 0 \\ j2 & 0 & -j2 \\ 0 & -26.25 \angle -66.8^\circ & -2+j2 \end{vmatrix}$$

$2 \angle -90^\circ$

$$\Delta_2 = (-5-j2) \left[ 0 + 52.5 \angle -156.8^\circ \right] + 50 \angle 0^\circ \left[ j2(-2+j2) \right]$$

$$\Delta_2 = 5.38 \angle 158.19^\circ \times 52.5 \angle -156.8^\circ + 50 \angle 0^\circ \left[ -4j - 4 \right]$$

$$\Delta_2 = 282.4 \angle -315^\circ + 50 \angle 0^\circ \times 5.65 \angle -135^\circ$$

$$\Delta_2 = 282.4 \angle -315^\circ + 282.5 \angle -135^\circ$$

$$\Delta_2 = \cancel{282.3} \cancel{199.6} + j\cancel{199.6} - \cancel{199.7} - j\cancel{199.7}$$

$$\Delta_2 = 0$$


$$\therefore I = 0$$



## Node analysis or voltage analysis :-
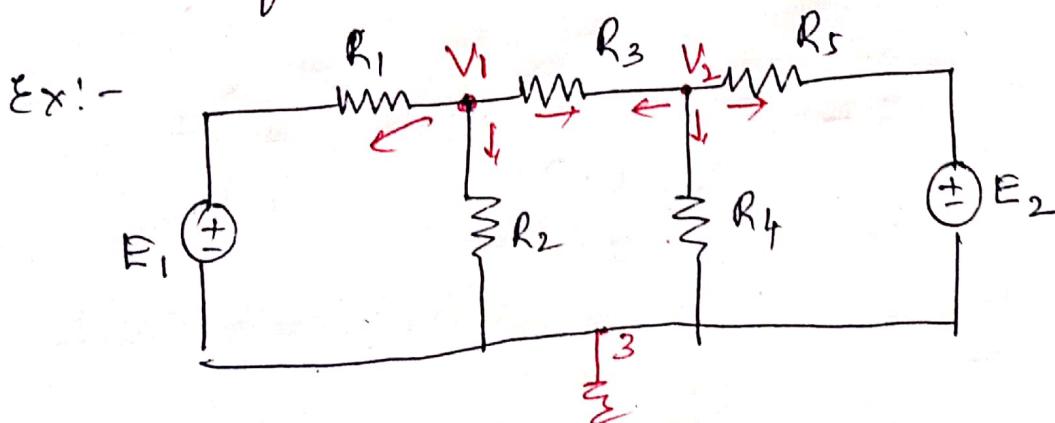
### Procedure :-

- All the principle nodes of the n/w are identified & one of them is taken as reference node at zero potential. Usually the node at which maximum no of branches are connected is taken as reference node.
- The remaining nodes are assigned with node voltages  $V_1, V_2, V_3 \dots$  etc.
- The node voltage equations are written using the KCL method.
- The node voltage equations are solved using Cramer's rule to get  $V_1, V_2, V_3 \dots$  etc.
- Once the node voltages are known the current in all the branches of the n/w can be found.



Applying KCL at node 1,

$$\frac{V_1 - E_1}{R_1} + \frac{V_1}{R_2} + \frac{V_1 - V_2}{R_3} = 0$$

$$\left[ \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right] V_1 - \frac{V_2}{R_3} = \frac{E_1}{R_1} \quad \text{--- (1)}$$


Applying KCL @ node 2.

$$\frac{V_2 - V_1}{R_3} + \frac{V_2}{R_4} + \frac{V_2 - E_2}{R_5} = 0$$

$$\frac{V_2}{R_3} - \frac{V_1}{R_3} + \frac{V_2}{R_4} + \frac{V_2}{R_5} - \frac{E_2}{R_5} = 0$$

$$-\frac{V_1}{R_3} + \left[ \frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5} \right] V_2 = \frac{E_2}{R_5} \quad \text{--- (2)}$$

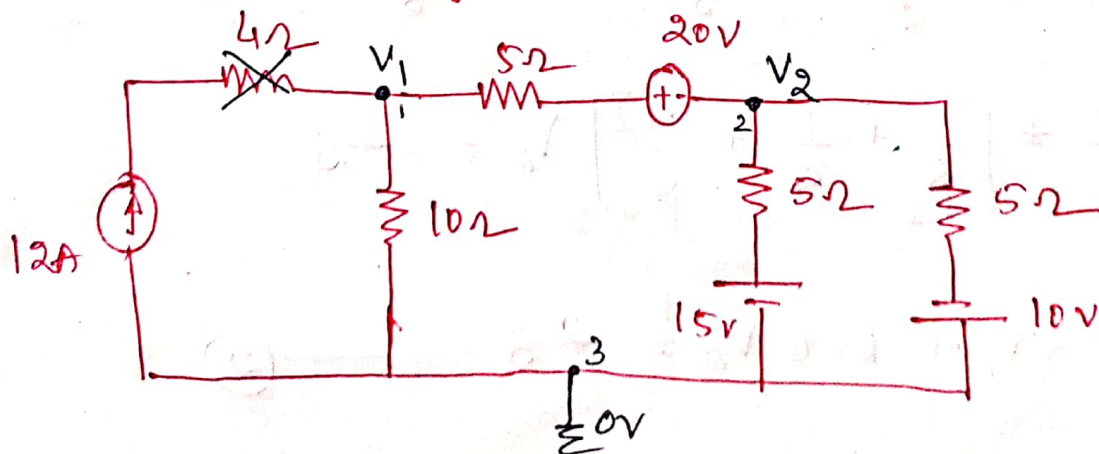1) In the network shown, find  $V_1$  &  $V_2$  using node voltage analysis.



Apply KCL at node 1

$$-12 + \frac{V_1}{10} + \frac{V_1 - 20 - V_2}{5} = 0$$

$$-12 + \frac{V_1}{10} + \frac{V_1}{5} - \frac{20}{5} - \frac{V_2}{5} = 0$$

$$-12 + \left[ \frac{1}{10} + \frac{1}{5} \right] V_1 - 4 - \frac{V_2}{5} = 0$$

$$\left[ \frac{1}{10} + \frac{1}{5} \right] V_1 - \frac{V_2}{5} = 16$$

$$0.3V_1 - 0.2V_2 = 16 \quad \text{--- (1)}$$

Apply KCL @ node 2.

$$\frac{V_2 + 20 - V_1}{5} + \frac{V_2 - 15}{5} + \frac{V_2 + 10}{5} = 0$$

$$\frac{V_2}{5} + 4 - \frac{V_1}{5} + \frac{V_2}{5} - 3 + \frac{V_2}{5} + 2 = 0$$


$$-\frac{V_1}{5} + \left[ \frac{1}{5} + \frac{1}{5} + \frac{1}{5} \right] V_2 = -3$$

$$-0.2V_1 + 0.6V_2 = -3 \quad \text{--- (2)}$$

$$V_1 = 64.28 \text{ V}$$

$$V_2 = 16.42 \text{ V}$$

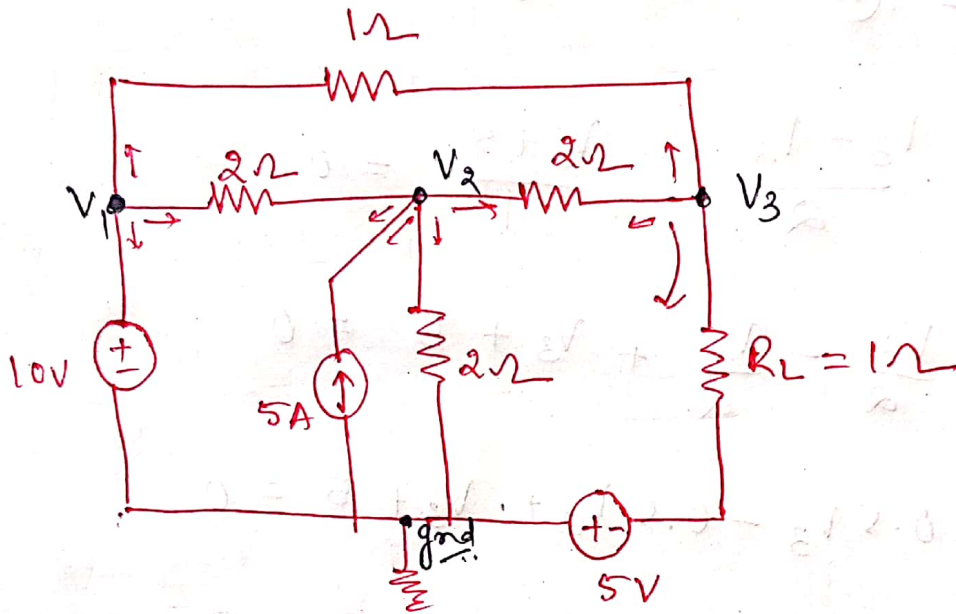2) Find 'I' through  $R_L$  in the circuit shown



From the figure

$$V_1 - 10 = 0$$

$$V_1 = 10 \text{ V}$$

Apply KCL @ node  $V_2$ .

$$\frac{V_2 - V_1}{2} + \frac{V_2}{2} - 5 + \frac{V_2 - V_3}{2} = 0$$

$$\frac{V_2}{2} - \frac{V_1}{2} + \frac{V_2}{2} - 5 + \frac{V_2}{2} - \frac{V_3}{2} = 0$$

$$0.5V_2 - 0.5V_1 + 0.5V_2 - 5 + 0.5V_2 - 0.5V_3 = 0$$

$$-0.5V_1 + 1.5V_2 - 0.5V_3 - 5 = 0$$



$$-0.5 \times 10 + 1.5V_2 - 0.5V_3 - 5 = 0$$

$$1.5V_2 - 0.5V_3 = 10 \quad \text{--- (1)}$$

Apply KCL @ node  $V_3$ .

$$\frac{V_3 - V_1}{1} + \frac{V_3 - V_2}{2} + \frac{V_3 + 5}{1} = 0$$

$$V_3 - V_1 + \frac{V_3}{2} - \frac{V_2}{2} + V_3 + 5 = 0$$

$$V_3 - 10 + 0.5V_3 - 0.5V_2 + V_3 + 5 = 0$$

$$-0.5V_2 + 2.5V_3 = 5 \quad \text{--- (2)}$$

Solving (1) & (2) we get-

$$V_3 = 3.57 \text{ volts}$$

Current through  $R_L$  is

$$I = \frac{V}{R}$$


$$I = \frac{V_3 + 5}{R_L}$$

$$I = \frac{3.57 + 5}{1}$$

$$I = 8.57 \text{ amp}$$



3) Find  $i_1$  using nodal analysis.

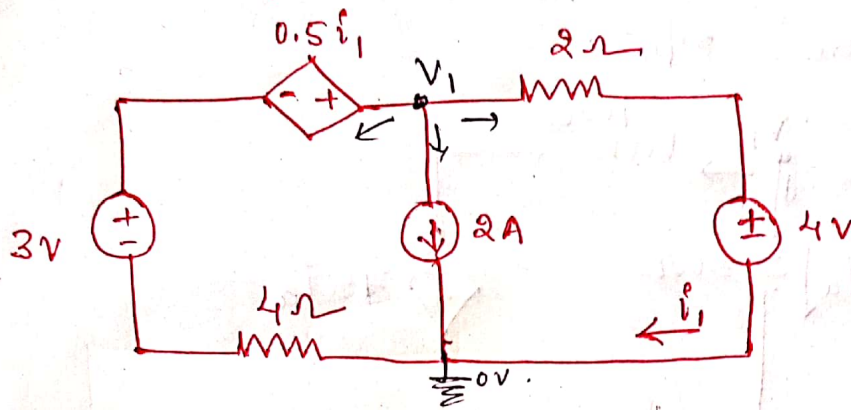

From the figure  $i_1 = \frac{V_1 - 4}{2}$

Apply KCL @ node  $V_1$

$$\frac{V_1 - 0.5i_1}{4} - 3 + 2 + \frac{V_1 - 4}{2} = 0$$

$$\frac{V_1}{4} - \frac{0.5i_1}{4} - 0.75 + 2 + 0.5V_1 - 2 = 0$$

$$0.25V_1 - 0.125 \left[ \frac{V_1 - 4}{2} \right] - 0.75 + 0.5V_1 = 0$$


$$0.75V_1 - 0.0625V_1 + 0.25 - 0.75 = 0$$

$$0.6875V_1 - 0.5 = 0$$

$$V_1 = \frac{0.5}{0.6875} = 0.727 \text{ volts}$$

$$\therefore i_1 = \frac{0.727 - 4}{2} = -1.636 \text{ Amp}$$

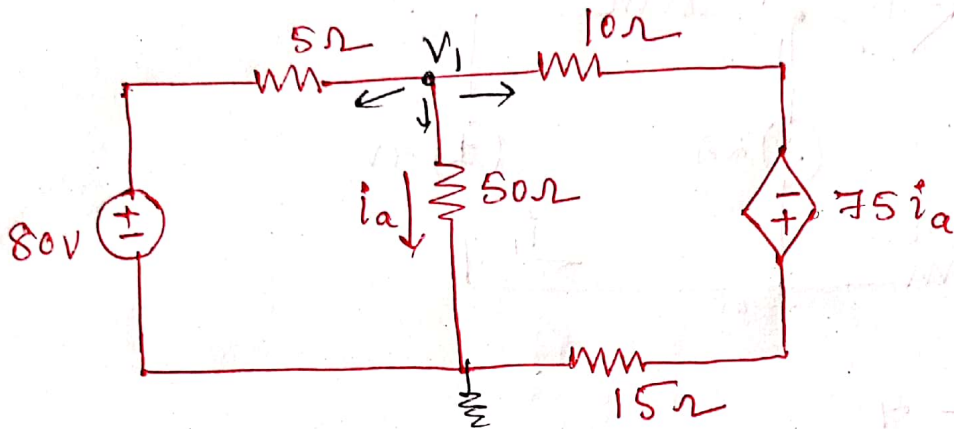4) Find power delivered by the dependent voltage source in the circuit.



From the figure,  $i_a = \frac{V_1}{50}$

Apply KCL @ node  $V_1$ ,

$$\frac{V_1 - 80}{5} + \frac{V_1}{50} + \frac{V_1 + 75i_a}{25} = 0$$

$$0.2V_1 - 16 + 0.02V_1 + 0.04V_1 + 3i_a = 0$$

$$0.26V_1 + 3i_a - 16 = 0$$

$$0.26V_1 + 3\left(\frac{V_1}{50}\right) = 16$$

$$0.32V_1 = 16$$

$$V_1 = \frac{16}{0.32} = 50 \text{ volts}$$

$$\therefore i_a = \frac{V_1}{50} = \frac{50}{50} = 1 \text{ Amp}$$

→ Current through dependent voltage source branch

$$= \frac{V_1 + 75 i_a}{25} = \frac{V_1 + 75 \left(\frac{V_1}{50}\right)}{25}$$





$$\rightarrow = \frac{50 + 75(1)}{25} = 5 \text{ Amp}$$

∴ power =  $V \times I$

$$= 75 i_a \times 5 = 75 \times 1 \times 5$$


$$\rightarrow = \underline{\underline{375 \text{ watts}}}$$

Note :-

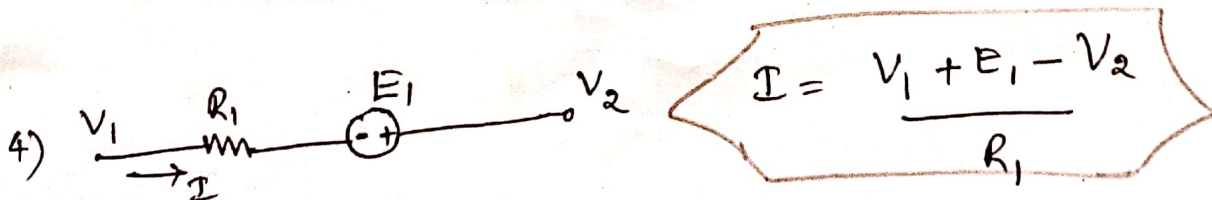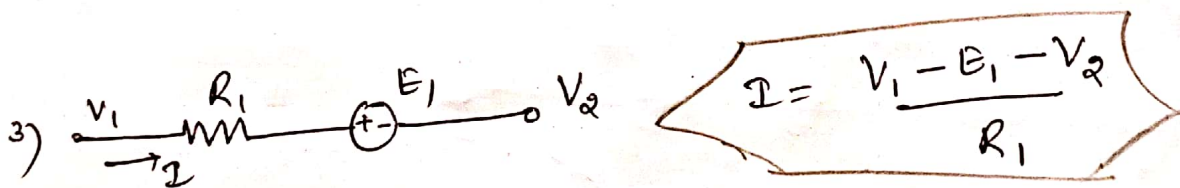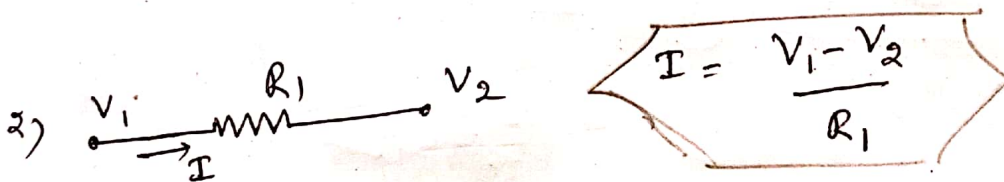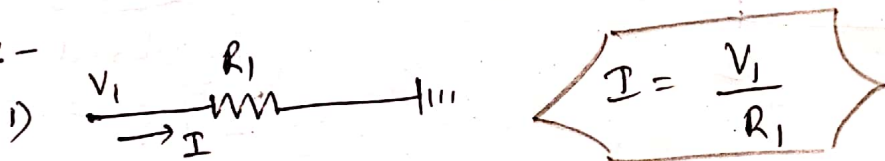



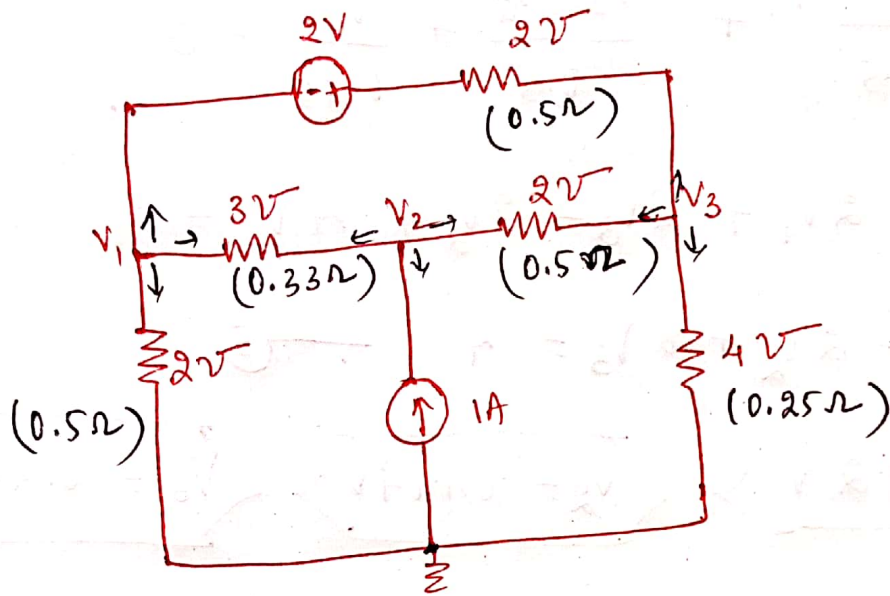5) In the circuit shown below, use nodal analysis to determine the voltages  $V_2$  &  $V_3$ .



Apply KCL @ node  $V_1$

$$\frac{V_1}{0.5} + \frac{V_1 - V_2}{0.33} + \frac{V_1 + 2 - V_3}{0.5} = 0$$

$$2V_1 + 3V_1 - 3V_2 + 2V_1 - 2V_3 + 4 = 0$$

$$7V_1 - 3V_2 - 2V_3 = -4 \quad \text{--- (1)}$$

@ node 2

$$\frac{V_2 - V_1}{0.33} + \frac{V_2 - V_3}{0.5} - 1 = 0$$

$$-3V_1 + 3V_2 + 2V_2 - 2V_3 - 1 = 0$$

$$-3V_1 + 5V_2 - 2V_3 = 1 \quad \text{--- (2)}$$

→ @ node 3

$$\frac{V_3 - 2 - V_1}{0.5} + \frac{V_3 - V_2}{0.5} + \frac{V_3}{0.25} = 0$$

$$2V_3 - 4 - 2V_1 + 2V_3 - 2V_2 + 4V_3 = 0$$


$$-2V_1 - 2V_2 + 8V_3 = 4 \quad \text{--- (3)}$$

$$V_1 = -0.382 \text{ V}$$

$$V_2 = 0.147 \text{ V}$$

$$V_3 = 0.441 \text{ V}$$

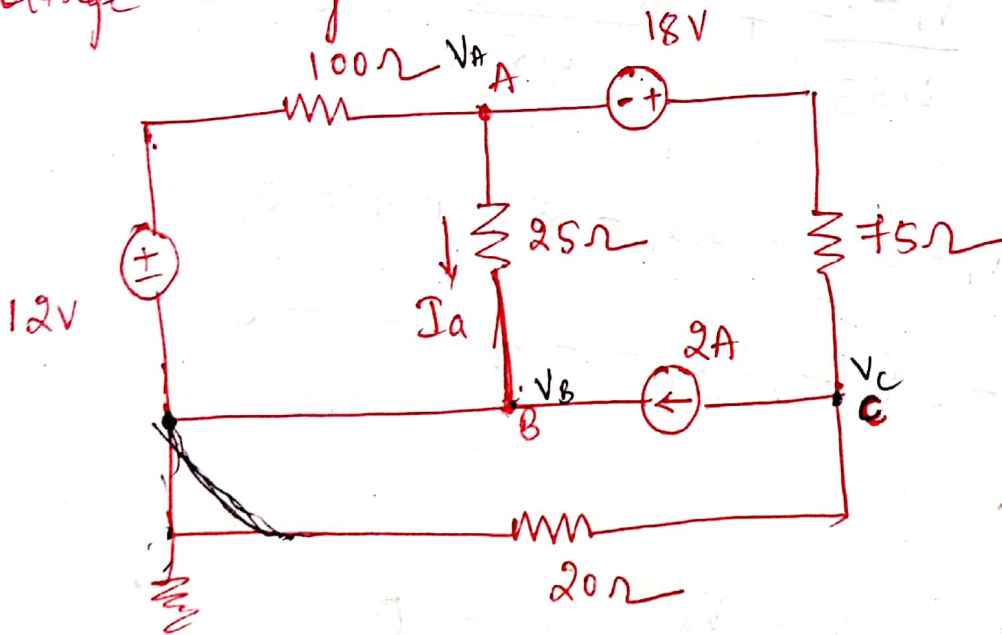6) Find  $I_a$  in the circuit shown using node voltage analysis.






## Super node :-

If the ideal voltage source [ dependent or independent voltage source ] is connected b/w any two non reference nodes, these nodes forms a super node.

Eg:-

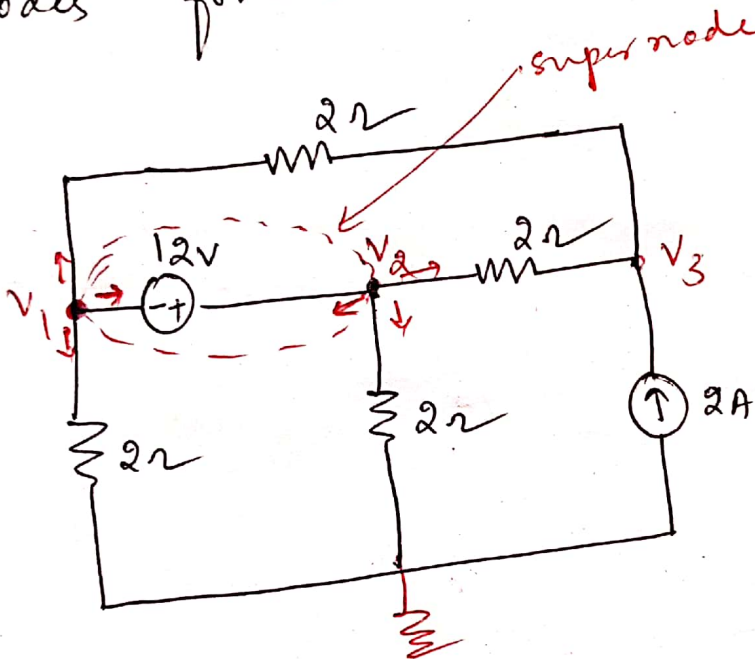

→ 12v voltage source exists b/w nodes 1 & 2. Hence node 1 & node 2 form super node


From super node

$$V_1 + 12 - V_2 = 0$$

$$V_1 - V_2 = -12$$

7) For the network shown below, find  $I_0$  using nodal analysis.

Jan-14  
10marks

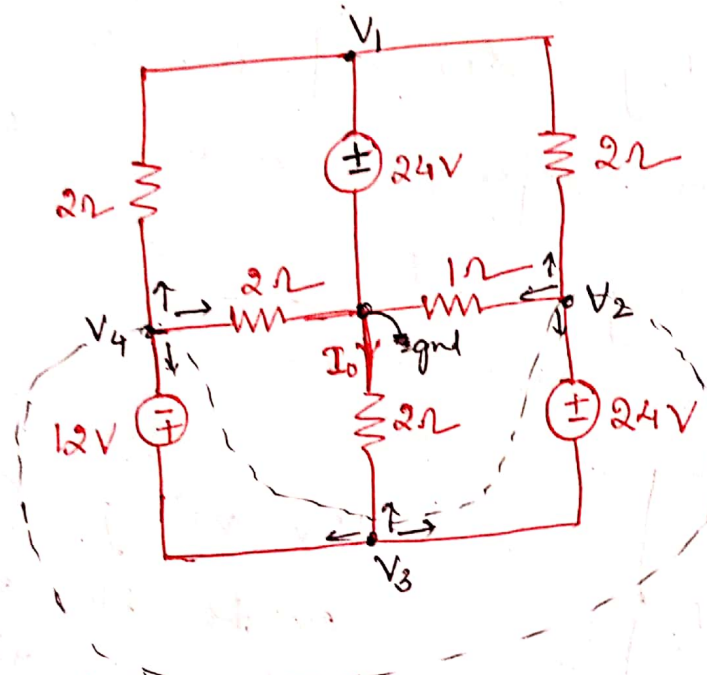

Super node 2-3-4

from the circuit:

$$V_1 - 24 = 0$$

$$V_1 = 24 \text{ volts} \quad \text{--- (1)}$$

→ 24V is in b/n 2 & 3

→ 12V is in b/n 4 & 3.

∴ 2-3-4 forms supernode.

from the super node,

$$V_2 - V_3 = 24 \text{ V} \quad \text{--- (2)}$$

$$V_3 - V_4 = 12 \text{ V} \quad \text{--- (3)}$$

Apply KCL @ node '2-3-4'

$$\frac{V_4 - V_1}{2} + \frac{V_4}{2} + \frac{V_2 - V_1}{2} + \frac{V_2}{1} + \frac{V_3}{2} = 0$$

$$2V_4 - 2V_1 + 2V_4 + 2$$

$$0.5V_4 - 0.5V_1 + 0.5V_4 + 0.5V_2 - 0.5V_1 + V_2 + 0.5V_3 = 0$$

$$-\overset{24}{V_1} + 1.5V_2 + 0.5V_3 + V_4 = 0$$

$$1.5V_2 + 0.5V_3 + V_4 = 24 \quad \text{--- (4)}$$

Solving (2), (3) & (4)

~~0.5V\_4 - 0.5V\_1 + 0.5V\_4 + 0.5V\_2 - 0.5V\_1 + V\_2 + 0.5V\_3 = 0~~

$$V_2 - V_3 + 0V_4 = 24 \quad \text{--- (2)}$$

$$0 + V_3 - V_4 = 12 \quad \text{--- (3)}$$

$$1.5V_2 + 0.5V_3 + V_4 = 24 \quad \text{--- (4)}$$

$$V_2 = 24V$$

$$V_3 = 0V$$


$$V_4 = -12V$$

From the figure

$$I_0 = \frac{0 - V_3}{2} = \underline{\underline{0 \text{ Amp}}}$$

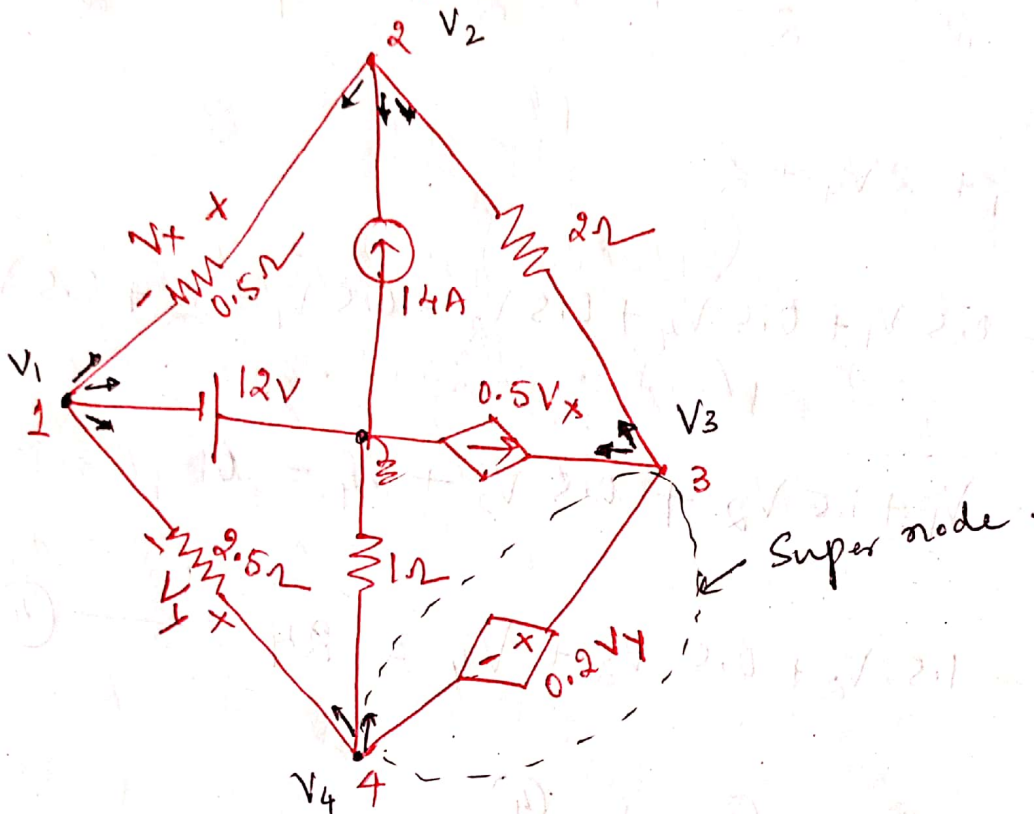8) Find the voltages at nodes 1, 2, 3, 4

Jan-8  
for the n/w using nodal analysis.



From the circuit,

$$V_1 + 12 = 0$$

$$V_1 = -12 \text{ volts}$$

Apply KCL @ node 2,

$$\frac{V_2 - V_1}{0.5} - 14 + \frac{V_2 - V_3}{2} = 0$$

$$2V_2 - 2V_1 - 14 + 0.5V_2 - 0.5V_3 = 0$$

$$-2x - 12 \cdot 24 \quad -2V_1 + 2.5V_2 - 0.5V_3 = 14$$

$$2.5V_2 - 0.5V_3 = 14 - 24$$



$$2.5V_2 - 0.5V_3 = -10 \quad \text{--- (1)}$$

→  $0.2V_1$  exists b/w node 3 & 4

∴ 3 & 4 forms super node.

From super node,

$$\frac{V_3 - V_2}{2} - 0.5V_x + \frac{V_4}{1} + \frac{V_4 - V_1}{2.5} = 0$$

$$0.5V_3 - 0.5V_2 - 0.5V_x + V_4 + 0.4V_4 - 0.4V_1 = 0$$

$$-0.4V_1 - 0.5V_2 + 0.5V_3 + 1.4V_4 - 0.5V_x = 0$$

But  $V_x = V_2 - V_1$  &  $V_1 = \underline{\underline{-12 \text{ volts}}}$ .

$$\therefore -0.4(-12) - 0.5V_2 + 0.5V_3 + 1.4V_4 - 0.5(V_2 - V_1) = 0.$$

$$\rightarrow 4.8 - 0.5V_2 + 0.5V_3 + 1.4V_4 - 0.5V_2 + 0.5V_1 = 0$$

$0.5 \times -12$   
 $-12$

$$\rightarrow 4.8 - V_2 + 0.5V_3 + 1.4V_4 - 6 = 0$$

$$-V_2 + 0.5V_3 + 1.4V_4 = 1.2 \quad \text{--- (2)}$$

From super node.

$$V_3 - V_4 = 0.2 V_y$$

But  $V_y = V_4 - V_1$

$$\rightarrow V_3 - V_4 = 0.2 (V_4 - V_1)$$

$$\rightarrow V_3 - V_4 = 0.2 V_4 - 0.2 V_1$$

or  $0.2 V_1 + V_3 - V_4 - 0.2 V_4 = 0$

$$0.2(-12) + V_3 - 1.2 V_4 = 0$$

$$V_3 - 1.2 V_4 = 2.4 \quad \text{--- (3)}$$

Solving (1), (2), & (3)


$$V_1 = -12V$$

$$V_2 = -4V$$

$$V_3 = 0V$$

$$V_4 = -2V$$

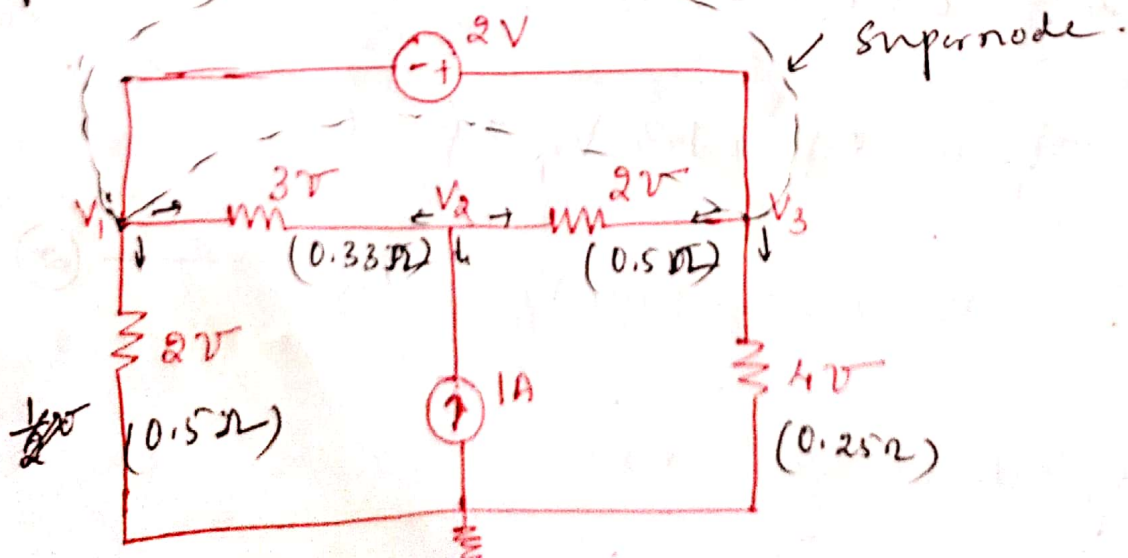9) In the circuit shown below, use nodal analysis to determine the voltages  $V_a$  &  $V_3$



From the super node (1-3)

$$\boxed{V_3 - V_1 = 2V} \rightarrow -V_1 + V_3 = 2V \quad \text{--- (1)}$$

KCL @ Super node (1-3)

$$\frac{V_1}{0.5} + \frac{V_1 - V_2}{0.33} + \frac{V_3 - V_2}{0.5} + \frac{V_3}{0.25} = 0$$

$$2V_1 + 3V_1 - 3V_2 + 2V_3 - 2V_2 + 4V_3 = 0$$

$$5V_1 - 5V_2 + 6V_3 = 0 \quad \text{--- (2)}$$

Apply KCL @ node 2

$$\frac{V_2 - V_1}{0.33} - 1 + \frac{V_2 - V_3}{0.5} = 0$$

$$3V_2 - 3V_1 - 1 + 2V_2 - 2V_3 = 0$$

$$-3V_1 + 5V_2 - 2V_3 = 1 \quad \text{--- (3)}$$

Solving (1), (2) & (3) we get -


$$\boxed{V_1 = -1.667 \text{ volts}}$$

$$\boxed{V_2 = -0.1667 \text{ volts}}$$

$$\boxed{V_3 = 0.833 \text{ volts}}$$



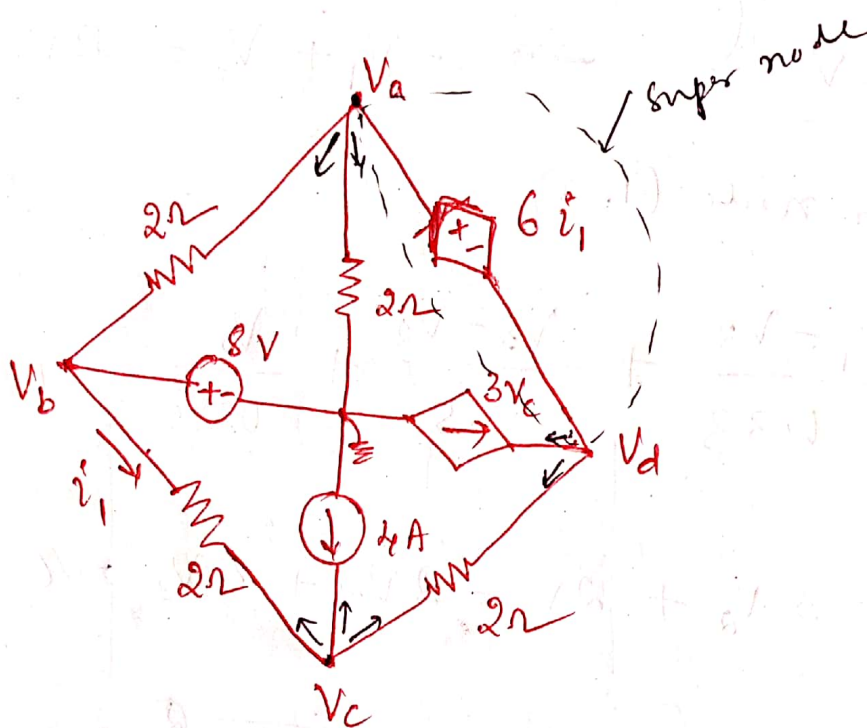10) Find  $V_c$  &  $V_d$  using nodal analysis.



From the figure, (@ node  $V_b$ )

$$V_b - 8 = 0 \Rightarrow \boxed{V_b = 8V}$$

Apply KCL @ node  $c$

$$\frac{V_c - V_b}{2} + \frac{V_c - V_d}{2} - 4 = 0$$

$$0.5V_c - 0.5V_b + 0.5V_c - 0.5V_d - 4 = 0$$

$$-0.5V_b + V_c - 0.5V_d - 4 = 0$$

$$-0.5(8) + V_c - 0.5V_d - 4 = 0$$



$$V_c - 0.5V_d = 8 \quad \text{--- (1)}$$

from super node, (a-d)

$$V_a - V_d = 6 i_1$$

from the figure,

$$i_1 = \frac{V_b - V_c}{2}$$

$$V_a - V_d = 3 \left[ \frac{V_b - V_c}{2} \right]$$

$$V_a - V_d = 3V_b - 3V_c$$

$$\boxed{V_a + 3V_c - V_d = 24} \quad \text{--- (2)}$$

$$V_a - V_d - 3V_b + 3V_c = 0$$

$$V_a - 3V_b + 3V_c - V_d = 0 \quad \text{--- (2)}$$

Apply KCL to super node (a-d)

$$\frac{V_a - V_b}{2} + \frac{V_a}{2} - 3V_c + \frac{V_d - V_c}{2} = 0$$

$$0.5V_a - 0.5V_b + 0.5V_a - 3V_c + 0.5V_d - 0.5V_c = 0$$

$$V_a - 0.5V_b - 3.5V_c + 0.5V_d = 0$$


$$\boxed{V_a - 3.5V_c + 0.5V_d = 4} \quad \text{--- (3)}$$

$$V_a = 9.14$$

$$V_c = -1.14$$

$$V_d = -18.28 \text{ volts}$$

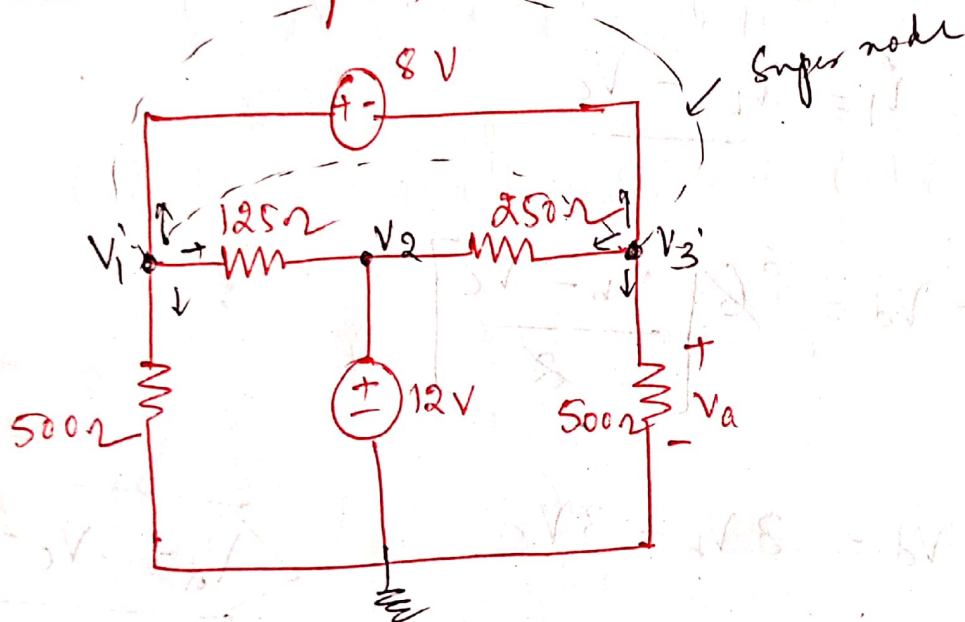1) For the electrical circuit, find  $V_a$  using nodal analysis



(a) node 2 :-

$$V_2 - 12 = 0 \Rightarrow V_2 = 12 \text{ V}$$

From super node (1-3)

$$V_1 - V_3 = 8 \text{ V} \quad \text{--- (1)}$$

Apply KCL to super node,

$$\frac{V_1}{500} + \frac{V_1 - V_2}{125} + \frac{V_3 - V_2}{250} + \frac{V_3}{500} = 0$$

$$2 \times 10^{-3} V_1 + 8 \times 10^{-3} V_1 - 0.096 + 4 \times 10^{-3} V_3 - 0.048 + 2 \times 10^{-3} V_3 = 0$$



$$10 \times 10^{-3} V_1 + 6 \times 10^{-3} V_3 = 0.144 \quad \text{--- (2)}$$

$$V_1 = 12V \quad V_3 = 4 \text{ volts}$$

From the figure.

$$V_a = V_3 = 4 \text{ volts}$$

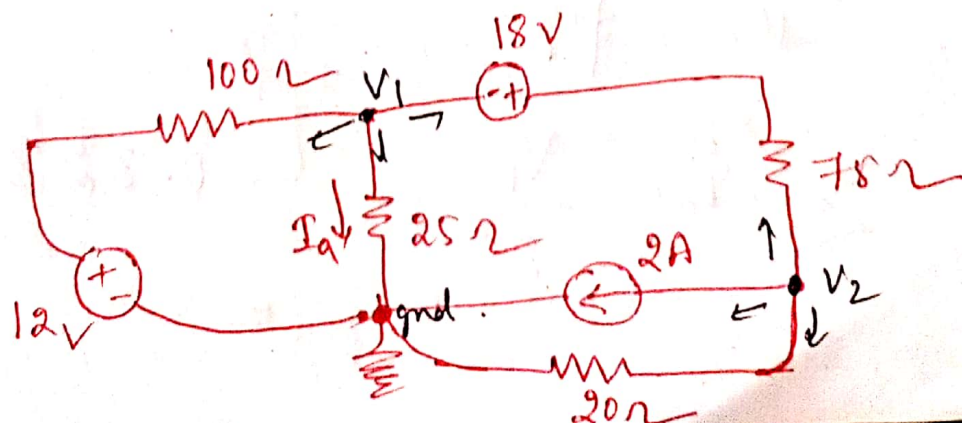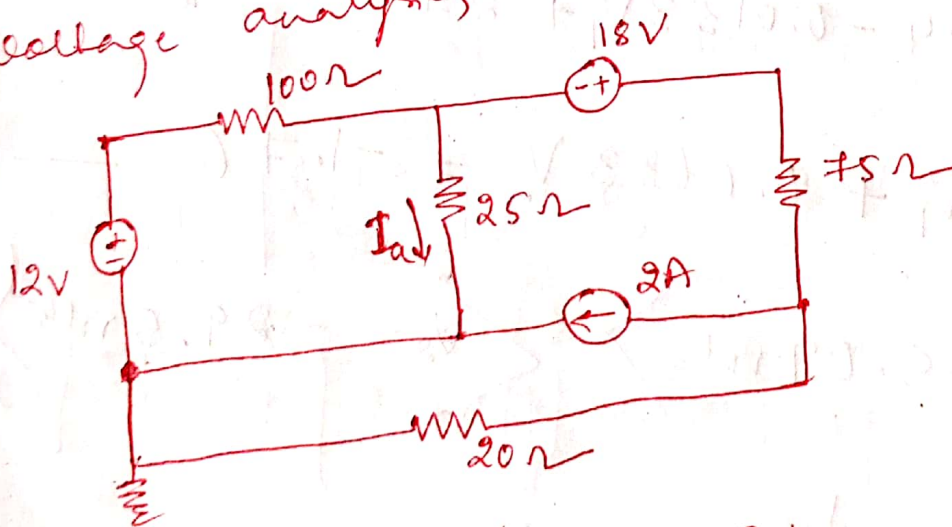6) Find  $I_a$  in the circuit shown using node voltage analysis





Apply KCL @ node 1

$$\frac{V_1 - 12}{100} + \frac{V_1}{25} + \frac{V_1 + 18 - V_2}{75} = 0$$

$$0.01V_1 - 0.12 + 0.04V_1 + 0.0133V_1 + 0.24 - 0.0133V_2 = 0$$

$$0.0633V_1 - 0.0133V_2 = -0.12 \quad \text{--- (1)}$$

Apply KCL @ node 2

$$\frac{V_2 - 18 - V_1}{75} + 2 + \frac{V_2}{20} = 0$$

$$0.0133V_2 - 0.24 - 0.0133V_1 + 2 + 0.05V_2 = 0$$

$$-0.0133V_1 + 0.0633V_2 = -1.76 \quad \text{--- (2)}$$

$$V_1 = -8.09 \text{ volts}$$

$$V_2 = -29.5 \text{ volts}$$


From the fig.

$$i_a = \frac{V_1}{25} = -0.323 \text{ volts}$$



# Problems on AC Analysis :-

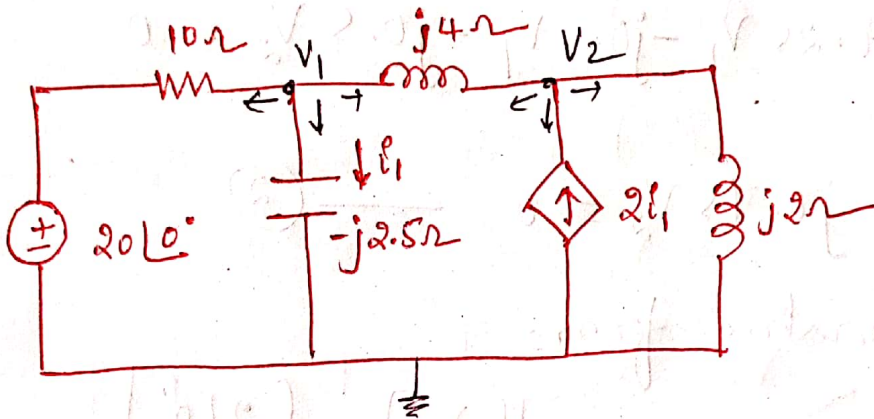1) Find  $i_1$  for the circuit using nodal analysis.



From the circuit -

$$i_1 = \frac{V_1}{-j2.5\Omega}$$

$$\begin{cases} \frac{1}{j} = -j \\ \frac{1}{-j} = j \end{cases}$$

Apply KCL @ node 1

$$\frac{V_1 - 20\angle 0^\circ}{10} + \frac{V_1}{-j2.5} + \frac{V_1 - V_2}{j4} = 0$$

$$\frac{V_1}{10} - \frac{20\angle 0^\circ}{10} + j \frac{V_1}{2.5} + (-j) \frac{V_1}{4} + j \frac{V_2}{4} = 0$$

$$0.1V_1 - 2\angle 0^\circ + j0.4V_1 - j0.25V_1 + j0.25V_2 = 0$$

$$\underbrace{[0.1 + j0.4 - j0.25]}_{j0.15} V_1 + j0.25V_2 = 2\angle 0^\circ \quad \text{--- (1)}$$

Apply KCL @ node 2.

$$\frac{V_2 - V_1}{j4} - 2i_1 + \frac{V_2}{j2} = 0$$

$$-j0.25(V_2 - V_1) - \frac{2V_1}{-j2.5} + (-j0.5)V_2 = 0$$

$$-j0.25V_2 + j0.25V_1 - j0.8V_1 - j0.5V_2 = 0$$

$$-j0.55V_1 - j0.75V_2 = 0 \quad \text{--- (2)}$$

in matrix form.

$$\begin{bmatrix} 0.1 + j0.15 & j0.25 \\ -j0.55 & -j0.75 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 2 \angle 0^\circ \\ 0 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 0.1 + j0.15 & j0.25 \\ -j0.55 & -j0.75 \end{vmatrix}$$

$$= [(0.1 + j0.15)(-j0.75) + (j0.25)(j0.55)]$$

$$\begin{aligned} &= 0.1125 - j0.075 - 0.1375 \\ &= -0.025 - j0.075 \end{aligned}$$

$$\Delta_1 = \begin{vmatrix} 2 \angle 0^\circ & j0.25 \\ 0 & -j0.75 \end{vmatrix}$$

$$\hookrightarrow = -j1.5$$


$$\therefore V_1 = \frac{\Delta_1}{\Delta} = \frac{-1.5j}{-0.025 - j0.075}$$

$$V_1 = 18.97 \angle 18.43^\circ \text{ V}$$

$$\therefore I_1 = \frac{18.97 \angle 18.43}{-j2.5} = \frac{18.97 \angle 18.43}{2.5 \angle -90^\circ}$$

$$I_1 = 7.59 \angle 108.43 \text{ Amp}$$

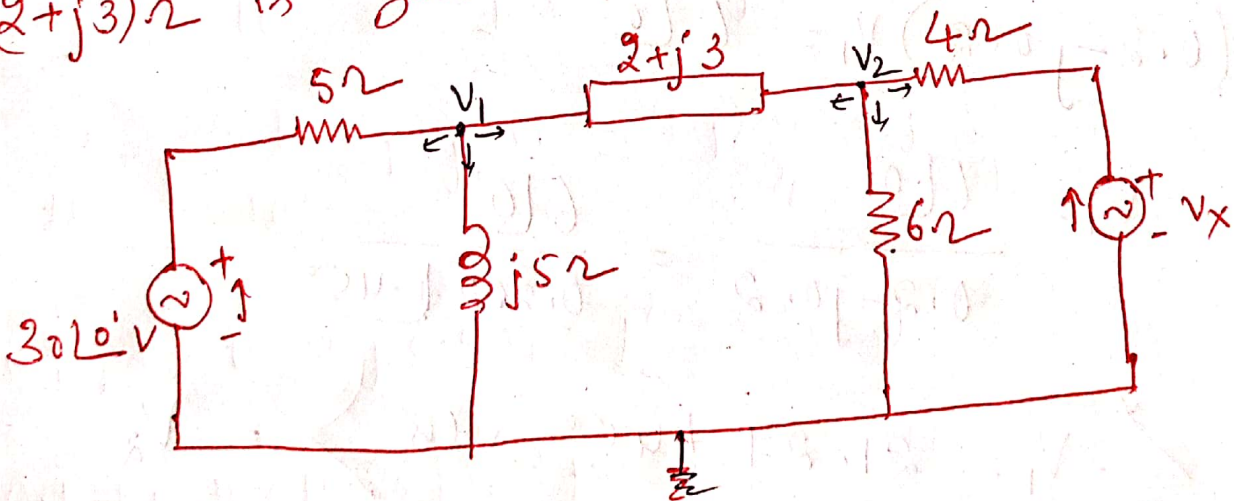2) Use the nodal analysis & find the value of  $V_x$  in the circuit shown in below fig such that the current through the impedance  $(2+j3)\Omega$  is zero



From the figure (data)

$$I_{(2+j3)\Omega} = \frac{V_1 - V_2}{2+j3}$$



Given the current  $I_{(2+3)\Omega} = 0$

$$\therefore 0 = \frac{V_1 - V_2}{2 + j3}$$

$$0 = V_1 - V_2$$

$$\Rightarrow V_1 = V_2 \quad (\because \text{Equipotential})$$

Apply KCL @ node 1,

$$\frac{V_1 - 30\angle 0^\circ}{5} + \frac{V_1}{j5} + \frac{V_1 - V_2}{2 + j3} = 0$$

$$0.2V_1 - 6\angle 0^\circ - j0.2V_1 = 0$$

$$(0.2 - j0.2)V_1 = 6\angle 0^\circ$$

$$V_1 = \frac{6\angle 0^\circ}{0.2 - j0.2} = \frac{6\angle 0^\circ}{0.2\angle -45^\circ}$$

$$V_1 = 21.21 \angle 45^\circ \text{ volts} = V_2$$

Apply KCL @ node 2,

$$\frac{V_2 - V_1}{2 + j3} + \frac{V_2}{6} + \frac{V_2 - V_x}{4} = 0$$




$$0.167 V_2 + 0.25 [V_2 - V_x] = 0$$

$$0.417 V_2 = 0.25 V_x$$

$$V_x = \frac{0.417 V_2}{0.25} = \frac{0.417 \times 21.27 \angle 45^\circ}{0.25}$$

$$V_x = 35.47 \angle 45^\circ \text{ volts}$$

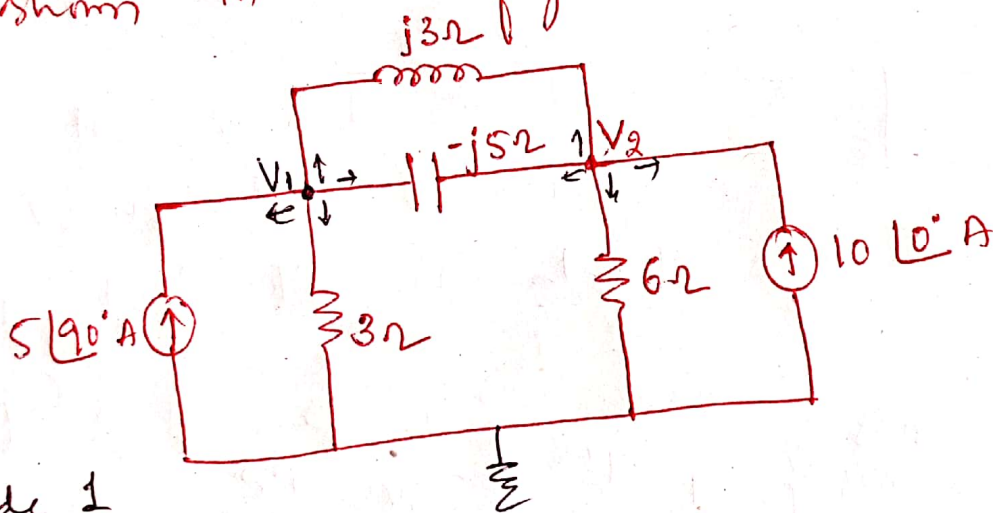3) Use nodal analysis to find  $V_2$  in the circuit shown in the figure.



At node 1

$$-5 \angle 90^\circ + \frac{V_1}{3} + \frac{V_1 - V_2}{-j5} + \frac{V_1 - V_2}{j3} = 0$$

$$0.33 V_1 + j0.2 V_1 - j0.2 V_2 + j0.33 V_1 + j0.33 V_2 = 5 \angle 90^\circ$$

$$[0.33 - j0.133] V_1 + j0.133 V_2 = 5 \angle 90^\circ \quad \text{--- (1)}$$

At node 2

$$\frac{V_2}{6} + \frac{V_2 - V_1}{-j5} + \frac{V_2 - V_1}{j3} - 10 \angle 0^\circ = 0$$

$$0.166 V_2 + j 0.2 V_2 - j 0.2 V_1 - j 0.333 V_2 + j 0.33 V_1 = 10 \angle 0^\circ$$

$$-j 0.133 V_1 + (0.166 - j 0.133) V_2 = 10 \angle 0^\circ$$

②

$$\Delta = \begin{vmatrix} 0.33 - j 0.133 & 0.133j \\ -0.133j & 0.166 - j 0.133 \end{vmatrix}$$

$$\Delta = [(0.33 - j 0.133)(0.166 - j 0.133) + (0.133j)(0.133j)]$$

$$= 0.0547 - j 0.022 - j 0.0442 - 0.01768 - 0.01768$$

$$= 0.0193 - j 0.0658$$

$$\Delta = \underline{\underline{0.0686 \angle -78.67^\circ}}$$

$$\Delta_2 = \begin{vmatrix} 0.33 - j 0.133 & 5j \\ -0.133j & 10 \end{vmatrix}$$

$$= (0.33 - j 0.133)10 + 5j(0.133j)$$


$$\Delta_2 = 3.33 - j1.33 - 0.665$$

$$\Delta_2 = 2.665 - j1.33 = 2.978 \angle -26.52^\circ$$

$$\therefore \dot{V}_2 = \frac{\Delta_2}{\Delta} = \frac{2.978 \angle -26.52^\circ}{0.0686 \angle -73.67^\circ}$$

$$V_2 = 43.41 \angle 47.15^\circ \text{ volts}$$

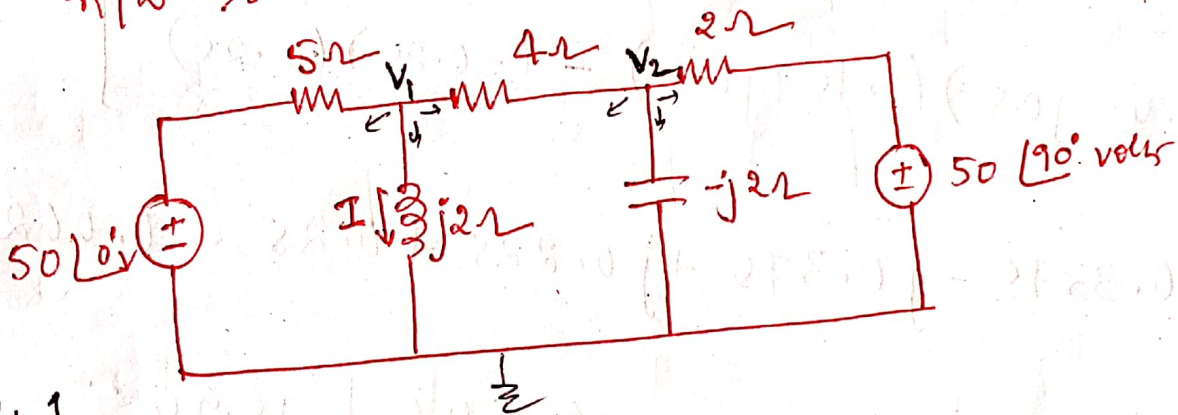4) Use node voltage technique to find  $I$  in the n/w shown.



@ node 1

$$\frac{V_1 - 50 \angle 0^\circ}{5} + \frac{V_1}{j2} + \frac{V_1 - V_2}{4} = 0$$

$$0.2V_1 - 10 \angle 0^\circ - j0.5V_1 + 0.25V_1 - 0.25V_2 = 0$$

$$(0.45 - j0.5)V_1 - 0.25V_2 = 10 \angle 0^\circ \quad \text{--- ①}$$



Ⓐ node 2

$$\frac{V_1 - V_2}{4} + \frac{V_2}{-j2} + \frac{V_2 - 50 \angle 90^\circ}{2} = 0$$

$$0.25V_1 - 0.25V_2 + j0.5V_2 + 0.5V_2 - 25 \angle 90^\circ = 0$$

$$-0.25V_1 + (0.75 + j0.5)V_2 = 25 \angle 90^\circ \quad \text{--- (2)}$$

$$\Delta = \begin{vmatrix} 0.45 - j0.5 & -0.25 \\ -0.25 & 0.75 + j0.5 \end{vmatrix}$$

$$\Delta = \left[ (0.45 - j0.5)(0.75 + j0.5) - (-0.25)(-0.25) \right]$$

$$= 0.3375 - j0.375 + j0.225 + 0.25 - 0.0625$$

$$\hookrightarrow = 0.525 - j0.15 = 0.546 \angle -15.94^\circ$$

$$\Delta_1 = \begin{vmatrix} 10 & -0.25 \\ 25j & 0.75 + j0.5 \end{vmatrix}$$

$$= 7.5 + j5 + j6.25$$




$$\Delta_1 = 7.5 + j11.25 = 13.52 \angle 56.3$$

$$V_1 = \frac{\Delta_1}{\Delta} = 24.76 \angle 72.24^\circ$$

$$I_1 = \frac{V_1}{j2} = \frac{24.76 \angle 72.24^\circ}{2 \angle 90^\circ}$$

$$I_1 = 12.38 \angle -17.76 \text{ Amp}$$

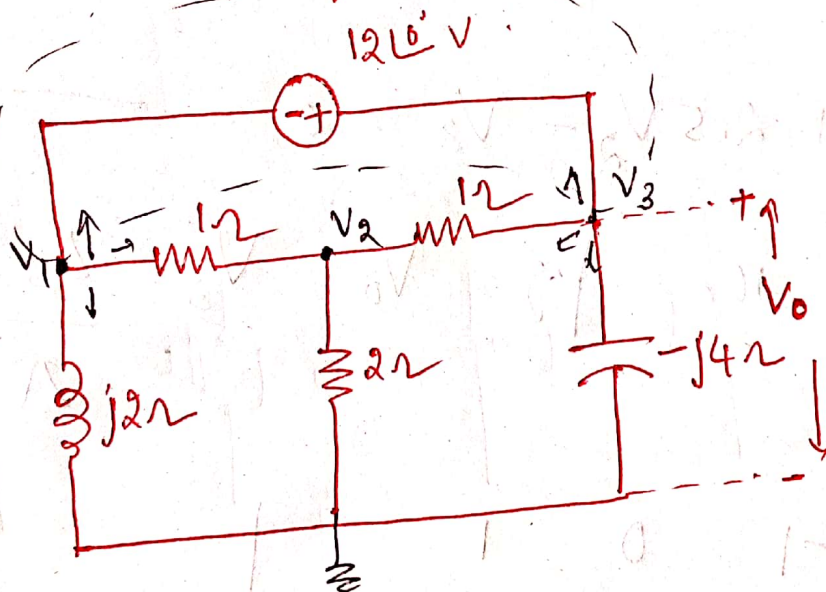5) Use nodal analysis to find  $V_0$  in the circ-



from Super node,

$$V_3 - V_1 = 12 \angle 0^\circ$$

$$\rightarrow -V_1 + 0V_2 + V_3 = 12 \angle 0^\circ$$

KCL @ Supernode,

$$\frac{V_1}{j2} + \frac{V_1 - V_2}{1} + \frac{V_3 - V_2}{1} + \frac{V_3}{-j4} = 0$$

$$-j0.5V_1 + V_1 - V_2 + V_3 - V_2 + j0.25V_3 = 0$$

$$(1 - j0.5)V_1 - 2V_2 + (1 + j0.25)V_3 = 0$$

————— (2)

KCL @ node 2

$$\frac{V_2 - V_1}{1} + \frac{V_2}{2} + \frac{V_2 - V_3}{1} = 0$$

$$V_2 - V_1 + 0.5V_2 + V_2 - V_3 = 0$$

$$-V_1 + 2.5V_2 - V_3 = 0$$

————— (3)

from the fig  $V_0 = V_3 = \frac{\Delta_3}{\Delta}$

$$\Delta = \begin{vmatrix} -1 & 0 & 1 \\ 1 - j0.5 & -2 & (1 + j0.25) \\ -1 & 2.5 & -1 \end{vmatrix}$$

$$\Delta = [-1(2 - 2.5 - j0.625) + 1(2.5 - j1.25 - 2)]$$

$$\Delta = [-1(-0.5 - j0.625) + 1(0.5 - j1.25)]$$

$$\Delta = 0.5 + j0.625 + 0.5 - j1.25$$

$$\Delta = 1 - 0.625j = 1.179 \angle -32^\circ$$

$$\Delta_3 = \begin{vmatrix} -1 & 0 & 12 \\ 1 - j0.5 & -2 & 0 \\ -1 & 2.5 & 0 \end{vmatrix}$$

$$\Delta_3 = [-1(0 - 0) + 12(2.5 - j \overset{j1.25}{\cancel{0.625}} - 2)]$$

$$\Delta_3 = 12(0.5 - j \overset{1.25}{\cancel{0.625}})$$

$$\hookrightarrow = 6 - j \overset{j15}{\cancel{7.5}} = \overset{= 6 - j15}{\cancel{9.6} \angle \cancel{51.3^\circ}}$$

$$\therefore V_0 = \frac{\overset{16.155 \angle -68.19^\circ}{\cancel{9.6} \angle \cancel{51.3^\circ}}}{1.179 \angle -32^\circ} = \overset{= 8.14 \angle -19.3^\circ}{\cancel{8.14} \angle \cancel{-19.3^\circ}}$$

$$V_0 = \frac{16.155 \angle -68.19^\circ}{1.179 \angle -32^\circ} = \underline{\underline{13.70 \angle -36.2^\circ}}$$




Millman's theorem :-

Statement:- "If  $n$  no of voltage sources  $E_1, E_2, E_3 \dots E_n$  with their internal impedances  $Z_1, Z_2 \dots Z_n$  resp are in parallel. Then these voltage sources may be replaced by a single voltage source of voltage  $E$  with the internal impedance  $Z$  where

$$E = \frac{E_1 Y_1 + E_2 Y_2 + E_3 Y_3 + \dots + E_n Y_n}{Y_1 + Y_2 + Y_3 + \dots + Y_n}$$

And  $Z = \frac{1}{Y_1 + Y_2 + \dots + Y_n}$

Explanation:-

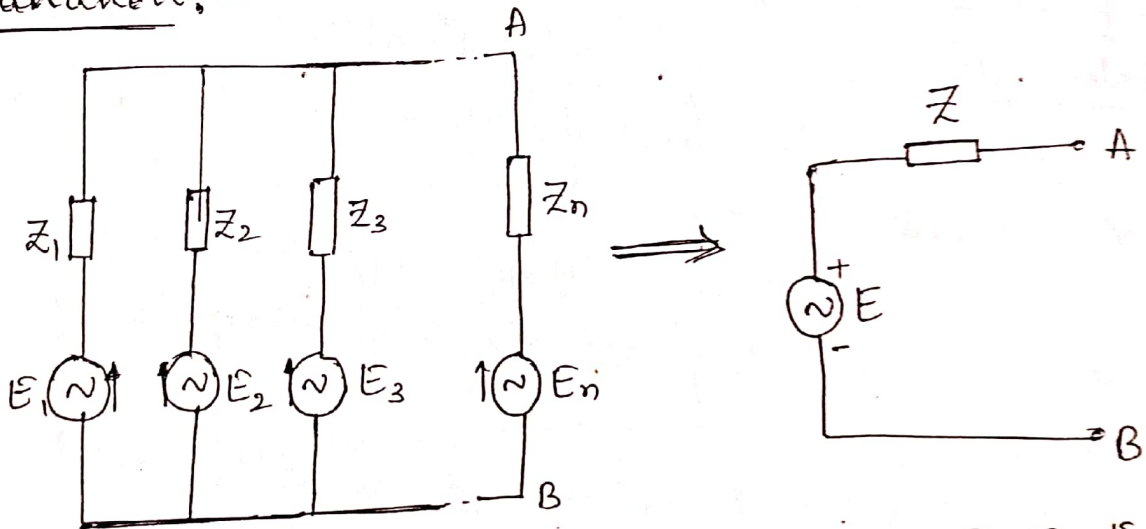

Consider  $n$  number of voltage sources  $E_1, E_2, E_3 \dots E_n$  with their internal impedances  $Z_1, Z_2, Z_3 \dots Z_n$  are connected in parallel as shown in fig above.

W.K.T  $I = I_1 + I_2 + I_3 + \dots + I_n$

But  $I = E Y$   
 $I_1 = E_1 Y_1$   
 $I_2 = E_2 Y_2 \dots I_n = E_n Y_n$  } — ①



where  $Y_1, Y_2, Y_3, \dots, Y_n$  are the admittances connected in parallel corresponding to impedances  $Z_1, Z_2, \dots, Z_n$  respectively

$$\therefore E = \frac{I}{Y}$$

$$E = \frac{I_1 + I_2 + I_3 + \dots + I_n}{Y_1 + Y_2 + \dots + Y_n}$$

$$E = \frac{E_1 Y_1 + E_2 Y_2 + E_3 Y_3 + \dots + E_n Y_n}{Y_1 + Y_2 + Y_3 + \dots + Y_n}$$

and  $Z = \frac{1}{Y} = \frac{1}{Y_1 + Y_2 + Y_3 + \dots + Y_n}$


hence the proof.

### 2) Superposition theorem:-

Statement:- "In any linear bilateral network containing more than one independent source, the current or voltage across any element in the network is equal to sum of the individual current or voltage produced by each source acting alone, setting all the other independent sources to zero."

If it is a voltage source, it is replaced by short circuit. If it is a current source, it is replaced by an open circuit.


Explanation:-

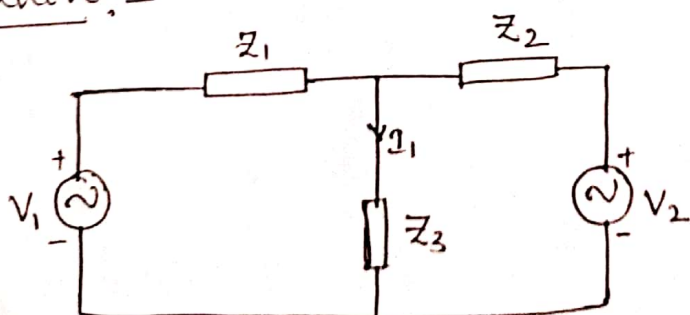

Consider a linear bilateral network having two voltage source as shown in fig above.

Let  $I_1$  be the current flowing through  $Z_3$  when both the voltage sources  $V_1$  &  $V_2$  are present in the circuit.

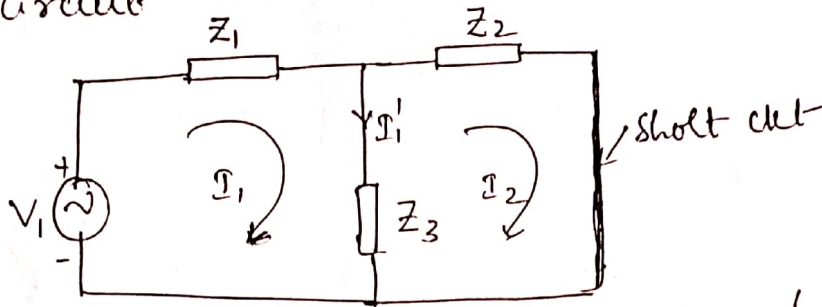
Case i) Consider the voltage source  $V_1$  only, replacing the other  $V_2$  by short circuit



Let  $I_1'$  is the current flowing through  $Z_3$ . Using any one of the n/w reduction method find the current  $I_1'$

$$I_1' = I_1 - I_2$$

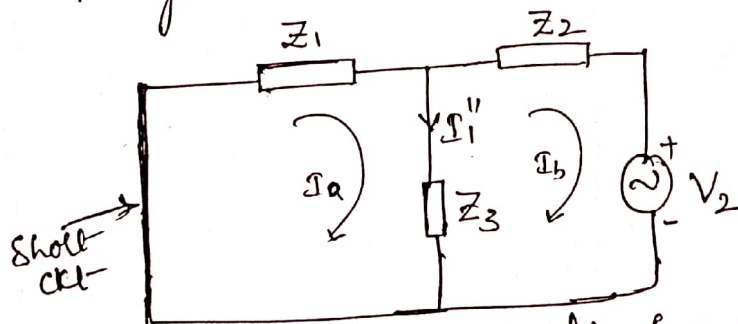Case ii) Consider the voltage source  $V_2$  only. Replacing the other voltage source  $V_1$  by short ckt, the resulting n/w is as shown.



Let  $I_1''$  is the current flowing through  $Z_3$ . Using any one of the n/w reduction method find the current  $I_1''$

$$\Rightarrow I_1'' = I_a - I_b$$

According to superposition theorem, the total current  $I_1$  through  $Z_3$  is the algebraic sum of the current through  $Z_3$  produced by  $V_1$  &  $V_2$  acting alone.


i.e., 
$$I_1 = I_1' + I_1''$$

hence the proof.

Reciprocity theorem :-

Statement:- "In any linear, bilateral network containing only one independent source, the ratio of excitation to response remains same (constant) when their positions are interchanged."

Explanation:-

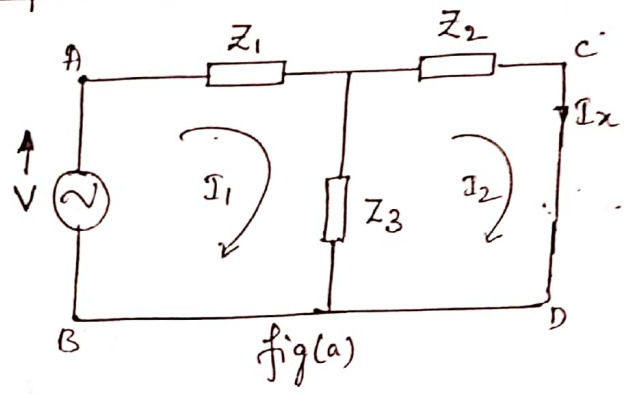


Consider a linear bilateral n/w as shown in fig(a). Let  $V$  volts is the excitation across  $AB$  &  $I_x$  is the response through  $CD$ , the ratio of excitation to response is  $\frac{V}{I_x}$ .

Now interchange the positions of excitation and response as shown in fig(b)

If  $V$  volts is placed across  $CD$ , it produces the same current  $I_x$  through  $AB$ .

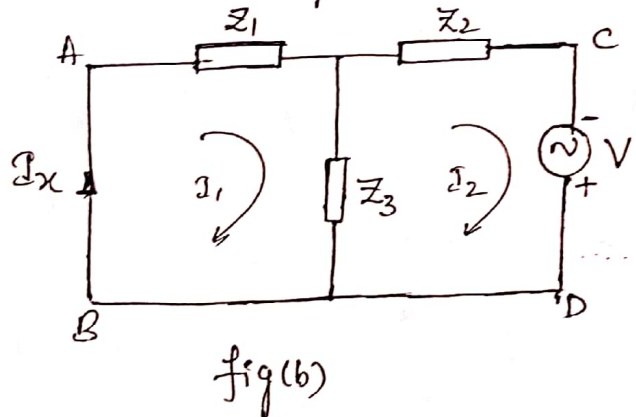Then according to reciprocity theorem the ratio of excitation to response remains same.



Proof:- For first loop (fig(a))

$$(Z_1 + Z_3)I_1 - Z_3 I_2 = V \quad \text{--- ①}$$

For second loop (fig(a))

$$-Z_3 I_1 + (Z_2 + Z_3)I_2 = 0 \quad \text{--- ②}$$

$$\therefore \Delta = \begin{bmatrix} Z_1 + Z_3 & -Z_3 \\ -Z_3 & Z_2 + Z_3 \end{bmatrix}$$



$$\Delta = (z_1 + z_3)(z_2 + z_3) - z_3^2$$

$$\Delta = z_1 z_2 + z_2 z_3 + z_3 z_1$$

$$\Delta_2 = \begin{bmatrix} z_1 + z_3 & V \\ -z_3 & 0 \end{bmatrix}$$

$$\Delta_2 = V z_3$$

from fig (a)  $I_x = I_2 = \frac{\Delta_2}{\Delta}$

$$I_x = \frac{V z_3}{z_1 z_2 + z_2 z_3 + z_3 z_1} \quad \text{--- (A)}$$

Now consider fig (b) :-

for 1st loop  $-z_1 I_1 - z_3(I_1 - I_2) = 0$

$$(z_1 + z_3) I_1 - z_3 I_2 = 0 \quad \text{--- (1)}$$

for second loop apply KVL,

$$-z_2 I_2 + V - z_3(I_2 - I_1) = 0$$

$$\cancel{(z_2 + z_3) I_2} - z_3 I_1 + (z_2 + z_3) I_2 = V \quad \text{--- (2)}$$

$$\Delta = \begin{bmatrix} (z_1 + z_3) & -z_3 \\ -z_3 & (z_2 + z_3) \end{bmatrix}$$

$$\Delta = z_1 z_2 + z_2 z_3 + z_3 z_1$$

$$\Delta_1 = \begin{bmatrix} 0 & -z_3 \\ V & z_1 + z_3 \end{bmatrix}$$

$$\Delta_1 = z_3 V$$



from fig (b)

$$I_1 = I_x = \frac{\Delta_1}{\Delta} = \frac{V z_3}{z_1 z_2 + z_2 z_3 + z_3 z_1} \quad \text{--- (B)}$$


from (A) & (B), reciprocity theorem is verified.

————— x —————

Thevenin's Theorem:-

Statement:- "For any linear bilateral complicated network connected to load may be replaced by a simple equivalent circuit consisting of a voltage source  $V_{th}$  in series with a resistor  $R_{th}$ , where  $V_{th}$  is the open-circuit voltage at the terminals and  $R_{th}$  is the input or equivalent resistance at its terminals when the independent sources are turned off or  $R_{th}$  is the ratio of open-circuit voltage to the short circuit current at the terminal pair."

Explanation:-

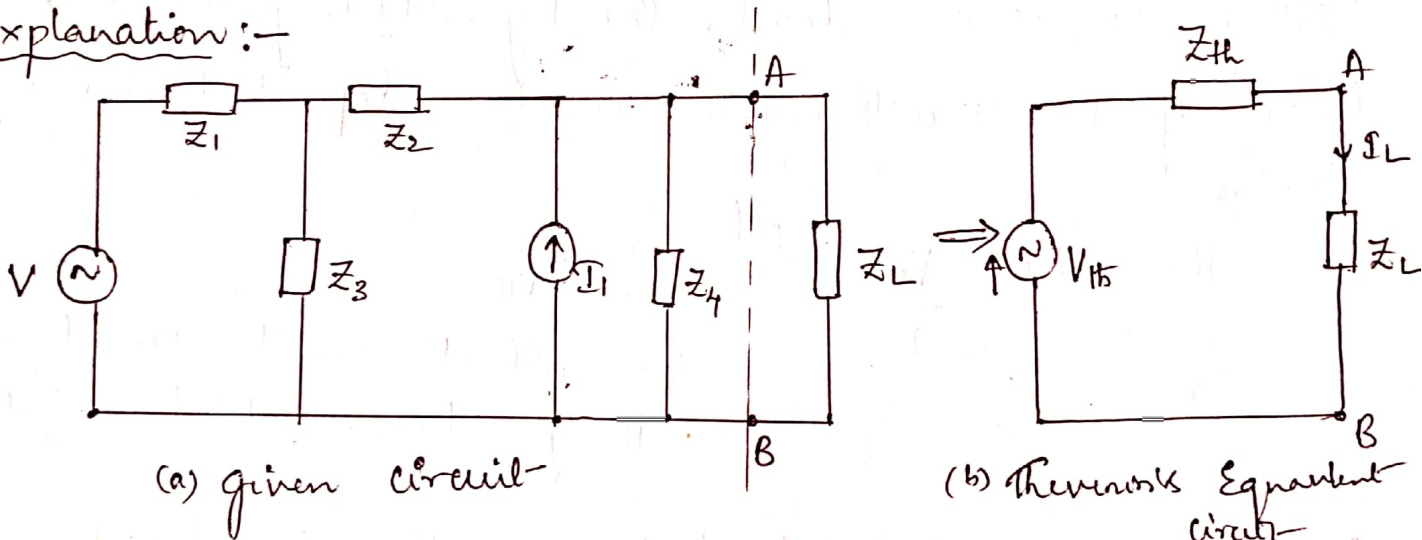

Consider a linear bilateral complicated n/w as shown in fig (a). According to Thevenin's theorem, the above complicated network can be reduced to a simple network as shown in fig (b).

The load current is calculated by,

$$I_L = \frac{V_{th}}{Z_{th} + Z_L}$$

Where,  $V_{th}$  → Thevenin's Equivalent voltage or open circuit voltage across the terminals A & B.

$Z_{th}$  → Equivalent impedance b/w the terminals A & B.

$Z_L$  → Load impedance.

Procedure:-

- 1) Remove the load impedance & create a open circuit across the load terminals A & B
- 2) Calculate open circuit voltage  $V_{th}$  across the load terminals
- 3) To find  $R_{th}$ :-

Case i) If the circuit contains only independent sources & resistors then deactivate the sources i.e, independent current sources are deactivated by opening them while independent voltage sources are deactivated by shorting them.

Case ii) If the circuit contains resistors, dependent & independent sources

then  $R_{th} = \frac{V_{oc}}{I_{sc}}$  where,  
 $V_{oc} = V_{th}$   
 $I_{sc}$  → short circuit current flowing through the short terminal a-b.

Case iii) If the circuit contains resistors & only dependent sources

1)  $V_{oc} = 0$  [ Since there is no energy source ]

2) Connect 1A current source to terminals a-b & determine  $V_{ab}$

3)  $R_{th} = \frac{V_{ab}}{1A}$

4) After finding  $V_{th}$  &  $R_{th}$ , write the Thevenin's equivalent circuit.



### \* Maximum Power transfer theorem :-

Statement :- "In any linear bilateral network, the maximum power is transferred from source to load when  
i) Load resistance is equal to source resistance.

i.e.,  $R_L = R_o$


ii) Load resistance is equal to magnitude of source impedance

i.e.,  $R_L = |Z_o|$

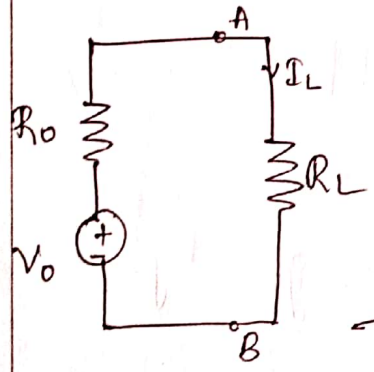iii) Load impedance is equal to complex conjugate of the source impedance.

i.e.,  $Z_L = Z_o^*$

Proof :- case i) when both source & load has resistance  
[DC circuits]



Where,  $V_o \rightarrow$  Source voltage.

$R_o \rightarrow$  Source resistance.

$R_L \rightarrow$  Load resistance.

The current flowing through the load is given by,

$$I_L = \frac{V_o}{R_o + R_L} \quad \text{--- ①}$$

The power delivered to the load is given by.

$$P = I_L^2 R_L \quad \text{--- ②}$$

$$P = \frac{V_o^2}{(R_o + R_L)^2} \times R_L$$

Power delivered to the load is maximum when,  $\frac{dP}{dR_L} = 0$



$$\frac{dP}{dR_L} = \frac{(R_0 + R_L)^2 \times V_0^2 - V_0^2 R_L \times 2(R_0 + R_L)}{[(R_0 + R_L)^2]^2} = 0$$

$$\Rightarrow (R_0 + R_L)^2 V_0^2 - V_0^2 R_L \times 2(R_0 + R_L) = 0$$

$$\Rightarrow (R_0^2 + R_L^2 + 2R_0 R_L) V_0^2 - V_0^2 [2R_0 R_L + 2R_L^2] = 0$$


$$\Rightarrow (R_0^2 + R_L^2 + 2R_0 R_L) V_0^2 = V_0^2 (2R_0 R_L + 2R_L^2)$$

$$R_0^2 + R_L^2 = 2R_L^2$$

$$R_0^2 = 2R_L^2 - R_L^2$$

$$R_0 = R_L$$

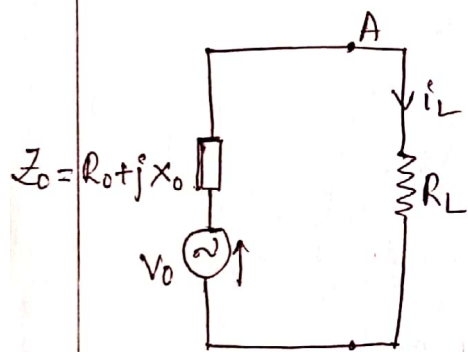Case ii) When source has impedance and load has resistance.



where,

$V_0 \rightarrow$  Source voltage.

$Z_0 \rightarrow$  Source impedance.

$R_L \rightarrow$  load resistance.

The current flowing through load is given by,

$$I_L = \frac{V_0}{Z_0 + R_L} = \frac{V_0}{R_0 + jX_0 + R_L}$$

$$I_L = \frac{V_0}{(R_0 + R_L) + jX_0}$$

$$I_L = \frac{V_0}{\sqrt{(R_0 + R_L)^2 + X_0^2}} \quad \text{--- ①}$$

The power delivered to the load is given by

$$P = I_L^2 R_L \quad \text{--- ②}$$

$$\therefore P = \frac{V_0^2 R_L}{(R_0 + R_L)^2 + X_0^2}$$

The power transferred to the load is max. when

$$\frac{dP}{dR_L} = 0$$

$$\frac{dP}{dR_L} = \frac{[(R_0 + R_L)^2 + X_0^2] \times V_0^2 - V_0^2 R_L \times 2(R_0 + R_L)}{[(R_0 + R_L)^2 + X_0^2]^2} = 0$$

$$\Rightarrow [(R_0 + R_L)^2 + X_0^2] V_0^2 = 2V_0^2 R_L (R_0 + R_L)$$

$$\Rightarrow R_0^2 + R_L^2 + 2R_0 R_L + X_0^2 = 2R_L R_0 + 2R_L^2$$

$$\Rightarrow R_0^2 + X_0^2 = 2R_L^2 - R_L^2$$

$$\Rightarrow R_0^2 + X_0^2 = R_L^2$$


$$\therefore R_L = \sqrt{R_0^2 + X_0^2}$$

$$R_L = R_0 + jX_0$$

$$\Rightarrow \boxed{R_L = |Z_0|}$$

Hence, the load resistance is equal to magnitude of source impedance is proved.

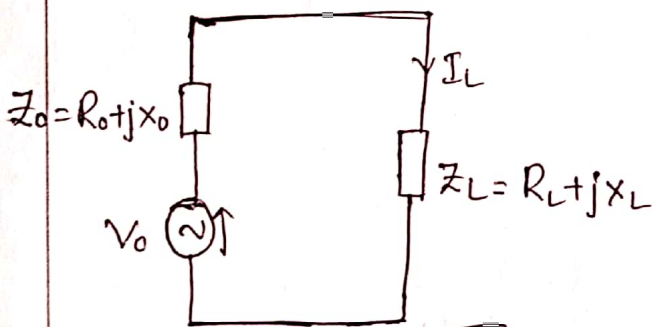case iii) Both source & load has impedances (AC circuits):



where,  $Z_0 \rightarrow$  Source impedance

$V_0 \rightarrow$  Source voltage.

$Z_L \rightarrow$  load impedance.

The current flowing through the load is

$$I_L = \frac{V_0}{Z_0 + Z_L} = \frac{V_0}{R_0 + jX_0 + R_L + jX_L}$$

$$I_L = \frac{V_0}{R_0 + R_L + j(X_0 + X_L)} = \frac{V_0}{\sqrt{(R_0 + R_L)^2 + (X_0 + X_L)^2}}$$

The power delivered to the load is,

$$P = I_L^2 Z_L$$

$$P = I_L^2 \times (R_L + jX_L) \quad (\text{since power consumed in inductor is zero})$$

$$P = I_L^2 R_L \quad \text{--- (2)}$$

Substitute (1) in (2), we get-

$$P = \left[ \frac{V_0^2}{\sqrt{(R_0 + R_L)^2 + (X_0 + X_L)^2}} \right]^2 \times R_L$$

$$P = \frac{V_0^2 R_L}{(R_0 + R_L)^2 + (X_0 + X_L)^2}$$

Power delivered to the load is max when  $\frac{dP}{dR_L} = 0$

$$\therefore \frac{dP}{dR_L} = \frac{[(R_0 + R_L)^2 + (X_0 + X_L)^2] V_0^2 - V_0^2 R_L \times 2(R_0 + R_L)}{[(R_0 + R_L)^2 + (X_0 + X_L)^2]^2} = 0$$

$$\Rightarrow [(R_0 + R_L)^2 + (X_0 + X_L)^2] V_0^2 = 2 V_0^2 R_L (R_0 + R_L)$$

$$\Rightarrow R_0^2 + R_L^2 + 2R_0 R_L + (X_0 + X_L)^2 = 2R_L R_0 + 2R_L^2$$

$$\Rightarrow R_0^2 + (X_0 + X_L)^2 = 2R_L^2 - R_L^2$$

$$\Rightarrow R_0^2 + (X_0 + X_L)^2 = R_L^2$$

$$\therefore R_L = \sqrt{R_0^2 + (X_0 + X_L)^2}$$

$$R_L = R_0 + j(X_0 + X_L)$$

$$R_L = R_0 + jX_0 + jX_L$$

$$R_L - jX_L = R_0 + jX_0$$

$$Z_L^* = Z_0$$

$$\therefore \boxed{Z_L = Z_0^*}$$


$$\left\{ \begin{array}{l} x + jy = \sqrt{x^2 + y^2} \\ Z_0 = R_0 + jX_0 \\ Z_L = R + jX_L \\ Z_L^* = R - jX_L \end{array} \right.$$



# Norton's Theorem :-

Statement :- "In any linear <sup>bi</sup> lateral complicated n/w connected to load may be replaced by a simple network containing a current source & an impedance in parallel with it. The current source 'I<sub>sc</sub>' is the short circuit current in load terminals & Z<sub>th</sub> is the value of impedance looking from the load terminals replacing all the voltage sources by short circuit & all the current sources by open circuit."

Explanation :-

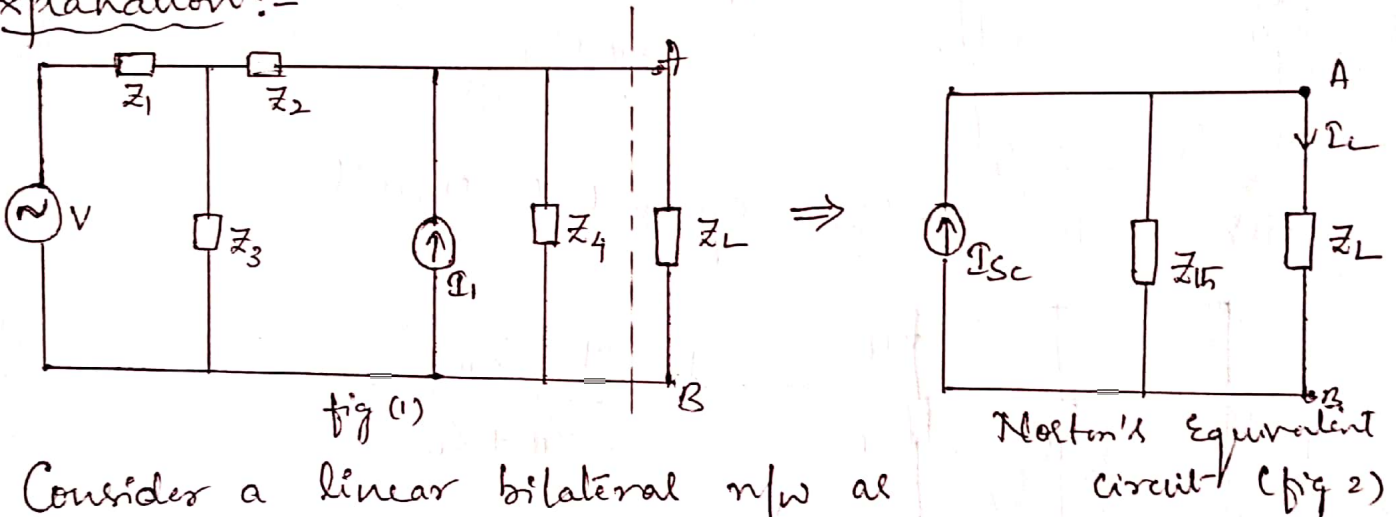

Consider a linear bilateral n/w as shown in fig (1)

According to Norton's theorem. The above complicated network can be reduced into a simple n/w as shown in fig (2)

The load current is calculated by using

$$I_L = \frac{I_{sc} \times Z_{th}}{Z_{th} + Z_L}$$

Where I<sub>sc</sub> → short circuit current or Norton's current  
Z<sub>th</sub> → Norton's equivalent imp. &  
Z<sub>L</sub> → load impedance.

Procedure :- 1) Remove the load impedance & short-circuit the load terminals A & B.



OC  $\rightarrow$  open circuit SC  $\rightarrow$  Short circuit

1. Calculate the short ckt current  $I_{sc}$  through the load terminals


2. Replace all the reg source by SC & all the current sources by OC.

3. Find the equivalent impedance  $Z_{th}$  ( $Z_N$ ) as looking from the load terminals

Thevenin's equivalent is the dual of Norton's equivalent


Comment on the above statement

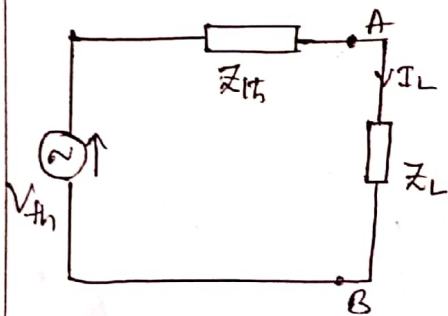Soln Consider the Thevenin's equivalent circuit



$$I_L = \frac{V_{th}}{Z_{th} + Z_L} \quad \text{--- (1)}$$

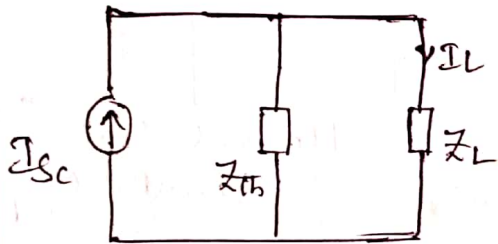Consider the Norton's equivalent circuit,



$$I_L = \frac{I_{sc} Z_{th}}{Z_{th} + Z_L} \quad \text{--- (2)}$$

from (1) & (2)

$$\frac{V_{th}}{Z_{th} + Z_L} = \frac{I_{sc} Z_{th}}{Z_{th} + Z_L}$$

$$\Rightarrow \boxed{V_{th} = I_{sc} \cdot Z_{th}} \quad \text{--- (3)}$$

$$\text{or } \boxed{I_{sc} = \frac{V_{th}}{Z_{th}}} \quad \text{--- (4)}$$

where,

$V_{th} \rightarrow$  Thevenin's reg

$I_{sc} \rightarrow$  Norton's current

$Z_{th} \rightarrow$  Thevenin's equivalent impedance

$\therefore$  Norton's equivalent circuit can be converted into Thevenin's equivalent circuit using equation (3) & the Thevenin's equivalent circuit can be converted into Norton's equivalent circuit by using eqn (4).

Norton's theorem :

Statement :

Any Linear, bilateral Complicated N/w. Connected to a load impedance can be replaced by a simple equivalent ckt containing a current source of current  $I_{sc}$  in parallel with impedance  $Z_{th}$ .

Where,  $I_{sc} \rightarrow$  Short ckt current in the load terminals.

$Z_{th} \rightarrow$  Equivalent impedance of the N/w as looking from the load terminals, replacing all the voltage sources by short ckt & all current sources by open ckt.

Explanation :

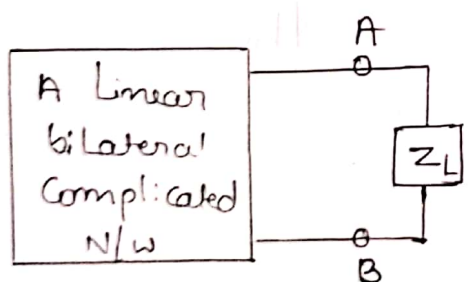


Fig (a) Complicated N/w

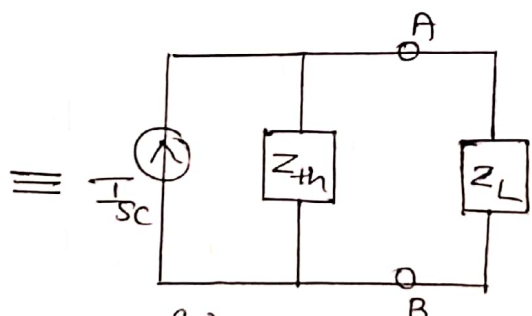


Fig (b). ~~Thevenin's~~ Norton's N/w.

Consider a linear, bilateral, Complicated N/w as shown in fig (a). According to ~~Thevenin's~~ Norton's theorem the Complicated N/w reduced to a simple as shown in fig (b).

The load current is 
$$I_L = \frac{I_{sc} \times Z_{th}}{Z_{th} + Z_L}$$

Where,  $I_{sc}$   $\rightarrow$  Short ckt. Current or Norton's Current.

$Z_{th}$   $\rightarrow$  Equivalent impedance w.r.t A & B

$Z_L$   $\rightarrow$  Load impedance.


### Procedure:-

- 1) Remove the load impedance & short the load terminals A & B.
- 2) Calculate the short ckt. Current  $[I_{sc}]$  through the load terminals.
- 3) Replace all the independent voltage sources by short ckt & all the independent current sources by open ckt.
- 4) Find the equivalent impedance w.r.t A & B.
- 5) Write the Norton's equivalent ckt.
- 6) Calculate the load current  $I_L = \frac{I_{sc} \times Z_{th}}{Z_{th} + Z_L}$

Jan  
SMKR

\* Theremin's equivalent is the dual of Norton's equivalent". Comment on the above statement & substantiate the same.


Theremin's equivalent ckt is

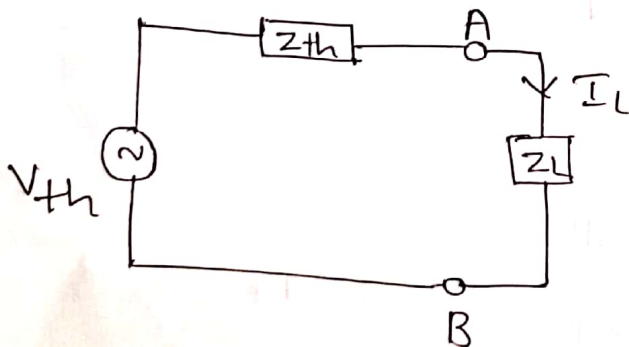

$$I_L = \frac{V_{th}}{Z_{th} + Z_L} \rightarrow \text{①}$$



Norton's equivalent CKT is

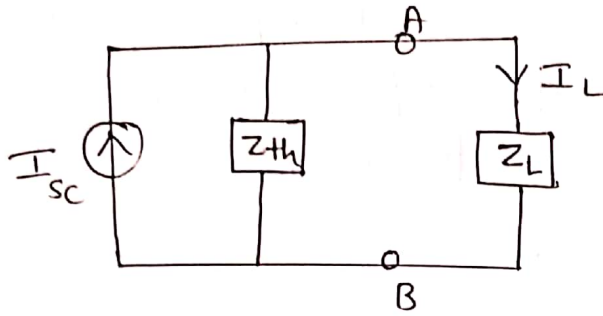

$$I_L = \frac{I_{sc} \times Z_{th}}{Z_{th} + Z_L} \longrightarrow \textcircled{2}$$

From ① & ②

$$\frac{V_{th}}{Z_{th} + Z_L} = \frac{I_{sc} \cdot Z_{th}}{Z_{th} + Z_L}$$

$$V_{th} = I_{sc} \cdot Z_{th} \longrightarrow \textcircled{3}$$

$$I_{sc} = \frac{V_{th}}{Z_{th}} \longrightarrow \textcircled{4}$$

Where  $V_{th} \rightarrow$  Thevenins voltage

$I_{sc} \rightarrow$  Norton's current

$Z_{th} \rightarrow$  Equivalent impedance




\* Norton's equivalent CKT can be converted into thevenins equivalent CKT by eqn ③

\* Thevenins equivalent CKT can be converted into Norton's equivalent CKT by eqn ④




Problems :

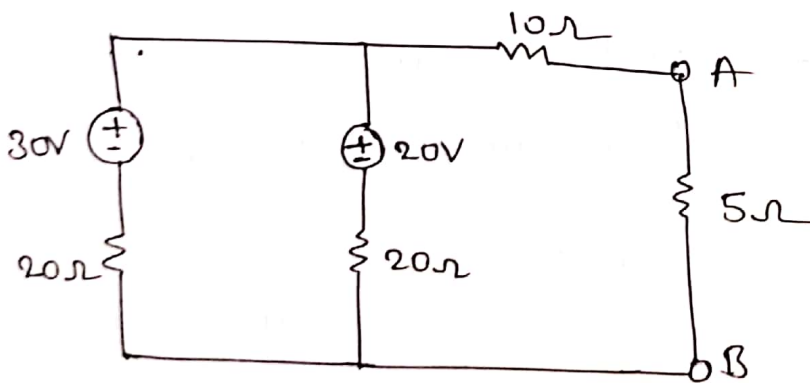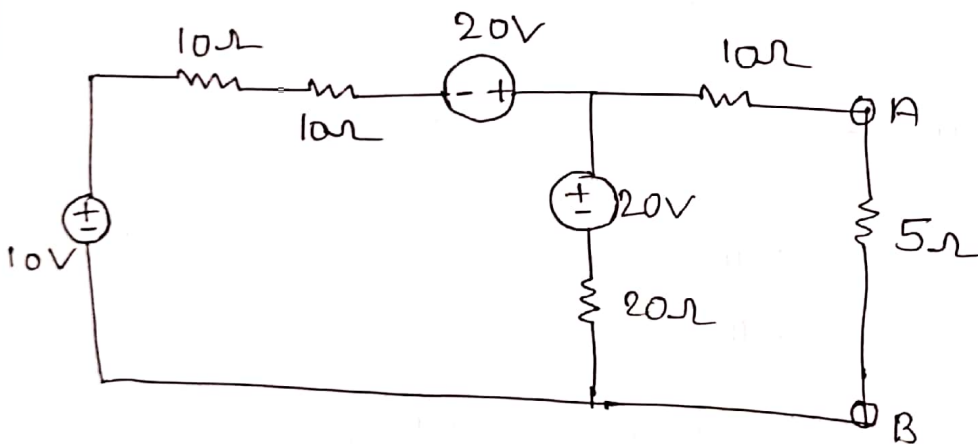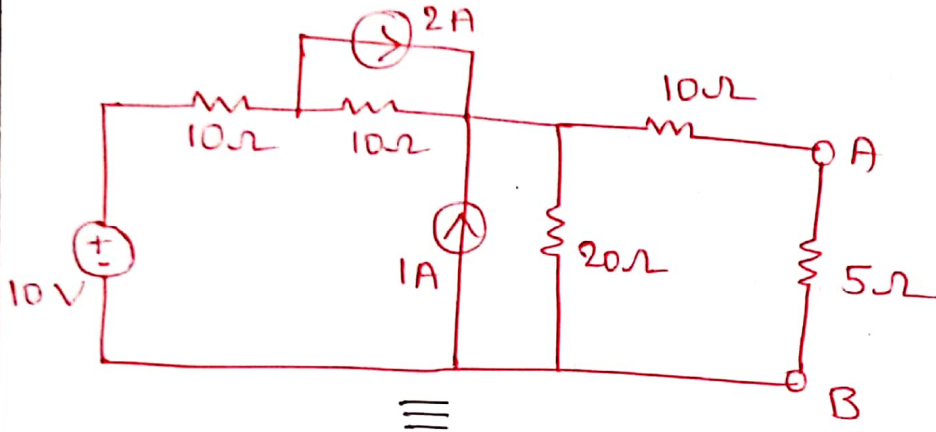
1) Draw the Thevenin's equivalent N/W & Norton's equivalent N/W for the N/W shown & also find current flowing through  $5\Omega$  resistor connected b/w A & B.



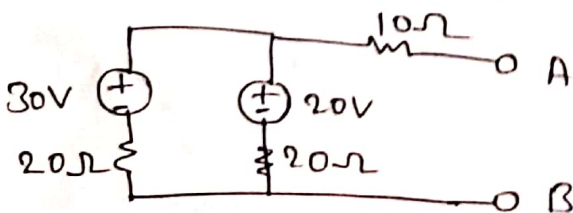Remove the Load & create open ckt b/w A & B



To find  $V_{th}$  :

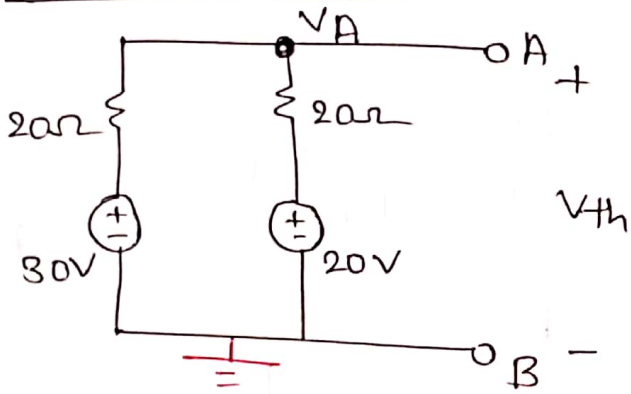

Apply KCL at node  $V_A$

$$\frac{V_A - 30}{20} + \frac{V_A - 20}{20} = 0$$


$$V_A - 30 + V_A - 20 = 0$$

$$2V_A - 50 = 0$$

$$V_A = \frac{50}{2} = 25 \text{ V}$$


$$\begin{aligned} \therefore V_{th} = V_{AB} &= V_A - V_B \\ &= 25 - 0 \\ &= \underline{\underline{25 \text{ V}}} \end{aligned}$$

To find  $R_{th}$  :

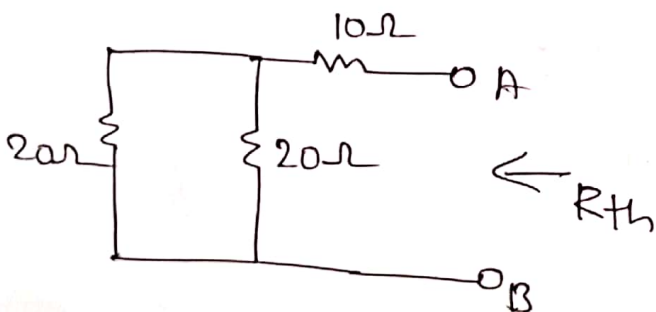

$$\begin{aligned} R_{th} &= (20 \parallel 20) + 10 \\ &= 10 + 10 \\ &= 20 \Omega \end{aligned}$$

Thevenins equivalent N/w :-

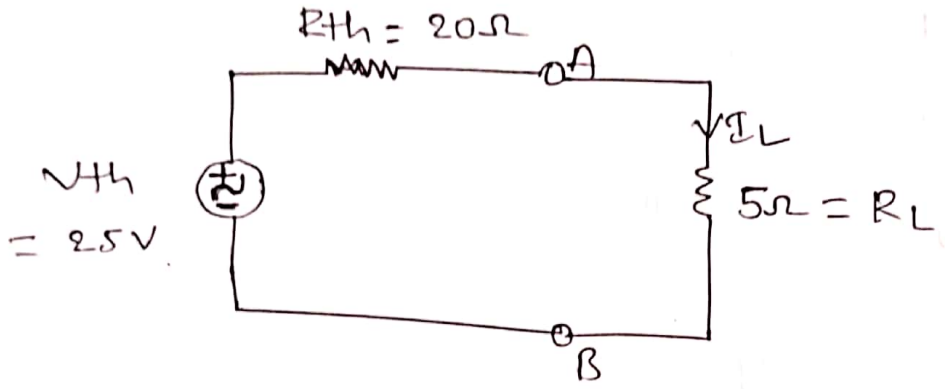

$$I_L = \frac{V_{th}}{R_{th} + R_L}$$


$$I_L = \frac{25}{20 + 5}$$

Norton's equivalent N/w :-

w.k.t

$$I_L = 1A$$
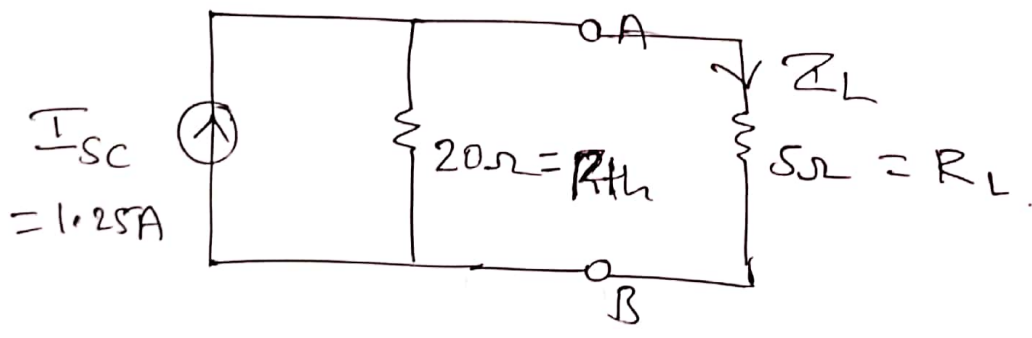
$$I_{sc} = \frac{V_{th}}{R_{th}} = \frac{25}{20} = 1.25A$$




$$I_L = \frac{I_{sc} R_{th}}{R_{th} + R_L}$$


$$= \frac{1.25 \times 20}{20 + 5}$$

$$I_L = 1A$$

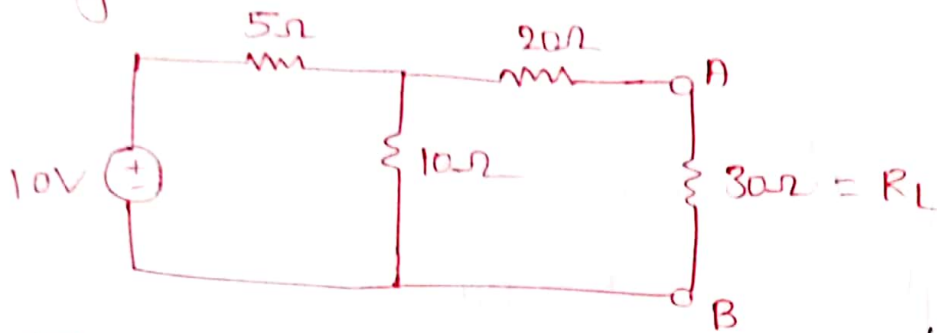2) Find the Current through  $30\Omega$  load resistor using Norton's theorem.



Remove the load & Create the short ckt.

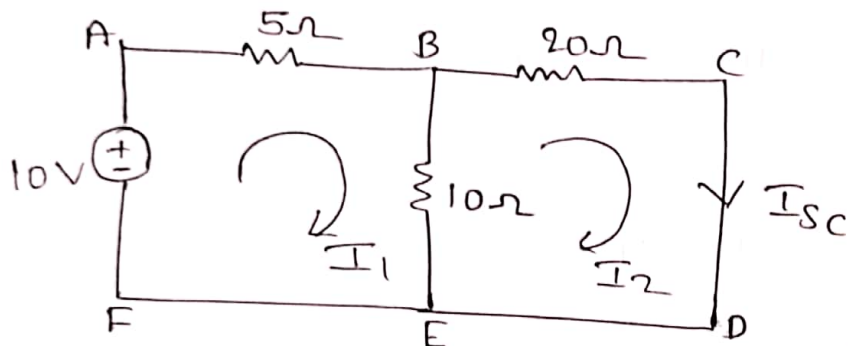

From the ckt

$$\therefore I_{sc} = ?$$

$$I_{sc} = I_e$$

KVL to the 1st loop:

$$10 - 5I_1 - 10[I_1 - I_2] = 0$$

$$10 - 5I_1 - 10I_1 + 10I_2 = 0$$

$$-15I_1 + 10I_2 = -10 \rightarrow \textcircled{1}$$

KVL to the 2nd loop:

$$-20I_2 - 10[I_2 - I_1] = 0$$

$$-20I_2 - 10I_2 + 10I_1 = 0$$

$$10I_1 - 30I_2 = 0 \rightarrow \textcircled{2}$$


Solving  $\textcircled{1}$  &  $\textcircled{2}$ .

$$I_1 = 0.857A \quad I_2 = 0.2857A$$



$$\therefore I_{sc} = I_2 = 0.2857 \text{ A}$$


To find  $R_{th}$  :

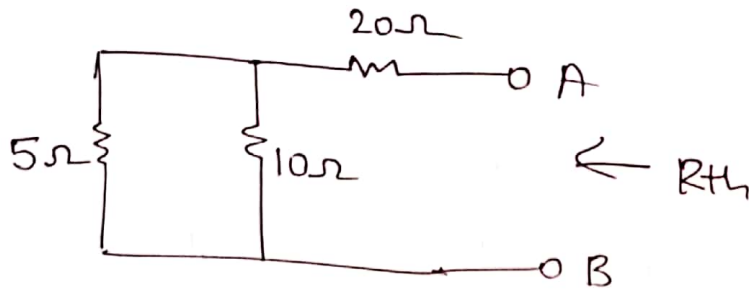

$$R_{th} = (5 \parallel 10) + 20$$

$$= 23.33 \Omega$$

Norton's equivalent N/W :-

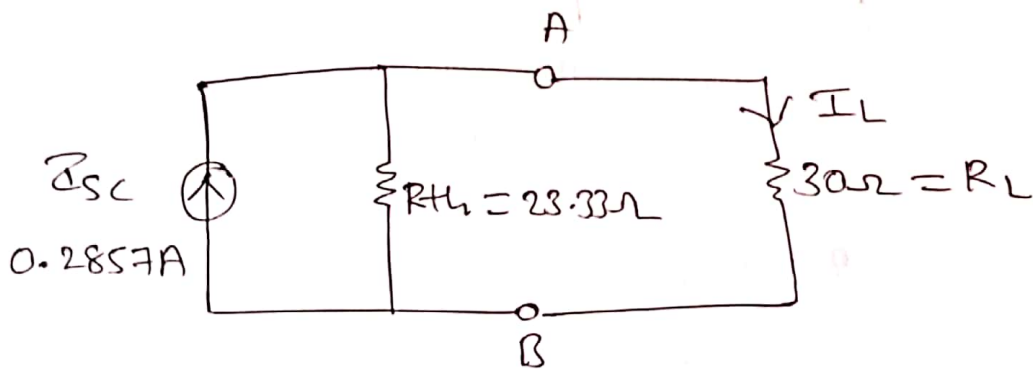


$$I_L = \frac{I_{sc} \times R_{th}}{R_{th} + R_L}$$


$$= \frac{0.2857 \times 23.33}{23.33 + 30}$$

$$I_L = \underline{0.125 \text{ A}}$$

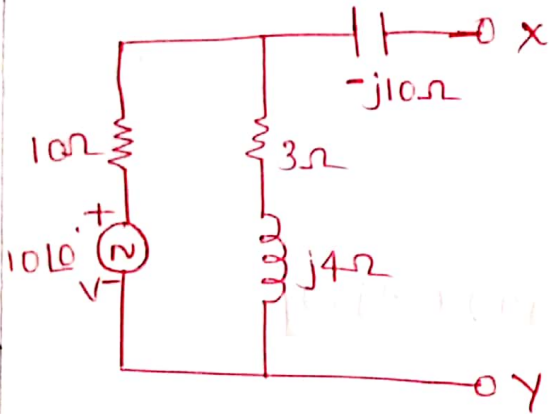3. Obtain the Norton's equivalent ckt for the NW shown



To find  $I_{sc}$ :

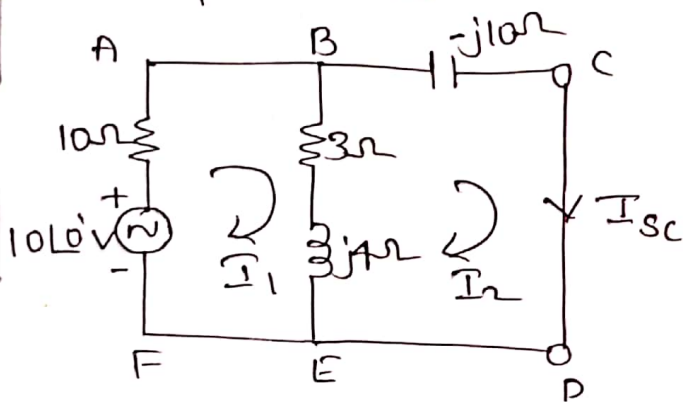

$$I_{sc} = I_2$$

Apply KVL to the 1<sup>st</sup> Loop

$$10\angle 0 - 10I_1 - 3[I_1 - I_2] - j4[I_1 - I_2] = 0$$

$$10\angle 0 - 10I_1 - 3I_1 + 3I_2 - j4I_1 + j4I_2 = 0$$

$$-13I_1 - j4I_1 + 3I_2 + j4I_2 = -10\angle 0$$

$$(-13 - j4)I_1 + (3 + j4)I_2 = -10\angle 0 \rightarrow \textcircled{1}$$

Apply KVL to the 2<sup>nd</sup> Loop..

$$+j10\Omega I_2 - (3 + j4)(I_2 - I_1) = 0$$

$$j10\Omega I_2 - (3 + j4)I_2 + (3 + j4)I_1 = 0$$

$$(3 + j4)I_1 + (-3 + j6)I_2 = 0 \rightarrow \textcircled{2}$$

$$\Delta = \begin{vmatrix} -13 - j4 & 3 + j4 \\ 3 + j4 & -3 + j6 \end{vmatrix}$$

$$= [(-13 - j4)(-3 + j6) - (3 + j4)(3 + j4)]$$

$$= 70 - 90j$$

$$\Delta_2 = \begin{vmatrix} -13 - j4 & -10 \angle 0^\circ \\ 3 + j4 & 0 \end{vmatrix}$$


$$= + (3 + j4)(10 \angle 0^\circ)$$

$$= 30 + 40j$$

$$\therefore I_{SC} = I_2 = \frac{\Delta_2}{\Delta} = \frac{30 + 40j}{70 - 90j} = -0.115 + 0.42j$$

$$= 0.439 \angle 105.3^\circ \text{ A}$$

To find  $Z_{th}$ :

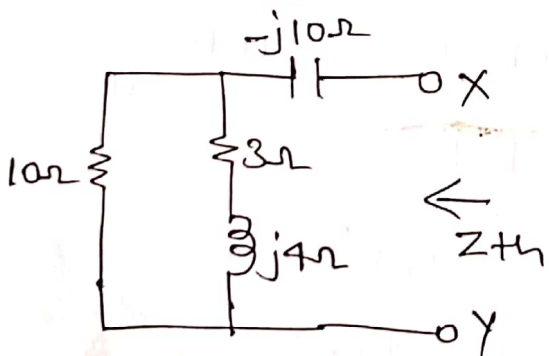


$$Z_{th} = \frac{10 * (3 + j4) - j10}{10 + 3 + j4}$$

$$= 2.97 - 7.84j$$

$$= 8.38 \angle -69.23^\circ \Omega$$

Norton's equivalent N/w:

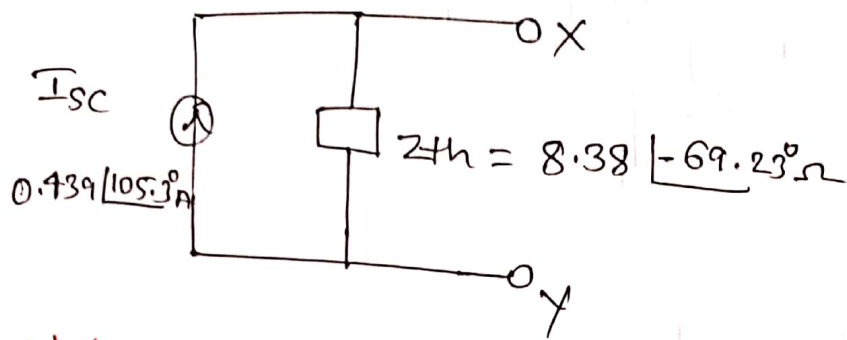

Note: If the given N/w consists of some dependent source, then these dependent sources must be kept as it is while calculating  $Z_{th}$  & should not be shorted or open ckted whether it is voltage or current source.

In such cases,  $Z_{th}$  is given by


$$Z_{th} = \frac{V_{th}}{I_{sc}}$$

where  $I_{sc} \rightarrow$  Norton's current


$V_{th} \rightarrow$  Thevenin's voltage.

Jan 08  
Dec 12  
4<sup>th</sup> July 14  
GMSB

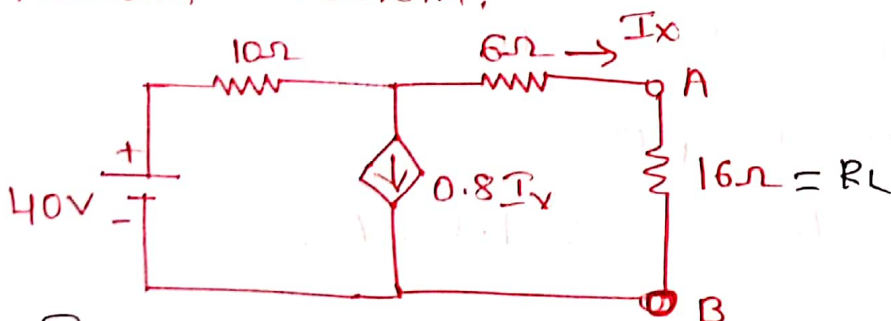
Find the current through  $16 \Omega$  resistor using Norton's theorem.



Remove the Load

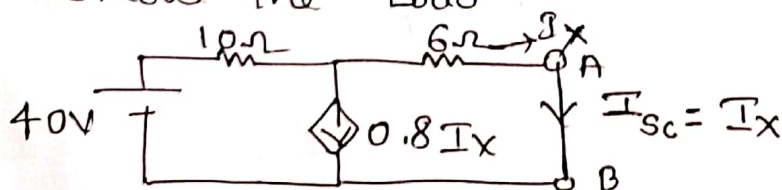



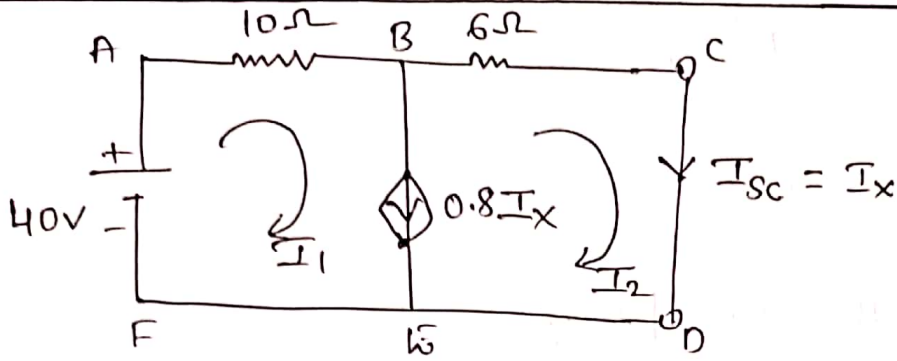

$$I_{sc} = I_x = I_2$$

$0.8I_x$  is in b/w two meshes  $\therefore$  it forms  
supermesh ABCDEFA.

$$I_1 - I_2 = 0.8I_x$$

$$I_1 - I_2 = 0.8I_2$$

$$I_1 - I_2 - 0.8I_2 = 0$$

$$I_1 - 1.8I_2 = 0$$

$\rightarrow$  ①

Apply KVL to the supermesh

$$-10I_1 - 6I_2 + 40 = 0$$

$$-10I_1 - 6I_2 = -40 \rightarrow \textcircled{2}$$



Solving ① & ②

$$I_1 = 3A \quad I_2 = 1.67A$$


$$\therefore I_{sc} = I_2 = 1.67A$$

To find  $Z_{th}$ :


creat open CKT b/w A & B

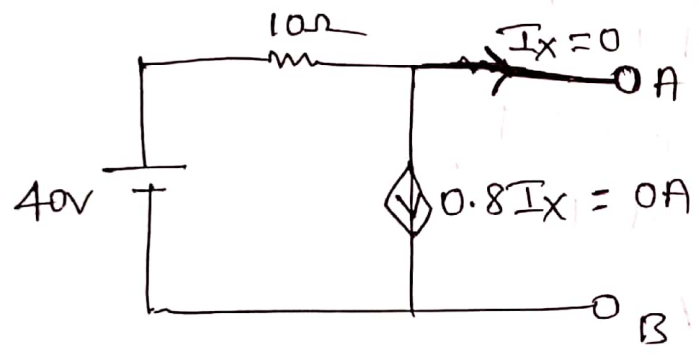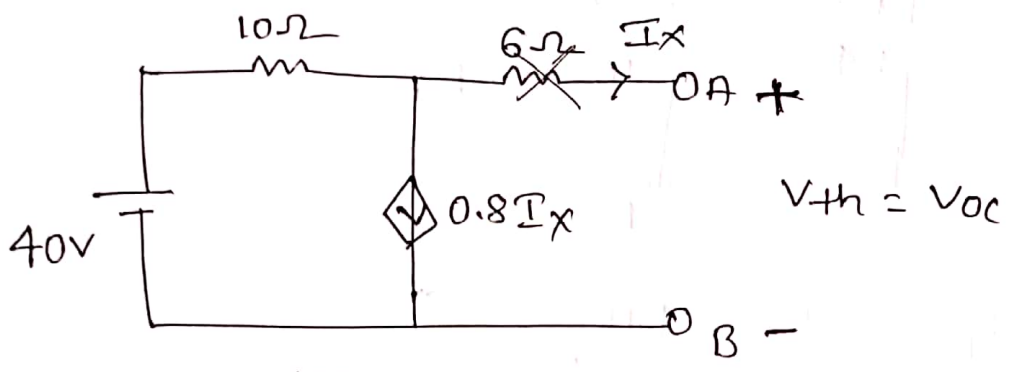

NO current flows through  $6\Omega$

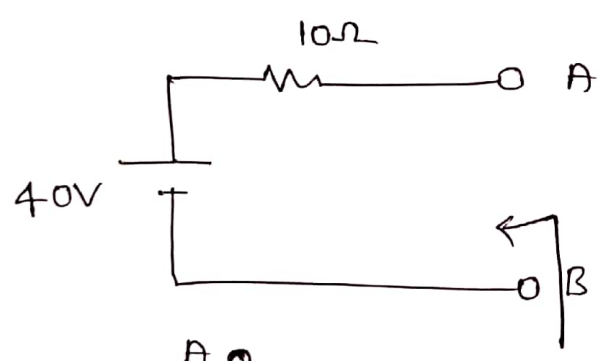

NO current flows through  $10\Omega$

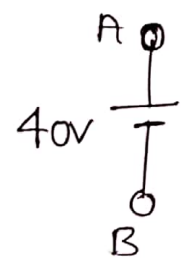


$\therefore V_{th} = V_{AB} = 40V$

$\therefore Z_{th} = \frac{V_{th}}{I_{sc}}$

$= \frac{40}{1.67} = 24\Omega = R_{th}$

∴ Norton's equivalent CKT

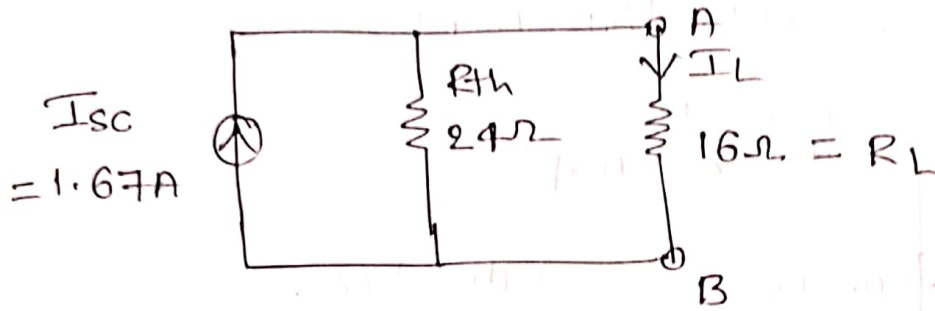

$$\begin{aligned} \therefore I_L &= \frac{I_{sc} \times R_{th}}{R_{th} + R_L} \\ &= \frac{1.67 \times 24}{24 + 16} \end{aligned}$$

$$\underline{I_L = 1A}$$

## Maximum power transfer theorem:

### Statement:

In any linear bilateral N/w, the Maximum power is transferred from source to load when

1) Load resistance = Source resistance i.e.  $R_L = R_S$

2) Load resistance = Magnitude of source impedance


$$\text{i.e. } R_L = |Z_S|$$

3) Load impedance = Complex Conjugate of source impedance

$$\text{i.e. } Z_L = Z_S^*$$

### Proof:

Case (1): P.T.  $R_L = R_S$

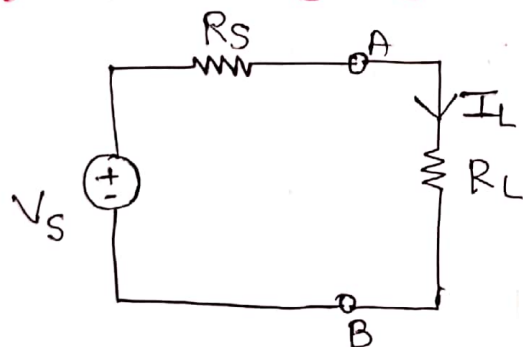

$V_S \rightarrow$  Source Voltage

$R_S \rightarrow$  Source resistance

$R_L \rightarrow$  Load resistance

The power delivered to the load is

$$P = I_L^2 R_L \rightarrow (1)$$

$$\text{But } I_L = \frac{V_S}{R_S + R_L} \rightarrow (2)$$

Substitute (2) in (1)

$$P = \frac{V_S^2}{(R_S + R_L)^2} \cdot R_L \rightarrow (3)$$



The power delivered to the load is maximum when  $\frac{dp}{dR_L} = 0 \rightarrow$  Maxima theorem.

$$\frac{dp}{dR_L} = 0$$

$$\frac{d}{dR_L} \left[ \frac{V_S^2}{(R_S + R_L)^2} R_L \right] = 0$$

$$\frac{(R_S + R_L)^2 V_S^2 - V_S^2 R_L \cdot 2 [R_S + R_L]}{(R_S + R_L)^4} = 0$$

$$(R_S + R_L)^2 V_S^2 - 2 V_S^2 R_S R_L - 2 V_S^2 R_L^2 = 0$$

$$(2 R_S R_L + R_S^2 + R_L^2) V_S^2 - 2 V_S^2 R_S R_L - 2 V_S^2 R_L^2 = 0$$


$$\cancel{2 R_S R_L V_S^2} + R_S^2 V_S^2 + R_L^2 V_S^2 - \cancel{2 V_S^2 R_S R_L} - 2 V_S^2 R_L^2 = 0$$

$$R_S^2 V_S^2 - R_L^2 V_S^2 = 0$$

$$R_S^2 V_S^2 = R_L^2 V_S^2$$

$$\therefore \boxed{R_L = R_S}$$

Case (2) : P.T  $R_L = |Z_g|$

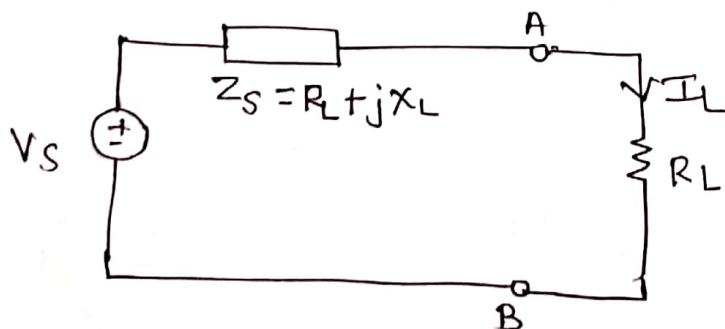

The power delivered to the load is

$$P = I_L^2 R_L \rightarrow \textcircled{1}$$

The load current is given by

$$I_L = \frac{V_S}{Z_S + R_L}$$

$$= \frac{V_S}{R_S + jX_S + R_L}$$

$$= \frac{V_S}{(R_S + R_L) + jX_S}$$

$$I_L = \frac{V_S}{\sqrt{(R_S + R_L)^2 + X_S^2}} \rightarrow \textcircled{2}$$

Substitute  $\textcircled{2}$  in  $\textcircled{1}$

$$P = \frac{V_S^2 R_L}{(R_S + R_L)^2 + X_S^2}$$

The power delivered to the load is maximum when

$$\frac{dP}{dR_L} = 0 \rightarrow \text{Maxima theorem}$$

$$\frac{d}{dR_L} \left[ \frac{V_S^2 R_L}{(R_S + R_L)^2 + X_S^2} \right] = 0$$

$$\left[ (R_S + R_L)^2 + X_S^2 \right] V_S^2 - V_S^2 R_L \cdot 2 [R_S + R_L] \cdot \frac{1}{(R_S + R_L)^2 + X_S^2} = 0$$

$$(R_S + R_L)^2 + X_S^2 - 2R_L(R_S + R_L) = 0$$

$$R_S^2 + R_L^2 + \cancel{2R_S R_L} + X_S^2 - \cancel{2R_S R_L} - 2R_L^2 = 0$$

$$R_S^2 + X_S^2 - R_L^2 = 0$$

$$R_L^2 = R_S^2 + X_S^2$$

$$R_L = \sqrt{R_S^2 + X_S^2}$$

$$R_L = |Z_S|$$


Case 3 : P.T  $Z_L = Z_S^*$

or

State & prove maximum power transfer theorem for AC Ckt.

or

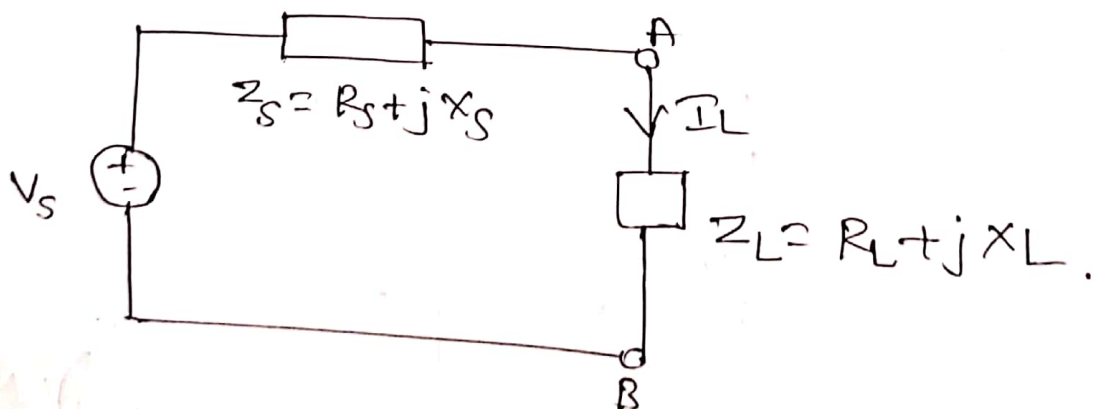P.T an alternating voltage source transfer maximum power to the load when the load impedance is equal to complex conjugate of the source impedance.



The power delivered to the load is

$$P = I_L^2 Z_L$$

$$P = I_L^2 [R_L + jX_L]$$

Power consumed by the inductor or Capacitor is zero

$$\therefore P = I_L^2 R_L \longrightarrow \textcircled{1}$$

The load current is given by

$$\begin{aligned} I_L &= \frac{V_S}{Z_S + Z_L} \\ &= \frac{V_S}{(R_S + jX_S) + (R_L + jX_L)} \end{aligned}$$

$$= \frac{V_S}{(R_S + R_L) + j(X_S + X_L)}$$

$$I_L = \frac{V_S}{\sqrt{(R_S + R_L)^2 + (X_S + X_L)^2}}$$

$$\textcircled{2} \text{ in } \textcircled{1} \longrightarrow \textcircled{2}$$

$$P = \frac{V_S^2 R_L}{(R_S + R_L)^2 + (X_S + X_L)^2}$$



The power delivered to the load is maximum

When  $\frac{dp}{dR_L} = 0$

$$\frac{d}{dR_L} \left[ \frac{V_S^2 R_L}{(R_S + R_L)^2 + (X_S + X_L)^2} \right] = 0$$

$$\frac{[(R_S + R_L)^2 + (X_S + X_L)^2] V_S^2 - V_S^2 R_L \cdot 2(R_S + R_L)}{((R_S + R_L)^2 + (X_S + X_L)^2)^2} = 0$$

$$(R_S + R_L)^2 + (X_S + X_L)^2 - 2R_L(R_S + R_L) = 0$$

$$R_S^2 + R_L^2 + \cancel{2R_S R_L} + X_S^2 + X_L^2 + \cancel{2X_S X_L} - \cancel{2R_L R_S} - 2R_L^2 = 0$$

$$R_S^2 + R_L^2 + (X_S + X_L)^2 - 2R_L^2 = 0$$

$$R_S^2 + (X_S + X_L)^2 - R_L^2 = 0$$

$$R_L^2 = R_S^2 + (X_S + X_L)^2$$

$$R_L = \sqrt{R_S^2 + (X_S + X_L)^2}$$

$$R_L = R_S + j(X_S + X_L)$$

$$R_L = R_S + jX_S + jX_L$$



$$R_L - jX_L = R_S + jX_S$$

$$Z_L^* = Z_S$$


$$\text{or } \boxed{Z_L = Z_S^*}$$

6-time Problems :-

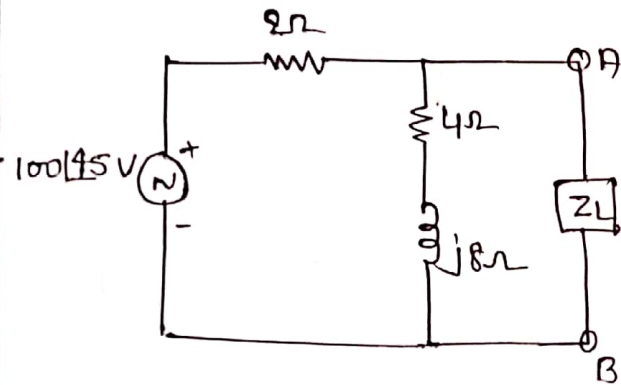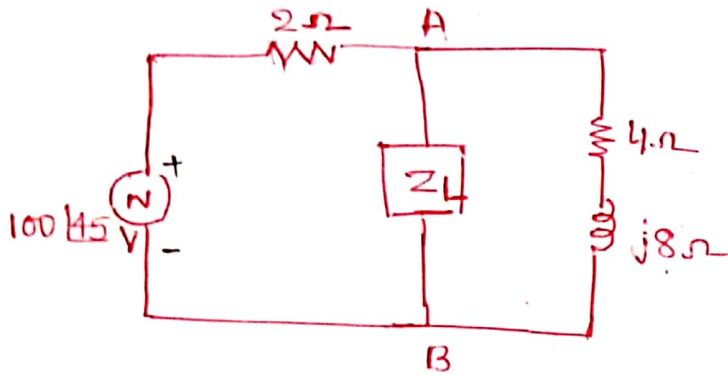1) The N/W shown in figure determine  $Z_L$  for which power transfer is maximum. Calculate the maximum power transferred to the load.



Remove the load

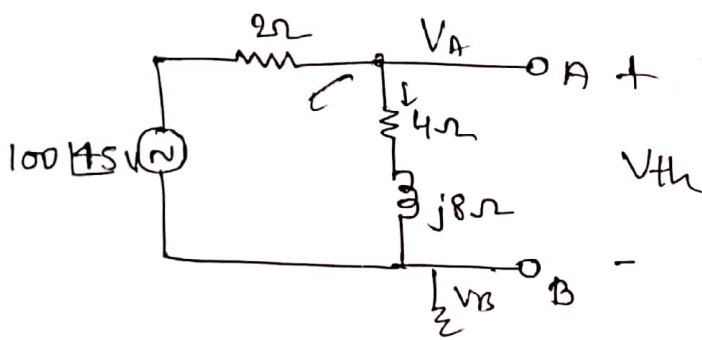

$$V_{th} = V_A - V_B \quad \text{and} \quad V_B = 0$$

$$\frac{V_A - 100 \angle 45^\circ}{2} + \frac{V_A}{4 + j8} = 0$$

$$0.5 V_A - 50 \angle 45^\circ + \frac{V_A}{8.94 \angle 63.43^\circ} = 0$$

~~$$V_{th} = \frac{100 \angle 45^\circ \times (4 + j8)}{2 + 4 + j8}$$~~

$$0.5 V_A - 50 \angle 45^\circ + 0.1118 \angle 63.43^\circ V_A = 0$$

~~$$V_{th} = 89.44 \angle 55.3^\circ \text{ V}$$~~


$$V_A = 89.4 \angle 55.3^\circ \text{ volts}$$

$$\rightarrow 0.5 V_A + 0.05 V_A - j0.099 V_A = 50 \angle 45^\circ$$

$$(0.55 - j0.099) V_A = 50 \angle 45^\circ$$

$$V_A = \frac{50 \angle 45^\circ}{0.558 \angle -10.2^\circ}$$


To find  $Z_{th}$  :-

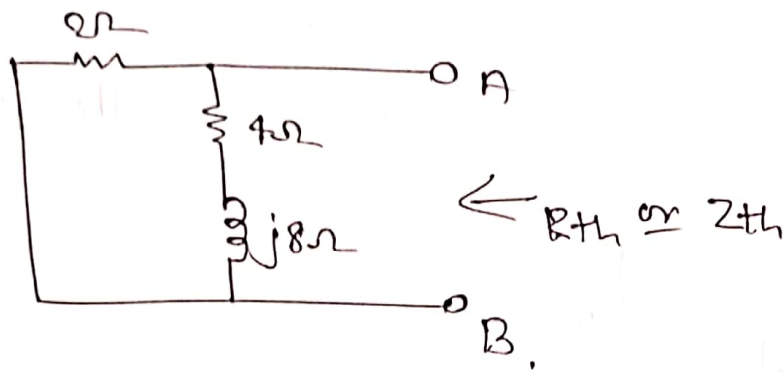

$$Z_{th} = \frac{2 \times (4 + j8)}{2 + 4 + j8}$$

$$Z_{th} = 1.76 + 0.32j$$

Thevenins equivalent N/W.

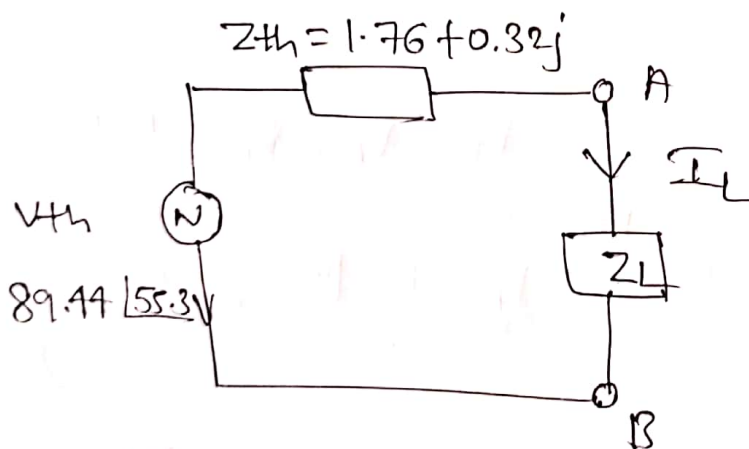

The power is maximum.

When  $Z_L = Z_S^*$

~~$Z_L = Z_{th}^*$~~   $Z_L = Z_{th}^*$

$$Z_L = 1.76 - 0.32j \Omega$$

$$\therefore I_L = \frac{V_{th}}{Z_{th} + Z_L} = \frac{89.44 / 55.3}{1.76 + 0.32j + 1.76 - 0.32j}$$

$$I_L = 25.41 \sqrt{55.3} \text{ A}$$

∴ Maximum power delivered is


$$P = I_L^2 \times R_L$$

$$= 25.41 \sqrt{55.3} \times 1.76$$



$$P = \underline{1.136 \text{ kW}}$$



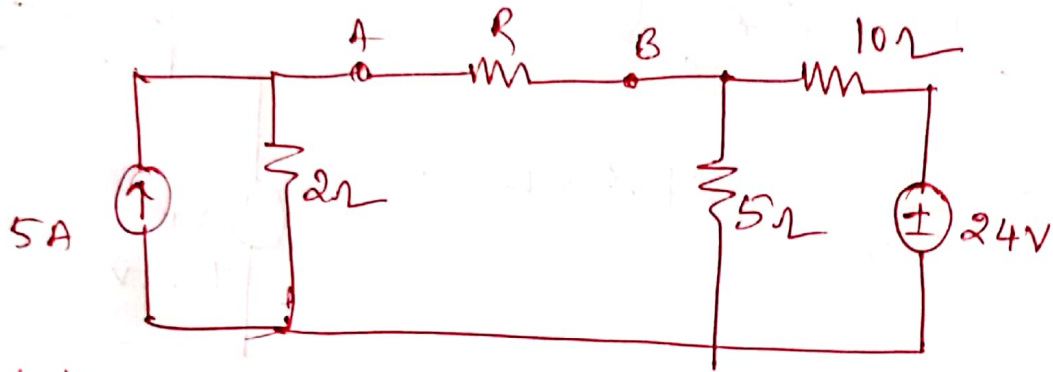2) What should be the value of  $R$  such that max power transfer can take place from the rest of the n/w to  $R$ . Obtain the amount of this power.




To find  $V_{th}$ :

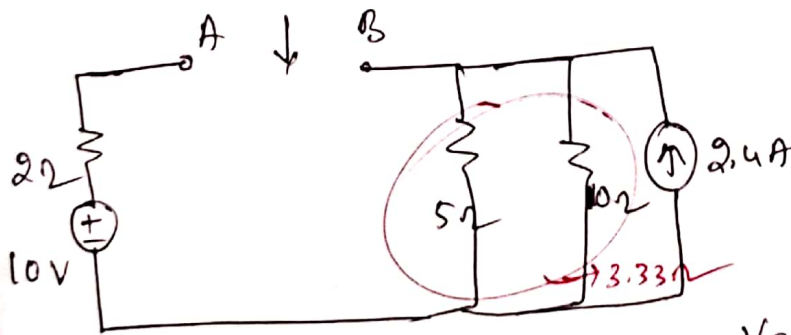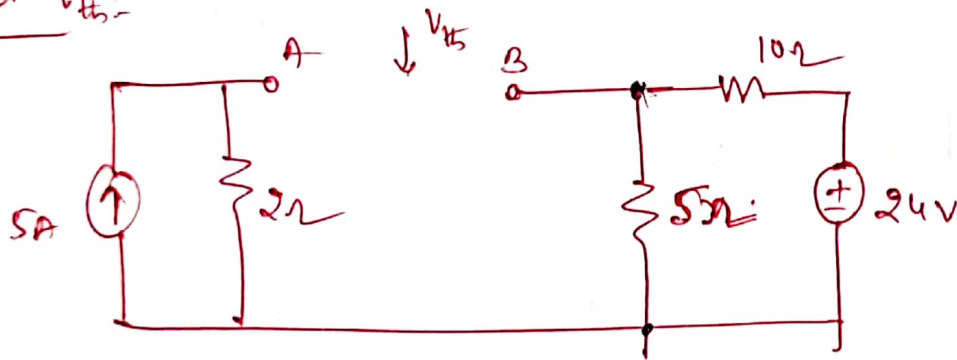

$$\frac{10 \times 5}{10 + 5} = \frac{50}{15}$$


$$I = 2.4 \times 3.33$$

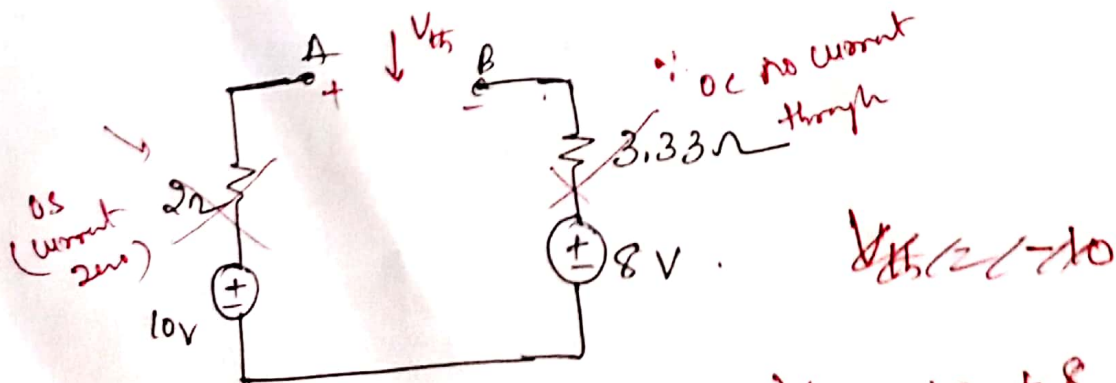

$$V_{th} - 10 + 8 = 0$$


$$V_{th} = 2V$$

To find  $R_{th}$  :

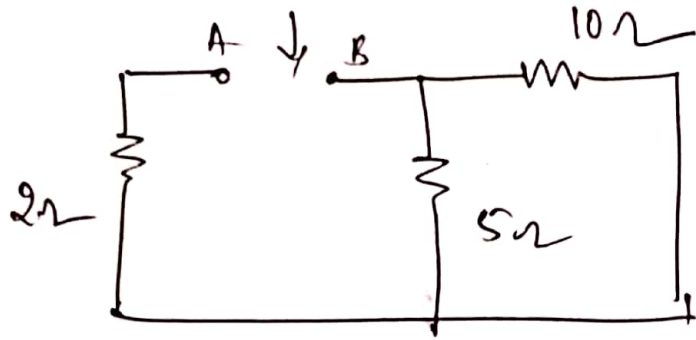

$$R_{th} = 2 + \frac{(10 \times 5)}{10 + 5}$$

$$R_{th} = 5.33 \Omega$$

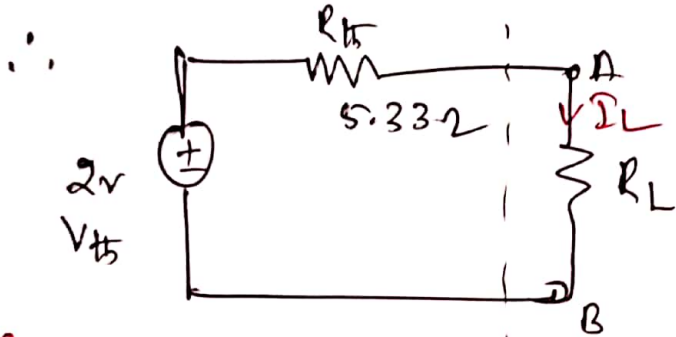

The equivalent circuit

Condition for Max power transfer theorem.

$$R_s = R_L \quad (\text{Here } R_{th} \text{ is } R_s)$$

$$\therefore R_L = 5.33 \Omega \quad (V_{th} \text{ is } V_s)$$

$$P = I_L^2 \times R$$

$$P = (0.188)^2 \times 5.33$$


$$P = 0.188 \text{ Watt.}$$

$$I_L = \frac{V_{th}}{R_{th} + R_L} = \frac{2}{5.33 + 5.33}$$


$$I_L = 0.188 \text{ A}$$

Jan 6 MKS

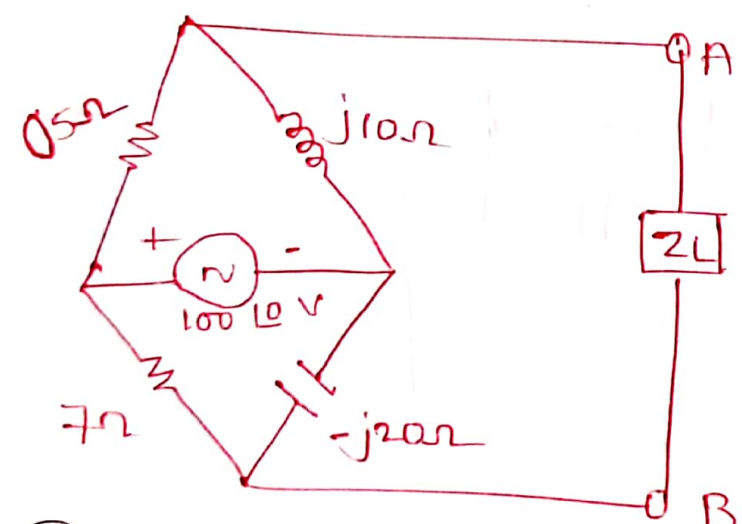3) Find the value of  $Z_L$  for which maximum power is transferred to the load  $Z_L$  from the N/w in the below fig.



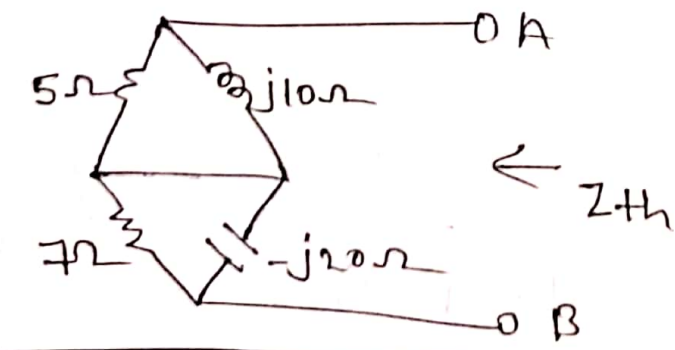Remove the load & create open ckt b/w A & B & find out  $Z_{th}$ .



$$Z_{th} = \left( \frac{5 \times j10}{5 + j10} \right) + \left( \frac{7 \times -j20}{7 - j20} \right)$$

$$Z_{th} = 10.24 - 0.183j \Omega = Z_s$$

Power is maximum.


$$\text{When } Z_L = Z_s^*$$

$$Z_L = 10.24 + 0.183j \Omega$$


Rec 12  
118



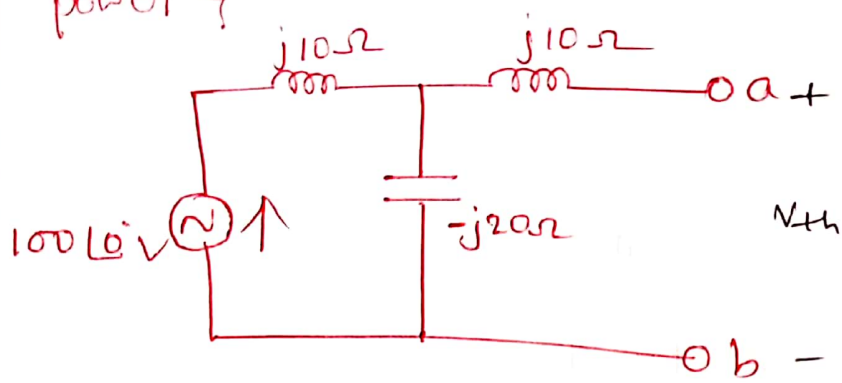4) What should be the value of a pure resistance to be connected across the terminals a & b in the circuit below fig. so that maximum power is transferred to the load. What is the max power?




To find  $V_{th}$ :

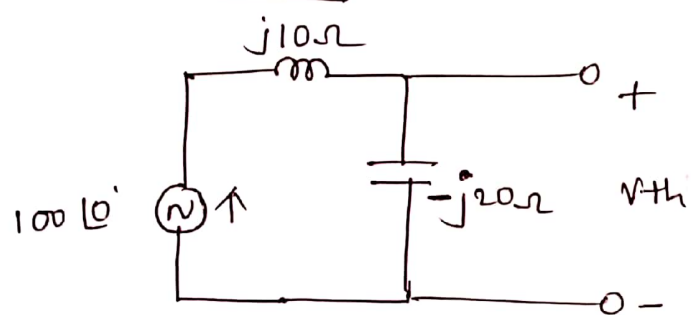

No current flows through  $j10\Omega$


$$\begin{aligned} \therefore V_{th} &= \frac{100\angle 0^\circ \times (-j20)}{j10 - j20} \\ &= 200 + 0j \\ &= 200\angle 0^\circ \text{ V} \end{aligned}$$

To find  $Z_{th}$ :

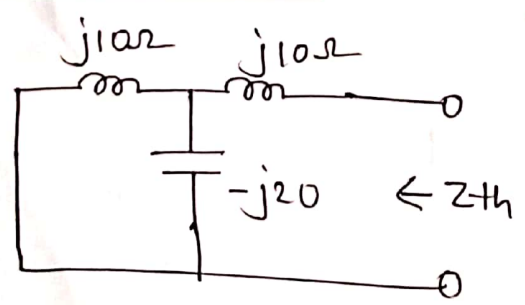

$$\begin{aligned} Z_{th} &= [j10 \parallel -j20] + j10 \\ &= \frac{j10 \times -j20}{j10 - j20} + j10 \\ &= 30j = 30\angle 90^\circ \Omega \end{aligned}$$

Thévenin's equivalent N/W:

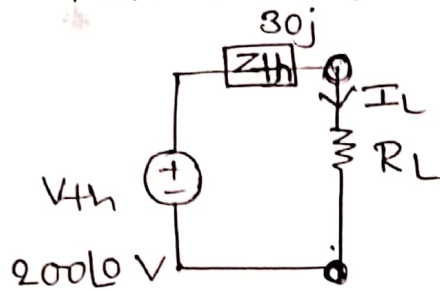

Power is maximum

$$\text{When } R_L = |Z_{th}|$$

$$= |j30|$$

$$= 30 \Omega$$

$$I_L = \frac{V_{th}}{Z_{th} + R_L}$$

$$= \frac{200\angle 0^\circ}{30j + 30}$$

$$I_L = 4.714 \angle -45^\circ \text{ A}$$


Max. Power is

$$P = I_L^2 R_L$$


$$= (4.714)^2 (30)$$

$$P = \underline{666.653 \text{ W}}$$

1) Using Superposition theorem, determine the current flowing through  $10\Omega$  resistance of the circuit shown.

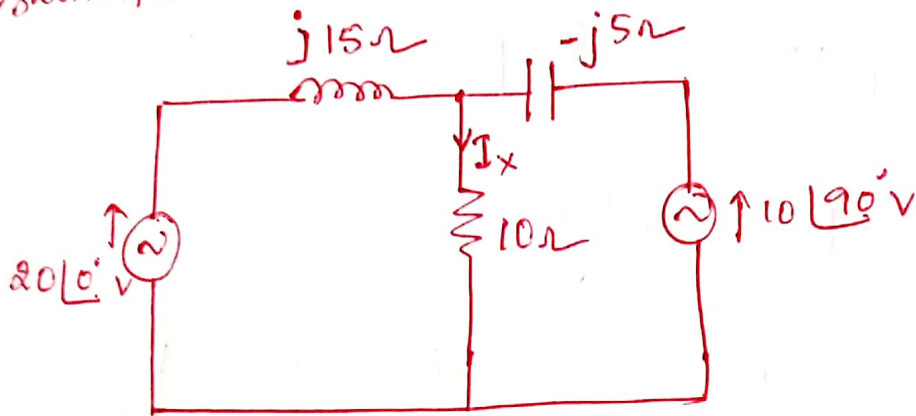

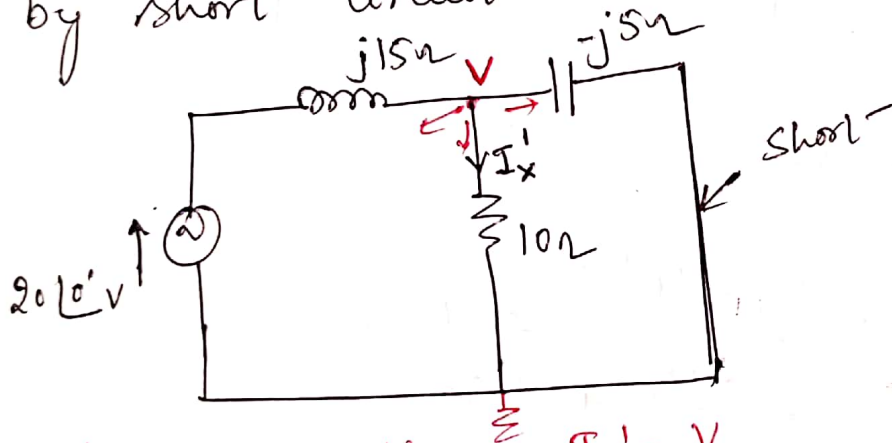Case 1: Consider only  $20\angle 0^\circ$  V & replace  $10\angle 90^\circ$  V by short circuit.



From the figure,  $I_{x'} = \frac{V}{10}$

KCL @ node V,

$$\frac{V - 20\angle 0^\circ}{j15} + \frac{V}{10} + \frac{V}{-j5} = 0$$

$$-j0.067V - 1.33\angle -90^\circ + 0.1V + j0.2V = 0$$


$$(0.1 + j0.133)V = 1.33\angle -90^\circ$$

$$V = \frac{1.33\angle -90^\circ}{0.166\angle 53.06^\circ} = 8.01\angle -143.06^\circ$$

$$I_x' = \frac{8.012 \angle -143.06^\circ}{10}$$

$$I_x' = 0.8 \angle -143.06 \text{ Amp} \quad \text{--- (1)}$$

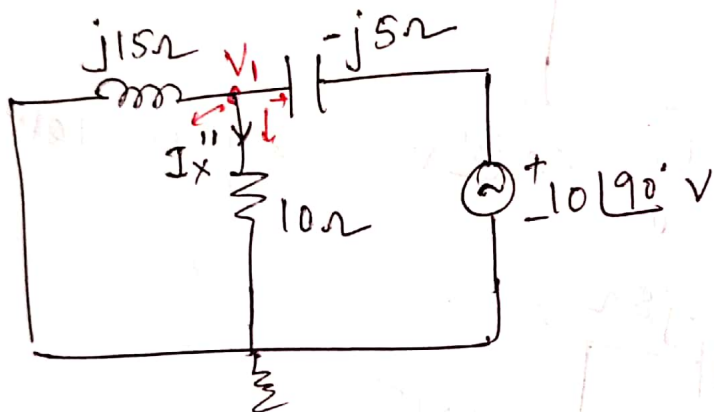Case 2: Consider  $10 \angle 90^\circ \text{ V}$  only.



from the fig

$$I_x'' = \frac{V_1}{10}$$

KCL @ node  $V_1$

$$\frac{V_1}{j15} + \frac{V_1}{10} + \frac{V_1 - 10 \angle 90^\circ}{-j5} = 0$$

$$-j0.067 V_1 + 0.1 V_1 + j0.2 V_1 - 2 \angle 180^\circ = 0$$

$$(0.1 + 0.133j) V_1 = 2 \angle 180^\circ$$

$$V_1 = \frac{2 \angle 180^\circ}{0.166 \angle 53.13^\circ} = 12 \angle 126.93$$

$$I_x'' = \frac{V_1}{10} = 1.2 \angle 126.93 \text{ Amp} \quad \text{--- (2)}$$




$$I_x = I_x' + I_x''$$



$$I_x = 0.8 \angle -143.17^\circ + 1.2 \angle 26.93^\circ$$


$$I_x = 1.43 \angle 160^\circ \text{ Amp.}$$

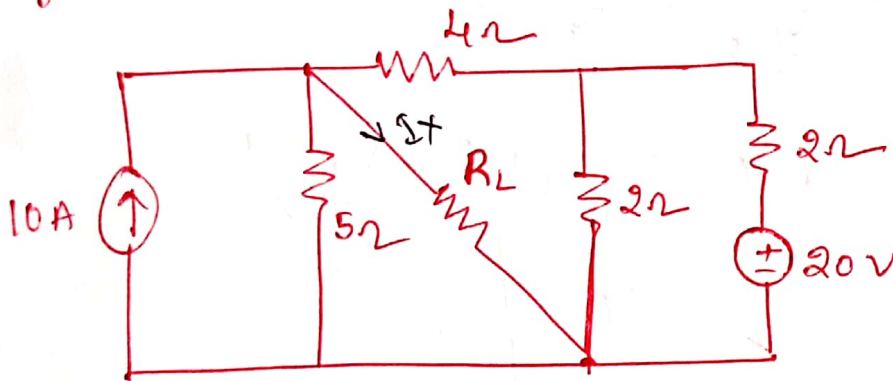2) Using Superposition theorem, find the current through  $R_L = 7.5 \Omega$



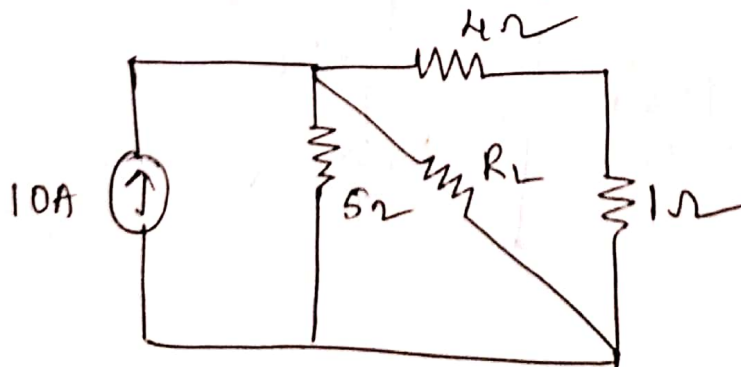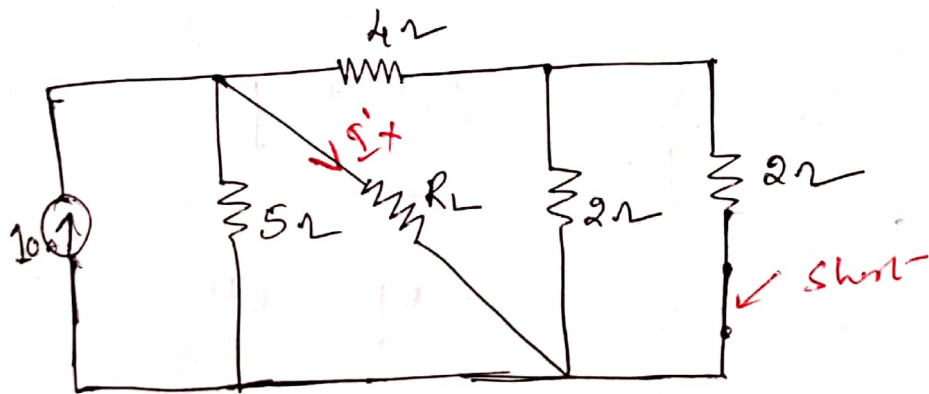Consider 10A source alone, short 20V source.



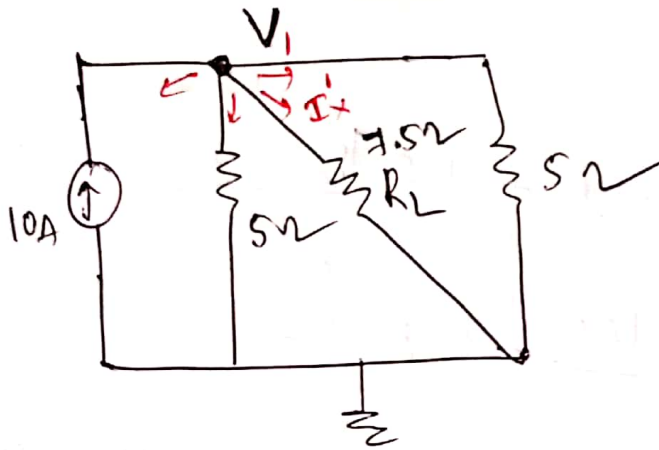

from the figure

$$I_x' = \frac{V_1}{7.5}$$

Apply KCL @ node v

$$-10 + \frac{V_1}{5} + \frac{V_1}{7.5} + \frac{V_1}{5} = 0$$


$$-10 + 0.2V_1 + 0.133V_1 + 0.2V_1 = 0$$

$$0.533V_1 = 10$$

$$V_1 = 18.76 \text{ volts}$$

$$I_x' = \frac{V_1}{7.5} = 2.5 \text{ Amp} \quad \text{--- (1)}$$

Consider 20V src & open current source.

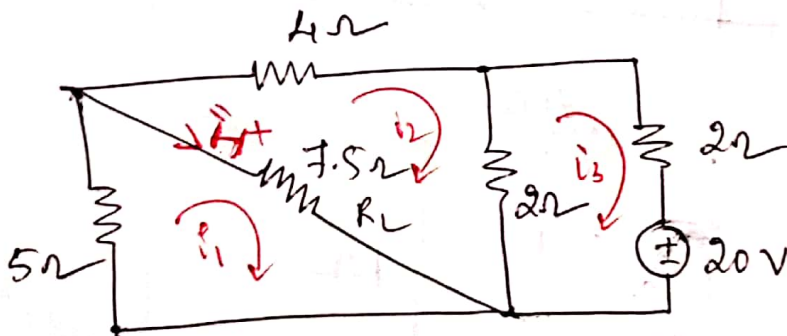

$$\text{loop 1} \rightarrow -7.5(i_1 - i_2) - 5i_1 = 0$$

$$-12.5i_1 + 7.5i_2 + 0i_3 = 0 \quad \text{--- (a)}$$

$$\text{loop 2} \rightarrow -4i_2 - 2(i_2 - i_3) - 7.5(i_2 - i_1) = 0$$

$$-4i_2 - 2i_2 + 2i_3 - 7.5i_2 + 7.5i_1 = 0$$

$$7.5i_1 - 13.5i_2 + 2i_3 = 0 \quad \text{--- (b)}$$

KVL to loop 3

$$-2i_3 - 20 - 2(i_3 - i_2) = 0$$

$$-2i_3 - 20 - 2i_3 + 2i_2 = 0$$

$$0i_1 + 2i_2 - 4i_3 = 20 \quad \text{--- (c)}$$

$$i_1 = -0.75A \quad i_2 = -1.25A \quad i_3 = -5.62 \text{ amp}$$

current through  $7.5\Omega$   $I_x'' = I_1 - i_2$





$$I_x'' = -0.75 - (-1.25)$$

$$\boxed{I_x'' = 0.5 \text{ Amp}} \quad \text{--- (d)}$$

$$\therefore I_x = I_x' + I_x''$$

$$\hookrightarrow = 2.5 + 0.5$$

$$\boxed{I_x = 3 \text{ Amp}}$$

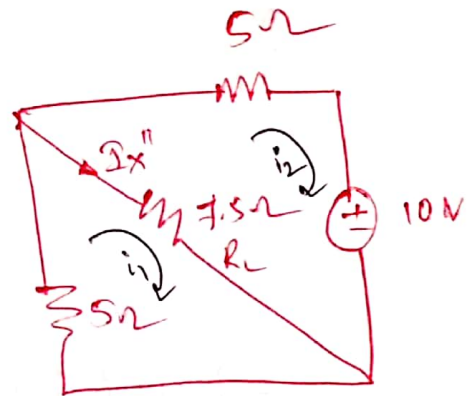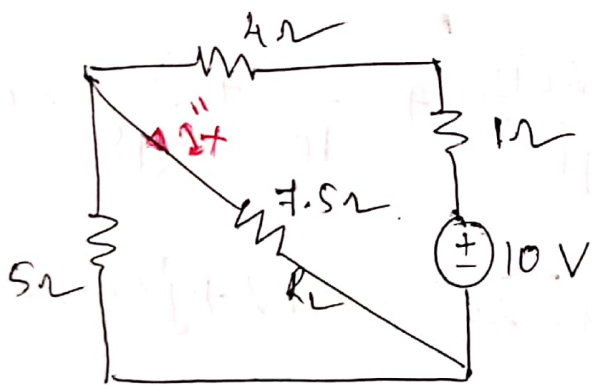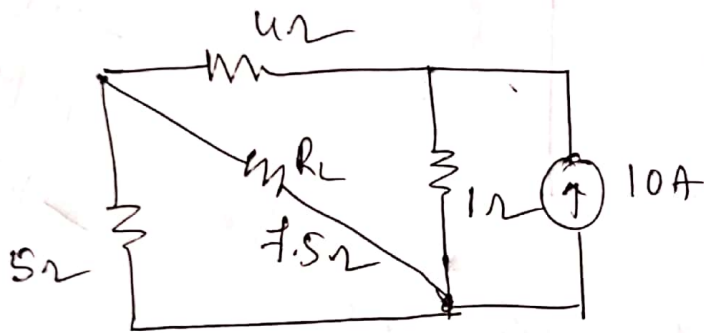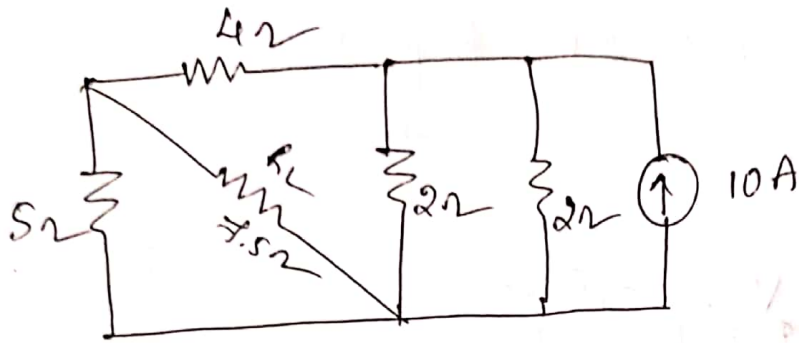

$$-7.5(i_1 - i_2) - 5i_1 = 0$$

$$-12.5i_1 + 7.5i_2 = 0 \quad \text{--- (1)}$$

$$-5i_2 - 10 - 7.5(i_2 - i_1) = 0$$


$$7.5i_1 - 12.5i_2 = 10 \quad \text{--- (2)}$$

$$i_1 = \underline{\underline{-0.75 \text{ amp}}} \quad i_2 = \underline{\underline{-1.25 \text{ amp}}} \quad \therefore I_{x''} = i_1 - i_2$$

$$\boxed{I_{x''} = 0.5 \text{ amp}}$$





Jan-18  
 Find the voltage  $V$  across  $3\Omega$  resistor using superposition theorem for the circuit shown.

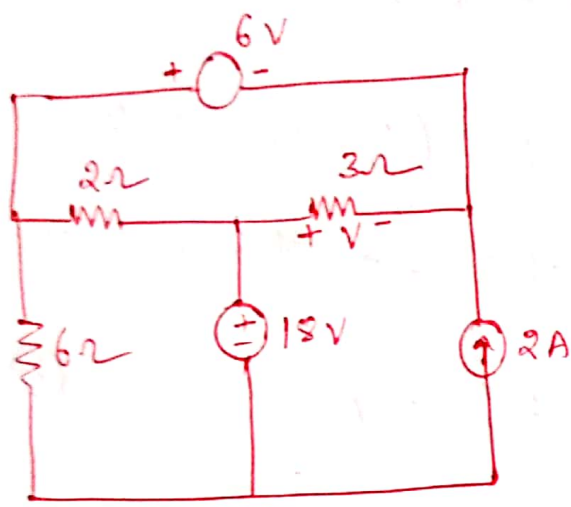

Case 1:

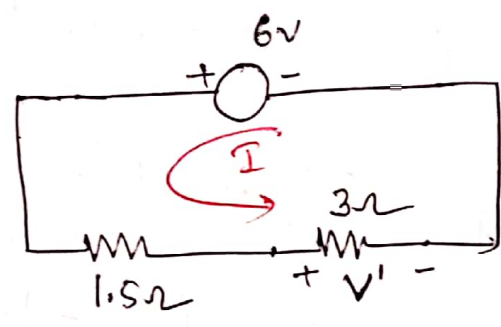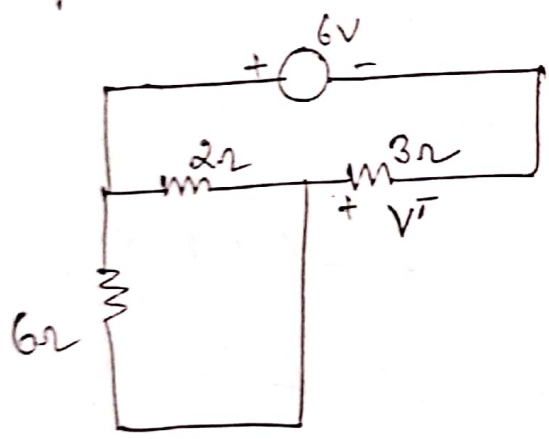Consider  $6V$   $v_s$  src, short ckt  $18V$  src & open ckt  $2A$  src.



$$6 - 1.5I - 3I = 0$$


$$4.5I = 6$$

$$I = 1.33A$$

$$\therefore V' = 3I = 4V \quad \text{--- (1)}$$

Case 2:

Consider  $18V$   $v_s$  src

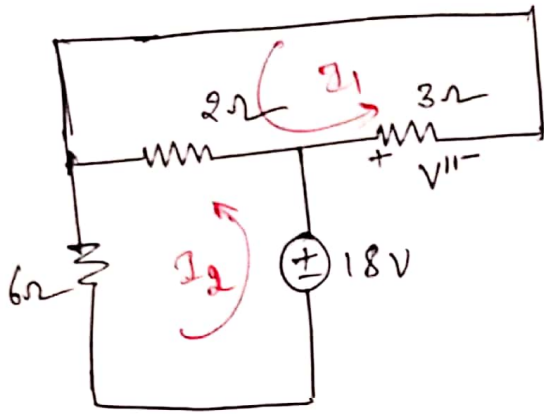

from the circuit  
 $V'' = 3I_1$

KVL to 1<sup>st</sup> loop

$$-2(I_1 - I_2) - 3I_1 = 0$$

$$-2I_1 + 2I_2 - 3I_1 = 0$$

$$-5I_1 + 2I_2 = 0 \quad \text{--- (1)}$$

KVL to 2<sup>nd</sup> loop

$$-2(I_2 - I_1) - 6I_2 + 18 = 0$$

$$2I_1 - 8I_2 = -18 \quad \text{--- (2)}$$



we get

$$I_1 = 1A \quad I_2 = 2.5A$$

$$\therefore V'' = 3I_1$$

$$V'' = 3V \quad \text{--- (3)}$$

Case 3 :- Consider 2A current source

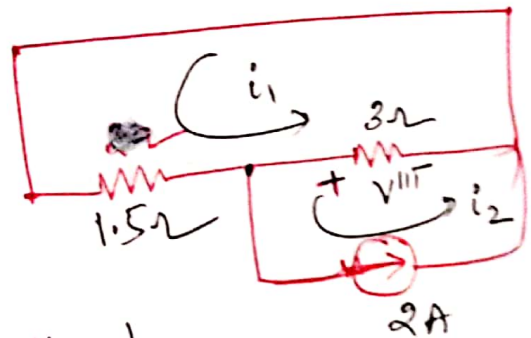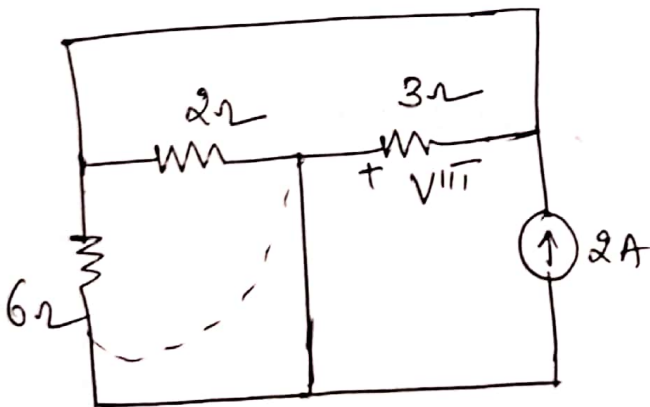

from the circuit

$$V''' = 3(i_2 - i_1)$$

$$\text{but } i_2 = 2 \text{ A}$$

$$-1.5 i_1 - 3(i_1 - i_2) = 0$$

$$-4.5 i_1 + 3 i_2 = 0$$

$$+4.5 i_1 = +3 \times 2$$

$$i_1 = \frac{6}{4.5} = 1.33 \text{ Amp}$$

$$\therefore V^{III} = 3(2 - 1.33) =$$

$$V^{III} = 3(2 - 1.33)$$

$$V^{III} = -2 \text{ volt} \quad \text{--- (3)}$$

$$\therefore V = V^I + V^{II} + V^{III} = 9 \text{ volts}$$

$$V^{III} = 3(i_2 - i_1) = 3(2 - 1.33)$$

$$= 3(2 - 1.33)$$


$$= -2 \text{ volt}$$

$$\therefore V = V' + V'' + V'''$$

$$V = 4 + 3 - 2$$

$$V = 5 \text{ volts}$$

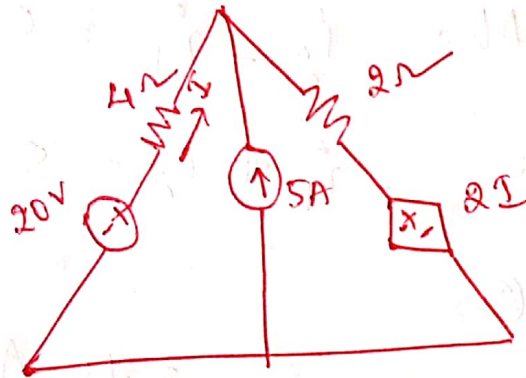5) For the ckt shown in below fig, find the current  $I$  using Superposition theorem.



Case i  
Consider 20V src, open ckt 5A current src & keep dependent src as it is,


KVL to loop

$$20 - 4i - 2i - 2I' = 0$$

from the fig  $I' = I$

$$20 - 6i - 2i = 0$$

$$8i = 20 \quad i = 2.5 \text{ Amp}$$

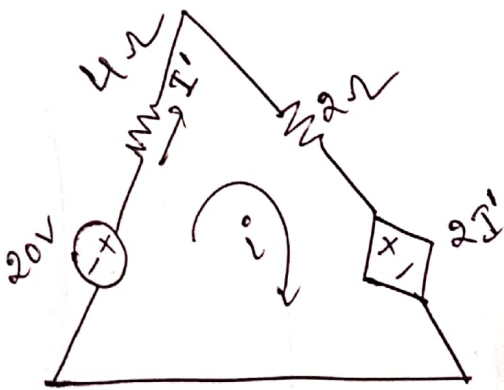


$$\therefore I = 2.5 \text{ amp} \quad \text{--- (A)}$$



Case ii)

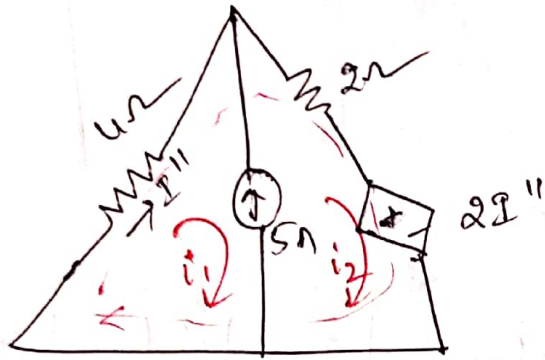Consider 5A current source & short 20V vs for Supermesh



$$-4i_1 - 2i_2 - 2i'' = 0$$

from fig  $i'' = i_1$

$$-4i_1 - 2i_2 - 2i_1 = 0$$

$$-6i_1 - 2i_2 = 0 \quad \text{--- (1)}$$

5A is b/w 1st & 2nd loop hence Supermesh.

Also  $i_2 - i_1 = 5$

or  $-i_1 + i_2 = 5 \quad \text{--- (2)}$

Solve (1) & (2),

$$i_1 = -1.25 \text{ A} \quad \& \quad i_2 = 3.75 \text{ Amp}$$

$$\therefore i'' = -1.25 \text{ Amp} \quad \text{--- (R)}$$


$\therefore$  from Superposition theorem.

$$I = I' + I''$$


$$I = 2.5 - 1.25$$

$$I = 1.25 \text{ Amp}$$

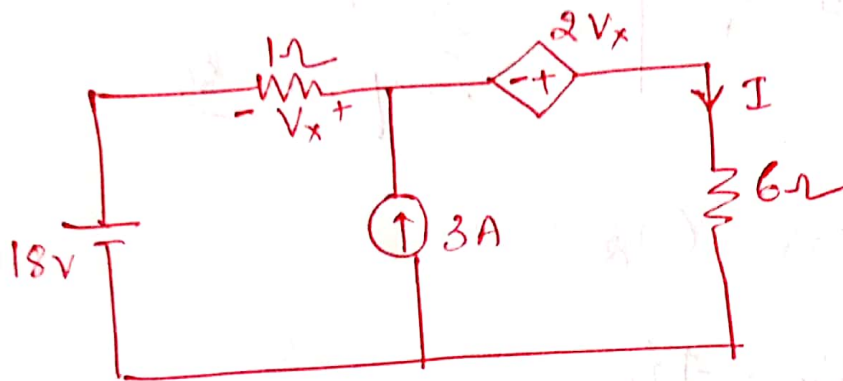6) Using Superposition theorem find the current in  $6\Omega$  resistor in the circuit shown.



Case i) Consider 18V src

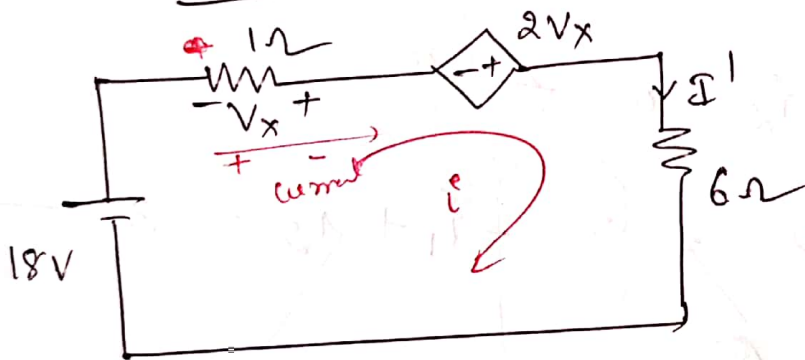

$$18 - 1i + 2V_x - 6i = 0$$

from the fig  $V_x = -1i$


$$18 - i + 2(-1i) - 6i = 0$$

$$-9i = -18$$

$$i = 2A$$

$$\therefore I' = i = 2A$$

Case ii) Consider 3A current src

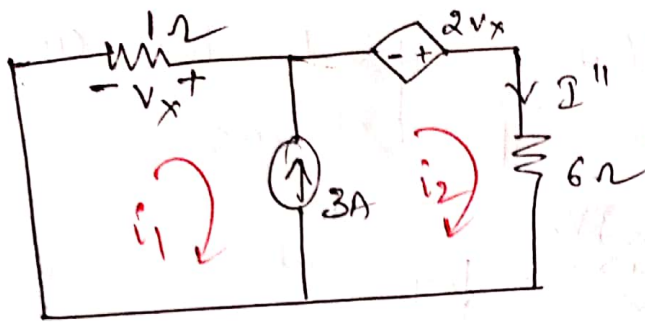

3A in b/m 2Ω +  
2nd loop here

Super mesh

$$-1i_1 + 2V_x - 6i_2 = 0$$

$$\text{but } V_x = -1i_1$$

$$-i_1 + 2(-1i_1) - 6i_2 = 0$$

$$-3i_1 - 6i_2 = 0 \quad \text{--- (1)}$$

$$\& i_2 - i_1 = 3 \implies -i_1 + i_2 = 3 \quad \text{--- (2)}$$

Solve (1) & (2)

$$\boxed{i_1 = -2A} \quad \boxed{i_2 = 1A}$$


$$\therefore \boxed{I'' = i_2 = 1A} \quad \text{--- (b)}$$

from superposition theorem.


$$I = I' + I''$$

$$I = 2 + 1 = 3 \text{ Amp}$$

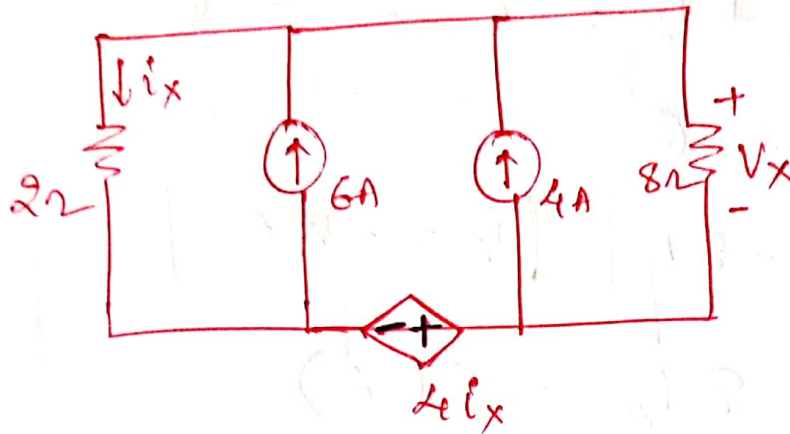7) Use super mesh theorem to find  $V_x$  in the ckt shown below.



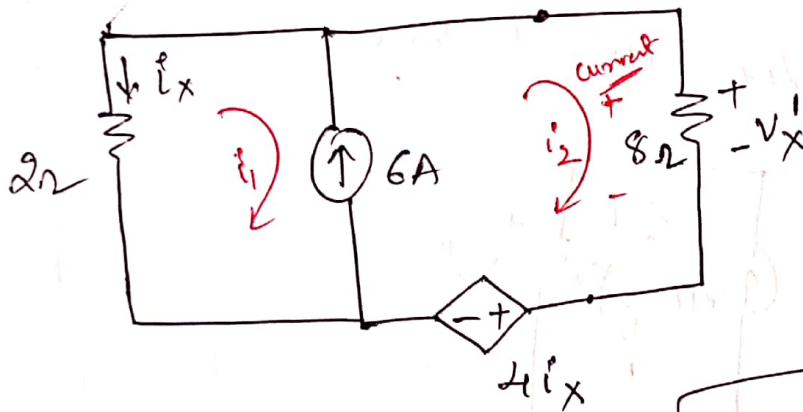Case i) Consider 6A current src. Open ckt left src



from the b/s

$$i_x = -i_1$$

$$V_x' = 8 i_2$$

& 6A src is b/m 1<sup>st</sup> & 2<sup>nd</sup> loop  $\therefore$  Supermesh

$$-2i_1 - 8i_2 - 4i_x = 0$$

$$-2i_1 - 8i_2 - 4(-i_1) = 0$$

$$2i_1 - 8i_2 = 0 \quad \text{--- (1)}$$



$$i_2 - i_1 = 6$$

$$\text{or } -i_1 + i_2 = 6 \quad \text{--- (2)}$$

Solve (1) & (2)


$$i_1 = -8 \text{ A}$$

$$i_2 = -2 \text{ A}$$

$$\therefore V_x' = 8 i_2 = 8(-2)$$

$$V_x' = -16 \text{ volts} \quad \text{--- (a)}$$

Case ii) Consider 4A current src

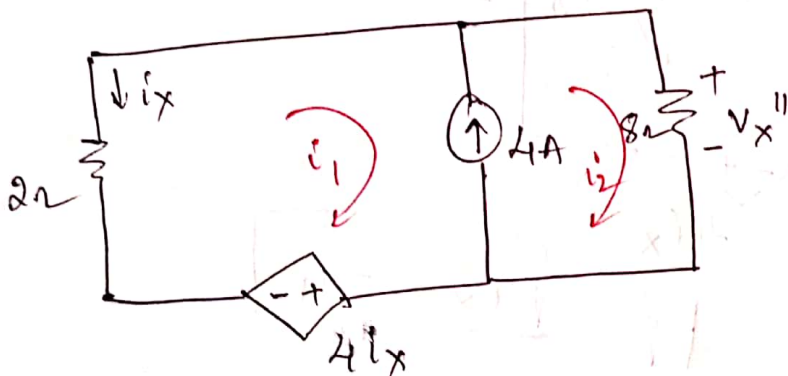

from the fig  $i_1 = -i_x \Rightarrow i_x = -i_1$

$$V_x'' = 8 i_2$$

→ 4A source is b/w 1st & 2nd loop hence  
super mesh

from KVL  
by  $i_2 - i_1 = 4 \rightarrow -i_1 + i_2 = 4 \quad \text{--- (1)}$

Supermesh  
(KVL)

$$-8i_2 - 4i_x - 2i_1 = 0$$

$$-8i_2 - 4(-i_1) - 2i_1 = 0$$

$$2i_1 - 8i_2 = 0 \quad \text{--- (2)}$$

Solve (1) & (2)

$$i_1 = -5.33 \text{ Amp}$$

$$i_2 = -1.33 \text{ Amp}$$

$$\therefore V_x'' = 8x - 1.33$$

$$V_x'' = -10.64 \text{ volts} \quad \text{--- (6)}$$


$$\therefore V_x' = V_x' + V_x''$$

$$V_x = -16 - 10.64$$


$$V_x = -26.64 \text{ volts}$$

# Thevenin's theorem :-

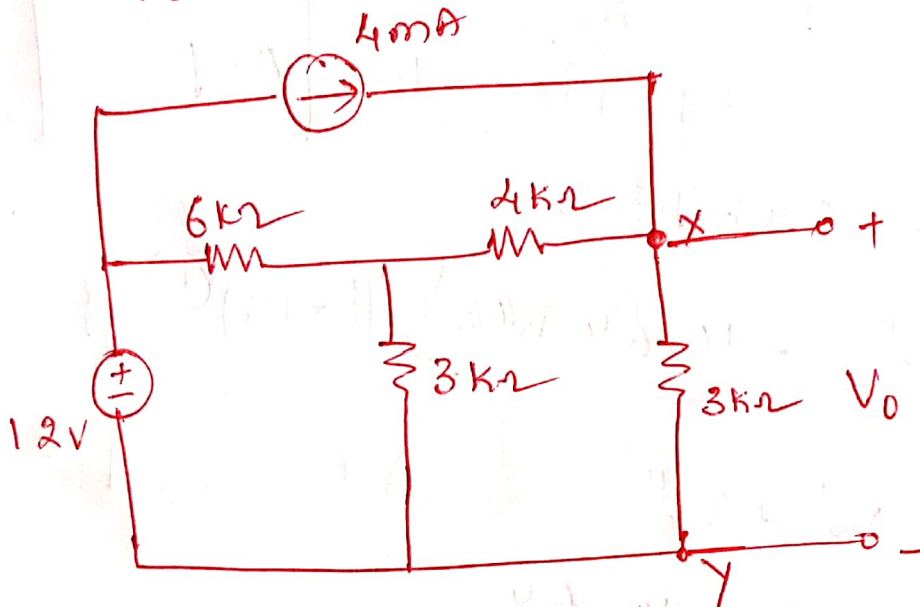1) Obtain the Thevenin equivalent of n/w shown in below fig b/w terminals X & Y. Also find  $V_0$



Remove the load & create open ckt

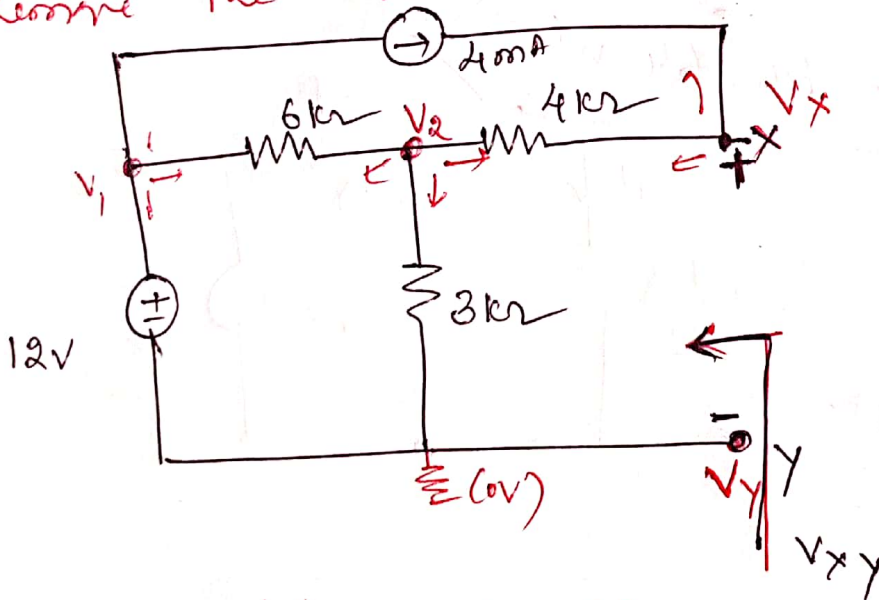

$$V_{xy} = V_x - V_y$$

which is nothing but  $V_{th}$

$$V_{th} = V_{xy}$$

KCL @ node 1

$$V_1 = 12V$$

KCL @ node 2

$$\frac{V_2 - V_1}{6k} + \frac{V_2}{3k} + \frac{V_2 - V_x}{4k} = 0$$

$$V_2 \left[ \frac{1}{6k} + \frac{1}{3k} + \frac{1}{4k} \right] - \frac{12}{6k} - \frac{V_x}{4k} = 0$$

$$0.75 \times 10^3 V_2 - 0.25 \times 10^3 V_x = 2 \times 10^3 \quad \text{--- (1)}$$

KCL @ node  $V_x$

$$-4 \times 10^3 + \frac{V_x - V_2}{4k} = 0$$

$$-0.25 \times 10^3 V_2 + 0.25 \times 10^3 V_x = 4 \times 10^3 \quad \text{--- (2)}$$

Solve (1) & (2)

$$\underline{V_2 = 12 \text{ volts}}$$


$$\underline{V_x = 28 \text{ volts}}$$

And  $V_y = 0$   $\because$  bottom node is grounded

$$\underline{\underline{V_{th} = V_{xy} = 28 \text{ volts}}}$$




To find  $R_{th}$  :-

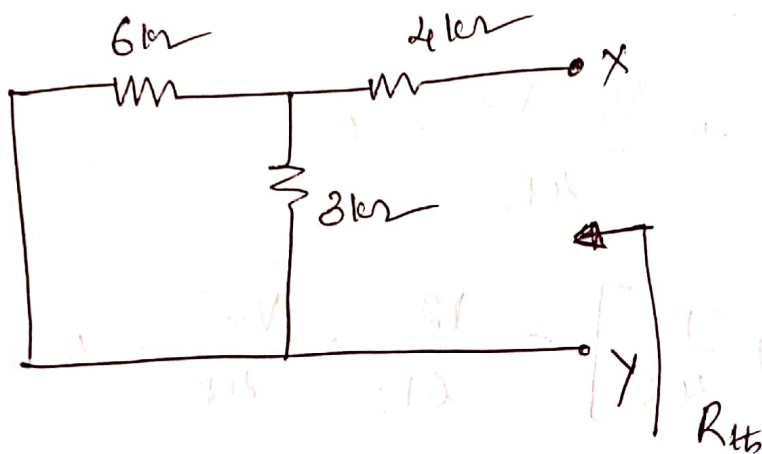

$$R_{th} = (6k \parallel 3k) + 4k$$

$$R_{th} = 6k\Omega$$

Thévenin's Equivalent circuit

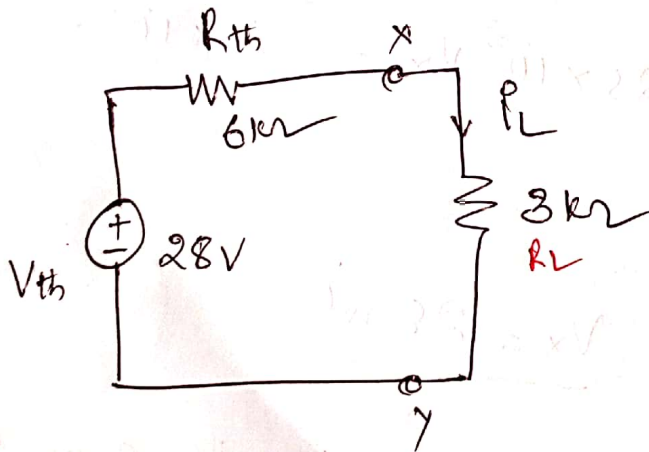

$$I_L = \frac{V_{th}}{R_{th} + R_L}$$

$$I_L = \frac{28}{6k + 3k}$$


$$I_L = 3.11 \text{ mA}$$

$$\therefore V_0 = I_L \times R_L = \underline{\underline{9.33 \text{ volts}}}$$

Case 2)

Problema

(2)

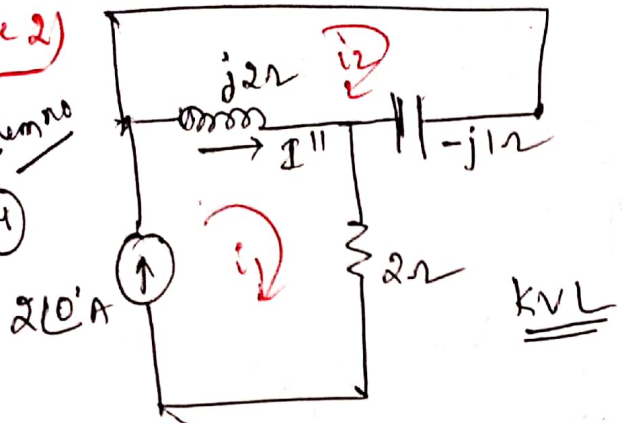

$$i_1 = 2\angle 0^\circ$$

$$j1(i_2) - j2(i_2 - i_1) = 0$$

$$j1 i_2 - j2 i_2 + j2 i_1 = 0$$


$$-j1 i_2 = -j2 i_1$$

~~$$i_2 = 2$$~~

$$i_2 = 2 \times 2 \angle 0^\circ = 4 \angle 0^\circ$$

$$\therefore I'' = i_1 - i_2 = 2 - 4 = -2 \text{ Amp}$$

Case iii) :-

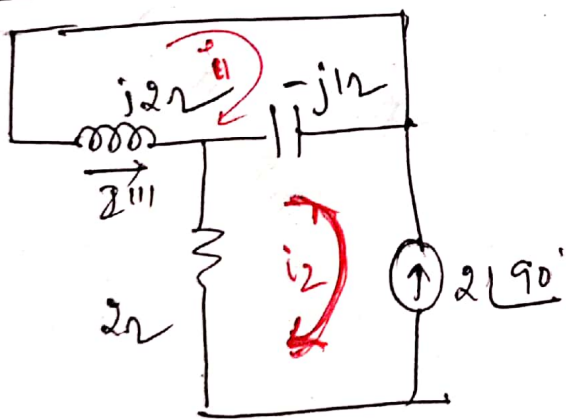

$$i_2 = -2\angle 90^\circ$$

$$\text{kvl: } j1(i_1 - i_2) - j2 i_1 = 0$$

$$j1 i_1 - j1 i_2 - j2 i_1 = 0$$

$$-j1 i_1 = j1 i_2$$

$$-i_1 = i_2 \quad i_1 = -i_2 = 2\angle 90^\circ$$

$$I''' = -i_1 = -2\angle 90^\circ$$

$$\therefore I = I' + I'' + I'''$$

$$I = 8 \angle -135^\circ \oplus -2 - 2 \angle 90^\circ$$


$$I = -5.65 - j5.65 - 2 - 2j$$

$$I = -7.65 - 7.65j$$


$$I = 10.83 \angle -135^\circ \text{ Amp}$$

# Thevenin's theorem :-

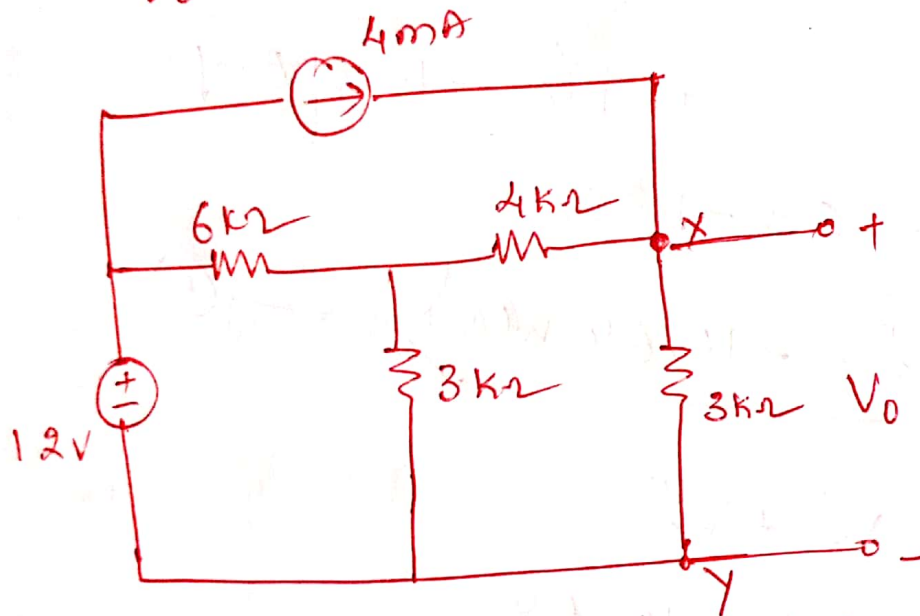1) Obtain the Thevenin equivalent of n/w shown on below fig b/w terminals x & y. Also find  $V_0$



Remove the load & create open ckt

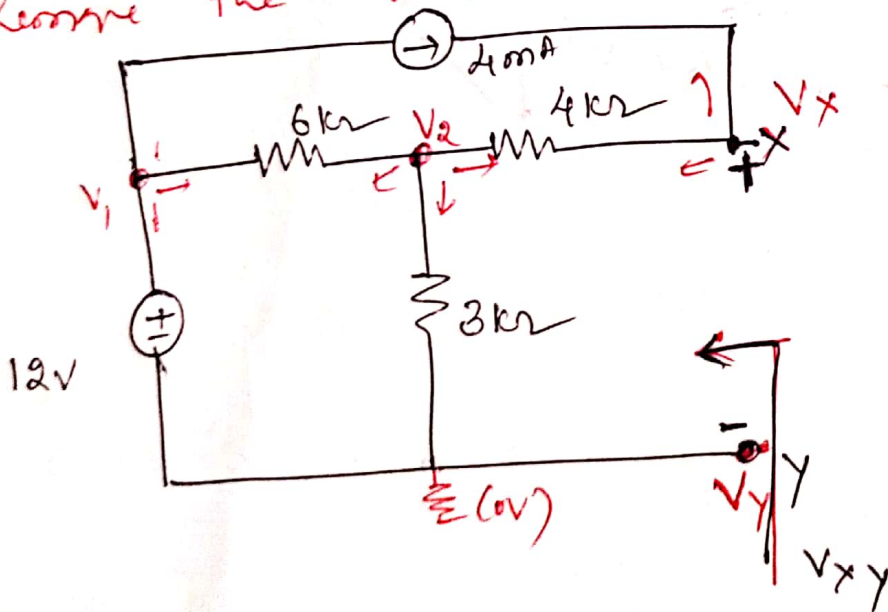

$$V_{xy} = V_x - V_y$$

which is nothing but  $V_{th}$

$$V_{th} = V_{xy}$$



KCL @ node 1

$$\boxed{V_1 = 12V}$$

KCL @ node 2

$$\frac{V_2 - V_1}{6k} + \frac{V_2}{3k} + \frac{V_2 - V_x}{4k} = 0$$

$$V_2 \left[ \frac{1}{6k} + \frac{1}{3k} + \frac{1}{4k} \right] - \frac{12}{6k} - \frac{V_x}{4k} = 0$$

$$0.75 \times 10^3 V_2 - 0.25 \times 10^3 V_x = 2 \times 10^3 \quad \text{--- (1)}$$

KCL @ node  $V_x$

$$-4 \times 10^3 + \frac{V_x - V_2}{4k} = 0$$

$$-0.25 \times 10^3 V_2 + 0.25 \times 10^3 V_x = 4 \times 10^3 \quad \text{--- (2)}$$

Solve (1) & (2)


$$\underline{V_2 = 12 \text{ volts}}$$

$$\underline{V_x = 28 \text{ volts}}$$

And  $\boxed{V_y = 0}$   $\because$  bottom node is grounded

$$\underline{\underline{V_{th} = V_{xy} = 28 \text{ volts}}}$$


To find  $R_{th}$  :-

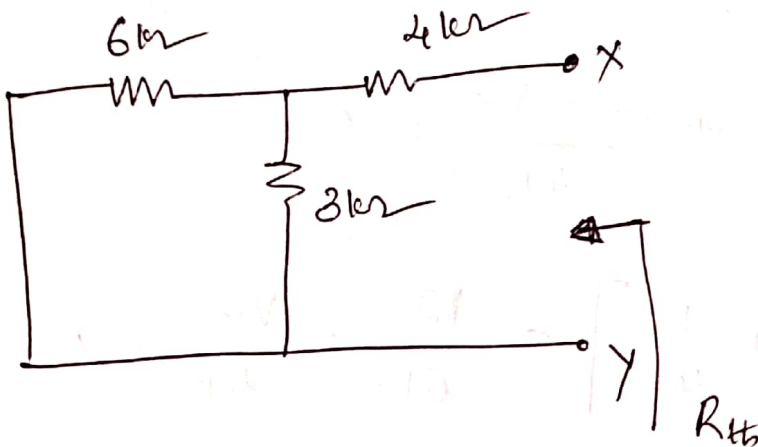

$$R_{th} = (6k \parallel 3k) + 4k$$

$$R_{th} = 6k\Omega$$

Thévenin's Equivalent circuit

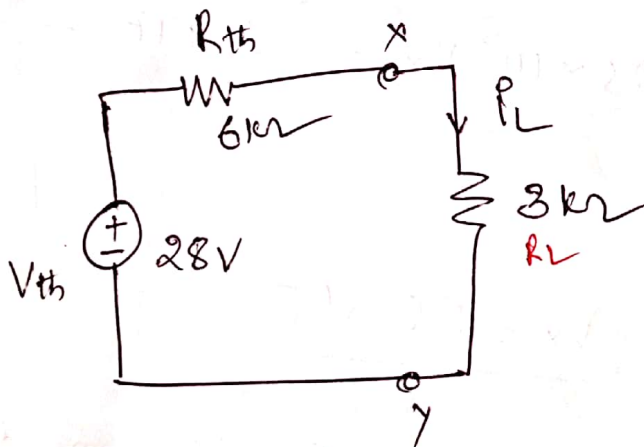



$$I_L = \frac{V_{th}}{R_{th} + R_L}$$

$$I_L = \frac{28}{6k + 3k}$$


$$I_L = 3.11 \text{ mA}$$

$$\therefore V_0 = I_L \times R_L = \underline{\underline{9.33 \text{ volts}}}$$

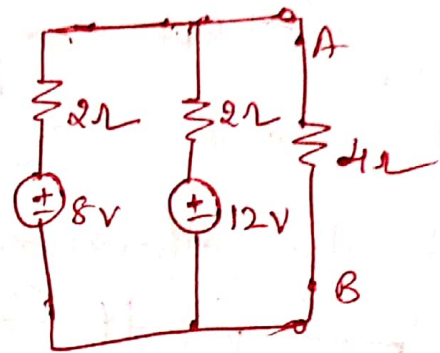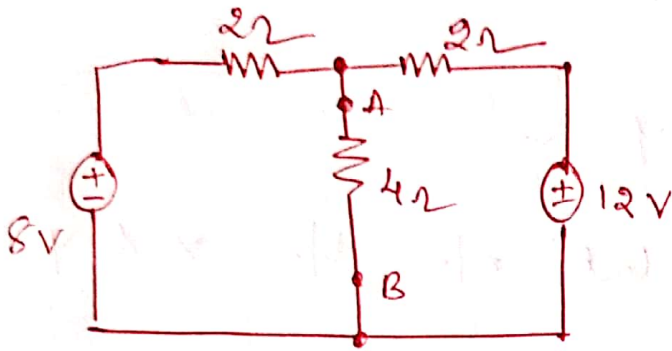2) Find the Thevenin's equivalent for the n/w at the load terminals A & B. If the load across A & B is  $4\Omega$ . Determine the load current.



To find  $V_{th}$

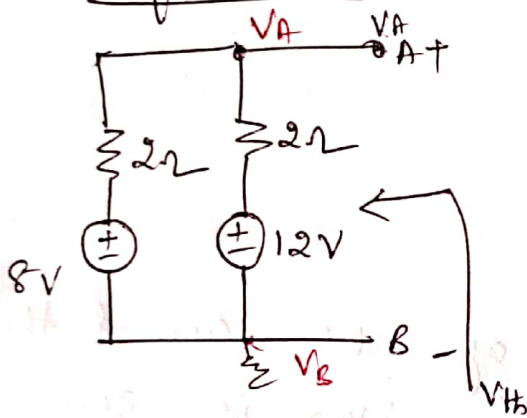

$$V_{th} = V_A - V_B$$

→ KCL @ node A

$$\frac{V_A - 8}{2} + \frac{V_A - 12}{2} = 0$$


$$0.5V_A - 4 + 0.5V_A - 6 = 0$$

$$V_A = 10 \text{ volts}$$

$$V_B = 0$$

$$\therefore V_{th} = 10 \text{ volts}$$


To find  $R_{th}$  :-

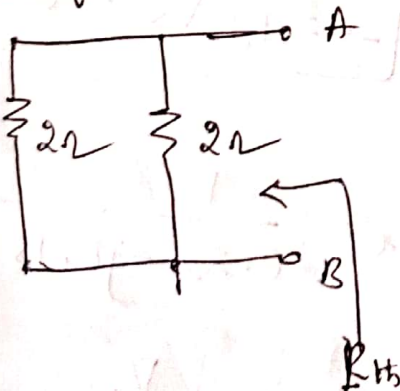

$$R_{th} = \frac{2 \times 2}{2 + 2} = 1\Omega$$

$$R_{th} = 1\Omega$$


Thevenins ckt :-

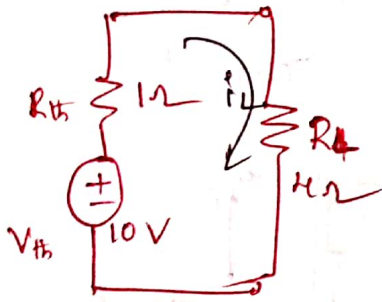

$$i_L = \frac{V_{th}}{R_{th} + R_L} = \frac{10}{4+1}$$


$$i_L = 2 \text{ A}$$

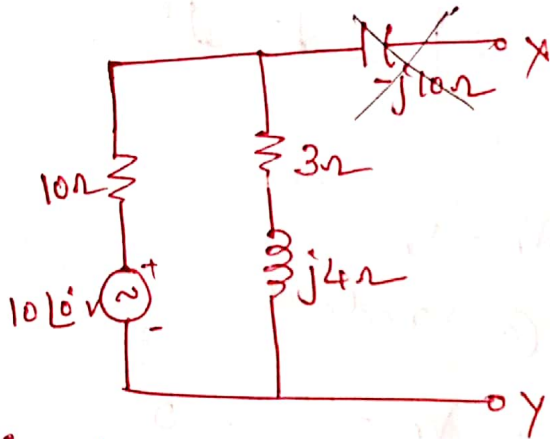8) Obtain the thevenins equivalent n/w b/w X & Y



To find  $V_{th}$  :-

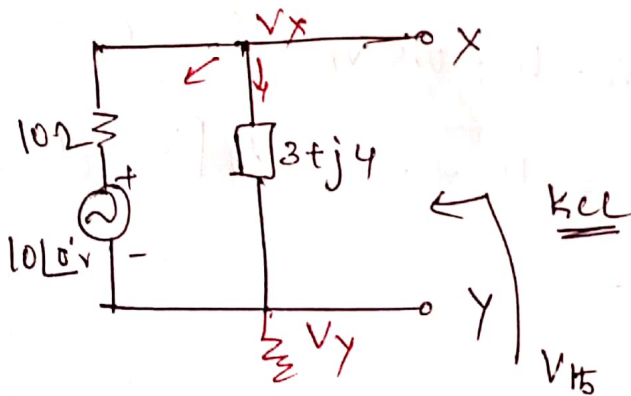Since open ckt current through  $-j10\Omega$  is zero



$$V_{th} = V_x - V_y$$

$$\frac{V_x - 10\angle 0^\circ}{10} + \frac{V_x}{3+j4} = 0$$

$$0.1V_x - 1\angle 0^\circ + 0.2 \angle -53.13^\circ V_x = 0$$

$$0.1V_x + (0.12 + j0.159)V_x = 1$$

$$(0.22 - j0.159)V_x = 1$$


$$\Rightarrow V_x = \frac{1}{0.22 - j0.159}$$

$$V_{th} = 3.676 \angle 36.03^\circ \text{ volts}$$

$$V_x = \frac{1}{0.27 \angle -35.8^\circ}$$



To find  $Z_{th}$  :-

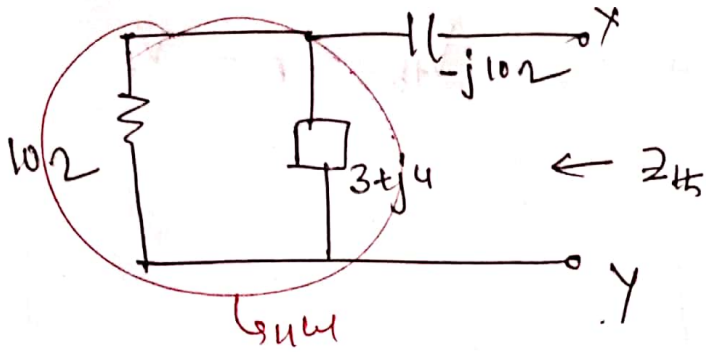

$$Z_1 = 10 \parallel (3 + j4)$$


$$Z_1 = \frac{10 \times (3 + j4)}{10 + 3 + j4}$$

$$Z_1 = \frac{30 + j40}{13 + j4} =$$


$$Z_{th} = -j10 +$$

$$Z_{th} = 8.38 \angle -69.22^\circ$$


Thevenin's equivalent ckt-

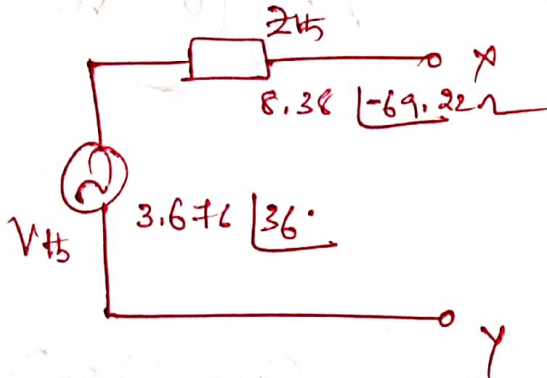

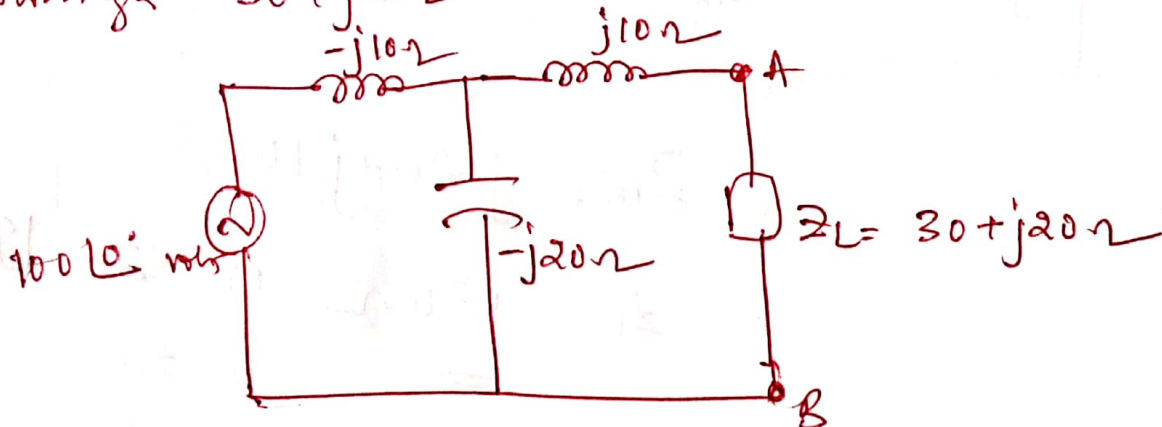4) Using Thevenin's theorem find the current flowing through  $30 + j20 \Omega$  in the ckt shown.



To find  $V_{th}$ :

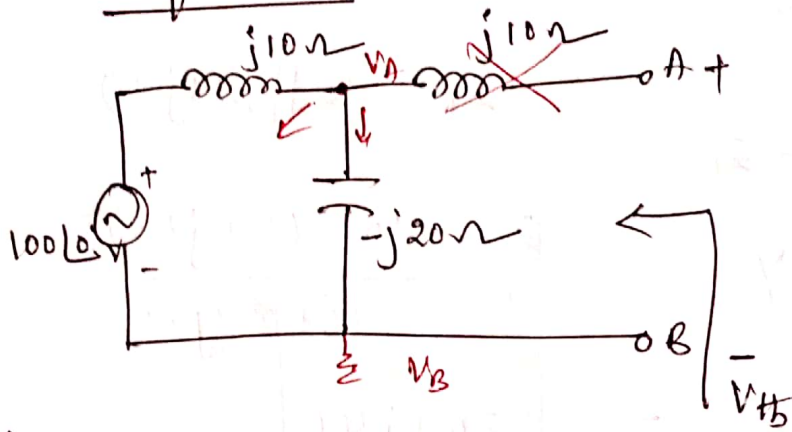

$$V_{th} = V_A - V_B$$

KCL:

@ A


$$\frac{V_A - 100\angle 0^\circ}{j10} + \frac{V_A}{-j20} = 0$$

$$-j0.1 V_A - 10\angle -90^\circ + j0.05 V_A = 0$$

$$-j0.05 V_A = 10\angle -90^\circ$$

$$V_A = \frac{10\angle -90^\circ}{0.05\angle -90^\circ} = \underline{\underline{200\angle 0^\circ \text{ volts}}}$$

To find  $R_{th}$  or  $Z_{th}$ :

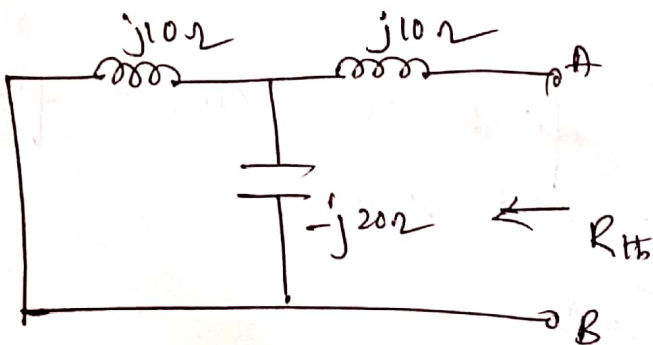


$$Z_{th} = \left( \frac{j10 \times -j20}{j10 - j20} \right) + j10$$

$$Z_{th} = j20 + j10$$

$$\underline{\underline{Z_{th} = j30\Omega \text{ or } 30\angle 90^\circ \Omega}}$$

## Thevenin's n/w

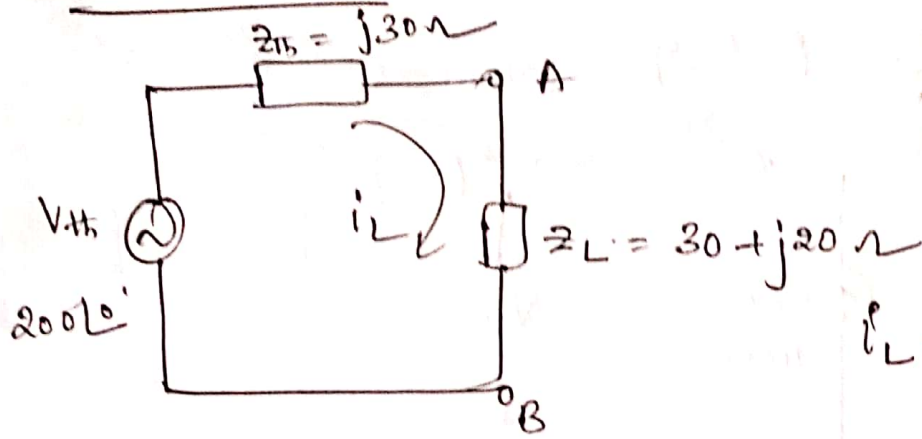

$$i_L = \frac{V_{th}}{Z_{th} + Z_L}$$

$$i_L = \frac{200\angle 0^\circ}{j30 + 30 + j20}$$

$$i_L = 3.43 \angle -59^\circ \text{ Amp}$$

Note :- If the given n/w consists of some dependent source, then these dependent source must be kept as it is while calculating  $Z_{th}$  & should not be shorted or open cktd. Whether it is voltage or current source.

In such cases,


$$Z_{th} = \frac{V_{th}}{I_{sc}}$$

where,

$I_{sc}$  → Short ckt current obtained by shorting the load terminals.


$V_{th}$  → Thevenin's  $v_o$  or open ckt  $v_o$  across load terminals.

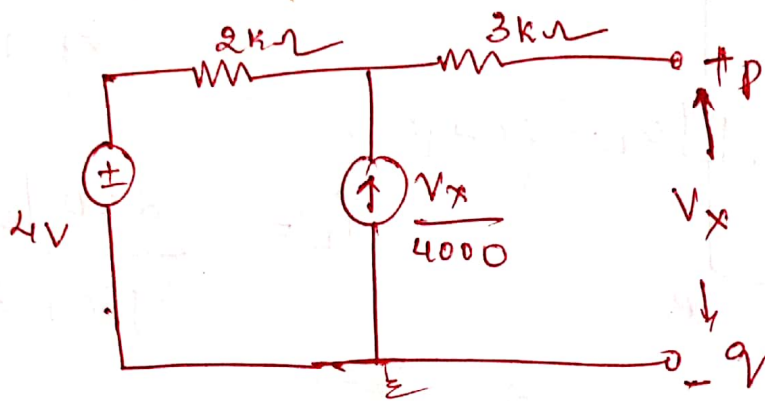5) For the circuit shown, obtain the Ther equivalent across terminals P & Q.



To find  $V_{th}$  :-

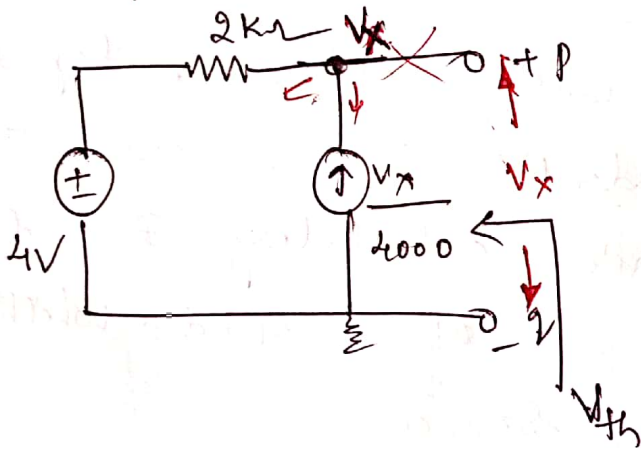Since no current flows through  $3k\Omega$



~~$V_{th} = 2k\Omega \cdot \frac{V_x}{4000}$~~   $V_{th} = V_x$

KCL :-  $\frac{V_x - 4}{2k} + \frac{V_x}{4000} = 0$

$V_x = V_P - V_Q$   
 $V_x = V_P$  (∵  $V_Q = 0$ )

$$\frac{V_x - 4}{2000} = \frac{V_x}{4000}$$



$$4000V_x - 16000 = 2000V_x$$

$$V_x = 8V$$

$$\therefore V_{th} = 8V$$



To find  $Z_{th}$  :

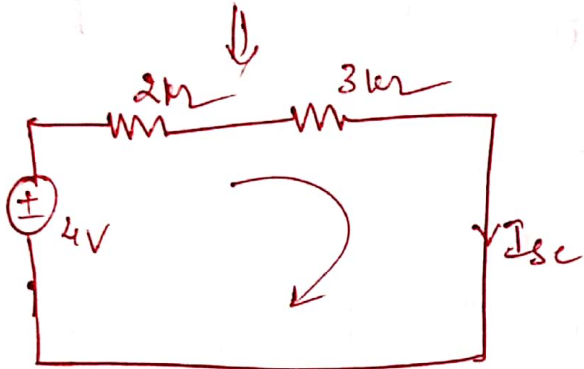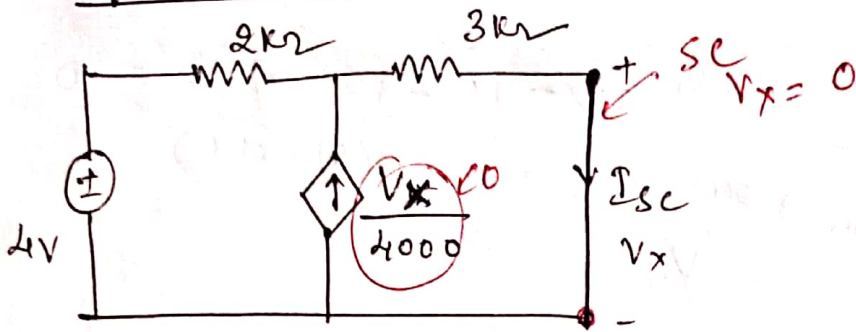


$$I_{sc} = \frac{4}{2k + 3k} = 0.8 \text{ mA}$$

$$\therefore Z_{th} = \frac{V_{th}}{I_{sc}} = \frac{8}{0.8 \text{ mA}}$$

$$Z_{th} = 10k\Omega$$


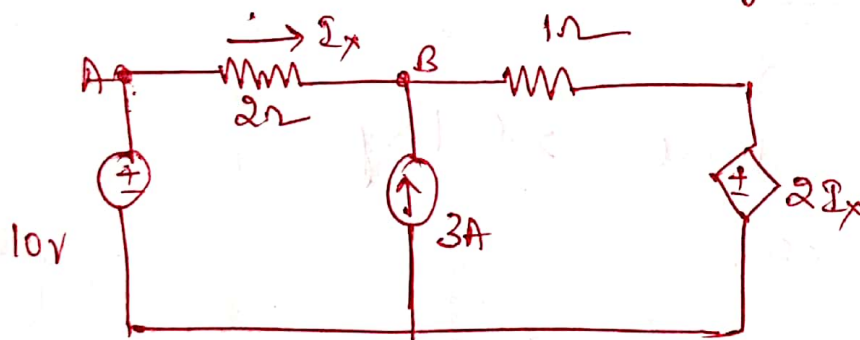
2) Obtain the current  $I_x$  by T. theorem




To find  $V_{th}$  :

Remove  $2\Omega$  resistance.

open circuit  $I_x = 0$

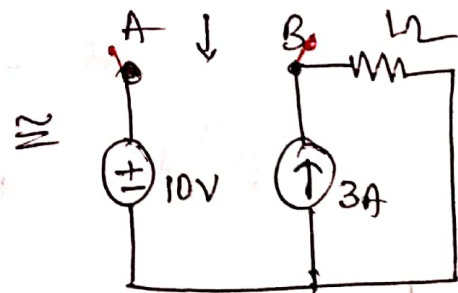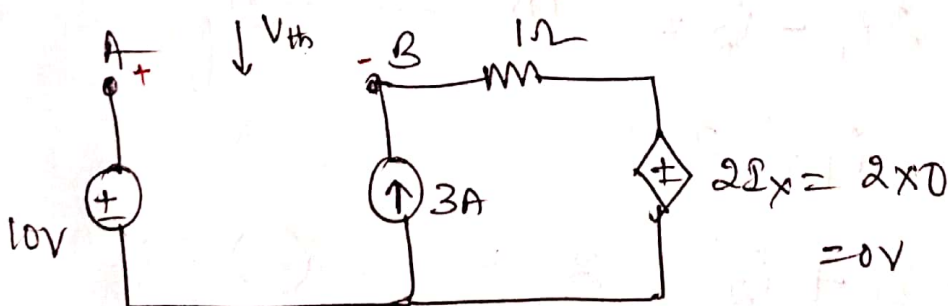


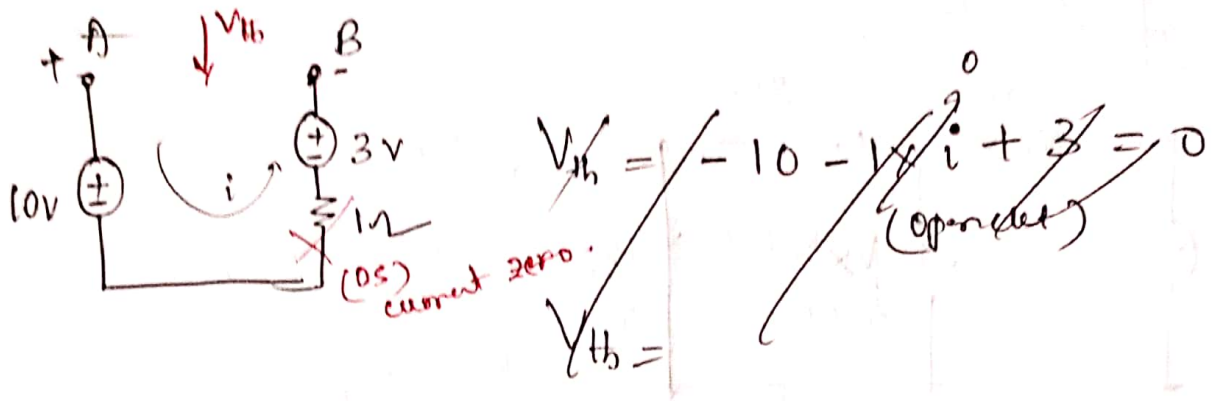

$$V_{th} - 10 + 3 = 0$$

$$V_{th} = 7V$$

To find  $R_{th}$  :-

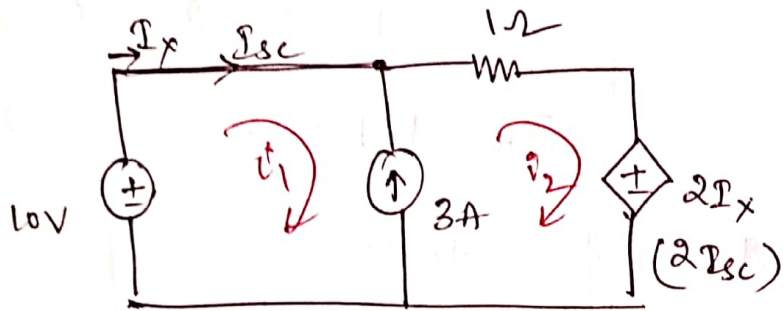

from the fig  
 $I_x = I_{sc}$

Also,  $I_{sc} = I_1$

→ 3A is in b/w 1st & 2nd loop.

∴ Supermesh.

$$-i_2 - 2I_{sc} + 10 = 0$$

$$-i_2 - 2i_1 + 10 = 0$$

$$\text{or } -2i_1 - i_2 = -10 \quad \text{--- (1)}$$

And  $i_2 - i_1 = 3$


$$\text{or } -i_1 + i_2 = 3 \quad \text{--- (2)}$$

Solve ① & ②

$$I_1 = 7/3 \text{ A} \quad I_2 = 16/3 \text{ Amp}$$

∴  $I_{sc} = I_1 = 7/3 \text{ A}$

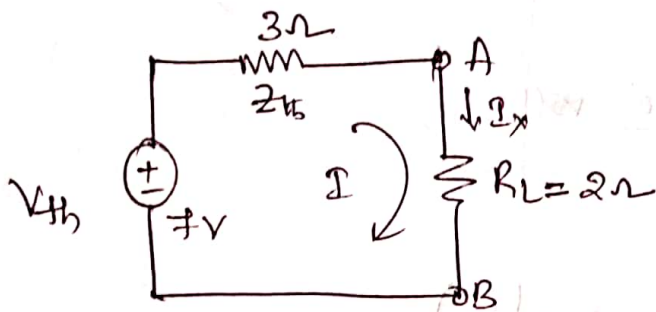∴  $Z_{th} = \frac{V_{th}}{I_{sc}} = \frac{7}{7/3} = 3 \Omega$




$$I = \frac{V_{th}}{Z_{th} + R_L}$$


$$I = \frac{7}{3 + 2} = 1.4 \text{ Amp}$$

⇒  $I_x = 1.4 \text{ Amp}$

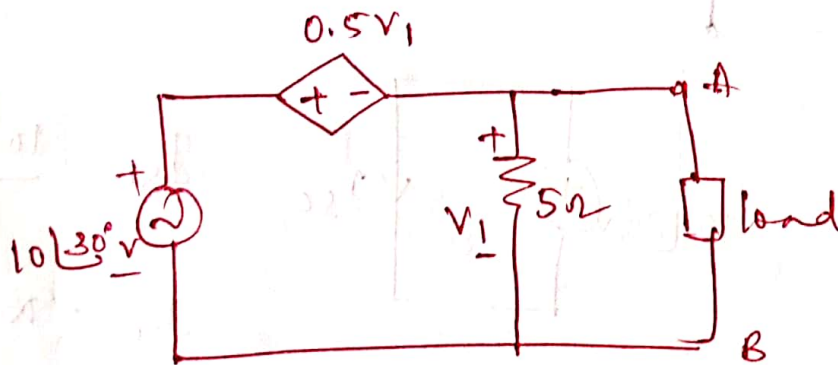3) Find the th. equivalent circuit across load.



Remove the load to find  $V_{th}$  :-

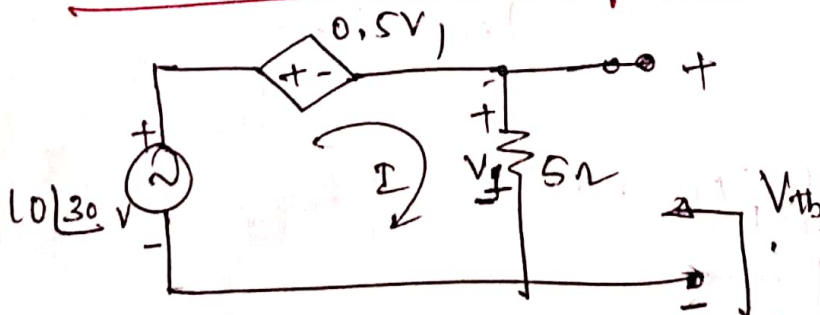

from the fig

$$V_{th} = V_1 = 5I$$


KVL  $-0.5V_1 - V_1 + 10\angle 30^\circ = 0$

$$-1.5V_1 = -10\angle 30^\circ$$


$$V_1 = 6.67\angle 30^\circ \text{ volts}$$

$\therefore V_{th} = 6.67\angle 30^\circ \text{ volts}$

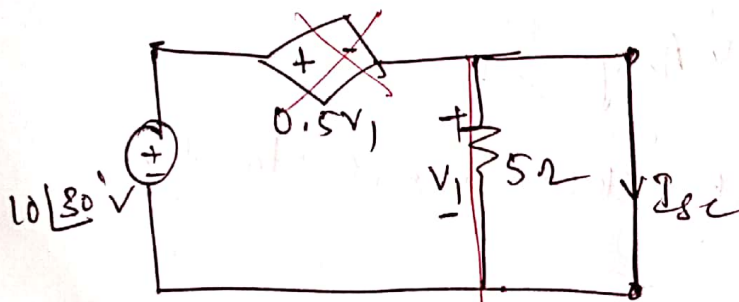to find  $R_{th}$   
(S.C the load terminals)



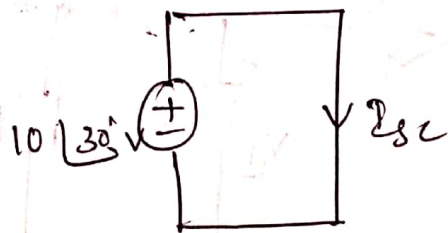
As there is a SC  
across  $5\Omega$ ,  
 $V_1 = 0$



$$I_{sc} = \frac{10\angle 30^\circ}{0}$$


$$I_{sc} = \infty$$

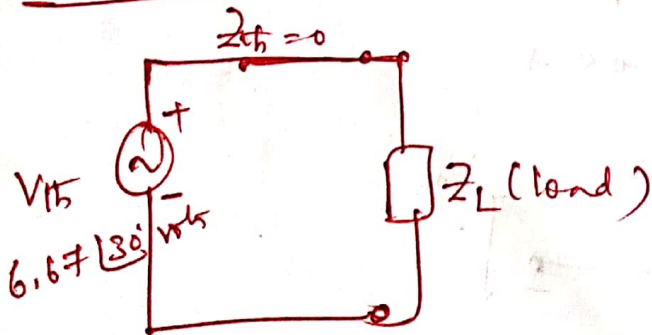Th. Eq. ckt :-  $\therefore Z_{th} = \frac{V_{th}}{I_{sc}} = 0\Omega$






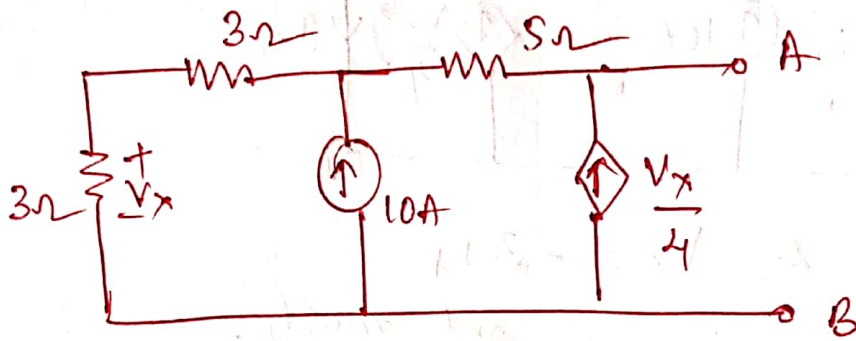4) Find the The eq of the n/w shown in fig



To find  $V_{th}$  :-

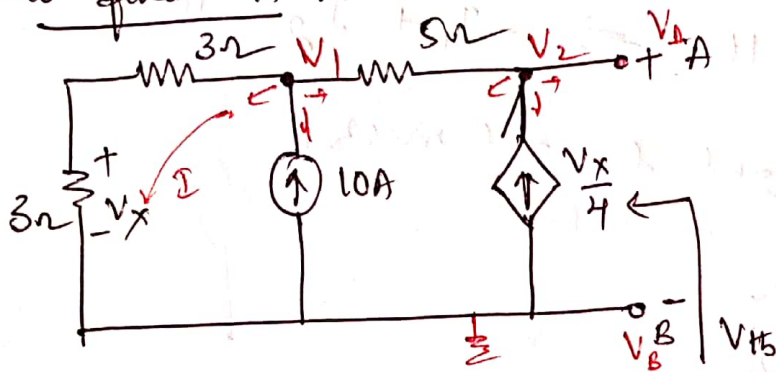

$$V_{th} = V_A - V_B$$

$$V_{th} = V_2$$

KCL @  $V_1$  :- 
$$\frac{V_1}{6} - 10 + \frac{V_1 - V_2}{5} = 0$$

$$0.367 V_1 - 0.2 V_2 = 10 \quad \text{--- (1)}$$

KCL @  $V_2$  
$$\frac{V_2 - V_1}{5} - \frac{V_x}{4} = 0$$

But  $V_x = 3I$  where  $I = \frac{V_1}{6}$

$$V_x = 3 \times \frac{V_1}{6} = \frac{V_1}{2} = 0.5 V_1$$

$$0.2 V_2 - 0.2 V_1 - \frac{0.5 V_1}{4} = 0$$


$$-0.325 V_1 + 0.2 V_2 = 0 \quad \text{--- (2)}$$

$$V_1 = 238.1V$$

$$V_2 = 386.9 \text{ volt}$$

$$\therefore V_{th} = 386.9 \text{ volt}$$

To find  $R_{th}$  :-

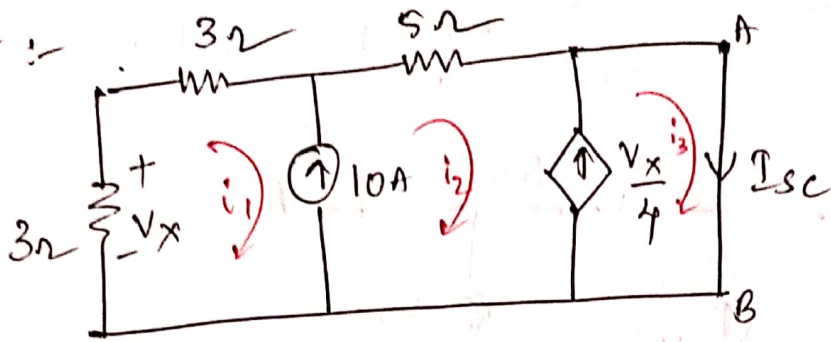

from the fig

$$I_{sc} = i_3 \quad \& \quad V_x = -3i_1$$

→ 10A is b/n  $i_1$  & 2nd mesh.

$$I_2 - I_1 = 10 \Rightarrow -I_1 + I_2 = 10 \quad \text{--- (1)}$$

→  $\frac{V_x}{4}$  is b/n 2nd & 3rd mesh.

$$i_3 - i_2 = \frac{V_x}{4}$$

$$i_3 - i_2 = -3i_1/4$$

$$0.75i_1 - i_2 + i_3 = 0 \quad \text{--- (2)}$$

∴ mesh (1), (2) & (2) forms loop mesh.

$$-3I_1 - 5i_2 - 3i_1 = 0$$

$$-6i_1 - 5i_2 = 0 \quad \text{--- (3)}$$

Solve (1), (3) & (2).  $I_1 = -4.545 A$


$$I_2 = 5.45$$

$$I_3 = 8.864 A$$

$$I_{sc} = 8.864 A$$


$$Z_{th} = \frac{V_{th}}{I_{sc}} = \frac{386.9}{8.864}$$

th eqt ckt :-

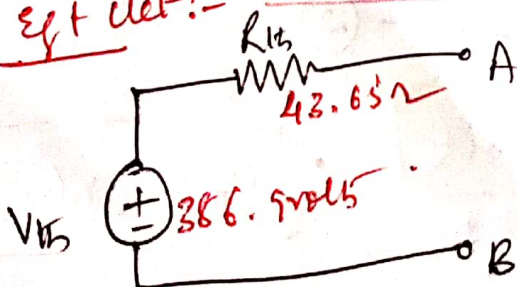


$$Z_{th} = 43.65 \Omega$$

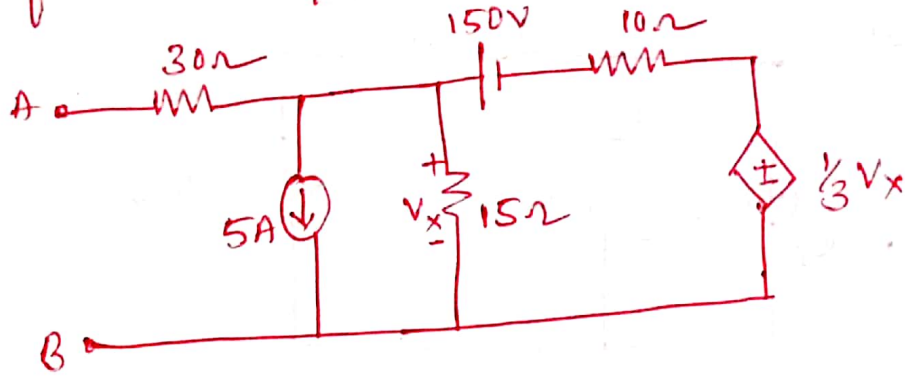5) Calculate Thevenin's equivalent ckt across AB for the n/w shown below.



To find  $V_{th}$ :

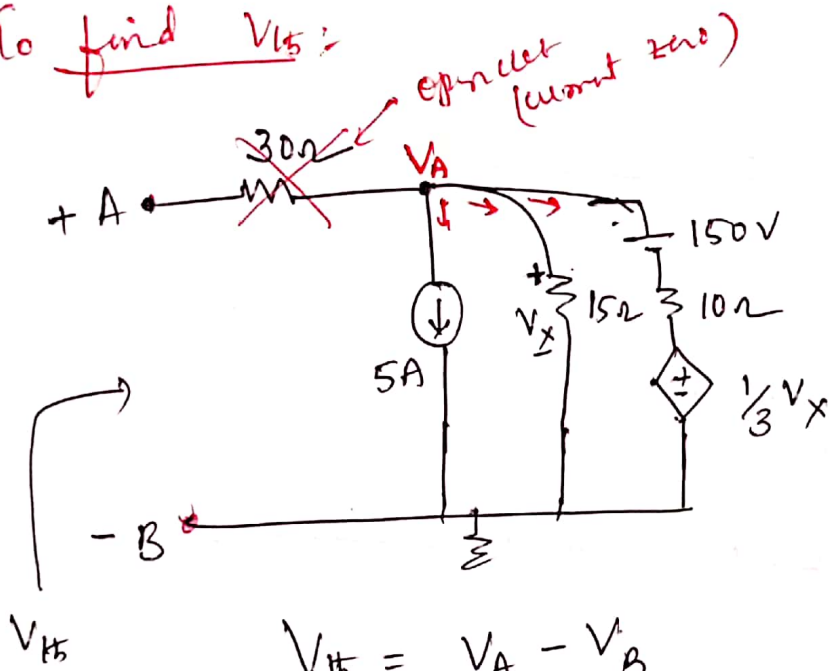

$$V_{th} = V_A - V_B$$

KCL @ A:

$$5 + \frac{V_A}{15} + \frac{V_A - 150 - 0.33V_x}{10} = 0$$

from the fig  $V_x = V_A$


$$5 + 0.066 V_A + 0.1 V_A - 15 - 0.033 V_A = 0$$

$$0.133 V_A = 10$$

$$V_A = 75.18 \text{ volts}$$

$$V_{th} = 75.18 \text{ volts}$$

To find  $R_{th}$  :

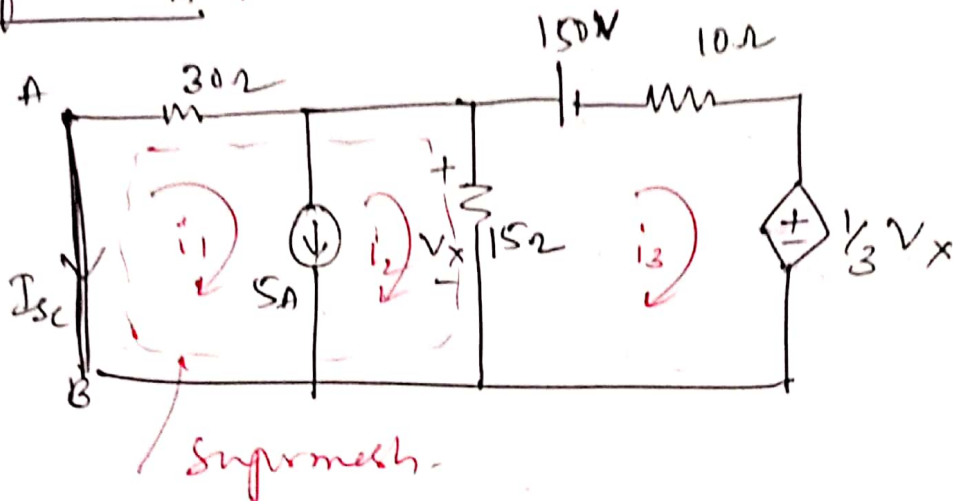

from the supermesh

$$i_1 - i_2 = 5 \quad \text{--- (1)}$$

→ KVL to supermesh

$$-30i_1 - 15(i_2 - i_3) = 0$$

$$-30i_1 - 15i_2 + 15i_3 = 0 \quad \text{--- (2)}$$

→ KVL to 3rd loop.

$$-150 - 10i_3 - 0.33V_x - 15(i_3 - i_2) = 0$$

$$-150 - 10i_3 - 0.33V_x - 15i_3 + 15i_2 = 0$$

from the fig.  $V_x = 15(i_2 - i_3)$

$$-150 - 25i_3 - \cancel{0.33} \times \overset{5}{15}(i_2 - i_3) + 15i_2 = 0$$

$$10i_2 - 20i_3 = 150 \quad \text{--- (3)}$$



$$i_1^p = -2A$$


$$i_2^p = -7A$$

$$i_3^p = -11A$$

$$\therefore I_{sc} = -I_1$$

$$I_{sc} = 2A$$
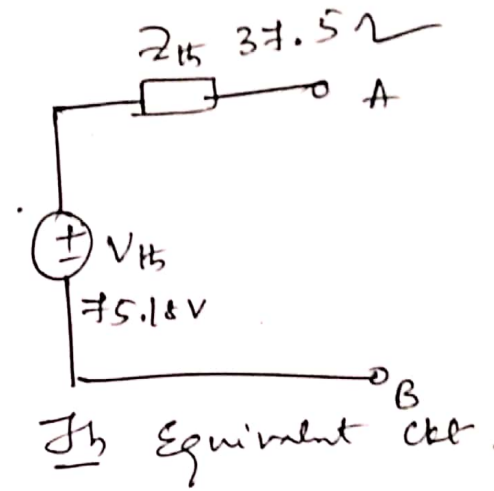
$$\therefore Z_{th} = \frac{V_{th}}{I_{sc}} = 37.5\Omega$$




Norton's Theorem :-

## Transient Behaviour & Initial Conditions

There are many reasons for studying initial & final conditions. The most important reason is that initial & final conditions evaluate the arbitrary constants in the general solution of differential equation.

\* Initial and final conditions in elements :-

1) The Inductor :-

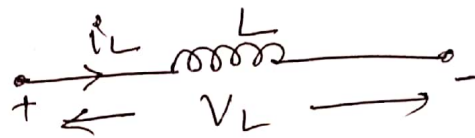

WKT voltage drop across inductor is  $V_L = L \frac{di_L}{dt}$

for dc current,  $\frac{di_L}{dt}$  becomes zero. Hence voltage across inductor is zero. Thus in steady state inductor acts as a short circuit.

Current through inductor is

$$i_L = \frac{1}{L} \int V_L dt$$

$$i_L = \frac{1}{L} \int_{-\infty}^t V_L dt$$

$$i_L = \frac{1}{L} \int_{-\infty}^{0^-} V_L dt + \frac{1}{L} \int_{0^-}^t V_L dt$$

At  $t = 0^+$

$$i_L(0^+) = i_L(0^-) + \frac{1}{L} \int_{0^-}^{0^+} V_L dt$$

$$i_L(0^+) = i_L(0^-)$$

Thus, current through inductor cannot change instantaneously.

If  $i_L(0^-) = 0$ , then  $i_L(0^+) = 0$ . This means that at  $t = 0^+$ , inductor will act as an open circuit.







If  $i_L(0^-) = I_0$ , then  $i_L(0^+) = I_0$ . This means that @  $t = 0^+$ , inductor acts as a current source  $I_0$  Amp.

The final condition of the inductor is derived from


$$V_L = L \frac{di_L}{dt}$$

$\frac{di_L}{dt} = 0$  under steady state cond<sup>n</sup>. Thus  $V_L = 0$

& hence L acts as short circuit at  $t = \infty$

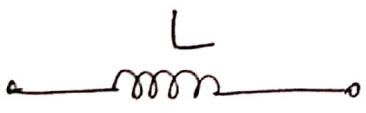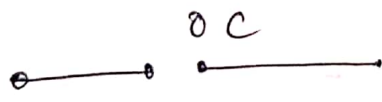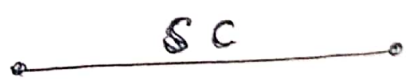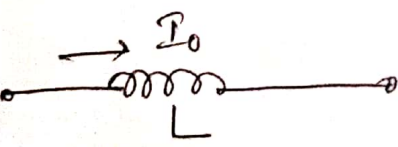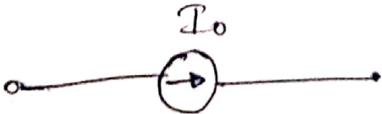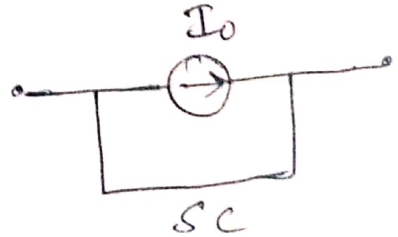Element	Equivalent ckt at $t = 0^+$	Equivalent ckt at $t = \infty$
		
		

2) The Capacitor :-

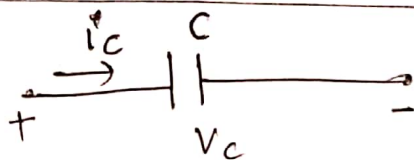

WKT,  $i_c = C \frac{dV_c}{dt}$

If dc  $v_g$  is applied to cap,  $\frac{dV_c}{dt}$  becomes zero. Then current through capacitor becomes zero i.e.,  $i_c = 0$ . Thus in steady state (dc)

Capacitor acts as open circuit.

Now,  $V_c = \frac{1}{C} \int_{-\infty}^t i_c dt$ .

$$V_c = \frac{1}{C} \int_{-\infty}^{0^-} i_c dt + \frac{1}{C} \int_{0^-}^t i_c dt$$

$$V_c = V_c(0^-) + \frac{1}{C} \int_{0^-}^t i_c dt$$

@  $t = 0^+$

$$V_c(0^+) = V_c(0^-) + \frac{1}{C} \int_{0^-}^{0^+} i_c dt$$

$$\therefore \boxed{V_c(0^+) = V_c(0^-)}$$

Thus  $v_g$  drop across cap cannot change instantaneously.




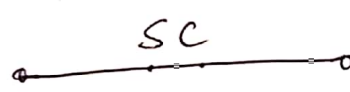
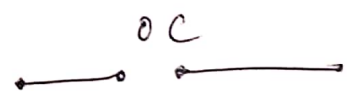
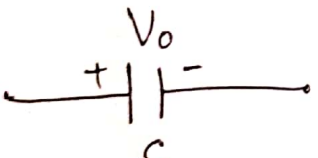

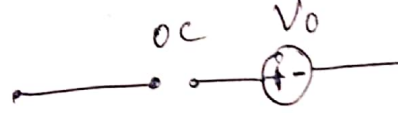
If  $V_c(0^-) = 0$ , then  $V_c(0^+) = 0$ . This means at  $t = 0^+$ , capacitor  $C$  acts as a short circuit.

If  $V_c(0^-) = V_0$  then  $V_c(0^+) = V_0$ , then  $C$  acts as  $v_g$  source of  $V_0$  volts.

Under steady state condition (dc) @  $t = \infty$

$\rightarrow i_c = C \frac{dV_c}{dt}$  is zero.

$\rightarrow C = \frac{q_c}{\phi} = \infty$  Capacitor acts as open circuit @  $t = \infty$

Element	Equivalent ckt at $t = 0^+$	Equivalent circuit at $t = \infty$
		
		

3) Resistor :- For a resistor, the relation b/w applied  $v_g$  & resulting current is given by

$$V = i \cdot R$$

Above eqn is linear & time independent.

The behaviour of R at  $t = 0^+$  & also at  $t = \infty$  is same.

\* Initial Value theorem :-

If  $F(s)$  is the Laplace transform of  $f(t)$ , then, initial value theorem states that,

$$\lim_{t \rightarrow 0^+} f(t) = \lim_{s \rightarrow \infty} sF(s) \quad \text{--- (1)}$$

The Laplace transform is very useful to find the initial value of the time function  $f(t)$ .

Proof :- WKT, the Laplace transform of the real differentiation,

$$L \left\{ \frac{df(t)}{dt} \right\} = sF(s) - f(0^-) \quad \text{--- (2)}$$

Taking limit as  $s \rightarrow \infty$  on both side,

$$\lim_{s \rightarrow \infty} L \left\{ \frac{df(t)}{dt} \right\} = \lim_{s \rightarrow \infty} [sF(s) - f(0^-)] \quad \text{--- (3)}$$

by defn of d.T WKT  $L[f(t)] = \int_{0^-}^{\infty} e^{-st} f(t) dt$

$$\lim_{s \rightarrow \infty} L \left\{ \frac{df(t)}{dt} \right\} = \lim_{s \rightarrow \infty} \int_{0^-}^{\infty} e^{-st} \left[ \frac{df(t)}{dt} \right] dt$$

as  $s \rightarrow \infty$   $e^{-st} = 0$

$\therefore$  LHS becomes zero of eqn (3)

$$\therefore 0 = \lim_{S \rightarrow \infty} [SF(S) - f(0^-)]$$

$$f(0^-) = \lim_{S \rightarrow \infty} SF(S)$$

$$\text{But } f(0^-) = f(0^+) \quad \therefore f(0^+) = \lim_{S \rightarrow \infty} SF(S)$$

$$\lim_{t \rightarrow 0^+} f(t) = f(0^+) = \lim_{S \rightarrow \infty} SF(S)$$

Final value theorem :-

The L.T is also useful to find the final value of the time function  $f(t)$ . Thus if  $F(s)$  is the L.T of  $f(t)$ , then the final value theorem states that,

$$\lim_{t \rightarrow \infty} f(t) = \lim_{S \rightarrow 0} SF(S) \quad \text{--- (1)}$$

Proof :- Consider the L.T of the differentials

$$L \left[ \frac{df(t)}{dt} \right] = SF(S) - f(0^-) \quad \text{--- (2)}$$

Taking limit as  $S \rightarrow 0$  on both side.

$$\lim_{S \rightarrow 0} \left[ L \frac{df(t)}{dt} \right] = \lim_{S \rightarrow 0} [SF(S) - f(0^-)] \quad \text{--- (3)}$$

Consider LHS

$$\lim_{s \rightarrow 0} L \frac{df(t)}{dt} = \lim_{s \rightarrow 0} \int_0^{\infty} e^{-st} \frac{df(t)}{dt} dt$$

as  $s \rightarrow 0$   $e^{-st} = 1$

$$\rightarrow = \int_0^{\infty} \frac{df(t)}{dt} dt$$

$$= f(t) \Big|_0^{\infty}$$

$$\rightarrow = \lim_{t \rightarrow \infty} [f(t) - f(0^-)]$$

$\therefore$  eqn (2) becomes.


$$\lim_{t \rightarrow \infty} [f(t) - f(0^-)] = \lim_{s \rightarrow 0} [sF(s) - f(0^-)]$$

$$\lim_{t \rightarrow \infty} f(t) = \lim_{s \rightarrow 0} sF(s)$$

Problems :-

1) In the n/w, K is closed at  $t=0$  with zero current in the inductor. Find the values of  $i$ ,  $\frac{di}{dt}$ ,  $\frac{d^2i}{dt^2}$  at  $t=0^+$ . If  $R=8\Omega$ ,

$L=0.2H$ .

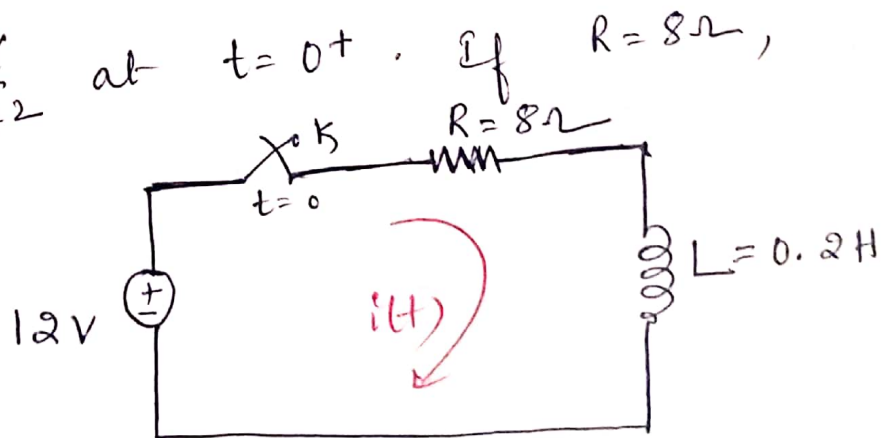




Soln :- Switch is closed at  $t=0$  means  $t=0^+$   
 then switch opens at  $t=0^-$   
 given @  $t=0$  (i.e.  $t=0^+$ ) zero current  
 in the inductor.

i.e.,  $i(0^+) = i(0^-) = 0$

$i_L(0)$   
 means  
 $i(0)$

@  $t=0^+$

KVL to loop

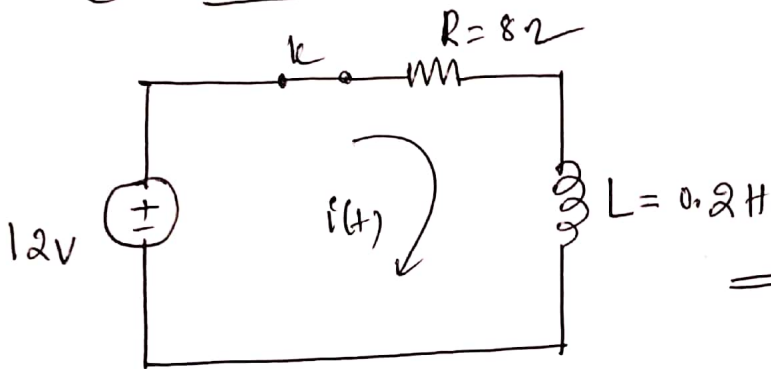

$$12 - 8i(t) - L \frac{di(t)}{dt} = 0 \quad \text{--- ①}$$

$$\Rightarrow 8i(t) + L \frac{di(t)}{dt} = 12$$

@  $t=0^+$   $i(0^+) = 0$

$$\therefore 0.2 \frac{di}{dt} = 12$$

$$\frac{di}{dt} = \frac{12}{0.2} = 60 \text{ A/sec}$$


Differentiating Eqs ①

$$-8 \frac{di(t)}{dt} - L \frac{d^2i(t)}{dt^2} = 0$$

$$-8 \times 60 - 0.2 \frac{d^2i}{dt^2} = 0$$

$$\frac{d^2i}{dt^2} = -2400 \text{ A/sec}^2$$

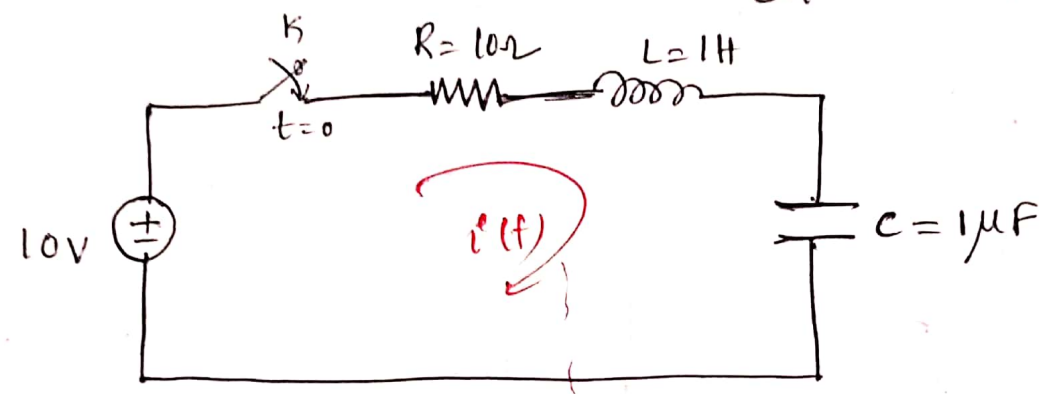2) In the n/w shown, the switch is closed at  $t=0$ . Determine  $i$ ,  $\frac{di}{dt}$ ,  $\frac{d^2i}{dt^2}$  at  $t=0^+$ .




→ In the problem it is not given. We have to indicate.

Given switch is closed at  $t=0$  means  $t=0^+$ , then switch is opened

@  $t=0^-$ . When the switch is in opened condition,

Circuit looks like

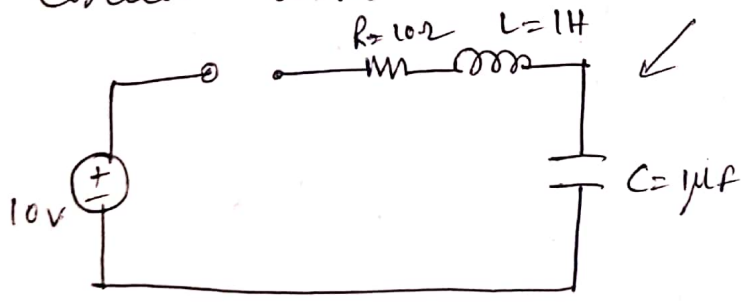


open loop ∴ no current flows

∴  $i(0^-) = i(0^+) = 0$

$V_c(0^-) = V_c(0^+) = 0$

@  $t=0^+$  (switch is closed)

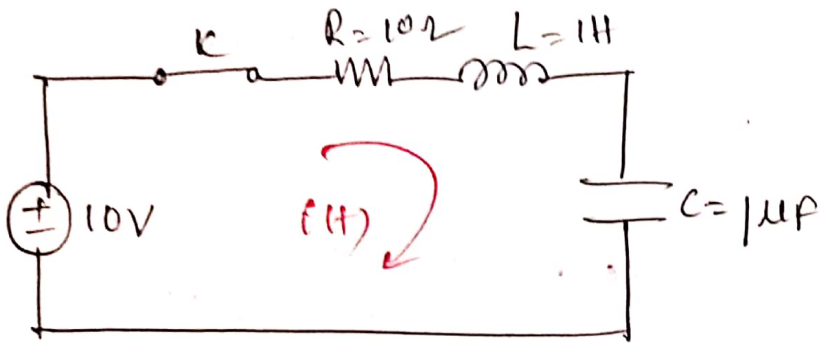

$$V_c = \frac{1}{C} \int i(t) dt$$

$$V_L = L \frac{di}{dt}$$

Apply KVL to loop.

$$10 - R i(t) - L \frac{di}{dt} - \frac{1}{C} \int i(t) dt = 0 \quad \text{--- ①}$$

$$\text{or } 10 - R i(t) - L \frac{di}{dt} - V_c = 0$$

$$\text{at } t = 0^+ \quad i(0^+) = 0 \quad \& \quad V_c(0^+) = 0$$

$$\therefore 10 - L \frac{di}{dt} = 0 \quad \Rightarrow \quad L \frac{di}{dt} = 10$$

$$\frac{di}{dt} = \frac{10}{L} = \frac{10}{1}$$

$$\frac{di}{dt} = 10 \text{ A/sec}$$

Differentiating eqn ①

$$-R \frac{di}{dt} - L \frac{d^2i}{dt^2} - \frac{e(t)}{C} = 0$$


@  $t = 0^+$ ,  $e(0^+) = 0$

$$-10 \times 10 - L \frac{d^2i}{dt^2} = 0$$

$$-\frac{d^2i}{dt^2} = 100$$

or  $\frac{d^2i}{dt^2} = -100 \text{ A/sec}^2$

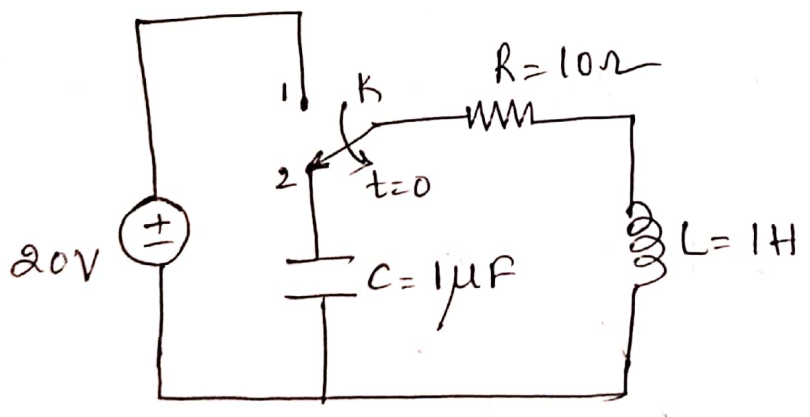3) The switch K is changed from position 1 to position 2 at  $t=0$ . Steady state condn has been reached in position 1. Find the values of  $i$ ,  $\frac{di}{dt}$  &  $\frac{d^2i}{dt^2}$  at  $t=0^+$ .




Given switch K is in position 2 at  $t=0$  (i.e.,  $t=0^+$ )

means it is in position 1 at  $t=0^-$

\* Also in position 1 Steady state condn is reached. WKT inductor acts as short ckt in this condn.



@  $(t=0^-)$

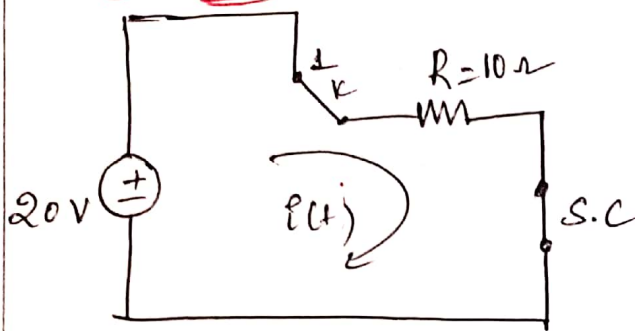

$$20 - 10 i(t) = 0$$

$$i(t) = \frac{20}{10} = 2 \text{ A}$$

$i(t) \Rightarrow i(0^-) = 2 \text{ A}$


WKT  $i(0^+) = i(0^-)$

$\therefore i(0^+) = i(0^-) = 2 \text{ Amp}$

Also  $V_C(0^-) = V_C(0^+) = 0$

( $\because$  no  $v_C$  across Capr)

@  $(t=0^+)$

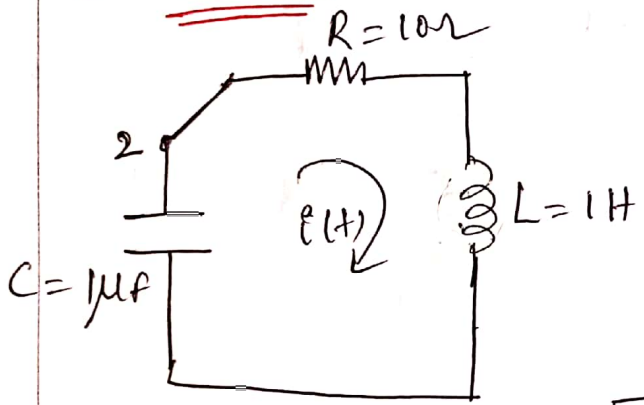

KVL to loop

$$-R i(t) - L \frac{di}{dt} - \underbrace{\frac{1}{C} \int i(t) dt}_{V_C} = 0$$

$$-R i(t) - L \frac{di}{dt} - V_C = 0$$

@  $t=0^+$ ,  $i(0^+) = 2$  &  $V_C(0^+) = 0$

$$-10 \times 2 - 1 \frac{di}{dt} = 0$$

$\frac{di}{dt} = -20 \text{ A/sec}$

Diff. Egn ①

$$-R \frac{di}{dt} - L \frac{d^2i}{dt^2} - \frac{i(t)}{C} = 0$$


$i(0^+) = 2$

$$-10 \times -20 - 1 \frac{d^2 i}{dt^2} - \frac{2}{1 \times 10^{-6}} = 0$$

$$\frac{d^2 i}{dt^2} = 200 - 2 \times 10^6$$


$$\frac{d^2 i}{dt^2} \approx -2 \times 10^6 \text{ A/sec}^2$$

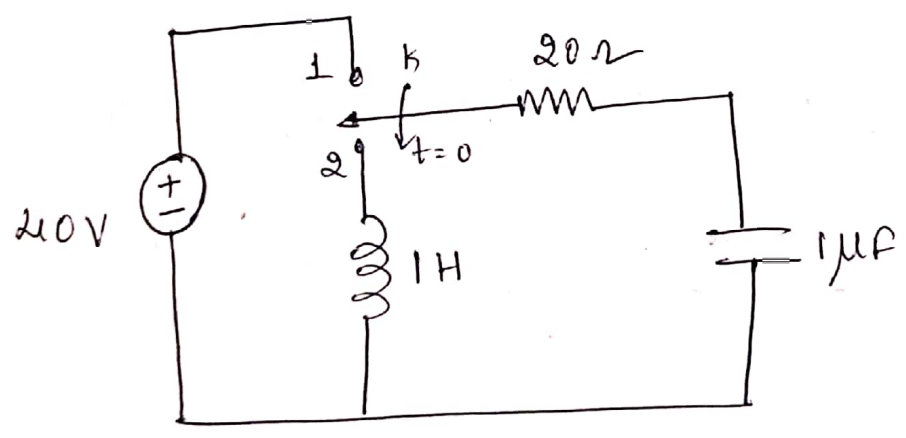4) In the n/w, the switch is moved from position 1 to position 2 at  $t=0$ . The steady state reached before switching. Calculate  $i$ ,  $\frac{di}{dt}$  &  $\frac{d^2 i}{dt^2}$  at  $t=0^+$ .



Given switch is in position 2 at  $t=0$  (i.e.  $t=0^+$ ) means in position 1 at  $t=0^-$ . The steady state reached. WKT @ steady state capacitor acts as open circuit

(∵ ec no current flows)

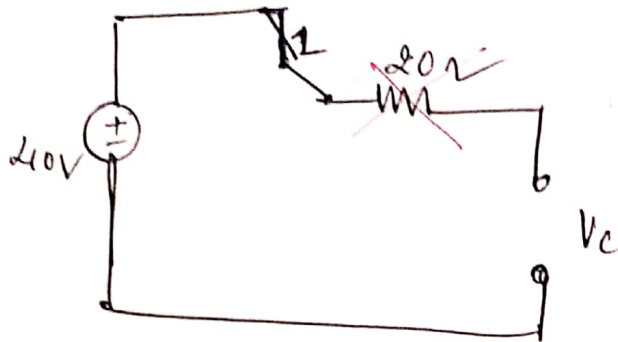


from the fig

$$V_c = 40 \text{ V}$$

$$\therefore V_c(0^+) = V_c(0^-) = 40 \text{ V}$$

Also 
$$i(0^+) = i(0^-) = 0$$

@  $t = 0^+$  switch in position 2

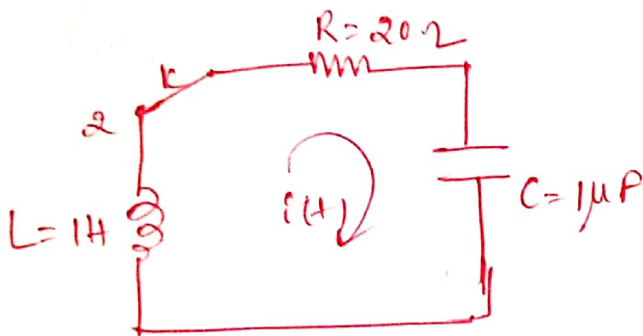

KVL to loop

$$-Ri(t) - \frac{1}{C} \int i(t) dt - L \frac{di}{dt} = 0$$

$$-Ri(t) - V_c - L \frac{di}{dt} = 0$$

@  $t = 0^+$   $i(0^+) = 0$  &  $V_c(0^+) = 40 \text{ V}$

$$-40 - 1 \frac{di}{dt} = 0 \Rightarrow \frac{di}{dt} = -40 \text{ A/sec}$$

Diff eqn ①

$$-R \frac{di}{dt} - \frac{i(t)}{C} - L \frac{d^2i}{dt^2} = 0$$

$$-20 \times -40 - 1 \frac{d^2i}{dt^2} = 0$$

$$\frac{d^2i}{dt^2} = 800 \text{ A/sec}^2$$

## -: Resonance :-

Resonance is defined as a phenomenon in which applied voltage & resulting current are in phase.

Resonance occurs in RLC circuit. During resonance phase angle between current & voltage is zero

$$\text{i.e., } \phi = 0$$

WKT Power factor =  $\cos \phi$

$$\text{P.f} = 1$$

$\therefore$  an AC circuit is said to be in resonance when the circuit P.f is Unity.

The resonant condition in ac circuit may be achieved,

1) By varying the frequency & the supply keeping the network elements constant.

(or)

2) By varying L or C, keeping frequency constant.




## Types of Resonance :-

There are two types of resonance

- i) Series resonance.
- 2) Parallel resonance.
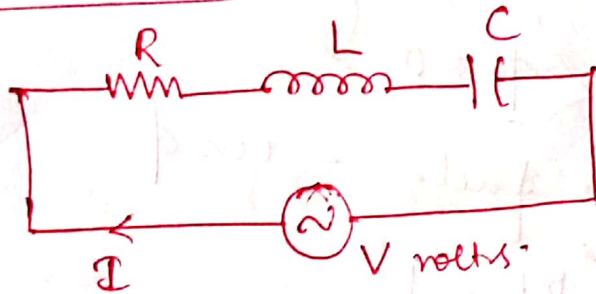
### Series resonance :-

Expression for resonant frequency in Series resonance :-



Consider a general RLC series circuit energised by a voltage source of  $V$  volts as shown in above figure.

The impedance of the circuit is given by

$$Z = R + j(X_L - X_C)$$

Where  $X_L = 2\pi fL$  &  $X_C = \frac{1}{2\pi fC}$

By varying supply frequency  $X_L$  is made equal to  $X_C$

$$\text{If } X_L = X_C$$

Then  $Z = R$

Current in phase with voltage.

$$\rightarrow \phi = 0$$

$$\rightarrow \text{Pf} = 1$$

Now the circuit is at resonance.

$\therefore$  At resonance.

$$X_L = X_C$$

$$2\pi f_0 L = \frac{1}{2\pi f_0 C}$$

[  $f_0$  = resonant-  
freq ].

$$(2\pi)^2 f_0^2 LC = 1$$

$$f_0^2 = \frac{1}{(2\pi)^2 LC}$$

$$f_0 = \frac{1}{2\pi \sqrt{LC}}$$

$$2\pi f_0 = \frac{1}{\sqrt{LC}} \Rightarrow$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

Voltage magnification or figure of merit  
or quality factor or Q-factor :-

The ratio of voltage developed across inductor or capacitor to the applied voltage is

Called voltage magnification.

$$\therefore Q = \frac{V_L \text{ or } V_C}{V}$$

$$\therefore Q = \frac{V_L}{V} \quad \text{or} \quad Q = \frac{V_C}{V}$$

$$Q = \frac{IX_L}{IR}$$

$$Q = \frac{IX_C}{IR}$$

$$Q = \frac{X_L}{R}$$

$$Q = \frac{X_C}{R}$$

Q-factor of inductor

Q-factor of capacitor.

Expression for Q-factor in Series resonance  $[Q_s] :-$

Q factor of series resonance is nothing but the Q-factor of inductor or Q-factor of capacitor.

Let  $Q_s$  be the Q-factor in series resonance,

$$\therefore Q_s = Q$$

$$Q_s = \frac{X_L}{R}$$

$$X_L = 2\pi f L$$
$$Q_s = \omega_0 L$$



$$Q_s = \frac{\omega_0 L}{R} = \frac{1}{\sqrt{LC}} \times \frac{L}{R}$$

$$Q_s = \frac{1}{\sqrt{L} \sqrt{C}} \times \frac{\sqrt{L} \times \sqrt{L}}{R}$$

$$Q_s = \frac{1}{R} \sqrt{\frac{L}{C}}$$

### Characteristics of Series resonant circuit :-

At resonance,

1)  $X_L = X_C$

2) The impedance of the circuit is minimum & is equal to the resistance of the circuit.

i.e.,  $Z = R$ .

3) The current in the circuit is maximum & it is in phase with voltage.

$$I = \frac{V}{R}$$


4) The power factor is unity.

i.e.,  $Pf = 1$



# Frequency resonance curve of series resonant

Circuit :-

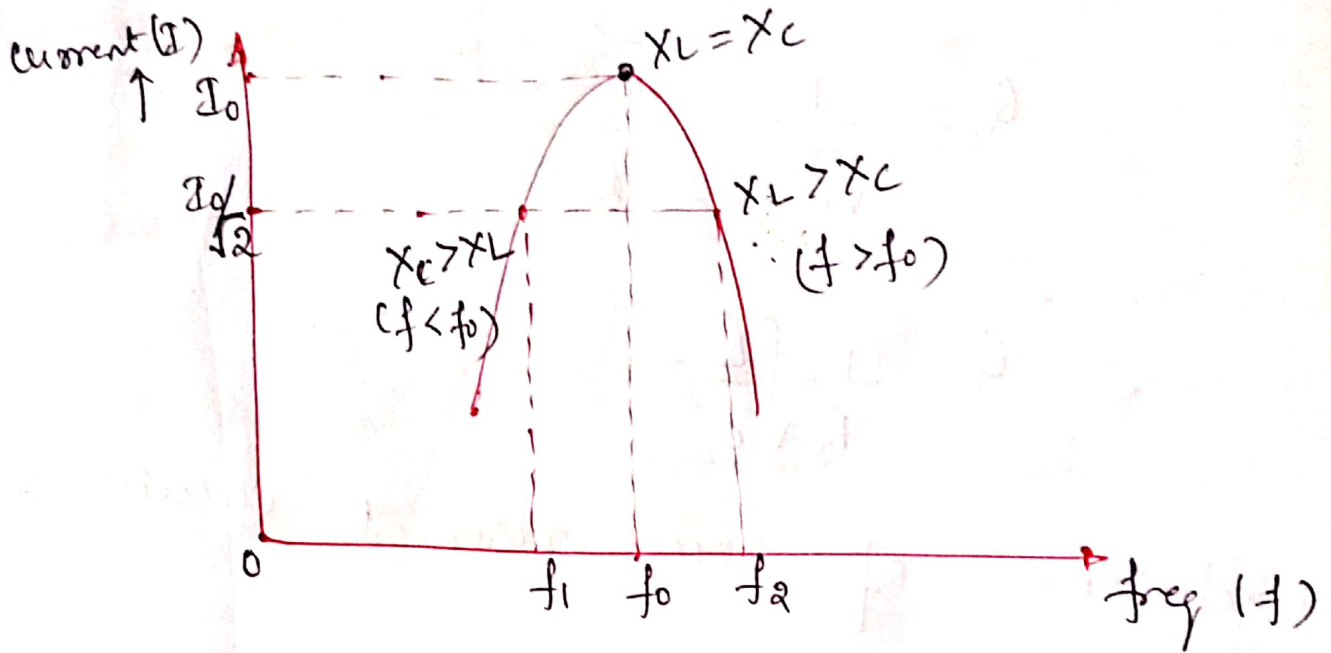

$I_0 \rightarrow$  maximum current or current @ resonance.

$f_1 \rightarrow$  Lower cutoff frequency. } Half power  
 $f_2 \rightarrow$  Upper cutoff frequency. } frequency.

The power at resonance =  $I_0^2 R \rightarrow$  maximum power.

$$I = \frac{I_0}{\sqrt{2}}$$

then power =  $I^2 R$

$$= \left( \frac{I_0}{\sqrt{2}} \right)^2 R$$

$$= \frac{I_0^2}{2} \times R = \frac{1}{2} \times I_0^2 R$$

$$\rightarrow = \frac{1}{2} \times \text{Maximum power}$$

∴ The frequencies  $f_1$  &  $f_2$  corresponding to  $\frac{I_0}{\sqrt{2}}$  or  $0.707 I_0$  are called cut off frequencies or half power frequencies. Because the o/p power is reduced to half of the maximum power.

\* Band width :-

The range or band of frequencies b/w  $f_1$  &  $f_2$  is called as Band width.

ie,  $\boxed{\text{Band width} = \Delta f = f_2 - f_1}$

\* Quality factor :-

Quality factor is defined as the ratio of resonant frequency to the band width.

ie,  $\boxed{Q = \frac{f_0}{\text{B.W}}}$

\* Selectivity :-


It is the reciprocal of Quality factor.

ie,  $\text{Selectivity} = \frac{1}{Q}$

$$\hookrightarrow = \frac{1}{(f_0/\text{B.W})} = \frac{\text{B.W}}{f_0}$$



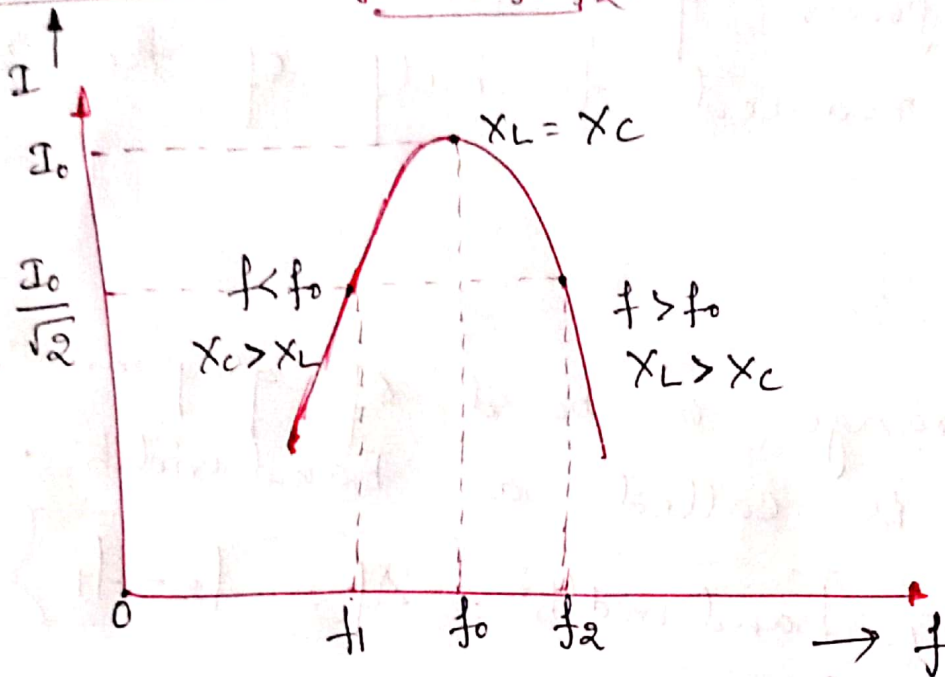\* Show that the resonant frequency is the geometric mean of the two half power frequencies i.e.  $f_0 = \sqrt{f_1 f_2}$



Let  $X_{C1} \rightarrow$  Capacitive reactance at  $f_1$

$X_{C2} \rightarrow$  Capacitive reactance at  $f_2$ .

$X_{L1} \rightarrow$  Inductive reactance at  $f_1$

$X_{L2} \rightarrow$  Inductive reactance at  $f_2$ .

The impedance of RLC series resonant circuit at  $f_1$  is

$$Z_1 = \sqrt{R^2 + (X_{C1} - X_{L1})^2} \quad (\because \text{at } f_1 \quad X_C > X_L)$$

The impedance of RLC series resonant circuit at  $f_2$  is

$$Z_2 = \sqrt{R^2 + (X_{L2} - X_{C2})^2} \quad (\because \text{at } f_2 \quad X_L > X_C)$$

we have,

$$Z_1 = Z_2$$

$$\sqrt{R^2 + (X_{C1} - X_{L1})^2} = \sqrt{R^2 + (X_{L2} - X_{C2})^2}$$

$$\Rightarrow \cancel{R^2} + (X_{C1} - X_{L1})^2 = \cancel{R^2} + (X_{L2} - X_{C2})^2$$

$$\Rightarrow (X_{C1} - X_{L1})^2 = (X_{L2} - X_{C2})^2$$

$$\Rightarrow X_{C1} - X_{L1} = X_{L2} - X_{C2}$$

$$X_{C1} + X_{C2} = X_{L2} + X_{L1} \quad \text{--- ①}$$

But  $X_{C1} = \frac{1}{2\pi f_1 C} = \frac{1}{\omega_1 C}$

$$X_{C2} = \frac{1}{2\pi f_2 C} = \frac{1}{\omega_2 C}$$

$$X_{L1} = 2\pi f_1 L = \omega_1 L$$

$$X_{L2} = 2\pi f_2 L = \omega_2 L$$

Substituting ② in eqn ①, we get-

$$\frac{1}{\omega_1 C} + \frac{1}{\omega_2 C} = \omega_2 L + \omega_1 L$$

$$\frac{1}{C} \left[ \frac{\omega_2 + \omega_1}{\omega_1 \omega_2} \right] = L [\omega_1 + \omega_2]$$



$$\frac{1}{C\omega_1\omega_2} = L$$

$$\text{or } \frac{1}{LC\omega_1\omega_2} = 1 \Rightarrow \frac{1}{LC} = \omega_1\omega_2 \quad \text{--- (3)}$$

$$\text{WKT } \omega_0 = \frac{1}{\sqrt{LC}}$$

$$\text{or } \omega_0^2 = \frac{1}{LC}$$

$\therefore$  Eqn (3) becomes

$$\omega_0^2 = \omega_1\omega_2$$

$$\omega_0 = \sqrt{\omega_1\omega_2}$$

$$2\pi f_0 = \sqrt{2\pi f_1 \cdot 2\pi f_2}$$

$$2\pi f_0 = \sqrt{(2\pi)^2 f_1 f_2}$$

$$(\sqrt{(2\pi)^2} \sqrt{f_1 f_2})$$

$$2\pi f_0 = 2\pi \sqrt{f_1 f_2}$$

$$\Rightarrow \boxed{f_0 = \sqrt{f_1 f_2}}$$

Expression for bandwidth or relationship b/w  
bandwidth & Q-factor:

Let  $f_1$  &  $f_2$  be the lower & upper half power frequencies &  $f_0$  be the resonant frequency.

$$\text{At } f_1, \quad I = \frac{V}{\sqrt{R^2 + (X_{C1} - X_{L1})^2}} \quad (\because \text{ @ } f_1 \quad X_C > X_L)$$

$$\text{Also @ } f_1, \quad I = \frac{I_0}{\sqrt{2}} \quad \text{where } I_0 = \frac{V}{R}$$

$$\frac{I_0}{\sqrt{2}} = \frac{V}{\sqrt{R^2 + (X_{C1} - X_{L1})^2}}$$

$$\frac{V}{\sqrt{2} R} = \frac{V}{\sqrt{R^2 + (X_{C1} - X_{L1})^2}}$$

$$\sqrt{R^2 + (X_{C1} - X_{L1})^2} = \sqrt{2} R$$

Squaring on B.S

$$R^2 + (X_{C1} - X_{L1})^2 = 2R^2$$

$$(X_{C1} - X_{L1})^2 = R^2$$

$$X_{L1} - X_{C1} = R \quad \text{--- (1)}$$

$$\text{@ } f_2, \quad I = \frac{V}{\sqrt{R^2 + (X_{L2} - X_{C2})^2}}$$

$$\text{Also @ } f_2, \quad I = \frac{I_0}{\sqrt{2}}, \quad \text{where } I_0 = \frac{V}{R}$$

$$\frac{I_0}{\sqrt{2}} = \frac{V}{\sqrt{R^2 + (X_{L2} - X_{C2})^2}}$$

$$\frac{V}{\sqrt{2} R} = \frac{V}{\sqrt{R^2 + (X_{L2} - X_{C2})^2}}$$

$$\sqrt{R^2 + (X_{L2} - X_{C2})^2} = \sqrt{2} R$$

Squaring on both side

$$R^2 + (X_{L2} - X_{C2})^2 = 2 R^2$$

$$(X_{L2} - X_{C2})^2 = R^2$$

$$X_{L2} - X_{C2} = R \quad \text{--- (2)}$$

(1) + (2) gives,

$$X_{L1} - X_{L1} + X_{L2} - X_{C2} = 2R$$

$$X_{C1} - X_{C2} + X_{L2} - X_{L1} = 2R$$



$$\frac{1}{\omega_1 C} - \frac{1}{\omega_2 C} + \omega_2 L - \omega_1 L = 2R$$

$$\frac{1}{C} \left[ \frac{\omega_2 - \omega_1}{\omega_1 \omega_2} \right] + L(\omega_2 - \omega_1) = 2R$$

$$(\omega_2 - \omega_1) \left[ \frac{1}{C\omega_1\omega_2} + L \right] = 2R$$

$$\omega_2 - \omega_1 = \frac{2R}{\left[ \frac{1}{C\omega_1\omega_2} + L \right]} \quad \begin{array}{l} \div L \\ \div L \end{array}$$

$$\omega_2 - \omega_1 = \frac{2R}{L} \frac{1}{\frac{1}{C\omega_1\omega_2 L} + 1}$$

$$\omega_2 - \omega_1 = \frac{2R/L}{1+1} = \frac{2R}{2} = R$$

$$\omega_2 - \omega_1 = \frac{2R}{L} \times \frac{1}{2}$$

$$\omega_2 - \omega_1 = \frac{R}{L} \times \frac{\omega_0}{\omega_0}$$

$$\omega_2 - \omega_1 = \frac{\omega_0 R}{L\omega_0}$$

$$\omega_2 - \omega_1 = \frac{\omega_0}{L\omega_0/R} = \frac{\omega_0}{\frac{XL}{R}}$$



$$\omega_2 - \omega_1 = \frac{\omega_0}{Q}$$

$$f_2 - f_1 = \frac{f_0}{Q}$$

or  $B.W = \frac{f_0}{Q}$

\* Impedance of a Series resonant Circuit in terms of freq deviation ( $\delta$ ) :-

Frequency deviation ( $\delta$ ) is defined as the ratio of the difference b/w applied frequency or operating freq & resonant frequency.

$$\text{i.e., } \delta = \frac{f - f_0}{f_0} = \frac{\omega - \omega_0}{\omega_0}$$

where  $f \rightarrow$  operating frequency.

$f_0 \rightarrow$  Resonant frequency.

The impedance of series resonance circuit is

$$Z = R + j(\omega L - \frac{1}{\omega C})$$

$$Z = R + j(\omega L - \frac{1}{\omega C})$$

$$Z = R + \left[ 1 + j \left( \frac{\omega L}{R} - \frac{1}{\omega C R} \right) \right]$$

$$Z = R \left[ 1 + j \left( \frac{\omega L}{R} \times \frac{\omega_0}{\omega_0} - \frac{1}{\omega C R} \times \frac{\omega_0}{\omega_0} \right) \right]$$

$$Z = R \left[ 1 + j \left( \frac{\omega_0 L}{R} \times \frac{\omega}{\omega_0} - \frac{1}{\omega_0 C R} \times \frac{\omega_0}{\omega} \right) \right]$$

$$Z = R \left[ 1 + j \left( Q \frac{\omega}{\omega_0} - Q \frac{\omega_0}{\omega} \right) \right]$$

$$Z = R \left[ 1 + j Q \left( \frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) \right] \quad \text{--- (1)}$$

WKT  $\delta = \frac{\omega - \omega_0}{\omega_0}$

$$\delta = \frac{\omega}{\omega_0} - 1 \quad \Rightarrow \quad \frac{\omega}{\omega_0} = \delta + 1 \quad \text{--- (2)}$$

Substitute eqn (2) in (1) we get-

$$Z = R \left[ 1 + j Q \left( \delta + 1 - \frac{1}{\delta + 1} \right) \right]$$

$$Z = R \left[ 1 + j Q \left( \frac{(\delta + 1)^2 - 1}{\delta + 1} \right) \right]$$

$$Z = R \left[ 1 + j Q \left[ \frac{\delta^2 + 1 + 2\delta - 1}{\delta + 1} \right] \right]$$

$$Z = R \left[ 1 + jQ \left( \frac{s^2 + 2s}{s+1} \right) \right]$$

$$Z = R \left[ 1 + jQ \frac{s(s+2)}{s+1} \right]$$


When  $s$  is too small

$$Z = R [1 + jQ 2s]$$

At resonance  $\rightarrow s = 0$

$$\therefore Z = R$$

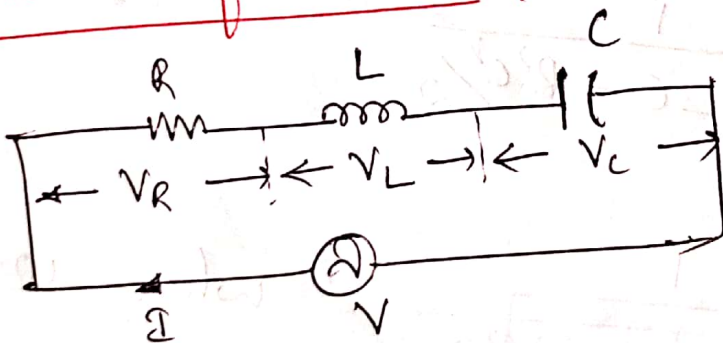\* Expression for  $f_{Lmax}$  and  $f_{Cmax}$  :-



Frequency at which voltage across the capacitor reaches its maximum is called  $f_{Cmax}$ .  $V_{Cmax}$  occurs earlier to  $f_0$ , for which  $X_C > X_L$ .

$$V_C = I X_C \Rightarrow V_C = \frac{V}{Z} \times \frac{1}{\omega C}$$



$$V_c = \frac{V}{\sqrt{R^2 + (X_c - X_L)^2}} \times \frac{1}{\omega C}$$

Squaring on both side

$$V_c^2 = \frac{V^2}{R^2 + \left(\frac{1}{\omega C} - \omega L\right)^2} \times \frac{1}{\omega^2 C^2}$$

$$L_p = \frac{V^2}{\omega^2 C^2} \left[ \frac{1}{R^2 + \frac{1}{\omega^2 C^2} + \omega^2 L^2 - 2 \times \frac{1}{\omega C} \times \omega L} \right]$$

$$L_p = \frac{V^2}{\omega^2 C^2 R^2 + \omega^2 C^2 \left( \frac{1}{\omega^2 C^2} + \omega^2 L^2 - \frac{2L}{C} \right)}$$

$$V_c^2 = \frac{V^2}{\omega^2 C^2 R^2 + 1 + \omega^4 L^2 C^2 - 2\omega^2 LC}$$

$$V_c^2 = \frac{V^2}{\omega^2 C^2 R^2 + (\omega^2 LC - 1)^2}$$

$V_c$  is max, when  $\frac{dV_c^2}{d\omega} = 0$

$$\frac{dV_c^2}{d\omega} = \frac{\text{Denominator} \times 0 - V^2 \{ 2\omega C^2 R^2 + 2(\omega^2 LC - 1) \times 2\omega LC \}}{\{ \omega^2 C^2 R^2 + (\omega^2 LC - 1)^2 \}^2} = 0$$

$$= -V^2 \{ 2\omega C^2 R^2 + 2(\omega^2 LC - 1) \times 2\omega LC \} = 0$$

As  $V \neq 0$   $2\omega C^2 R^2 + 2(\omega^2 LC - 1) \times 2\omega LC = 0$

$$2\omega C \{ CR^2 + 2\omega^2 L^2 C - 2L \} = 0$$

$$CR^2 + 2\omega^2 L^2 C - 2L = 0$$

$$\omega^2 = \frac{1}{LC} - \frac{R^2}{2L^2} \quad \text{or} \quad \omega = \sqrt{\frac{1}{LC} - \frac{R^2}{2L^2}}$$



$$f_{\max} = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{2L^2}}$$

$f_{\max}$  is the freq at which  $V_{\max}$  occurs.  $V_{\max}$  occurs after  $f_0$  for which  $X_L > X_C$ .

$$V_L = I X_L = \frac{V}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}} \times \omega L$$

$$V_L = \frac{V \omega L}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}} = \frac{V \omega L}{\sqrt{R^2 + \omega^2 L^2 + \frac{1}{\omega^2 C^2} - 2 \times \omega L \times \frac{1}{\omega C}}}$$

$$\rightarrow = \frac{V \omega L \times \omega C}{\sqrt{\omega^2 C^2 R^2 + \omega^4 L^2 C^2 + 1 - \frac{2L}{C} \omega^2 C^2}}$$

$$\rightarrow = \frac{V \omega L \times \omega C}{\sqrt{\omega^2 C^2 R^2 + (\omega^2 LC - 1)^2}}$$

$$V_L = \frac{V \omega^2 LC}{\sqrt{\omega^2 C^2 R^2 + (\omega^2 LC - 1)^2}}$$

Squaring on both side

$$V_L^2 = \frac{V^2 \omega^4 L^2 C^2}{\omega^2 C^2 R^2 + (\omega^2 LC - 1)^2}$$

$$V_L \text{ is max } \frac{dV_L^2}{d\omega} = 0$$

$$\frac{dV_L^2}{d\omega} = \frac{\{ \omega^2 C^2 R^2 + (\omega^2 LC - 1)^2 \}^2 \times 4 \omega^3 V^2 L^2 C^2 - V^2 \omega^4 L^2 C^2 \{ 2 \omega C^2 R^2 + 2(\omega^2 LC - 1) \times 2\omega LC \}}{\{ \omega^2 C^2 R^2 + (\omega^2 LC - 1)^2 \}^2} = 0$$

$$4 \left\{ \omega^2 C^2 R^2 + (\omega^2 LC - 1)^2 \right\} - \omega \left\{ 2 \omega C^2 R^2 + 4 \omega^3 L^2 C^2 - 4 \omega LC \right\} = 0 \quad (6)$$

$$= 4 \omega^2 C^2 R^2 + 4 \omega^4 L^2 C^2 + 4 - 8 \omega^2 LC - 2 \omega^2 C^2 R^2 - 4 \omega^4 L^2 C^2 + 4 \omega^2 LC = 0$$

$$= \cancel{2 \omega^2 C^2 R^2} - \cancel{2 \omega^2 C^2 R^2} \quad 2 \omega^2 C^2 R^2 - 4 \omega^2 LC + 4 = 0$$

$$4 \omega^2 LC - 2 \omega^2 C^2 R^2 = 4$$

$$\omega^2 = \frac{2}{2LC - C^2 R^2}$$

$$\omega^2 = \frac{1}{LC - \frac{R^2 C^2}{2}}$$


$$\omega = \sqrt{\frac{1}{LC - \frac{R^2 C^2}{2}}}$$

$$f_{Lmax} = \frac{1}{2\pi} \sqrt{\frac{1}{LC - \frac{R^2 C^2}{2}}}$$

\* Resonance by varying circuit elements :-

Resonance can <sup>also</sup> be obtained by keeping  $f$  constant & by varying  $L$  &  $C$ .

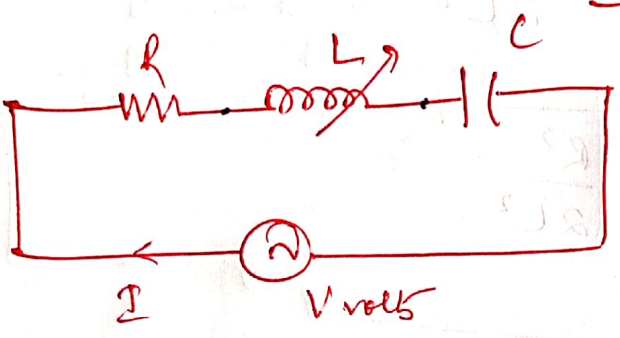The resonance is made by varying  $L$  is termed as inductive tuning.



$X_C$  remains unchanged since both  $f$  &  $C$  are fixed.

$X_L$  varies as  $L$  varies since  $X_L = 2\pi fL$

Let  $L_R$  denotes the inductance at resonance

WKT  $V_L = I X_L$

$X_L = 2\pi fL$

$$V_L = \frac{V}{\sqrt{R^2 + (X_L - X_C)^2}} \times X_L$$

$V_L$  is ~~max~~  $\rightarrow$   $\frac{dV_L^2}{dL} = 0$

Squaring ;  $V_L^2 = \frac{V^2 X_L^2}{R^2 + (X_L - X_C)^2}$



$$V_L \text{ is max if } \frac{dV_L^2}{dx_L} = 0$$

$$\frac{dV_L^2}{dx_L} = \frac{[R^2 + (x_L - x_C)^2] V^2 \times 2x_L - V^2 x_L^2 (2(x_L - x_C))}{\{R^2 + (x_L - x_C)^2\}^2} = 0$$

$$\Rightarrow 2V^2 x_L [R^2 + x_L^2 + x_C^2 - 2x_L x_C] - V^2 x_L^2 (2x_L - 2x_C) = 0$$

$$\Rightarrow 2x_L V^2 R^2 + \cancel{2V^2 x_L^3} + 2V^2 x_L x_C^2 - \underline{4V^2 x_L^2 x_C} - \cancel{2V^2 x_L^3} + \underline{2V^2 x_L^2 x_C} = 0$$

$$\Rightarrow V^2 (2x_L R^2 + 2x_L x_C^2 - 2x_L^2 x_C) = 0$$

$$\text{or } 2x_L R^2 + 2x_L x_C^2 - 2x_L^2 x_C = 0$$

$$2x_L [R^2 + x_C^2 - x_L x_C] = 0$$

$$R^2 + x_C^2 = x_L x_C$$

$$R^2 + x_C^2 = \underline{2\pi f L} x \frac{1}{\underline{2\pi f C}}$$


$$L_R = C [R^2 + x_C^2]$$



## Resonance by varying circuit elements :-
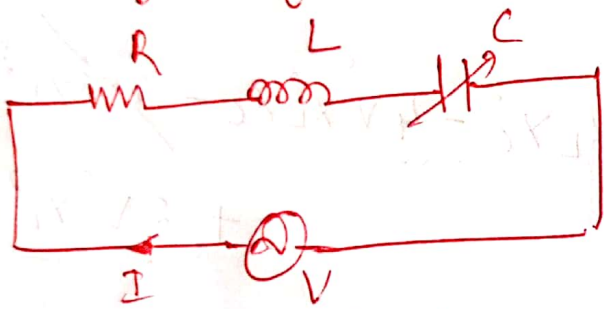
### By varying Capacitance :-

S.T the value of the capacitor for maximum voltage across it in case of capacitive tuning of series resonance is  $C_R = \frac{L}{R^2 + X_L^2}$



Let  $C_R$  denotes the capacitance at resonance.

Here  $X_L$  is fixed  $\because$   $f$  &  $L$  are fixed.

WKT,  $V_C = I X_C$

$$V_C = \frac{V}{\sqrt{R^2 + (X_C - X_L)^2}} X_C$$

Squaring on both side.

$$V_C^2 = \frac{V^2 X_C^2}{R^2 + (X_C - X_L)^2}$$

Voltage across the cap is maximum i.e.

$V_C$  is max if  $\frac{dV_C^2}{dX_C} = 0$

$$\frac{dV_c^2}{dx_c} = \frac{[R^2 + (x_c - x_L)^2] \times 2V^2 x_c - V^2 x_c^2 [2(x_c - x_L)]}{[R^2 + (x_c - x_L)^2]^2} = 0$$

$$\Rightarrow [R^2 + x_c^2 + x_L^2 - 2x_c x_L] 2V^2 x_c - 2x_c^3 V^2 + 2V^2 x_c^2 x_L = 0$$

$$\Rightarrow 2V^2 x_c R^2 + 2V^2 x_c^3 + 2V^2 x_c x_L^2 - 4V^2 x_c^2 x_L - 2V^2 x_c^3 + 2V^2 x_c^2 x_L = 0$$

$$\Rightarrow 2V^2 [R^2 x_c + x_c x_L^2 - 2x_c^2 x_L + x_c^2 x_L] = 0$$

$$x_c [R^2 + x_L^2 - 2x_c x_L + x_c x_L] = 0$$

$$\Rightarrow R^2 + x_L^2 - x_c x_L = 0$$


$$\Rightarrow R^2 + x_L^2 = x_c x_L$$

$$\Rightarrow R^2 + x_L^2 = \frac{1}{2\pi f C} \times 2\pi f L$$

$$\Rightarrow C_R = \frac{L}{R^2 + x_L^2}$$

## Parallel Resonance :-
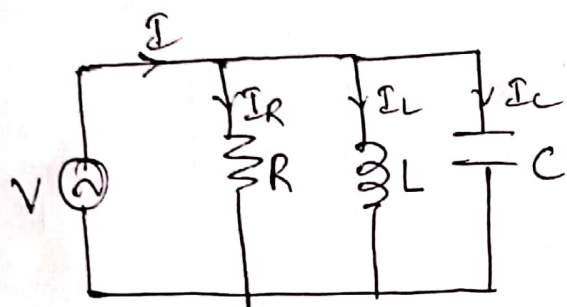
### 1) General parallel resonance circuit :-



WKT

$$I = I_R + I_L + I_C$$

(from KCL)

from  
KCL,

$$I = I_R + I_L + I_C$$

$$\frac{V}{Z} = \frac{V}{R} + \frac{V}{jX_L} + \frac{V}{-jX_C}$$

$$\frac{1}{Z} = \frac{1}{R} - j\frac{1}{X_L} + j\frac{1}{X_C}$$

$$\frac{1}{Z} = \frac{1}{R} + j\left(\frac{1}{X_C} - \frac{1}{X_L}\right)$$

$$Y = G + jB$$

Where  $Y = \frac{1}{Z} \rightarrow$  admittance

$$G = \frac{1}{R} \rightarrow \text{Conductance}$$

$$B = \left(\frac{1}{X_C} - \frac{1}{X_L}\right) \rightarrow \text{Susceptance}$$

At resonance the net susceptance is zero.

$$\therefore B = 0$$



$$\frac{1}{X_C} - \frac{1}{X_L} = 0$$


$$\omega_0 C - \frac{1}{\omega_0 L} = 0$$

$$\omega_0 C = \frac{1}{\omega_0 L}$$

$$\omega_0^2 = \frac{1}{LC} \Rightarrow \omega_0 = \frac{1}{\sqrt{LC}}$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$
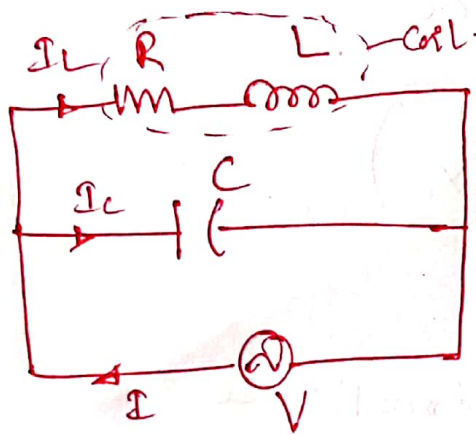
## 2) Practical parallel resonance circuit



The circuit consists of an inductive coil of resistance  $R$  & inductance  $L$  Henry, which is connected in parallel with the capacitance  $C$  farad. This comb<sup>n</sup> is connected across alternating supply.

$$I = I_L + I_C$$



$$\frac{V}{Z} = \frac{V}{R + jX_L} + \frac{V}{-jX_C}$$

$$\frac{1}{Z} = \frac{1}{R + jX_L} + \frac{j}{X_C}$$

$$\frac{1}{Z} = \frac{1}{R + jX_L} \times \frac{R - jX_L}{R - jX_L} + \frac{j}{X_C}$$

$$\frac{1}{Z} = \frac{R - jX_L}{R^2 + X_L^2} + \frac{j}{X_C}$$

$$\frac{1}{Z} = \frac{R}{R^2 + X_L^2} - \frac{jX_L}{R^2 + X_L^2} + \frac{j}{X_C}$$

$$\frac{1}{Z} = \frac{R}{R^2 + X_L^2} + j \left[ \frac{1}{X_C} - \frac{X_L}{R^2 + X_L^2} \right]$$

$$Y = G + jB$$

At resonance susceptance is zero. (i.e.  $B=0$ )

$$\frac{1}{X_C} - \frac{X_L}{R^2 + X_L^2} = 0$$

$$\frac{1}{X_C} = \frac{X_L}{R^2 + X_L^2}$$

$$\cancel{\omega_0} C = \frac{\cancel{\omega_0} L}{R^2 + \omega_0^2 L^2}$$

$$R^2 + \omega_0^2 L^2 = \frac{L}{C}$$

$$\omega_0^2 L^2 = \frac{L}{C} - R^2$$

$$\omega_0^2 = \frac{L}{C \times L^2} - \frac{R^2}{L^2}$$

$$\omega_0^2 = \frac{1}{LC} - \frac{R^2}{L^2}$$

$$\omega_0 = \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

$$f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

(a) resonance ( $B=0$ )

$$Y = \frac{R}{R^2 + \omega L^2}$$


$$Y = \frac{R}{R^2 + \omega_0^2 L^2} \rightarrow \frac{L}{C}$$

$$Y = \frac{CR}{L}$$

$Z = \frac{L}{RC} \rightarrow$  which is called as dynamic impedance

$$Z_d = \frac{L}{RC}$$

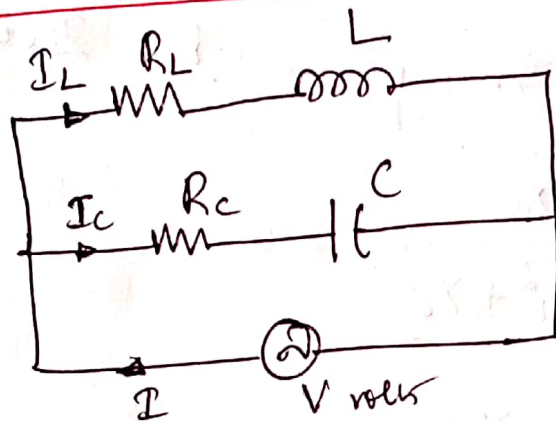3) Parallel resonance circuit when the resistance of the capacitor is considered :-



$$I_C = \frac{V}{Z} = \frac{V}{R_C - jX_C}$$

From the circuit-

$$I = I_L + I_C$$

$$\frac{V}{Z} = \frac{V}{R_L + jX_L} + \frac{V}{R_C - jX_C}$$

$$\frac{1}{Z} = \frac{1}{R_L + jX_L} + \frac{1}{R_C - jX_C}$$

$$\frac{1}{Z} = \frac{1}{R_L + jX_L} \times \frac{R_C - jX_C}{R_C - jX_C} + \frac{1}{R_C - jX_C} \times \frac{R_L + jX_L}{R_L + jX_L}$$

$$\frac{1}{Z} = \frac{R_C - jX_C}{R_C^2 + X_C^2} + \frac{R_L + jX_L}{R_L^2 + X_L^2}$$

$$\frac{1}{Z} = \frac{R_L}{R_L^2 + X_L^2} - \frac{jX_L}{R_L^2 + X_L^2} + \frac{R_C}{R_C^2 + X_C^2} + \frac{jX_C}{R_C^2 + X_C^2}$$

$$\frac{1}{Z} = \frac{R_L}{R_L^2 + X_L^2} + \frac{R_C}{R_C^2 + X_C^2} + j \left[ \frac{X_C}{R_C^2 + X_C^2} - \frac{X_L}{R_L^2 + X_L^2} \right]$$

$$Y = G + jB.$$

At resonance net susceptance is zero (i.e.,  $B=0$ )

$$\frac{X_C}{R_C^2 + X_C^2} - \frac{X_L}{R_L^2 + X_L^2} = 0$$

$$\frac{X_C}{R_C^2 + X_C^2} = \frac{X_L}{R_L^2 + X_L^2}$$

$$X_C (R_L^2 + X_L^2) = X_L (R_C^2 + X_C^2)$$

$$\frac{1}{\omega_0 C} (R_L^2 + \omega_0^2 L^2) = \omega_0 L (R_C^2 + \frac{1}{\omega_0^2 C^2})$$

$$\frac{1}{LC} (R_L^2 + \omega_0^2 L^2) = \omega_0^2 (R_C^2 + \frac{1}{\omega_0^2 C^2})$$

$$\frac{R_L^2}{LC} + \omega_0^2 \frac{L}{C} = \omega_0^2 R_C^2 + \frac{1}{C^2}$$

$$\frac{R_L^2}{LC} - \frac{1}{C^2} = \omega_0^2 R_C^2 - \omega_0^2 \frac{L}{C}$$



$$\frac{R_L^2}{LC} - \frac{1}{C^2} = \omega_0^2 \left( R_C^2 - \frac{L}{C} \right)$$

$$\text{or } \omega_0^2 = \frac{\frac{R_L^2}{LC} - \frac{1}{C^2}}{R_C^2 - \frac{L}{C}}$$

$$\omega_0^2 = \frac{\frac{1}{LC} \left( R_L^2 - \frac{L}{C} \right)}{\left( R_C^2 - \frac{L}{C} \right)}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \sqrt{\frac{R_L^2 - L/C}{R_C^2 - L/C}}$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}} \sqrt{\frac{R_L^2 - L/C}{R_C^2 - L/C}}$$

Impedance at resonance :-


$$Y_0 = \frac{R_L}{R_L^2 + X_L^2} + \frac{R_C}{R_C^2 + X_C^2} \quad (\text{from (1)})$$

$$Z_0 = \frac{1}{Y_0}$$

Current at resonance

$$I_0 = \frac{V}{Z_0} = V Y_0 = V \left[ \frac{R_L}{R_L^2 + X_L^2} + \frac{R_C}{R_C^2 + X_C^2} \right]$$

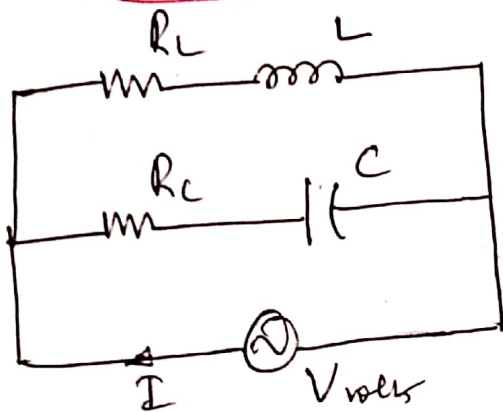\* S.T the parallel ckt is resonant at all frequencies if  $R_L = R_C = \sqrt{\frac{L}{C}}$



WKT,

$$f_0 = \frac{1}{2\pi\sqrt{LC}} \sqrt{\frac{R_L^2 - L/C}{R_C^2 - L/C}}$$

if  $R_L = R_C$  then

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

(a) resonance ( $B=0$ )

$$\frac{X_C}{R^2 + X_C^2} - \frac{X_L}{R_L^2 + X_L^2} = 0$$

$$\frac{X_C}{R_C^2 + X_C^2} = \frac{X_L}{R_L^2 + X_L^2}$$

$$\frac{\frac{1}{\omega_0 C}}{R_C^2 + \frac{1}{\omega_0^2 C^2}} = \frac{\omega_0 L}{R_L^2 + \omega_0^2 L^2}$$

$$\frac{\omega_0 C}{\omega_0^2 C^2 R_c^2 + 1} = \frac{\omega_0 L}{R_L^2 + \omega_0^2 L^2}$$

$$\cancel{\omega_0} C [R_L^2 + \omega_0^2 L^2] = \cancel{\omega_0} L [\omega_0^2 C^2 R_c^2 + 1]$$

$$\frac{C R_L^2}{L C} + \frac{\omega_0^2 L^2 C}{L C} = \frac{\omega_0^2 C^2 R_c^2 L}{L C} + \frac{L}{L C} \quad \div LC$$

$$\frac{R_L^2}{L} + \omega_0^2 L = \omega_0^2 C R_c^2 + \frac{1}{C}$$

$$\text{Given } R_L = R_c = \sqrt{\frac{L}{C}}$$

$$R_L^2 = R_c^2 = \frac{L}{C}$$

$$\frac{L}{L C} + \omega_0^2 L = \omega_0^2 \cancel{L} \times \frac{L}{\cancel{L}} + \frac{1}{C}$$

$$\therefore \boxed{\frac{1}{C} + \omega_0^2 L = \frac{1}{C} + \omega_0^2 L}$$


Hence whatever the value of  $\omega_0$ ,

$$RHS = LHS.$$

Any change in the value of  $\omega_0$  equally affects both sides.

In other words, the circuit is resonant at all frequencies.
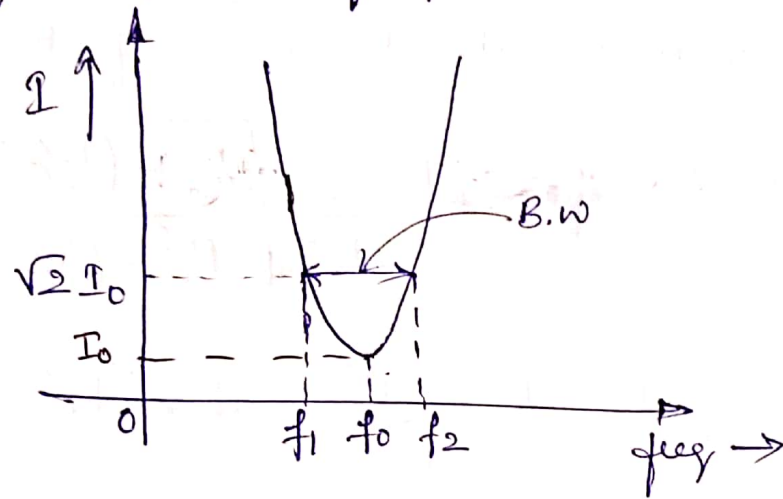
## Frequency response of parallel resonance circuit:-



$$C \uparrow \\ b \frac{f_2 - f_1}{f_0} \uparrow$$

Since the current at resonance is minimum, the circuit is called as antiresonant circuit or rejector circuit.

Also, the impedance of the  $||^{\text{th}}$  resonance circuit is max @ resonance.

The chars of the  $||^{\text{th}}$  resonant circuit are,

- 1) The impedance at resonance will be purely resistive & will be maximum.
- 2) Total current in the circuit is minimum & will be in phase with the applied  $V_g$ .



3) The power factor at resonance will be unity.

4) Parallel resonance circuit is known as antiresonance & Impedance at resonance is known as dynamic resistance ( $Z_d$ )

### Comparison between Series and parallel resonance

<u>Parameter</u>	<u>Series Circuit</u>	<u>Parallel circuit</u>
1) Impedance	$Z = R$ minimum	$Z_d = \frac{L}{CR}$ maximum
2) Power factor	unity	unity
3) Resonance freq	$f_0 = \frac{1}{2\pi\sqrt{LC}}$	$f_0 = \frac{1}{2\pi\sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}}$
4) Current at resonance	Current is maximum at resonance, $I_0 = \frac{V}{R}$ & will be in phase with the applied voltage.	Current is minimum at resonance $I_0 = \frac{V}{Z_d}$ & will be in phase with the applied voltage.

## Series Resonance

Note:- 1)  $f_0 = \frac{1}{2\pi\sqrt{LC}}$  Resonant frequency.

2)  $Z = R$  } @ resonance  
3)  $X_L = X_C$  }  
4)  $I_0 = \frac{V}{R}$  }

5)  $Q = \frac{X_L}{R} = \frac{\omega_0 L}{R} = \frac{2\pi f_0 L}{R}$

6)  $Q = \frac{X_C}{R} = \frac{1}{\omega_0 C R}$

7)  $B.W = \frac{f_0}{Q}$  &  $B.W = f_2 - f_1$

8)  $V_C = I X_C$  &  $V_L = I X_L$

9)  $f_{Lmax} = \frac{1}{2\pi} \sqrt{\frac{1}{LC - \frac{R^2 C^2}{2}}}$

10)  $f_{Cmax} = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{2L^2}}$

11)  $f_0 = \sqrt{f_1 f_2}$

12)  $f_1 = f_0 - \frac{R}{4\pi L}$  &  $f_2 = f_0 + \frac{R}{4\pi L}$

## Problems :-

- 1) A series RLC circuit has  $R=10\Omega$ ,  $L=0.1\text{H}$  &  $C=100\mu\text{F}$  is connected across 200V variable freq source. Find i)  $f_0$  ii)  $Z$  at this freq. iii)  $V_L$  drop across  $L$  &  $C$  @ this freq. iv) Q-factor v) B.W vi) The freq @ which voltage across inductor is max. vii) the freq at which  $V_L$  across capacitor is max.

Given :-

$$R=10\Omega$$

$$L=0.1\text{H}$$

$$C=100\mu\text{F}$$

$$V=200\text{V}$$

i)  $f_0 = ?$

ii)  $Z$  @  $f_0$

iii)  $V_L$  &  $V_C$  @  $f_0$

iv) Q v) B.W

vi)  $f_{L\text{max}} = ?$

vii)  $f_{C\text{max}} = ?$

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$= \frac{1}{2\pi\sqrt{0.1 \times 100 \times 10^{-6}}}$$

$$f_0 = 50.32\text{Hz}$$

$$Z = R = 10\Omega$$

$$V_L = I \times L = \frac{V}{R} \times 2\pi f_0 L$$

$$V_L = \frac{200}{10} \times 2\pi \times 50.32 \times 0.1$$

$$V_L = 632.33\text{V}$$



$$V_c = I \times X_c$$

$$V_c = \frac{V}{R} \times \frac{1}{2\pi f_0 C} = \frac{200}{10} \times \frac{1}{2\pi \times 50.32 \times 100 \times 10^{-6}}$$

$$V_c = 632.57 \text{ volts}$$

or  $V_L = V_c = 632.57 \text{ volts}$

$$Q = \frac{X_L}{R} = \frac{2\pi f_0 L}{R} = 3.16$$

$$Q = 3.16$$

$$B.W = \frac{f_0}{Q}$$

$$\Rightarrow B.W = 15.92 \text{ Hz}$$

$$f_{Lmax} = \frac{1}{2\pi} \sqrt{\frac{1}{LC - \frac{R^2 C^2}{2}}}$$

$$f_{Lmax} = 51.63 \text{ Hz}$$

$$f_{Cmax} = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{2L^2}}$$

$$f_{Cmax} = 49.05 \text{ Hz}$$



2) A Series RLC circuit consists of  $50\Omega$  resistance,  $0.2\text{H}$  inductance & capacitance of  $10\mu\text{F}$  with an apply  $v_r$  of  $20\text{V}$ . Determine i) Resonant freq. ii) Q-factor iii) Upper & lower cut off freq & also find the B.W.

Given.

$$R = 50\Omega$$

$$L = 0.2\text{H}$$

$$C = 10\mu\text{F}$$

$$V = 20\text{V}$$

i)  $f_0 = ?$

ii)  $Q = ?$

iii)  $f_1$  &  $f_2 = ?$

iv) B.W. = ?

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$f_0 = \frac{1}{2\pi\sqrt{0.2 \times 10 \times 10^{-6}}}$$

$$f_0 = 112.54\text{Hz}$$

$$Q = \frac{X_L}{R} = \frac{2\pi f_0 L}{R}$$

$$Q = \frac{2\pi \times 112.54 \times 0.2}{50}$$

$$Q = 2.82$$

$$f_1 = f_0 - \frac{R}{4\pi L} = 94.39\text{Hz}$$

$$f_1 = 94.39\text{Hz}$$

$$f_2 = f_0 + \frac{R}{4\pi L} = 134.18\text{Hz}$$

$$f_2 = 134.18\text{Hz}$$

$$\therefore B.W = f_2 - f_1 \quad \text{or} \quad B.W = \frac{f_0}{Q}$$

$$B.W = 39.79 \text{ Hz}$$

$$B.W = \frac{112.54}{2.82} = 39.9 \text{ Hz}$$

2) A series RLC circuit consists of  $R = 10 \Omega$ ,  $L = 0.01 \text{ H}$  &  $C = 0.01 \mu\text{F}$  is connected across a supply of  $10 \text{ mV}$ . Determine.

- i)  $f_0$     ii) B.W    iii)  $Q$     iv)  $I_0$     v)  $f_1$  &  $f_2$ .

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$f_0 = \frac{1}{2\pi\sqrt{0.01 \times 0.01 \times 10^{-6}}}$$

$$f_0 = 15.91 \text{ kHz}$$

$$Q = \frac{X_L}{R} = \frac{2\pi f_0 L}{R}$$

$$Q = 99.96$$

$$Q = \frac{f_0}{B.W} \quad \Rightarrow \quad B.W = \frac{f_0}{Q} = 159.16 \text{ Hz}$$

$$f_1 = f_0 - \frac{R}{4\pi L}$$

$$f_1 = 15.83 \text{ kHz}$$

$$f_2 = f_0 + \frac{R}{4\pi L}$$

$$f_2 = 15.91 \times 10^3 + \frac{10}{4\pi \times 0.01}$$

$$f_2 = 15.99 \text{ kHz}$$

$$I_0 = \frac{V}{R} = \frac{10 \times 10^{-3}}{10}$$

$$I_0 = 1 \text{ mAmp}$$

4) A coil of resistance  $20\Omega$  & inductance  $10 \text{ mH}$  is in series with a capacitance & is supplied with a constant voltage, variable  $f$  source. The maximum current is  $2 \text{ A}$  at  $1000 \text{ Hz}$ . Find the cut off frequencies.

Given:

WKT,

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$R = 20\Omega$$

$$L = 10 \times 10^{-3} \text{ H}$$

$$I_0 = 2 \text{ A}$$

$$f_0 = 1000 \text{ Hz}$$

$$f_1 = ?$$

$$f_2 = ?$$

$$f_0^2 = \frac{1}{4\pi^2 LC}$$

$$C = \frac{1}{4\pi^2 L f_0^2}$$

$$C = 2.53 \mu\text{F}$$



$$f_1 = f_0 - \frac{R}{4\pi L}$$

$$f_1 = 1000 - \frac{20}{4\pi \times 10 \times 10^{-3}}$$

$$f_1 = 854.02 \text{ Hz}$$

$$f_2 = f_0 + \frac{R}{4\pi L}$$

$$f_2 = 1000 + \frac{20}{4\pi \times 10 \times 10^{-3}}$$

$$f_2 = 1172.33 \text{ Hz}$$

5) An RLC series ckt draws a maximum current of 15A when connected to 230V - 50Hz supply. If the Q-factor is 5, find the parameters of the circuit.

Given,

$$I_0 = 15 \text{ A}$$

$$f_0 = 50 \text{ Hz}$$

$$V = 230 \text{ V}$$

$$Q = 5$$

$$R = ? \quad L = ?$$

$$C = ?$$

WKT,  $I_0 = \frac{V}{R}$

$$R = \frac{V}{I_0} = 15.33 \Omega$$

$$R = 15.33 \Omega$$



$$\rightarrow Q = \frac{X_L}{R}$$

$$X_L = QR$$

$$2\pi f_0 L = Q \cdot R \quad \rightarrow \quad L = \frac{Q \times R}{2\pi f_0} = \frac{5 \times 15.33}{2\pi \times 50}$$

$$L = 0.24 \text{ H}$$

$$\rightarrow Q = \frac{X_C}{R}$$

$$\text{or } X_C = QR$$

$$\frac{1}{2\pi f_0 C} = QR \quad \Rightarrow \quad C = \frac{1}{2\pi f_0 QR}$$

$$C = 41.52 \mu\text{F}$$

6) An RLC series circuit has  $R = 50\Omega$ ,  $L = 0.5\text{H}$  &  $C = 20\mu\text{F}$ . of a constant voltage of  $200\text{V}$  at variable freq is applied. Find the frequency at which resonance occurs. Also find the max v<sub>r</sub> drop across L & C.

Given:

$$R = 50\Omega$$

$$L = 0.5\text{H}$$

$$C = 20\mu\text{F}$$

WKT.

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$f_0 = \frac{1}{2\pi\sqrt{0.5 \times 20 \times 10^{-6}}}$$

$$f_0 = 50.33 \text{ Hz}$$

to find  $V_{Lmax}$  :-

$$f_{Lmax} = \frac{1}{2\pi} \sqrt{\frac{1}{LC - \frac{R^2 C^2}{2}}}$$

$$f_{Lmax} = 51.63 \text{ Hz}$$

$$V_{Lmax} = I X_L$$

$$= \frac{V}{Z} X_L$$

$$= \frac{V}{\sqrt{R^2 + (X_L - X_C)^2}} \times X_L$$

Now  $X_L$  &  $X_C$  @  $f_{Lmax}$

$$X_L = 2\pi f_{Lmax} L$$

$$X_C = \frac{1}{2\pi f_{Lmax} C}$$

$$= 2\pi \times 51.63 \times 0.5$$

$$= 162.2 \Omega$$

$$X_C = 154.13 \Omega$$

$$\therefore V_{Lmax} = \frac{200}{\sqrt{50^2 + (162.2 - 154.13)^2}} \times 162.2$$

$$V_{Lmax} = 640.54 \text{ volts}$$

To find  $V_{\text{max}}$  :-

$$f_{\text{max}} = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{2L}}$$

$$f_{\text{max}} = 49.69 \text{ Hz}$$

$X_L$  &  $X_C$  @  $f_{\text{max}}$

$$X_L = 2\pi f_{\text{max}} L$$

$$X_C = \frac{1}{2\pi f_{\text{max}} C}$$

$$X_L = 156.12 \Omega$$

$$X_C = 160.13 \Omega$$

$$V_{\text{max}} = I X_C$$

$$= \frac{V}{Z} X_C$$

$$= \frac{V}{\sqrt{R^2 + (X_C - X_L)^2}} X_C$$

$$= \frac{200}{\sqrt{R^2 + (160.13 - 156.12)^2}} \times 160.12$$

$$V_{\text{max}} = 638.46 \text{ volts}$$



Ex 10.2

$$I_0 = \frac{V}{R} = \frac{200}{50} = 4 \text{ Amp.}$$

$$V_L = I_0 \times L$$

$$= I_0 \times 2\pi f_0 L$$

$$= 4 \times 2\pi \times 50.33 \times 0.5$$

$$V_C = I_0 \times C$$

$$= I_0 \times \frac{1}{2\pi f_0 C}$$

$$V_L = 632.46 \text{ volts}$$

$$V_C = 632.46 \text{ volts}$$

$$X_L = X_C$$

@ resonance.

$$X_L = X_C = 158.115 \Omega$$

7) A voltage of  $100\sqrt{2} \sin \omega t$  is applied to an RLC series circuit. At resonance freq, the vg across the inductor is 500V, the B.W is 50 Hz. The impedance at resonance is  $75 \Omega$ , find  $f_0$  & constants of the circuit.

Given :-

$$V = 100\sqrt{2} \sin \omega t$$

$$\text{At } f_0, V_L = 500 \text{ volts.}$$

$$\text{B.W} = 50 \text{ Hz.}$$

$$Z = R = 75 \Omega$$

$$f_0 = ?$$

$$R, L \text{ \& } C = ?$$

$$V = \underbrace{100\sqrt{2}}_{V_m} \sin \omega t$$

$$V_{\text{rms}} = \frac{V_m}{\sqrt{2}} = 100 \text{ volts}$$

$$\therefore V = V_{\text{rms}} = 100 \text{ volts}$$



$$Q = \frac{V_L}{V} = \frac{500}{100}$$

$$Q = 5$$

WKT  $Q = \frac{f_0}{\text{B.W}}$

$$f_0 = 5 \times 50$$

$$f_0 = 250 \text{ Hz}$$

At resonance  $Z = R = 75 \Omega$

$$R = 75 \Omega$$

$$Q = \frac{X_L}{R}$$

$$X_L = QR$$

$$2\pi f_0 L = QR$$

$$L = \frac{QR}{2\pi f_0}$$

$$L = \frac{5 \times 75}{2\pi \times 250}$$

$$L = 0.23 \text{ H}$$

$$Q = \frac{X_C}{R}$$

$$\frac{1}{2\pi f_0 C} = QR$$

$$C = \frac{1}{2\pi f_0 QR}$$

$$C = \frac{1}{2\pi \times 250 \times 5 \times 75}$$

$$C = 1.69 \mu\text{F}$$

8) A voltage of  $E = 100 \sin \omega t$  is applied to an RLC series circuit at resonant freq, the  $V_C$  across the capacitor found to be 400V. The B.W is 75 Hz, the impedance at resonance is  $100 \Omega$ . Find the resonant freq & the constants of the circuit.

Given :-  $E = 100 \sin \omega t$

$E = 100 \sin \omega t$

$V_C = 400 V$

B.W = 75 Hz

$Z = R = 100 \Omega$

$f_0 = ?$

$R, L, C = ?$

$E_{rms} = V_{rms} = 100$

$V_{rms} = \frac{V_m}{\sqrt{2}} = \frac{100}{\sqrt{2}}$

$V_{rms} = 70.71 \text{ volts}$

$Q = \frac{V_C}{V} = \frac{400}{70.71} = 5.65$

WKT  $Q = \frac{f_0}{\text{B.W}}$

$f_0 = 5.65 \times 75 = 423.75 \text{ Hz}$

$f_0 = 423.75 \text{ Hz}$

$$Q = \frac{X_L}{R}$$

$$X_L = QR$$

$$2\pi f_0 L = QR$$

$$L = \frac{5.65 \times 100}{2\pi \times 423.75}$$

$$L = 0.21 \text{ H}$$

$$Q = \frac{X_C}{R}$$

$$QR = \frac{1}{2\pi f_0 C}$$

$$C = \frac{1}{2\pi f_0 QR}$$

$$C = \frac{1}{2\pi \times 423.75 \times 5.65 \times 100}$$

$$C = 0.66 \mu\text{F}$$

$$Z = R = 100 \Omega$$

9) A coil of resistance  $20 \Omega$  & inductance  $1 \text{ H}$  is connected in series with a capacitor. The resonant freq is  $100 \text{ rad/sec}$ . If the supply


is  $230 \text{ V} - 50 \text{ Hz}$ , find the

i) Line Current

ii) P.f

iii)

voltage across the coil & cap.

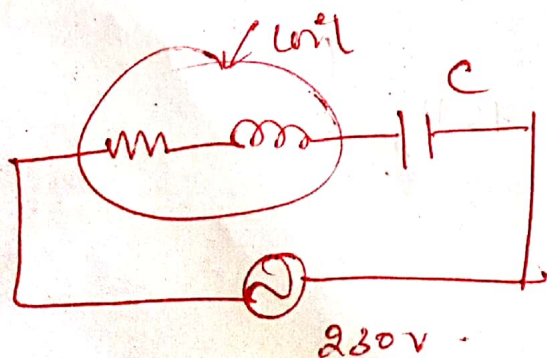



$$R = 20 \Omega$$

To find line current,

$$L = 1 \text{ H}$$

$$I = \frac{V}{Z}$$

$$\omega_0 = 100 \text{ rad/sec}$$

$$V = 230 \text{ V, } 50 \text{ Hz}$$

$$I = \frac{V}{\sqrt{R^2 + (X_L - X_C)^2}}$$

$$I = ?$$

$$P-f = ?$$

$$V_{\text{coil}} = ?$$

$$I = \frac{230}{\sqrt{20^2 + (314.15 - 31.83)^2}} = 0.812 \text{ A}$$

WKT,  $X_L = 2\pi fL$

$$X_C = \frac{1}{2\pi fC}$$

$$X_L = 2\pi \times 50 \times 1$$

$$X_C = \frac{1}{2\pi \times 50 \times 100 \mu}$$

$$X_L = 314.15 \Omega$$

$$X_C = 31.83 \Omega$$

WKT,  $\omega_0 = \frac{1}{\sqrt{LC}}$

$$\omega_0^2 = \frac{1}{LC}$$

$$C = \frac{1}{L\omega_0^2} = 100 \mu\text{F}$$

$$I = 0.812 \text{ Amp}$$



$$\text{Power factor} = \frac{R}{Z}$$

$$\hookrightarrow = \frac{20}{\sqrt{R^2 + (X_L - X_C)^2}} = \frac{20}{\sqrt{20^2 + (314.15 - 31.83)^2}}$$

$$\text{P.o.f} = 0.07$$

V<sub>g</sub> across the coil.

$$V_{\text{coil}} = I_{\text{coil}} \times Z_{\text{coil}}$$

$$V_{\text{coil}} = 0.812 \times 314.79$$

$$V_{\text{coil}} = 255.6 \text{ volts}$$

$$V_C = I \times X_C$$

$$\hookrightarrow = 0.812 \times 31.83$$

$$V_C = 25.84 \text{ volts}$$

$$Z_{\text{coil}} = \sqrt{R^2 + X_L^2}$$

$$= \sqrt{20^2 + (314.15)^2}$$

$$\hookrightarrow = 314.79 \Omega$$

10) A 220V, 100Hz AC source supplies a series RLC circuit with a capc & a coil. If the coil has 50mΩ resistance & 5mH inductance, find at a resonant freq of 100Hz what is the value of capacitor. Also calculate the Q-factor & half power frequencies of the circuit.

Given.

$$V = 220 \text{ volts}$$

$$f = 100 \text{ Hz}$$

$$R = 50 \text{ m}\Omega$$

$$L = 5 \text{ mH}$$

$$\text{At } f_0 = 100 \text{ Hz.}$$

$$C = ?$$

$$Q = ?$$

$$f_1 \text{ \& } f_2 = ?$$

WKT

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

Squaring

$$C = \frac{1}{4\pi^2 L f_0^2}$$

$$C = \frac{1}{4\pi^2 \times 5 \times 10^{-3} \times (100)^2}$$

$$C = 506.6 \mu\text{F}$$

$$Q = \frac{X_L}{R}$$

$$Q = \frac{2\pi f_0 L}{R}$$

$$Q = 62.83$$

$$f_1 = f_0 - \frac{R}{4\pi L}$$

$$f_1 = 100 - \frac{50 \times 10^{-3}}{4\pi \times 5 \times 10^{-3}}$$

$$f_1 = 99.20 \text{ Hz}$$

$$f_2 = f_0 + \frac{R}{4\pi L}$$

$$f_2 = 100 + \frac{50 \times 10^{-3}}{4\pi \times 5 \times 10^{-3}}$$

$$f_2 = 100.8 \text{ Hz}$$

11) A series RLC circuit has a resistance of  $10\Omega$  an inductance of  $0.3H$  & a capce of  $100\mu F$ . The applied  $v_g$  is  $230V$ . Find i)  $f_0$  ii)  $Q$  iii) lower & upper cut-off  $f_s$  iv) B.W v) Current at resonance vi) Currents at  $f_1$  &  $f_2$  vii)  $v_g$  across inductance at resonance.

given

$$R = 10\Omega$$

$$L = 0.3H$$

$$C = 100\mu F$$

$$V = 230V$$

$$f_0 =$$

$$Q =$$

$$f_1 =$$

$$f_2 =$$

$$B.W =$$

$$I_0 =$$

Current at  $f_1$  &  $f_2$


$$\text{@ } f_1 \quad I = \frac{I_0}{\sqrt{2}} =$$

$$V_L = I_0 \times L$$

$$I_0 = I_0 \times 2\pi f_0 L$$

$$V_L =$$

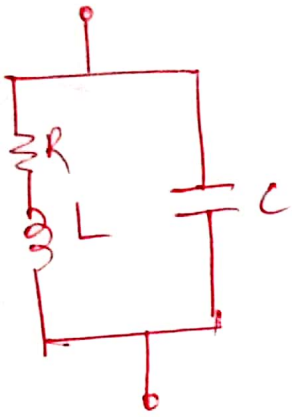1) If  $R = 25\Omega$ ,  $L = 0.5H$  &  $C = 5\mu F$ , find the  $\omega_0$ ,  $f_0$ ,  $Q$  & B.W for the circuit shown below.



WKT,

$$f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

$$f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{0.5 \times 5\mu} - \frac{25^2}{(0.5)^2}}$$

$$f_0 = 100.58 \text{ Hz}$$

$$\omega_0 = 2\pi f_0$$

$$\omega_0 = 2\pi \times 100.58$$

$$\omega_0 = 631.96 \text{ rad/sec}$$

$$Q = \frac{\omega_0 L}{R}$$

$$Q = \frac{631.96 \times 0.5}{25}$$

$$Q = 12.64$$


$$\text{B.W} = \frac{f_0}{Q}$$

$$\text{B.W} = \frac{100.58}{12.64}$$

$$\text{B.W} = 50 \text{ rad/sec}$$



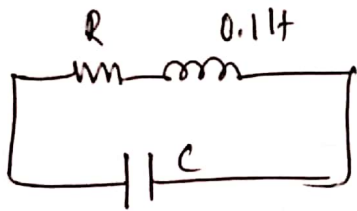2) In the Ckt given, an inductance of  $0.1\text{H}$  having a  $Q$ -factor of  $5$  is in ll with a cap. Determine the value of capacitor & coil resistance at resonant f of  $500\text{ rad/sec}$ .



$$Q = \frac{X_L}{R}$$

$$R = ?$$

$$R = \frac{X_L}{Q} = \frac{\omega_0 L}{Q}$$

$$C = ?$$

$$\omega_0 = 500\text{ rad/sec}$$

$$R = \frac{500 \times 0.1}{5}$$

$$L = 0.1\text{H}$$

$$Q = 5$$

$$R = 10\Omega$$

WKT,

$$f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

$$\omega_0^2 = \frac{1}{LC} - \frac{R^2}{L^2}$$

$$\frac{1}{LC} = \omega_0^2 + \frac{R^2}{L^2}$$

$$\frac{1}{C} = L \left[ \omega_0^2 + \frac{R^2}{L^2} \right] = 0.1 \left[ 500^2 + \frac{10^2}{0.1^2} \right]$$

$$C = 38.46 \mu\text{F}$$

3) A coil of  $20\Omega$  resistance has an inductance of  $0.2\text{H}$  & is connected in  $\text{ll}^{\text{u}}$  with  $100\mu\text{F}$  cap. cal the f<sub>0</sub> at which the circuit will act as a non-inductive resistance & also find the value of non-inductive resistance.

↳ pure resistance. (dynamic resistance)

$$R = 20\Omega$$

$$L = 0.2\text{H}$$

$$C = 100\mu\text{F}$$

$$f_0 = ?$$

$$Z_d = ?$$


$$f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

$$f_0 = 31.83 \text{ Hz}$$

$$Z_d = \frac{L}{RC} = \frac{0.2}{20 \times 100 \times 10^{-6}}$$

$$Z_d = 100\Omega$$

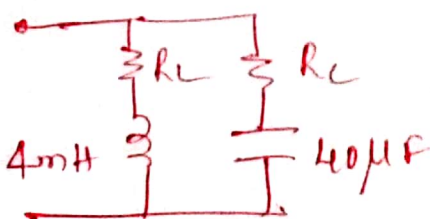
4) Determine  $R_L$  &  $R_C$  for which the circuit shown below resonates at all frequencies



WKT,  $R_L = R_C = \sqrt{\frac{L}{C}}$

$$R_L = R_C = 10\Omega$$

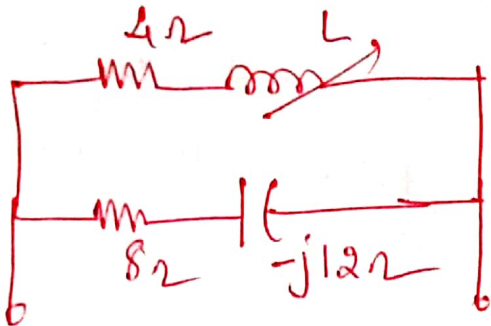5) Find the value of  $L$  for which the ckt gives in below figure resonance at  $\omega = 5000 \text{ rad/sec}$ .



WKT,

$$\frac{1}{Z} = \frac{1}{Z_1} + \frac{1}{Z_2}$$

$$Y = \frac{1}{4 + jX_L} \times \frac{4 - jX_L}{4 - jX_L} + \frac{1}{8 - j12} \times \frac{8 + j12}{8 + j12}$$

$$Y = \frac{4 - jX_L}{4^2 + X_L^2} + \frac{8 + j12}{64 + 12^2}$$

$$Y = \frac{4}{16 + X_L^2} + \frac{8}{208} - j \frac{X_L}{16 + X_L^2} + j \frac{12}{208}$$

(a) resonance ( $B=0$ )

$$\frac{12}{208} = \frac{X_L}{16 + X_L^2}$$

$$12(16 + X_L^2) = 208 X_L$$

$$192 + 12X_L^2 = 208 X_L$$

$$12X_L^2 - 208X_L + 192 = 0$$

$$X_L = 16.36 \Omega \quad \text{or} \quad X_L = 0.978 \Omega$$

$$\omega_0 L = 16.36$$

$$L = \frac{16.36}{5000}$$


$$L = 3.272 \text{ mH}$$

$$\omega_0 L = 0.978$$

$$L = \frac{0.978}{5000}$$

$$L = 0.196 \text{ mH}$$

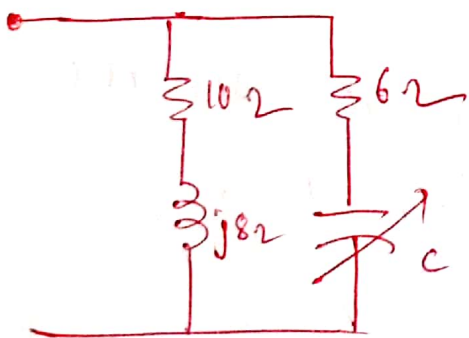6) Find the value of C for which the circuit gives in fig resonant at 750 Hz.



$$Y = \frac{1}{10 + j8} + \frac{1}{6 - jX_C}$$

$$Y = \frac{1}{10 + j8} \times \frac{10 - j8}{10 - j8} + \frac{1}{6 - jX_C} \times \frac{6 + jX_C}{6 + jX_C}$$

$$f = 750 \text{ Hz}$$

$$Y = \frac{10 - j8}{100 + 64} + \frac{6 + jX_C}{36 + X_C^2}$$

$$Y = \frac{10}{164} - \frac{j8}{164} + \frac{6}{36 + X_C^2} + \frac{jX_C}{36 + X_C^2}$$



$$Y = G + jB \quad \text{@ resonance } B = 0$$

$$\frac{X_c}{36 + X_c^2} = \frac{8}{164}$$

$$164X_c = 288 + 8X_c^2$$

$$8X_c^2 - 164X_c + 288 = 0$$

$$X_c = 18.56 \Omega$$

$$\text{or } X_c = 1.94 \Omega$$

$$\frac{1}{\omega_0 C} = 18.56 \Omega$$

$$\frac{1}{2\pi f_0 C} = 1.94$$


$$C = \frac{1}{2\pi f_0 \times 18.56}$$

$$C = \frac{1}{2\pi \times 750 \times 1.94}$$

$$C = 11.43 \mu\text{F}$$

$$C = 109.38 \mu\text{F}$$

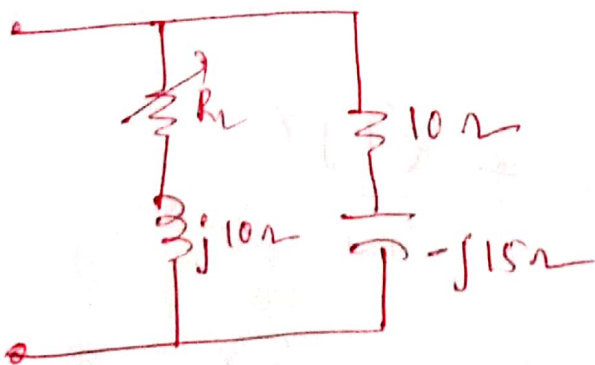3) Find the value of  $R_L$  for which, the ckt shown in below fig is ~~low~~ resonant.



$$Y = \frac{1}{R_L + j10} + \frac{1}{10 - j15}$$

$$Y = \frac{R_L - j10}{R_L^2 + 10^2} + \frac{10 + j15}{10^2 + 15^2}$$

$$Y = \frac{R_L}{R_L^2 + 100} + \frac{10}{100 + 225} + j \left[ \frac{15}{225} - \frac{10}{R_L^2 + 100} \right]$$

*reactance*  
 $B = 0$

$$\Rightarrow \frac{15}{225} = \frac{10}{R_L^2 + 100}$$

$$15[R_L^2 + 100] = 2250$$

$$15R_L^2 + 1500 = 2250$$

$$15R_L^2 = 2250 - 1500$$


$$15R_L^2 = 750$$

$$R_L^2 = \frac{750}{15}$$

$$R_L^2 = 116.67$$

$$R_L = 10.8 \Omega$$

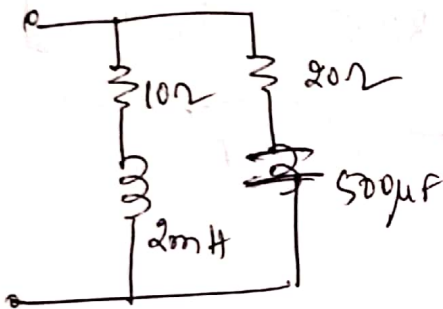8) An inductive coil of resistance  $10\Omega$  & inductance  $2\text{mH}$  is connected in parallel with another branch consisting of a resistance of  $20\Omega$  in series with a capacitance of  $500\mu\text{F}$ . Find the resonant freq & the corresponding current, when the applied  $v_r$  is  $230\text{V}$ .



$$R_L = 10\Omega$$

$$R_C = 20\Omega$$

$$L = 2\text{mH}$$

$$C = 500\mu\text{F}$$

$$f_0 = ?$$

$$I_0 = ?$$

$$V = 230\text{V}$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}} \sqrt{\frac{R_L^2 - L/C}{R_C^2 - L/C}}$$

$$f_0 = \frac{1}{2\pi\sqrt{2 \times 10^{-3} \times 500 \times 10^{-6}}} \sqrt{\frac{100 - \frac{2 \times 10^{-3}}{500 \times 10^{-6}}}{400 - \frac{2 \times 10^{-3}}{500 \times 10^{-6}}}}$$

$$f_0 = 78.36 \text{ Hz}$$

$$I_0 = V Y_0$$

$$I_0 = V \left[ \frac{R_L}{R_L^2 + X_L^2} + \frac{R_C}{R_C^2 + X_C^2} \right]$$

$$X_L = 2\pi f_0 L$$

$$X_C = \frac{1}{2\pi f_0 C}$$

$$X_L = 0.98\Omega$$

$$X_C = 4.06\Omega$$

$$I_0 = 230 \left[ \frac{10}{100 + 0.982} + \frac{20}{400 + 4.062} \right]$$

$$I_0 = 33.82 \text{ Amp}$$

9) A circuit has inductive reactance of  $20\Omega$  at  $50\text{Hz}$  in series with a resistance of  $15\Omega$  for an applied  $v_s$  of  $200\text{V}$  at  $50\text{Hz}$ . Calculate

1) Phase angle b/w current & voltage

2) the current.

3) The value of shunting capacitance to bring the ckt to resonance & the current at resonance

$$X_L = 20\Omega$$

$$f = 50\text{Hz}$$


$$R = 15\Omega$$

$$V = 200\text{V}$$

1)  $\phi = ?$

2)  $I = ?$

3)  $C = ?$   
 $I_0 = ?$  } @  $f_0$

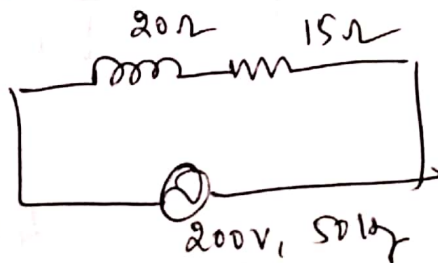

$$\phi = \tan^{-1} \left( \frac{X_L}{R} \right)$$


$$\phi = 53.13^\circ$$

$$I = \frac{V}{Z} = \frac{V}{R + jX_L}$$



$$I = \frac{200}{15 - j20} = 4.8 - j6.4$$
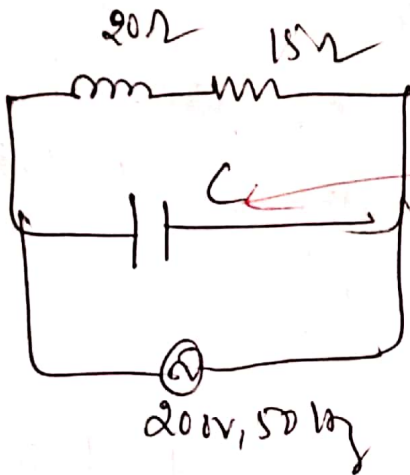
$$I = 8 \angle -53.13^\circ \text{ amp}$$



Shunt  
capacitor

$$f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

$$f_0^2 = \frac{1}{4\pi^2} \left[ \frac{1}{LC} - \frac{R^2}{L^2} \right]$$

$$4\pi f_0^2 = \frac{1}{LC} - \frac{R^2}{L^2}$$

$$X_L = 20$$

$$2\pi f_0 L = 20$$

$$L = \frac{20}{2\pi \times 50}$$

$$L = \underline{\underline{0.0637 \text{ H}}}$$

$$\frac{1}{LC} = 4\pi f_0^2 + \frac{R^2}{L^2}$$

$$\frac{1}{C} = L \left[ 4\pi f_0^2 + \frac{R^2}{L^2} \right]$$

$$\frac{1}{C} = 0.0637 \left[ 4\pi^2 \times (50)^2 + \frac{15^2}{(0.0637)^2} \right]$$

$$\frac{1}{C} = 6322.26$$

$$C = 158.17 \mu\text{F}$$

$$I_0 = \frac{V}{Z_d} \quad \text{where} \quad Z_d = \frac{L}{R C}$$

$$I_0 = \frac{200}{26.55}$$

$$Z_d = \frac{0.0637}{15 \times 158.17 \times 10^{-6}}$$

$$Z_d = 26.55 \Omega$$

$$I_0 = 7.533 \text{ amp}$$

10) A parallel resonant ckt has a capacitance of  $100 \mu\text{F}$  in one branch & an inductance of  $100 \mu\text{H}$  with a resistance of  $10 \Omega$  in the other branch, the line voltage is  $100\text{V}$ .  
Find 1)  $f_0$  2)  $I_L$  &  $I_C$  3)  $I$  &  $Z$  at resonance

$$R = 10 \Omega$$

$$L = 100 \mu\text{H}$$

$$C = 100 \mu\text{F}$$

$$V = 100\text{V}$$

$$f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

$$f_0 = 1.59 \text{ MHz}$$

$$I_L = \frac{V}{Z_L} = \frac{V}{R + jX_L}$$

$$X_L = 2\pi f_0 L$$

$$= \frac{100}{10 + j999.02}$$

$$X_L = 999.02 \Omega$$

$$I_L = 0.1 \angle -89.42 \text{ Amp}$$

$$I_C = \frac{V}{Z_C} = \frac{V}{-jX_C}$$

$$I_C = \frac{100}{-j1 \times 10^3}$$

$$X_C = \frac{1}{2\pi f_0 C}$$

$$X_C = 10 \Omega$$

$$I_C = \frac{100}{1 \times 10^3} \angle 90$$

$$I_C = 0.1 \angle 90 \text{ amp}$$

$$Z_d = \frac{L}{R_C} = 100 \mu\text{H}$$

$$I_0 = \frac{V}{Z_d} = 1 \text{ mAmp}$$


## Module-5 Two-Port Network Parameters

(1)
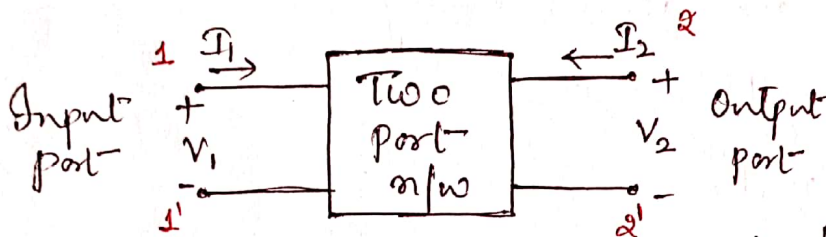
### Representation of a two-port network:-

A two-port network is a four terminal network. Two input terminals & two output terminals.  $V_1$  &  $I_1$  are the variables at input port &  $V_2$  &  $I_2$  are the variables at output port. Out of 4 variables  $V_1, I_1, V_2$  &  $I_2$ , two of them chosen as independent variables & the remaining two as dependent variables.

11'  $\rightarrow$  i/p port.  
22'  $\rightarrow$  o/p port.



Two-port networks are important in modeling electronic devices & system components.

For eg: In electronics, two port n/ws are employed to model transistors & op-amps.

Other examples of electrical components modeled by two ports are transformers & transmission lines.

The parameters of a two-port n/w completely describes the physical behavior of any electronic devices.


Thus knowing the parameters of a two-port n/w permits us to describe its operation when it is connected to a larger network.

Two port n/w parameters are classified as

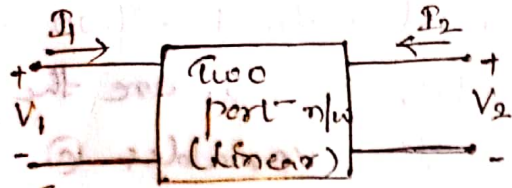- 1) Impedance parameters or Z-parameters. (Open-ckt)
- 2) Admittance parameters or Y-parameters (Short-ckt)
- 3) Hybrid parameters or h-parameters
- 4) Transmission parameters or ABCD parameters or T-parameters.



⇒ Impedance Parameters (or Z-parameters or Open ckt-impedance parameters)



The n/w shown in figure is assumed to be linear & no independent sources

Then using superposition theorem, we can write the I/P & output voltages as the sum of two components, one due to  $I_1$  & other due to  $I_2$ .

Z-parameters eqns are described by,

$$V_1 = Z_{11} I_1 + Z_{12} I_2 \quad \text{--- (1)}$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 \quad \text{--- (2)}$$

In matrix form,

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

The Z-parameters are defined as follows,


$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} \quad \text{Open circuit input impedance parameter.}$$

$$Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} \quad \text{Open circuit- reverse transfer impedance.}$$

$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} \quad \text{Open circuit- forward transfer impedance.}$$

$$Z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0} \quad \text{Open circuit- output impedance parameter}$$

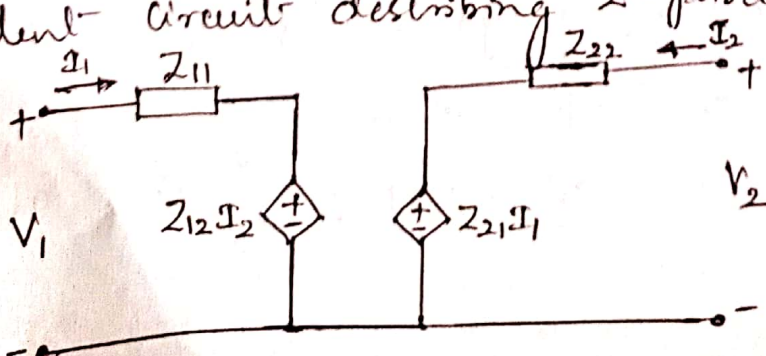Equivalent circuit describing Z-parameters are,




If  $Z_{12} = Z_{21}$  i.e., the transfer impedances are equal then such a n/w is called the "RECIPROCAL NETWORK"

If  $Z_{11} = Z_{22}$  then such a n/w is called a Symmetrical n/w.

⇒ Admittance Parameters or Y-Parameters (or Short-circuit

Admittance parameters)

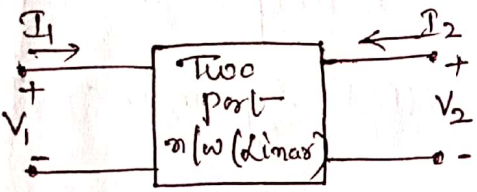

The n/w shown in figure is assumed to be linear & no independent sources.

Then using superposition theorem, we can write the I/p & output currents as the sum of two components, one due to  $V_1$  & other due to  $V_2$ .

Y-parameters eqns are described by,

$$I_1 = Y_{11} V_1 + Y_{12} V_2 \quad \text{--- ①}$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2 \quad \text{--- ②}$$

In matrix form,

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

Y-Parameters are defined as follows,

$Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0}$  Short circuit input admittance parameters.


$Y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0}$  Short circuit reverse transfer admittance parameters.

$Y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0}$  Short circuit forward transfer admittance.

$Y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0}$  Short circuit output admittance parameter.



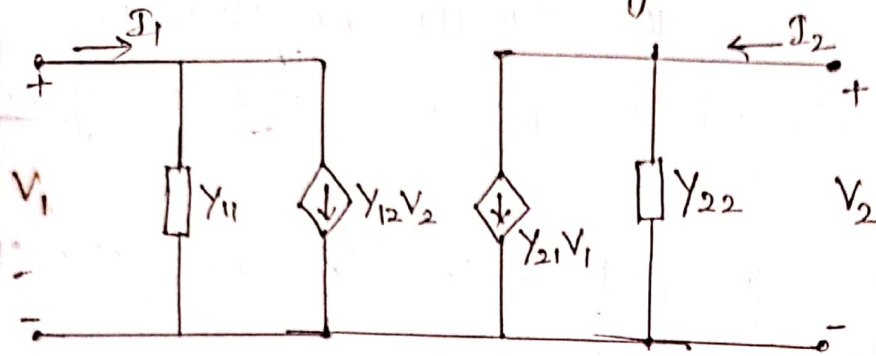Equivalent circuit describing Y-parameters are,




If  $Y_{12} = Y_{21}$  then such a network is called a "reciprocal n/w"

& If  $Y_{11} = Y_{22}$  then such a network is called "symmetrical n/w"

⇒ Hybrid Parameters or h-parameters :-

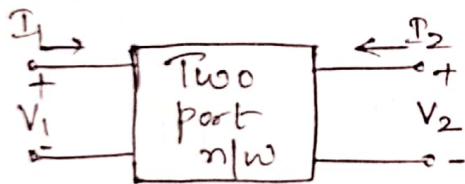Hybrid parameters are very useful in constructing models for transistors. h-parameters completely describes the internal behaviour of transistors (BJT's).



h-parameters eqns are described by,

$$V_1 = h_{11} I_1 + h_{12} V_2 \quad \text{--- (1)}$$

$$I_2 = h_{21} I_1 + h_{22} V_2 \quad \text{--- (2)}$$

In matrix form,

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

h-parameters are defined as follows,


$h_{11} = \frac{V_1}{I_1} \Big|_{V_2=0}$  Short-circuit input impedance parameter.

$h_{12} = \frac{V_1}{V_2} \Big|_{I_1=0}$  known as reverse-voltage gain.

$h_{21} = \frac{I_2}{I_1} \Big|_{V_2=0}$  known as forward-current gain.

$h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0}$  known as Open-circuit Output Admittance parameter.

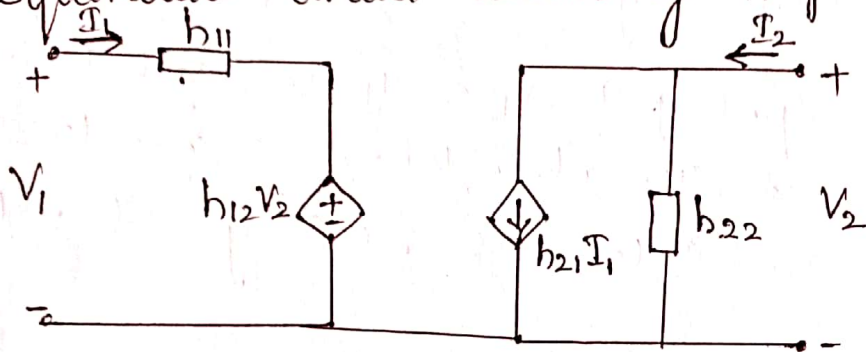
Equivalent circuit describing h-parameters,



If  $h_{12} = -h_{21}$  then the circuit is said to be reciprocal n/w

& If  $h_{11}h_{22} - h_{12}h_{21} = 1$  or  $\Delta h = 1$  then the n/w is said to be Symmetrical n/w.

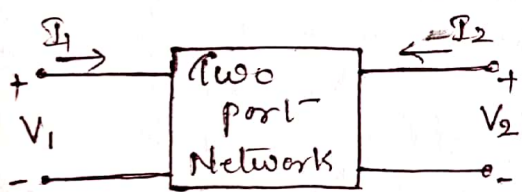⇒ Transmission parameters or ABCD parameters or T-parameters.



The T-parameters eqns are described

by,  $V_1 = AV_2 - BI_2$  — (1)

$I_1 = CV_2 - DI_2$  — (2)

In matrix form,

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

T-parameters are mainly used in analysis of Transmission lines & Cascaded networks. & hence they are called as transmission parameters.

T-parameters are defined as,

$A = \left. \frac{V_1}{V_2} \right|_{I_2=0}$  reverse voltage gain with o/p port open circuited

$B = \left. \frac{V_1}{-I_2} \right|_{V_2=0}$  reverse transfer impedance



$C = \frac{I_1}{V_2} \Big|_{I_2=0}$  reverse transfer admittance.


$D = \frac{I_1}{-I_2} \Big|_{V_2=0}$  reverse current gain with o/p port short cktd.

Quantities at the input port  $V_1$  &  $I_1$  are called as sending end voltages & currents. Where as quantities at the output port are called as receiving end voltages & currents.

T and  $\pi$  network representations of a two port network

Practically the transmission lines, filters & attenuators are represented in the form of equivalent T or  $\pi$  networks. Thus if the Y-parameters are known, an equivalent  $\pi$  n/w can be easily constructed & if the Z-parameters are known an equivalent T n/w can be made.

Equivalent T-network:

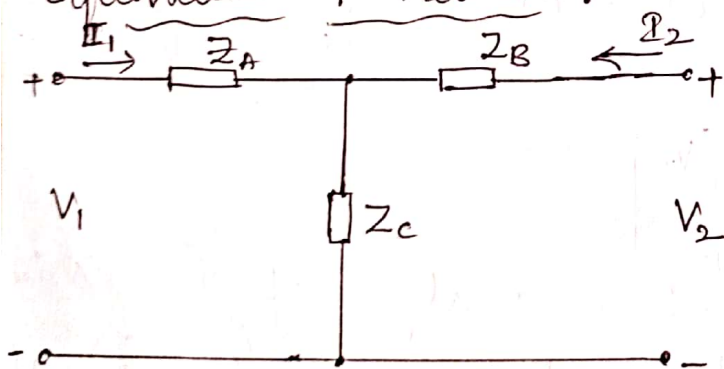

It is required to determine  $Z_A$ ,  $Z_B$  &  $Z_c$  in terms of  $Z_{11}$ ,  $Z_{12}$ ,  $Z_{21}$  &  $Z_{22}$ .

w.k.T  $Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0}$

$\therefore Z_{11} = Z_A + Z_c$

Also  $Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0}$


(When  $I_1=0$  current through  $Z_A$  is zero,  $\therefore$  it can be neglected)

$Z_{22} = Z_B + Z_c$

&  $Z_{12} = Z_{21} = Z_c$

If Z-parameters of the n/w are known, the equivalent T n/w can be found out using the above relations.

Equivalent  $\pi$  network :-

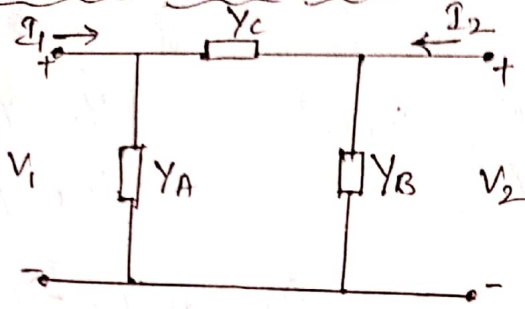

It is required to find  $Y_A, Y_B$  &  $Y_C$  in terms of Y-parameters.

W.K.T  $Y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0}$

When  $V_2=0$ , i.e. o/p port shorted

then  $Y_B$  becomes zero,  $\therefore \boxed{Y_{11} = Y_A + Y_C}$

Similarly  $\boxed{Y_{22} = Y_B + Y_C}$

Also,  $Y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0}$ ,  $Y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0}$

$\boxed{Y_{12} = Y_{21} = -Y_C}$

Thus knowing Y-parameters of a 2-port n/w, elements of  $\pi$  n/w can be found out using the relations derived above.

Relations between two parameters :-

1) Z-parameters in terms of Y-parameters

The equations describing Z-parameters are

$V_1 = Z_{11} I_1 + Z_{12} I_2$  — (1)

$V_2 = Z_{21} I_1 + Z_{22} I_2$  — (2)

The equations describing Y-parameters are

$I_1 = Y_{11} V_1 + Y_{12} V_2$  — (3)

$I_2 = Y_{21} V_1 + Y_{22} V_2$  — (4)

Y-parameters in matrix form,

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

By using Cramer's rule,

$$V_1 = \frac{\Delta_1}{\Delta Y}, \quad V_2 = \frac{\Delta_2}{\Delta Y} \quad \text{where } \Delta Y = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix}$$

$$V_1 = \frac{\begin{vmatrix} I_1 & Y_{12} \\ I_2 & Y_{22} \end{vmatrix}}{\Delta Y}$$

$$\Delta Y = Y_{11} Y_{22} - Y_{12} Y_{21}$$

$$V_1 = \frac{Y_{22} I_1 - Y_{12} I_2}{\Delta Y} = \frac{Y_{22}}{\Delta Y} I_1 - \frac{Y_{12}}{\Delta Y} I_2$$

$$V_1 = \frac{Y_{22}}{\Delta Y} I_1 - \frac{Y_{12}}{\Delta Y} I_2 \quad \text{--- (5)}$$

Comparing equations (5) & (1)

$$\boxed{Z_{11} = \frac{Y_{22}}{\Delta Y}} \quad \boxed{Z_{12} = \frac{-Y_{12}}{\Delta Y}}$$

$$\text{Also, } V_2 = \frac{\begin{vmatrix} Y_{11} & I_1 \\ Y_{21} & I_2 \end{vmatrix}}{\Delta Y}$$

$$V_2 = \frac{Y_{11} I_2 - Y_{21} I_1}{\Delta Y}$$

$$V_2 = \frac{Y_{11}}{\Delta Y} I_2 - \frac{Y_{21}}{\Delta Y} I_1 \quad \text{Rearranging the terms}$$

$$V_2 = -\frac{Y_{21}}{\Delta Y} I_1 + \frac{Y_{11}}{\Delta Y} I_2 \quad \text{--- (6)}$$



Comparing eqn (2) & (6)

$$Z_{21} = -\frac{Y_{21}}{\Delta Y}$$

$$Z_{22} = \frac{Y_{11}}{\Delta Y}$$

$$\therefore \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} \frac{Y_{22}}{\Delta Y} & -\frac{Y_{12}}{\Delta Y} \\ -\frac{Y_{21}}{\Delta Y} & \frac{Y_{11}}{\Delta Y} \end{bmatrix}$$

2) Z-parameters in terms of h-parameters :  
The equations describing Z-parameters are,

$$V_1 = Z_{11} I_1 + Z_{12} I_2 \quad \text{--- (1)}$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 \quad \text{--- (2) } \checkmark$$

The equations describing h-parameters are,

$$V_1 = h_{11} I_1 + h_{12} V_2 \quad \text{--- (3)}$$

$$\checkmark I_2 = h_{21} I_1 + h_{22} V_2 \quad \text{--- (4)}$$

From eqn (4)  $I_2 = h_{21} I_1 + h_{22} V_2$

$$h_{22} V_2 = I_2 - h_{21} I_1$$

$$V_2 = \frac{I_2}{h_{22}} - \frac{h_{21}}{h_{22}} I_1$$

$$\text{or } V_2 = -\frac{h_{21}}{h_{22}} I_1 + \frac{1}{h_{22}} I_2 \quad \text{--- (5)}$$

Comparing (2) & (5)

$$Z_{21} = -\frac{h_{21}}{h_{22}}$$

$$Z_{22} = \frac{1}{h_{22}}$$

Substitute eqn (5) in eqn (3), we get-

$$V_1 = h_{11} I_1 + h_{12} \left[ -\frac{h_{21}}{h_{22}} I_1 + \frac{1}{h_{22}} I_2 \right]$$




$$V_1 = h_{11} I_1 - \frac{h_{12} h_{21}}{h_{22}} I_1 + \frac{h_{12}}{h_{22}} I_2$$

$$V_1 = \left( \frac{h_{11} h_{22} - h_{12} h_{21}}{h_{22}} \right) I_1 + \frac{h_{12}}{h_{22}} I_2$$

$$V_1 = \frac{\Delta h}{h_{22}} I_1 + \frac{h_{12}}{h_{22}} I_2 \quad \text{where } \Delta h = h_{11} h_{22} - h_{12} h_{21} \quad \text{--- (6)}$$

Comparing (1) & (6), we get
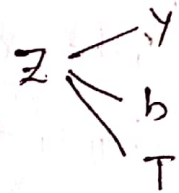
$$\boxed{Z_{11} = \frac{\Delta h}{h_{22}}}, \quad \boxed{Z_{12} = \frac{h_{12}}{h_{22}}}$$



$$\therefore \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} \frac{\Delta h}{h_{22}} & \frac{h_{12}}{h_{22}} \\ -\frac{h_{21}}{h_{22}} & \frac{1}{h_{22}} \end{bmatrix}$$

3) Z-parameters in terms of T-parameters

Z-parameters equations are, T-parameters eqns are.

$$V_1 = Z_{11} I_1 + Z_{12} I_2 \quad \text{--- (1)}$$

$$V_1 = A V_2 - B I_2 \quad \text{--- (3)}$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 \quad \text{--- (2)}$$

$$I_1 = C V_2 - D I_2 \quad \text{--- (4)}$$

from eqn (4),  $I_1 = C V_2 - D I_2$

$$C V_2 = I_1 + D I_2$$

$$V_2 = \frac{1}{C} I_1 + \frac{D}{C} I_2 \quad \text{--- (5)}$$

Comparing this with eqn (2).

$$\boxed{Z_{21} = \frac{1}{C}} \quad \boxed{Z_{22} = \frac{D}{C}}$$

from eqn, (3).

$$V_1 = A \left[ \frac{1}{C} I_1 + \frac{D}{C} I_2 \right] - B I_2$$

$$V_1 = \frac{A}{C} I_1 + \frac{AD}{C} I_2 - B I_2$$

$$V_1 = \frac{A}{C} I_1 + \frac{(AD - BC)}{C} I_2 \quad \text{--- (6)}$$

Comparing (6) with eqn (1), we get,

$$\boxed{Z_{11} = \frac{A}{C}} \quad \boxed{Z_{12} = \frac{AD - BC}{C}}$$

$$\therefore \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} \frac{A}{C} & \frac{AD - BC}{C} \\ \frac{1}{C} & \frac{D}{C} \end{bmatrix}$$

4) Y-parameters in terms of Z-parameters:

The equations describing Y-parameters are,

$$I_1 = Y_{11} V_1 + Y_{12} V_2 \quad \text{--- (1)}$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2 \quad \text{--- (2)}$$

The equations describing Z-parameters are,

$$V_1 = Z_{11} I_1 + Z_{12} I_2 \quad \text{--- (3)}$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 \quad \text{--- (4)}$$

In matrix form, 
$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

But  $I_1 = \frac{\Delta_1}{\Delta Z}$ ,  $I_2 = \frac{\Delta_2}{\Delta Z}$        $\Delta Z = \begin{vmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{vmatrix}$

$$I_1 = \frac{\begin{vmatrix} V_1 & Z_{12} \\ V_2 & Z_{22} \end{vmatrix}}{\Delta Z}$$

$$\Delta Z = Z_{11} Z_{22} - Z_{12} Z_{21}$$

$$I_1 = \frac{V_1 Z_{22} - V_2 Z_{12}}{\Delta Z} = \frac{Z_{22}}{\Delta Z} V_1 - \frac{Z_{12}}{\Delta Z} V_2 \quad \text{--- (5)}$$

Comparing ⑤ with eqn ①, we get-

$$Y_{11} = \frac{Z_{22}}{\Delta Z}$$

$$Y_{12} = -\frac{Z_{12}}{\Delta Z}$$

Similarly,  $I_2 = \frac{\begin{vmatrix} Z_{11} & V_1 \\ Z_{21} & V_2 \end{vmatrix}}{\Delta Z}$

$$I_2 = \frac{Z_{11} V_2 - Z_{21} V_1}{\Delta Z}$$

$$I_2 = \frac{Z_{11}}{\Delta Z} V_2 - \frac{Z_{21}}{\Delta Z} V_1 \quad \text{rearranging the terms}$$

$$\text{or } I_2 = -\frac{Z_{21}}{\Delta Z} V_1 + \frac{Z_{11}}{\Delta Z} V_2 \quad \text{--- ⑥}$$

Comparing ⑥ with eqn ②, we get-

$$Y_{21} = -\frac{Z_{21}}{\Delta Z}$$

$$Y_{22} = \frac{Z_{11}}{\Delta Z}$$

$$\therefore \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} \frac{Z_{22}}{\Delta Z} & -\frac{Z_{12}}{\Delta Z} \\ -\frac{Z_{21}}{\Delta Z} & \frac{Z_{11}}{\Delta Z} \end{bmatrix}$$

5. Y-Parameters in terms of h-parameters:

Y-parameters eqns are

h-parameters eqns are,

$$I_1 = Y_{11} V_1 + Y_{12} V_2 \quad \text{--- ①}$$

$$V_1 = h_{11} I_1 + h_{12} V_2 \quad \text{--- ③}$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2 \quad \text{--- ②}$$

$$I_2 = h_{21} I_1 + h_{22} V_2 \quad \text{--- ④}$$

From ③,  $V_1 = h_{11} I_1 + h_{12} V_2$

$$I_1 = \frac{V_1 - h_{12} V_2}{h_{11}} = \frac{1}{h_{11}} V_1 - \frac{h_{12}}{h_{11}} V_2 \quad \text{--- ⑤}$$



Comparing (5) & (1).

$$Y_{11} = \frac{1}{h_{11}}$$

$$Y_{12} = \frac{-h_{12}}{h_{11}}$$

Substitute (5) in eqn (4)

$$I_2 = h_{21} \left[ \frac{1}{h_{11}} V_1 - \frac{h_{12}}{h_{11}} V_2 \right] + h_{22} V_2$$

$$I_2 = \frac{h_{21}}{h_{11}} V_1 - \frac{h_{21} h_{12}}{h_{11}} V_2 + h_{22} V_2$$

$$I_2 = \frac{h_{21}}{h_{11}} V_1 + V_2 \left[ h_{22} - \frac{h_{21} h_{12}}{h_{11}} \right]$$

$$\begin{matrix} \text{---} \rightarrow & \text{---} \circlearrowleft & \text{---} \swarrow \\ & h_{11} h_{22} - h_{21} h_{12} & \Delta h \end{matrix}$$


$$I_2 = \frac{h_{21}}{h_{11}} V_1 + \frac{\Delta h}{h_{11}} V_2 \quad \text{--- (6)}$$

Comparing (6) & (2), we get.

$$Y_{21} = \frac{h_{21}}{h_{11}}$$

$$Y_{22} = \frac{\Delta h}{h_{11}}$$
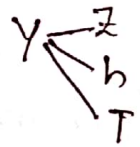
$$\therefore \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} \frac{1}{h_{11}} & \frac{-h_{12}}{h_{11}} \\ \frac{h_{21}}{h_{11}} & \frac{\Delta h}{h_{11}} \end{bmatrix}$$



ex Y-Parameters in terms of T-Parameters:

Y-parameters eqns are,

T-parameters eqns are

$$I_1 = Y_{11} V_1 + Y_{12} V_2 \quad \text{--- (1)}$$

$$V_1 = A V_2 - B I_2 \quad \text{--- (3)}$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2 \quad \text{--- (2)}$$

$$I_1 = C V_2 - D I_2 \quad \text{--- (4)}$$

From (3)  $V_1 = A V_2 - B I_2$

or  $I_2 = \frac{A V_2 - V_1}{B} = -\frac{1}{B} V_1 + \frac{A}{B} V_2 \quad \text{--- (5)}$



Comparing ② & ⑤

$$Y_{21} = -\frac{1}{B}$$

$$Y_{22} = \frac{A}{B}$$

from equation ④,

$$I_1 = CV_2 - D \left[ -\frac{1}{B} V_1 + \frac{A}{B} V_2 \right]$$

$$I_1 = CV_2 + \frac{D}{B} V_1 - \frac{AD}{B} V_2$$

$$I_1 = \left( C - \frac{AD}{B} \right) V_2 + \frac{D}{B} V_1$$

$$\text{or } I_1 = \frac{D}{B} V_1 + \frac{BC - AD}{B} V_2 \quad \text{--- ⑥}$$

Comparing ① & ⑥.

$$Y_{11} = \frac{D}{B}$$

$$Y_{12} = \frac{BC - AD}{B}$$

$$\therefore \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} \frac{D}{B} & \frac{BC - AD}{B} \\ -\frac{1}{B} & \frac{A}{B} \end{bmatrix}$$

\* h-parameters in terms of z-parameters :-

h-parameters eqns are

$$V_1 = h_{11} I_1 + h_{12} V_2 \quad \text{--- ①}$$

$$I_2 = h_{21} I_1 + h_{22} V_2 \quad \text{--- ②}$$

z-parameters eqns are

$$V_1 = Z_{11} I_1 + Z_{12} I_2 \quad \text{--- ③}$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 \quad \text{--- ④}$$

From eqn ④

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

$$I_2 = \frac{V_2 - Z_{21} I_1}{Z_{22}} = \frac{1}{Z_{22}} V_2 - \frac{Z_{21}}{Z_{22}} I_1$$

$$I_2 = -\frac{Z_{21}}{Z_{22}} I_1 + \frac{1}{Z_{22}} V_2 \quad \text{--- (5)}$$

Comparing eqn (2) & (5)

$$h_{21} = -\frac{Z_{21}}{Z_{22}}$$

$$h_{22} = \frac{1}{Z_{22}}$$

From (3),  $V_1 = Z_{11} I_1 + Z_{12} \left[ -\frac{Z_{21}}{Z_{22}} I_1 + \frac{1}{Z_{22}} V_2 \right]$

$$V_1 = Z_{11} I_1 + \frac{Z_{12}}{Z_{22}} V_2 - \frac{Z_{12} Z_{21}}{Z_{22}} I_1$$

$$V_1 = \left[ \frac{Z_{11} Z_{22} - Z_{12} Z_{21}}{Z_{22}} \right] I_1 + \frac{Z_{12}}{Z_{22}} V_2$$

$$V_1 = \frac{\Delta Z}{Z_{22}} I_1 + \frac{Z_{12}}{Z_{22}} V_2 \quad \text{where } \Delta Z = Z_{11} Z_{22} - Z_{12} Z_{21} \quad \text{--- (6)}$$

Comparing (1) & (6), we get,

$$h_{11} = \frac{\Delta Z}{Z_{22}}$$

$$h_{12} = \frac{Z_{12}}{Z_{22}}$$

$$\therefore \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} = \begin{bmatrix} \frac{\Delta Z}{Z_{22}} & \frac{Z_{12}}{Z_{22}} \\ -\frac{Z_{21}}{Z_{22}} & \frac{1}{Z_{22}} \end{bmatrix}$$



8) h-parameters in terms of Y-parameters

h-parameters equations are,

$$V_1 = h_{11} I_1 + h_{12} V_2 \quad \text{--- (1)}$$

$$I_2 = h_{21} I_1 + h_{22} V_2 \quad \text{--- (2)}$$

Y-parameters eqns are

$$I_1 = Y_{11} V_1 + Y_{12} V_2 \quad \text{--- (3)}$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2 \quad \text{--- (4)}$$

From (3)  $I_1 = Y_{11} V_1 + Y_{12} V_2$

$$V_1 = \frac{1}{Y_{11}} I_1 - \frac{Y_{12}}{Y_{11}} V_2 \quad \text{--- (5)}$$

Compare (5) with (1), we get.

$$h_{11} = \frac{1}{Y_{11}}$$

$$h_{12} = -\frac{Y_{12}}{Y_{11}}$$

From (4),

$$I_2 = Y_{21} \left[ \frac{1}{Y_{11}} I_1 - \frac{Y_{12}}{Y_{11}} V_2 \right] + Y_{22} V_2$$

$$I_2 = \frac{Y_{21}}{Y_{11}} I_1 - \frac{Y_{21} Y_{12}}{Y_{11}} V_2 + Y_{22} V_2$$

$$I_2 = \frac{Y_{21}}{Y_{11}} I_1 + V_2 \left[ \frac{Y_{11} Y_{22} - Y_{12} Y_{21}}{Y_{11}} \right] \rightarrow \Delta Y \quad \text{--- (6)}$$

Compare (6) with (2), we get,

$$h_{21} = \frac{Y_{21}}{Y_{11}}$$

$$h_{22} = \frac{\Delta Y}{Y_{11}}$$

$$\therefore \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} = \begin{bmatrix} \frac{1}{Y_{11}} & -\frac{Y_{12}}{Y_{11}} \\ \frac{Y_{21}}{Y_{11}} & \frac{\Delta Y}{Y_{11}} \end{bmatrix}$$

q. h-parameters in terms of T-parameters:

h-parameters eqns are

$$V_1 = h_{11} I_1 + h_{12} V_2 \quad \text{--- (1)}$$

$$I_2 = h_{21} I_1 + h_{22} V_2 \quad \text{--- (2)}$$

T-parameters eqns are,

$$V_1 = A V_2 - B I_2 \quad \text{--- (3)}$$

$$I_1 = C V_2 - D I_2 \quad \text{--- (4)}$$

From (4), 
$$I_2 = \frac{C V_2 - I_1}{D}$$

$$I_2 = \frac{C}{D} V_2 - \frac{1}{D} I_1 \Rightarrow I_2 = -\frac{1}{D} I_1 + \frac{C}{D} V_2 \quad \text{--- (5)}$$



Comparing (5) with eqn (2)

$$h_{21} = \frac{-1}{D}$$

$$h_{22} = \frac{C}{D}$$

From eqn (3),

$$V_1 = AV_2 - B \left[ \frac{-1}{D} I_1 + \frac{C}{D} V_2 \right]$$

$$V_1 = AV_2 + \frac{B}{D} I_1 - \frac{BC}{D} V_2 = \frac{(AD-BC)}{D} V_2 + \frac{B}{D} I_1$$

$$\Rightarrow V_1 = \frac{B}{D} I_1 + \frac{(AD-BC)}{D} V_2 \text{ --- (6)}$$

Comparing (6) with (1)

$$h_{11} = \frac{B}{D}$$

$$h_{12} = \frac{AD-BC}{D}$$

$$\therefore \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} = \begin{bmatrix} \frac{B}{D} & \frac{AD-BC}{D} \\ -\frac{1}{D} & \frac{C}{D} \end{bmatrix}$$

106 T-parameters in terms of Z-parameters

T-parameters eqns are

$$V_1 = AV_2 - BI_2 \text{ --- (1)}$$

$$I_1 = CV_2 - DI_2 \text{ --- (2)}$$

Z-parameters eqns are

$$V_1 = Z_{11} I_1 + Z_{12} I_2 \text{ --- (3)}$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 \text{ --- (4)}$$

From (4),


$$I_1 = \frac{V_2 - Z_{22} I_2}{Z_{21}}$$

$$I_1 = \frac{1}{Z_{21}} V_2 - \frac{Z_{22}}{Z_{21}} I_2 \text{ --- (5)}$$

from (2) & (5)

$$C = \frac{1}{Z_{21}}$$

$$D = \frac{Z_{22}}{Z_{21}}$$

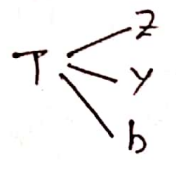



From (3),  $V_1 = Z_{11} \left[ \frac{1}{Z_{21}} V_2 - \frac{Z_{22}}{Z_{21}} I_2 \right] + Z_{12} I_2$

$$V_1 = \frac{Z_{11}}{Z_{21}} V_2 - \frac{Z_{11} Z_{22}}{Z_{21}} I_2 + Z_{12} I_2$$

$$V_1 = \frac{Z_{11}}{Z_{21}} V_2 + I_2 \left[ \frac{Z_{12} Z_{21} - Z_{11} Z_{22}}{Z_{21}} \right]$$

$$V_1 = \frac{Z_{11}}{Z_{21}} V_2 - \frac{(Z_{11} Z_{22} - Z_{12} Z_{21})}{Z_{21}} I_2 \quad \Delta Z$$

$$\therefore V_1 = \frac{Z_{11}}{Z_{21}} V_2 - \frac{\Delta Z}{Z_{21}} I_2 \quad \text{--- (6)}$$

Comparing (6) & (1) we get.

$$A = \frac{Z_{11}}{Z_{21}}$$

$$B = \frac{\Delta Z}{Z_{21}}$$

$$\therefore \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \frac{Z_{11}}{Z_{21}} & \frac{\Delta Z}{Z_{21}} \\ \frac{1}{Z_{21}} & \frac{Z_{22}}{Z_{21}} \end{bmatrix}$$

11) T-parameters in terms Y-parameters

T-parameters eqns are

$$V_1 = A V_2 - B I_2 \quad \text{--- (1)}$$

$$I_1 = C V_2 - D I_2 \quad \text{--- (2)}$$

Y-parameters eqns are,

$$I_1 = Y_{11} V_1 + Y_{12} V_2 \quad \text{--- (3)}$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2 \quad \text{--- (4)}$$

from (4)

$$V_1 = \frac{I_2 - Y_{22} V_2}{Y_{21}}$$

$$V_1 = -\frac{Y_{22}}{Y_{21}} V_2 + \frac{1}{Y_{21}} I_2 \quad \text{--- (5)}$$

Comparing ① & ⑤, we get-

$$A = \frac{-Y_{22}}{Y_{21}}$$

$$B = \frac{-1}{Y_{21}}$$

from ③) 
$$I_1 = Y_{11} \left[ \frac{-Y_{22}}{Y_{21}} V_2 + \frac{1}{Y_{21}} I_2 \right] + Y_{12} V_2$$

$$I_1 = -\frac{Y_{11} Y_{22}}{Y_{21}} V_2 + \frac{Y_{11}}{Y_{21}} I_2 + Y_{12} V_2$$

$$I_1 = -\left( \frac{Y_{11} Y_{22} - Y_{12} Y_{21}}{Y_{21}} \right) V_2 + \frac{Y_{11}}{Y_{21}} I_2$$

or 
$$I_1 = \frac{-\Delta Y}{Y_{21}} V_2 + \frac{Y_{11}}{Y_{21}} I_2 \quad \text{--- ⑥}$$

Comparing ⑥ & ⑦ we get,

$$C = \frac{-\Delta Y}{Y_{21}}$$

$$D = \frac{-Y_{11}}{Y_{21}}$$

$$\therefore \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \frac{-Y_{22}}{Y_{21}} & \frac{-1}{Y_{21}} \\ \frac{-\Delta Y}{Y_{21}} & \frac{-Y_{11}}{Y_{21}} \end{bmatrix}$$

12) T-parameters in terms of h-parameters :-

T-parameters eqns are

h-parameters eqns are

$$V_1 = AV_2 - BI_2 \quad \text{--- ①}$$

$$V_1 = h_{11} I_1 + h_{12} V_2 \quad \text{--- ③}$$

$$I_1 = CV_2 - DI_2 \quad \text{--- ②}$$

$$I_2 = h_{21} I_1 + h_{22} V_2 \quad \text{--- ④}$$

from eqn ④) 
$$I_1 = \frac{I_2 - h_{22} V_2}{h_{21}}$$

$$I_1 = -\frac{h_{22}}{h_{21}} V_2 + \frac{1}{h_{21}} I_2 \quad \text{--- ⑤}$$

Comparing (5) with (2)

$$C = \frac{-h_{22}}{h_{21}}$$

$$D = \frac{-1}{h_{21}}$$

From (3),  $V_1 = h_{11} \left[ \frac{-h_{22}}{h_{21}} V_2 + \frac{1}{h_{21}} I_2 \right] + h_{12} V_2$

$$V_1 = -\frac{h_{11} h_{22}}{h_{21}} V_2 + \frac{h_{11}}{h_{21}} I_2 + h_{12} V_2$$

$$V_1 = -\left[ \frac{h_{11} h_{22} - h_{12} h_{21}}{h_{21}} \right] V_2 + \frac{h_{11}}{h_{21}} I_2$$

$$\left. \begin{aligned} & V_2 \left( h_{12} - \frac{h_{11} h_{22}}{h_{21}} \right) \\ & V_2 \left[ \frac{h_{12} h_{21} - h_{11} h_{22}}{h_{21}} \right] \\ & - \left( \frac{h_{11} h_{22} - h_{12} h_{21}}{h_{21}} \right) \end{aligned} \right\}$$

or  $V_1 = -\frac{\Delta h}{h_{21}} V_2 + \frac{h_{11}}{h_{21}} I_2$  — (6)

Comparing (6) with (1)

$$A = \frac{-\Delta h}{h_{21}}$$

$$B = \frac{-h_{11}}{h_{21}}$$

$$\therefore \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \frac{-\Delta h}{h_{21}} & \frac{-h_{11}}{h_{21}} \\ \frac{-h_{22}}{h_{21}} & \frac{-1}{h_{21}} \end{bmatrix}$$

∴ Symmetry & Reciprocity of two-port n/w.

"Symmetry & reciprocity are the two imp characteristics of two-port n/w. A network is said to be symmetrical if it exhibits the same characteristics when its ports are interchanged."

For 2-parameters, if the impedance measured at one point is equal to the impedance measured @ the other port with remaining port open cktd, the n/w is said



to be symmetrical.

$$Z_{11} = Z_{22}$$

"A n/w is said to be reciprocal, if it exhibits the property that the ratio of source to response @ both ports are same."

For Z-parameters, if  $Z_{12} = Z_{21}$ , the network is said to be reciprocal.

2) Y-parameters :-

Condition of symmetry for y-parameters is  $Y_{12} = Y_{22}$

& Condition of reciprocity is  $Y_{12} = Y_{21}$ .

3) h-parameters :-

For h-parameters, condition of symmetry is  $\Delta h = 1$

$$\text{i.e., } h_{11}h_{22} - h_{12}h_{21} = 1$$

& the condition of reciprocity is  $h_{12} = -h_{21}$

4) ABCD or T-parameters :

T-n/w is said to be symmetrical if  $A = D$  &

it is said to be reciprocal if  $AD - BC = 1$ .



Parameters	Condition of symmetry	Cond <sup>n</sup> of reciprocity
a) Z	$Z_{11} = Z_{22}$	$Z_{12} = Z_{21}$
b) Y	$Y_{11} = Y_{22}$	$Y_{12} = Y_{21}$
c) h	$\Delta h = 1$	$h_{12} = -h_{21}$
d) T	$A = D$	$AD - BC = 1$



## Problems on Two-port network :-

1) Problems on dependent source [ Always use KCL method ]

1) find the y-parameters.

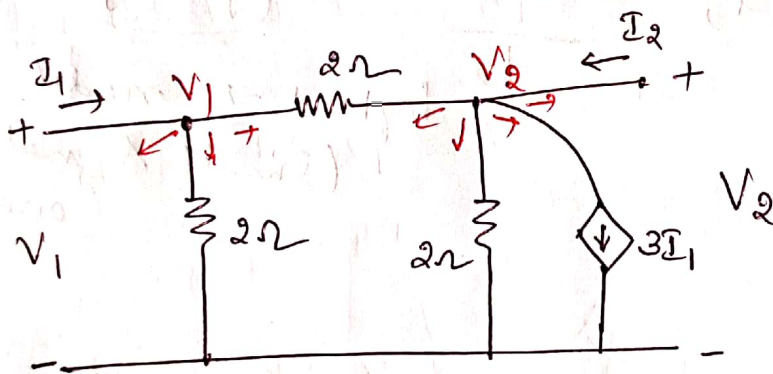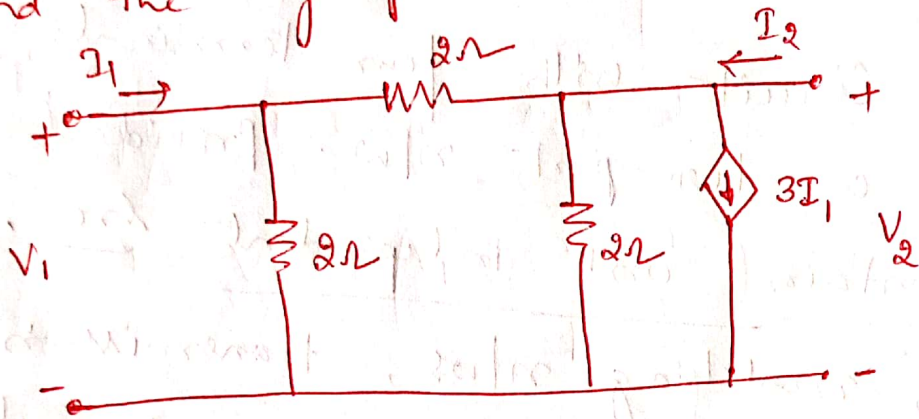

Apply KCL @ node 1

$$-I_1 + \frac{V_1}{2} + \frac{V_1 - V_2}{2} = 0$$

$$-I_1 + \frac{V_1}{2} + \frac{V_1}{2} - \frac{V_2}{2} = 0$$

$$I_1 = V_1 - \frac{V_2}{2} \Rightarrow I_1 = V_1 - 0.5V_2 \quad \text{--- (1)}$$

Comparing with std eqn

$$I_1 = Y_{11} V_1 + Y_{12} V_2$$

$$Y_{11} = 1 \text{ S}$$

$$Y_{12} = -0.5 \text{ S}$$

Apply KCL @ node 2.

$$\frac{V_2 - V_1}{2} + \frac{V_2}{2} + 3I_1 - I_2 = 0$$

$$\frac{V_2}{2} - \frac{V_1}{2} + \frac{V_2}{2} + 3(\underbrace{I_1}_{\text{eqn 1}}) - I_2 = 0$$

$$V_2 - 0.5 V_1 + 3(V_1 - 0.5 V_2) - I_2 = 0$$

$$V_2 - 0.5 V_1 + 3V_1 - 1.5 V_2 - I_2 = 0$$

$$I_2 = 2.5 V_1 - 0.5 V_2 \quad \text{--- (2)}$$

Comparing with std eqn


$$I_2 = Y_{21} V_1 + Y_{22} V_2$$

$$Y_{21} = 2.5 \text{ S}$$

$$Y_{22} = -0.5 \text{ S}$$

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} 1 & -0.5 \\ 2.5 & -0.5 \end{bmatrix} \text{ S}$$

2) Find Y-parameters

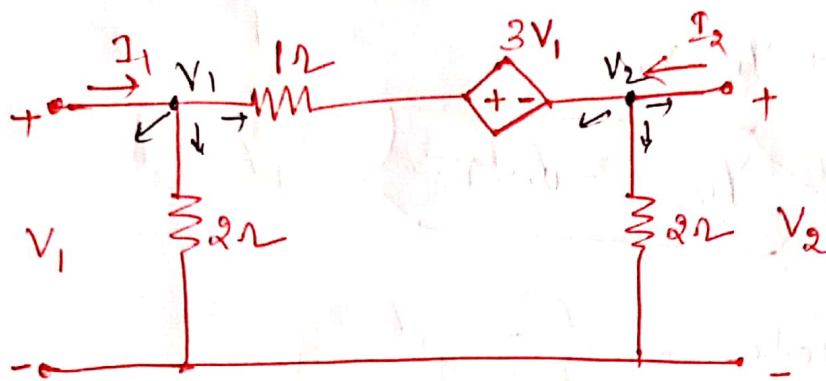

Apply KCL @ node 1.

$$-I_1 + \frac{V_1}{2} + \left( \frac{V_1 - 3V_1 - V_2}{1} \right) = 0$$

$$-I_1 + 0.5V_2 + V_1 - 3V_1 - V_2 = 0$$

$$I_1 = -1.5V_1 - V_2 \quad \text{--- (1)}$$

Compare with std eqn  $I_1 = Y_{11}V_1 + Y_{12}V_2$

$$Y_{11} = -1.5 \text{ S} \quad Y_{12} = -1 \text{ S}$$

Apply KCL @ node 2

$$\frac{V_2}{2} + \frac{V_2 + 3V_1 - V_1}{1} - I_2 = 0$$

$$0.5V_2 + V_2 + 3V_1 - V_1 - I_2 = 0$$

$$I_2 = 2V_1 + 1.5V_2$$



Compare with std eqn



$$I_2 = Y_{21} V_1 + Y_{22} V_2$$

$$Y_{21} = 2 \text{ S}$$

$$Y_{22} = 1.5 \text{ S}$$

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} -1.5 & -1 \\ 2 & 1.5 \end{bmatrix} \text{ S}$$

find 'y' & 'z' parameters

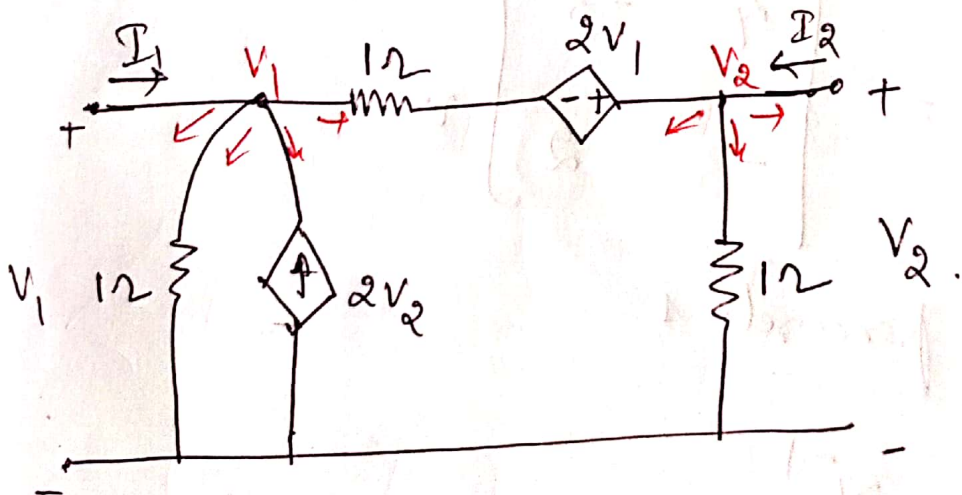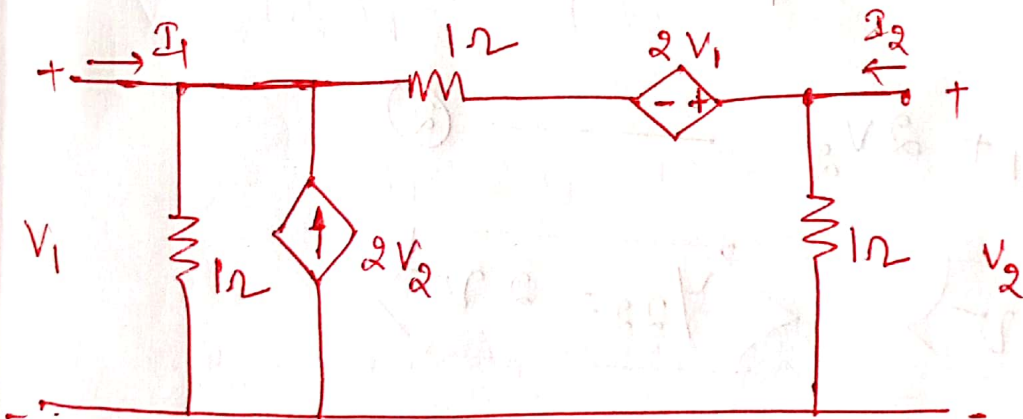



$$-I_1 + \frac{V_1}{1} - 2V_2 + V_1 + \frac{2V_1 - V_2}{1} = 0$$

$$-I_1 + V_1 - 2V_2 + V_1 + 2V_1 - V_2 = 0$$

$$I_1 = 4V_1 - 3V_2 \quad \text{--- (1)}$$

$$Y_{11} = 4 \text{ S}$$

$$Y_{12} = -3 \text{ S}$$

Apply KCL @ node 2.

$$\frac{V_2 - 2V_1 - V_1}{1} + \frac{V_2}{1} - I_2 = 0$$

$$I_2 = -3V_1 + 2V_2 \quad \text{--- (2)}$$

$$Y_{21} = -3 \text{ S}$$

$$Y_{22} = 2 \text{ S}$$

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} 4 & -3 \\ -3 & 2 \end{bmatrix} \mathbf{v}$$

To find z-parameters

$$\mathbf{z} = \mathbf{Y}^{-1}$$

$$\begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} = \begin{bmatrix} \frac{Y_{22}}{\Delta Y} & \frac{-Y_{12}}{\Delta Y} \\ \frac{-Y_{21}}{\Delta Y} & \frac{Y_{11}}{\Delta Y} \end{bmatrix}$$


$$\Delta Y = Y_{11} Y_{22} - Y_{12} Y_{21}$$

$$\Delta Y = 4 \times 2 - (-3)(-3)$$

$$\Delta Y = 8 - 9 = -1$$

$$\begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} = \begin{bmatrix} -2 & -3 \\ -3 & -4 \end{bmatrix}$$

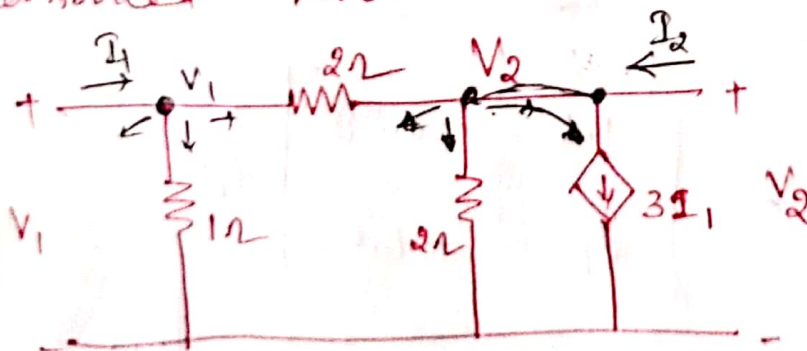4) Find Y & Z parameters for the n/w which contains current controlled src.



KCL @ node 1

$$-I_1 + \frac{V_1}{1} + \frac{V_1 - V_2}{2} = 0$$

$$I_1 = 1.5V_1 - 0.5V_2 \quad \text{--- (1)}$$

or

Comparing

$$Y_{11} = 1.5 \text{ S}$$

$$Y_{12} = -0.5 \text{ S}$$

KCL @ node 2

$$\frac{V_2 - V_1}{2} + \frac{V_2}{2} + 3I_1 - I_2 = 0$$

$$\frac{V_2}{2} - \frac{V_1}{2} + \frac{V_2}{2} + 3I_1 - I_2 = 0$$

$$I_2 = 0.5V_2 - 0.5V_1 + 0.5V_2 + 3I_1$$

$$I_2 = -0.5V_1 + V_2 + 3[1.5V_1 - 0.5V_2] \quad \text{--- from eqn (1)}$$

$$I_2 = 4V_1 - 0.5V_2 \quad \text{--- (2)}$$

or Comparing

$$Y_{21} = 4 \text{ S}$$

$$Y_{22} = -0.5 \text{ S}$$

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} 1.5 & -0.5 \\ 4 & -0.5 \end{bmatrix} \text{ S}$$

$$Z = Y^{-1} = \begin{bmatrix} \frac{Y_{22}}{\Delta Y} & -\frac{Y_{12}}{\Delta Y} \\ -\frac{Y_{21}}{\Delta Y} & \frac{Y_{11}}{\Delta Y} \end{bmatrix} \quad \begin{matrix} \frac{-0.5}{1.25} & \frac{+0.5}{1.25} \\ \frac{-4}{1.25} & \frac{1.5}{1.25} \end{matrix}$$




$$\Delta Y = Y_{11} Y_{22} - Y_{12} Y_{21}$$

$$\Delta Y = 1.25 \text{ v}$$

$$\underline{\underline{Z = \begin{bmatrix} -0.4 & 0.4 \\ -3.2 & 1.2 \end{bmatrix} \Omega}}$$

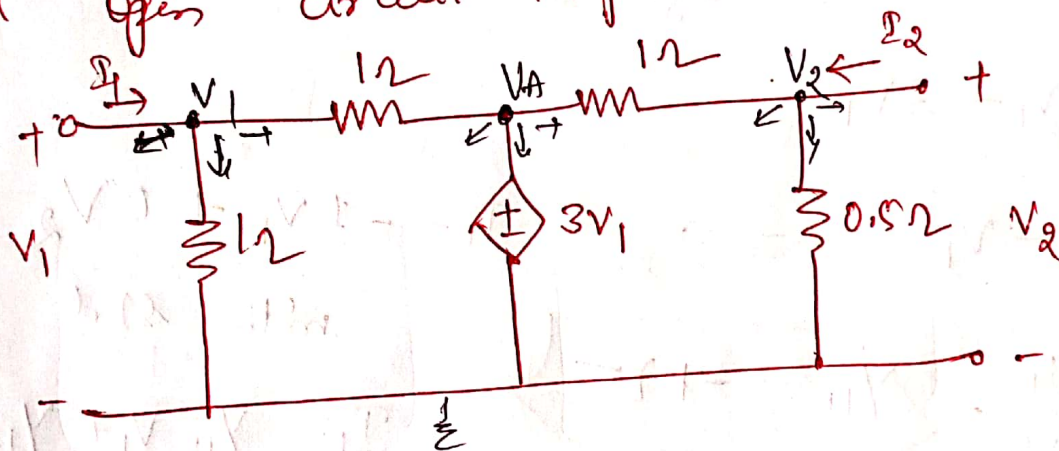5) Find open circuit impedance parameters



KCL @ node 1

$$-I_1 + \frac{V_1}{1} + \frac{V_1 - V_A}{1} = 0$$

$$I_1 = 2V_1 - V_A \quad \text{--- (1)}$$

@ node A

$$V_A = 3V_1 \quad \text{--- (2)}$$

@ node 2

$$\frac{V_2 - V_A}{1} + \frac{V_2}{0.5} - I_2 = 0$$



$$V_2 - 3V_1 + 2V_2 = I_2$$

$$\text{or } I_2 = -3V_1 + 3V_2 \quad \text{--- (2)}$$

on comparing with  $I_2 = Y_{21} V_1 + Y_{22} V_2$

$$Y_{21} = -3 \Omega$$

$$Y_{22} = 3 \Omega$$

Substitute  $V_A$  in eqn (1)

$$I_1 = 2V_1 - 3V_1$$

$$I_1 = -V_1$$



$$I_1 = -1V_1 + 0V_2$$

with std eqn

$$\Rightarrow \frac{I_1}{V_1} = Y_{11} = -1 \Omega$$

$$I_1 = Y_{11} V_1 + Y_{12} V_2$$

$$Y_{12} = 0 \Omega$$


$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} -1 & 0 \\ -3 & 3 \end{bmatrix} \Omega$$

$$Z = Y^{-1} = \begin{bmatrix} \frac{Y_{22}}{\Delta Y} & -\frac{Y_{12}}{\Delta Y} \\ -\frac{Y_{21}}{\Delta Y} & \frac{Y_{11}}{\Delta Y} \end{bmatrix} = \begin{bmatrix} \frac{3}{-3} & 0 \\ \frac{+3}{-3} & \frac{-1}{-3} \end{bmatrix}$$

$$\Delta Y = Y_{11} Y_{22} - Y_{12} Y_{21} = -3$$

$$Z = \begin{bmatrix} -1 & 0 \\ -1 & 1/3 \end{bmatrix} \Omega$$

6) Find Y parameters

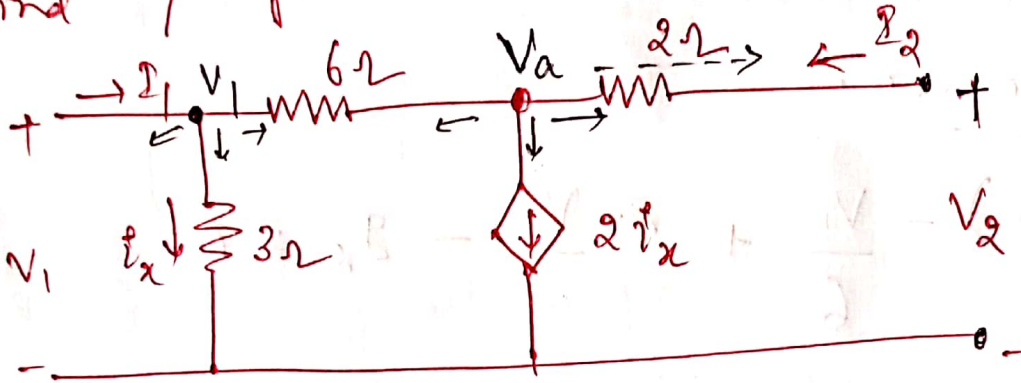

KCL @ node 1

$$-I_1 + \frac{V_1}{3} + \frac{V_1 - V_a}{6} = 0 \quad \text{--- (1)}$$

KCL @ node a

$$\frac{V_a - V_1}{6} + 2I_x - I_2 = 0 \quad \text{--- (2)}$$

from the figure,

$$I_x = \frac{V_1}{3}$$

$$I_2 = \frac{V_2 - V_a}{2}$$

$$2I_2 = V_2 - V_a \Rightarrow V_a = V_2 - 2I_2$$

Eqn (1) becomes

$$-I_1 + \frac{V_1}{3} + \frac{V_1}{6} - \frac{1}{6} [V_2 - 2I_2]$$

$$I_1 = \frac{V_1}{3} + \frac{V_1}{6} - \frac{V_2}{6} + \frac{2I_2}{6}$$

$$I_1 - 0.33I_2 = 0.5V_1 - 0.166V_2 \quad \text{--- } \textcircled{*}$$

eqn ② becomes.

$$\left( \frac{V_2 - 2I_2}{6} \right) - \frac{V_1}{6} + 2 \times \frac{V_1}{3} - I_2 = 0$$

$$\frac{V_2}{6} + \frac{I_2}{3} - \frac{V_1}{6} + \frac{2V_1}{3} - I_2 = 0$$

or  $0.5V_1 + 0.166V_2 = I_2 + \frac{I_2}{3} = 1.33I_2$

or  $I_2 = 0.375V_1 + 0.125V_2$  ---  $\textcircled{3}$

on comparing with  $I_2 = Y_{21}V_1 + Y_{22}V_2$ .

$$Y_{21} = 0.375 \text{ } \Omega^{-1}$$

$$Y_{22} = 0.125 \text{ } \Omega^{-1}$$

from  $\textcircled{*}$

$$I_1 = 0.5V_1 - 0.166V_2 + 0.33(0.375V_1 + 0.125V_2)$$

$$I_1 = 0.5V_1 - 0.166V_2 + 0.12375V_1 + 0.04125V_2$$



$$I_1 = 0.625 V_1 - 0.125 V_2$$


on comparing with

$$I_1 = Y_{11} V_1 + Y_{12} V_2$$

$$Y_{11} = 0.625 \text{ S} \quad Y_{12} = -0.125 \text{ S}$$

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} 0.625 & -0.125 \\ 0.375 & 0.125 \end{bmatrix} \text{ S}$$

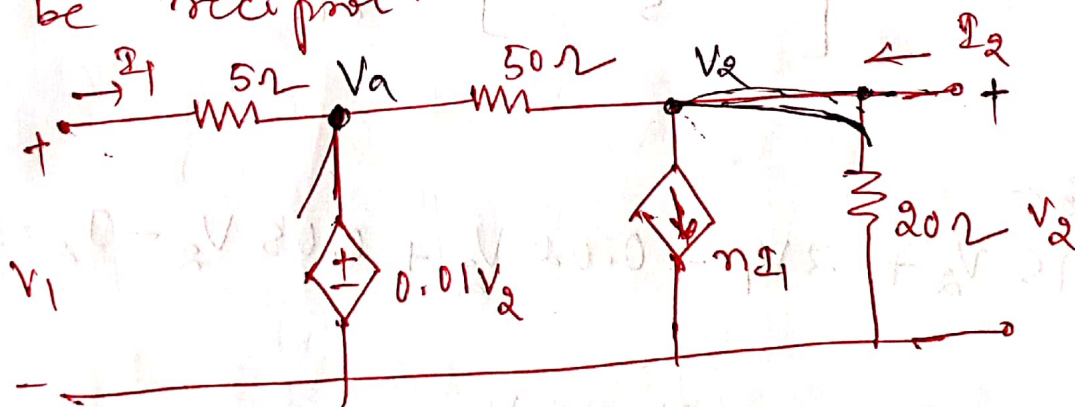4) Find  $Y_{12}$  &  $Y_{21}$  for the n/w for  $n=10$ .  
 what is the value of 'n' for the n/w to be reciprocal.



from the figure

$$V_a = 0.01 V_2 \quad \text{--- (1)}$$

KCL @ node 2.

$$\frac{V_2 - V_a}{50} + n I_1 + \frac{V_2}{20} - I_2 = 0 \quad \text{--- (2)}$$



$$\frac{V_2}{50} - \frac{0.01 V_2}{50} + 10 I_1 + \frac{V_2}{20} - I_2 = 0$$

$$0.0198 V_2 + 10 I_1 + \frac{V_2}{20} - I_2 = 0$$

from the fig

$$I_1 = \frac{V_1 - V_a}{5}$$

$$I_1 = \frac{V_1 - 0.01 V_2}{5} \quad \text{--- (3)}$$

$$0.0198 V_2 + 10 \left[ \frac{V_1 - 0.01 V_2}{5} \right] + \frac{V_2}{20} - I_2 = 0$$

$$0.0198 V_2 + 2 V_1 - 0.02 V_2 + 0.05 V_2 - I_2 = 0$$

$$I_2 = 2 V_1 + 0.0498 V_2$$

Comparing with std eqn.

$$I_2 = Y_{21} V_1 + Y_{22} V_2$$

$$Y_{21} = 2 \text{ V}$$

$$Y_{22} = 0.0498 \text{ V}$$

$$5I_1 = V_1 - 0.01 V_2$$

$$I_1 = 0.2V_1 - 0.002 V_2$$

Compare with  $I_1 = Y_{11} V_1 + Y_{12} V_2$

$$Y_{11} = 0.2 \text{ S}$$

$$Y_{12} = -0.002 \text{ S}$$

Conditions for reciprocal


$$Y_{12} = Y_{21}$$

$$-0.002 = 2$$

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} 0.2 & -0.002 \\ 2 & 0.0498 \end{bmatrix}$$

$$n = 0.001 \quad \text{or} \quad n = 1000$$

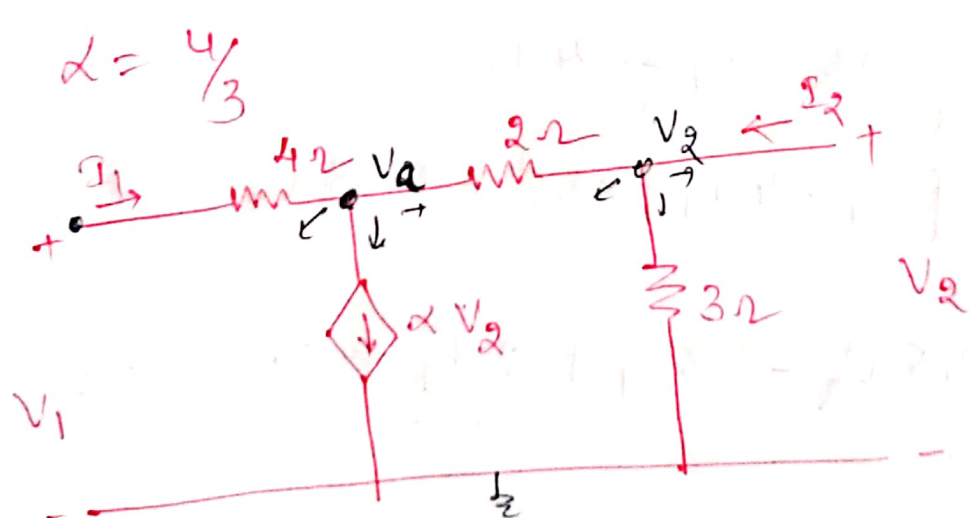\*\*  
8) Find the Z-parameters for the n/w take



KCL @ node a

$$-I_1 + \alpha V_2 + \frac{V_a - V_2}{2} = 0$$

$$I_1 = \frac{4}{3} V_2 + \frac{V_a}{2} - \frac{V_2}{2} \quad \text{--- (1)}$$

KCL @ node 2:

$$\frac{V_2 - V_a}{2} + \frac{V_2}{3} - I_2 = 0$$

$$\frac{V_2}{2} - \frac{V_a}{2} + \frac{V_2}{3} - I_2 = 0 \quad \text{--- (2)}$$

from the  $I_1 = \frac{V_1 - V_a}{4}$

$$4I_1 = V_1 - V_a$$

$$V_a = \underline{V_1} - 4I_1$$

Eqn (2) becomes

$$0.5 V_2 - [V_1 - 4I_1] \times 0.5 + 0.33 V_2 = I_2$$

of  $I_2 = 0.5 V_2 - 0.5 V_1 + \underline{2 I_1} + 0.33 V_2 \quad \text{--- (2)*}$

Eqn (1) becomes.

$$I_1 = 1.33 V_2 + \frac{(V_1 - 4 I_1)}{2} - 0.5 V_2$$

$$I_1 = 1.33 V_2 + 0.5 V_1 - 2 I_1 - 0.5 V_2$$

$$3 I_1 = 0.5 V_1 + 0.83 V_2$$

$$\text{or } I_1 = \underline{0.166 V_1 + 0.2766 V_2} \quad \text{--- (3)}$$

Comparing with  $I_1 = Y_{11} V_1 + Y_{12} V_2$

$$Y_{11} = 0.166 \text{ } \Omega^{-1}$$

$$Y_{12} = 0.2766 \text{ } \Omega^{-1}$$

Similarly (3) in (2)\*

$$I_2 = 0.5 V_2 - 0.5 V_1 + 2 [0.166 V_1 + 0.2766 V_2] + 0.33 V_2$$

$$I_2 = -0.168 V_1 + 1.386 V_2$$

Comparing with  $I_2 = Y_{21} V_1 + Y_{22} V_2$

$$Y_{21} = -0.168 \text{ } \Omega^{-1}$$

$$Y_{22} = 1.386 \text{ } \Omega^{-1}$$



$$Z = Y^{-1} = \begin{bmatrix} \frac{Y_{22}}{\Delta Y} & -\frac{Y_{12}}{\Delta Y} \\ -\frac{Y_{21}}{\Delta Y} & \frac{Y_{11}}{\Delta Y} \end{bmatrix}$$


$$\Delta Y = Y_{11} Y_{22} - Y_{12} Y_{21}$$

$$\Delta Y = 0.276$$

$$\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} \frac{1.386}{0.276} & -\frac{0.2766}{0.276} \\ \frac{-(-0.168)}{0.276} & \frac{0.166}{0.276} \end{bmatrix}$$

$$\underline{\underline{[Z] = \begin{bmatrix} 5.02 & -1 \\ 0.608 & 0.6 \end{bmatrix}}}$$

Q) find Y parameters

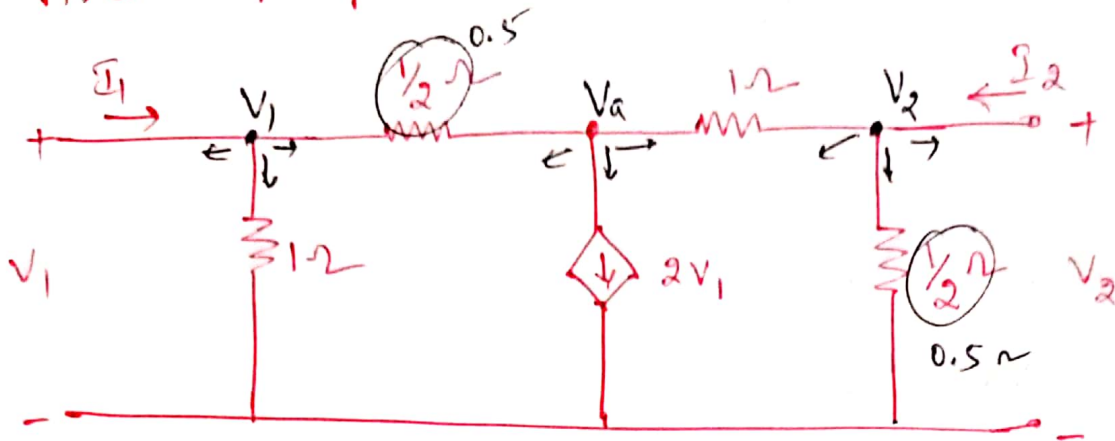

KCL @ node 1

$$-I_1 + \frac{V_1}{1} + \frac{V_1 - V_a}{0.5} = 0$$

$$-I_1 + V_1 + \frac{V_1}{0.5} - \frac{V_a}{0.5} = 0 \quad \text{--- (i)}$$

(a) node a:

$$\frac{V_a - V_1}{0.5} + 2V_1 + \frac{V_a - V_2}{1} = 0$$

$$\frac{V_a}{0.5} - \cancel{\frac{V_1}{0.5}} + \cancel{2V_1} + V_a - V_2 = 0$$

$$2V_a + \cancel{2V_1} + V_a - V_2 = 0 \quad \text{--- (ii)}$$

(a) node 2

$$\frac{V_2 - V_a}{1} + \frac{V_2}{0.5} - I_2 = 0$$

$$V_2 - V_a + 2V_2 - I_2 = 0 \quad \text{--- (2)}$$

from (2)

$$3V_a = V_2$$

$$V_a = \frac{V_2}{3}$$

$\therefore$  eqn (1) becomes.

$$-I_1 + V_1 + \frac{V_1}{0.5} - \frac{V_2}{3 \times 0.5} = 0$$

$$\text{or } I_1 = 3V_1 - 0.666 V_2$$

$$\therefore Y_{11} = 3 \text{ } \Omega \quad Y_{12} = -0.66 \text{ } \Omega$$

eqn (3)

becomes, 
$$V_2 - \frac{V_2}{3} + \frac{V_2}{0.5} = I_2$$


$$\text{or } I_2 = 2.667 V_2$$

$$\therefore I_2 = 0 V_1 + 2.667 V_2$$

$$Y_{21} = 0 \text{ } \Omega \quad Y_{22} = 2.667 \text{ } \Omega$$

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} 3 & -0.66 \\ 0 & 2.667 \end{bmatrix} \text{ S}$$

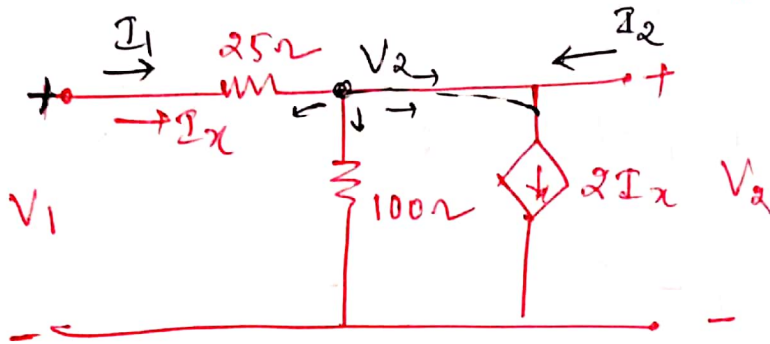10) Find the Y Parameters of the n/w shown



→ KCL @ node 2 :

$$-I_1 + \frac{V_2}{100} + 2I_x - I_2 = 0$$

from the fig.

$$I_x = I_1 \quad \text{--- (1)}$$

$$-I_1 + \frac{V_2}{100} + 2I_1 - I_2 = 0 \quad \text{--- (2)}$$

from the figure,

$$I_1 = \frac{V_1 - V_2}{25}$$

$$I_1 = 0.04 V_1 - 0.04 V_2 \quad \text{--- (3)}$$

Compare with std eqn

$$Y_{11} = 0.04 \text{ S}$$

$$Y_{12} = -0.04 \text{ S}$$



from eq (2),

$$I_1 + 0.01 V_2 - I_2 = 0$$

$$I_2 = I_1 + 0.01 V_2$$

Substituting (3) in the above eqn

$$I_2 = [0.04 V_1 - 0.04 V_2] + 0.01 V_2$$


$$I_2 = 0.04 V_1 - 0.03 V_2 \quad \text{--- (4)}$$

Comparing with std eqn

$$Y_{21} = 0.04 \text{ S} \quad Y_{22} = -0.03 \text{ S}$$

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} 0.04 & -0.04 \\ 0.04 & -0.03 \end{bmatrix} \text{ S}$$

11) Find the T-parameters for the n/w.

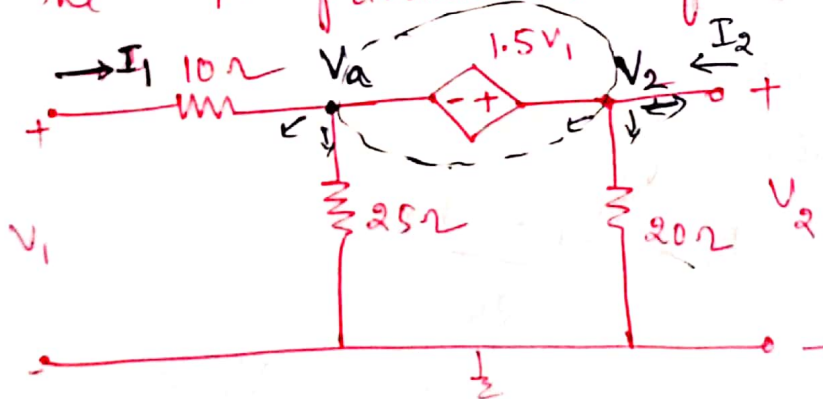

Since  $1.5V_1$  is b/w  $V_a$  &  $V_2$  it leads to super node.

$$V_2 - V_a = 1.5V_1 \quad \text{--- (1)}$$

Applying KCL to super node.

$$-I_1 + \frac{V_1}{25} + \frac{V_2}{20} - I_2 = 0 \quad \text{--- (2)}$$

from the fig.

$$I_1 = \frac{V_1 - V_a}{10}$$

$$10I_1 = V_1 - V_a$$

$$V_a = V_1 - 10I_1$$

Eqn (1) becomes.

$$V_2 - [V_1 - 10I_1] - 1.5V_1 = 0$$

$$V_2 - V_1 + 10I_1 - 1.5V_1 = 0$$

$$10I_1 = 2.5V_1 - V_2$$

$$\text{or } I_1 = 0.25V_1 - 0.1V_2$$

Compare with std eqn.

$$Y_{11} = 0.25 \text{ S}$$

$$Y_{12} = -0.1 \text{ S}$$

Eqn (2) is now.

$$I_2 = -[0.25V_1 - 0.1V_2] + 0.04[V_1 - 10I_1] + 0.05V_2$$

$$I_2 = -0.25V_1 + 0.1V_2 + 0.04V_1 - 0.4I_1 + 0.05V_2$$

$$I_2 = \underbrace{-0.25V_1} + \underbrace{0.1V_2} + \underbrace{0.04V_1} - 0.4 [0.25V_1 - 0.1V_2] + \underbrace{0.05V_2}$$

$$I_2 = -0.21V_1 + 0.15V_2 - 0.1V_1 + 0.04V_2$$

$$I_2 = -0.31V_1 + 0.19V_2$$

Comparing with std eqn.

$$Y_{21} = -0.31 \text{ S}$$

$$Y_{22} = 0.19 \text{ S}$$

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} 0.25 & -0.1 \\ -0.31 & 0.19 \end{bmatrix} \text{ S}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 0.633 & 3.23 \\ 0.053 & 0.05 \end{bmatrix}$$

$$V_1 = AV_2 - BI_2 \quad \text{--- (1)}$$

$$I_1 = Y_{11}V_1 + Y_{12}V_2 \quad \text{--- (2)}$$

$$I_1 = CV_2 - DI_2 \quad \text{--- (3)}$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2 \quad \text{--- (4)}$$

$$Y_{21}V_1 = I_2 - Y_{22}V_2$$

$$V_1 = \frac{Y_{22}}{Y_{21}}V_2 + \frac{1}{Y_{21}}I_2 \quad \text{--- (5)}$$

$$A = \frac{-Y_{22}}{Y_{21}} = \frac{-0.19}{-0.31} = 0.633$$

$$B = -\frac{1}{Y_{21}} = \frac{-1}{-0.31} = 3.23$$

eqn ③ becomes.

$$I_1 = Y_{11} \left[ \frac{-Y_{22}}{Y_{21}} V_2 + \frac{1}{Y_{21}} I_2 \right] + Y_{12} V_2$$

$$I_1 = -\frac{Y_{11} Y_{22}}{Y_{21}} V_2 + \frac{Y_{11}}{Y_{21}} I_2 + Y_{12} V_2$$

$$I_1 = \frac{(-Y_{11} Y_{22} + Y_{21} Y_{12})}{Y_{21}} V_2 + \frac{Y_{11}}{Y_{21}} I_2$$

$$I_1 = \frac{-\Delta Y}{Y_{21}} V_2 + \frac{Y_{11}}{Y_{21}} I_2$$

$$C = \frac{-\Delta Y}{Y_{21}} \quad D = -\frac{Y_{11}}{Y_{21}} = \frac{-0.25}{-0.31} = 0.05$$

$$\Delta Y = 0.25 \times 0.19 - [(-0.1)(-0.31)] = 0.0165$$

$$C = \underline{\underline{0.053}}$$



12) The eqns that describes behaviour of n/w are

$$11 I_1 + 4 I_2 = 5V_1$$

$$4 I_1 + 6 I_2 = 5V_2 \quad \text{Find } Y \text{ parameters.}$$

Given  $5V_1 = 11 I_1 + 4 I_2$

$$V_1 = \frac{11}{5} I_1 + \frac{4}{5} I_2$$

$$V_1 = 2.2 I_1 + 0.8 I_2 \quad \text{--- (1)}$$

$$5V_2 = 4 I_1 + 6 I_2$$

$$V_2 = \frac{4}{5} I_1 + \frac{6}{5} I_2$$

$$V_2 = 0.8 I_1 + 1.2 I_2 \quad \text{--- (2)}$$

WKT  $V_1 = Z_{11} I_1 + Z_{12} I_2 \quad \text{--- (3)}$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 \quad \text{--- (4)}$$

From (1) & (3)

$$Z_{11} = 2.2 \Omega \quad \& \quad Z_{12} = 0.8 \Omega$$

From (2) & (4)

$$Z_{21} = 0.8 \Omega \quad \& \quad Z_{22} = 1.2 \Omega$$

$$\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} 2.2 & 0.8 \\ 0.8 & 1.2 \end{bmatrix}$$

13) The impedance parameters of the T n/w are given by  $\begin{bmatrix} 50 & 25 \\ 25 & 100 \end{bmatrix}$ . Find the parameters of the T-n/w.

$$\text{Given } \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} 50 & 25 \\ 25 & 100 \end{bmatrix}$$

WKT  $Z_{11} = Z_A + Z_C$

$$Z_{22} = Z_B + Z_C$$

&  $Z_{12} = Z_{21} = Z_C$

$$\therefore Z_C = 25 \Omega$$

$$\therefore Z_A = Z_{11} - Z_C$$


$$Z_A = 50 - 25$$

$$Z_A = 25 \Omega$$


$$Z_B = Z_{22} - Z_C$$

$$Z_B = 100 - 25$$

$$Z_B = 75 \Omega$$

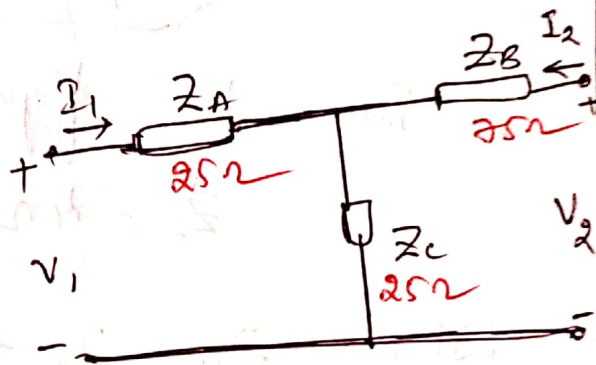

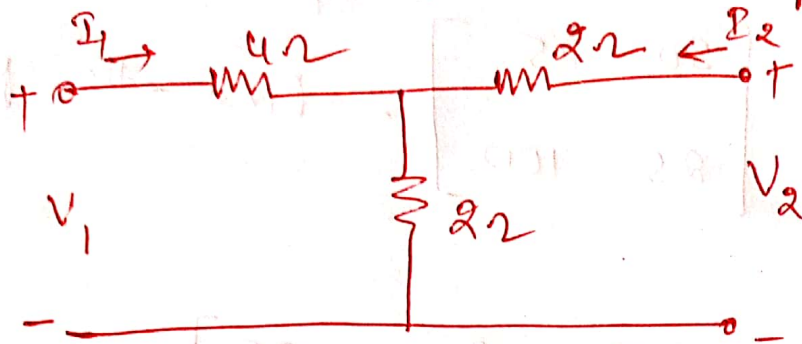14) Determine Y parameters of the T-network



For T-network first find  $Z$  & then

$$Y = Z^{-1}$$

from the figure

$$Z_A = 4\Omega, \quad Z_B = 2\Omega, \quad Z_C = 2\Omega$$

WKT

$$Z_{11} = Z_A + Z_C \quad Z_{12} = Z_{21} = Z_C$$

$$Z_{11} = 6\Omega$$

$$Z_{12} = Z_{21} = 2\Omega$$

$$\& \quad Z_{22} = Z_B + Z_C$$

$$Z_{22} = 4\Omega$$

$$\therefore \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} 6 & 2 \\ 2 & 4 \end{bmatrix} \Omega$$


$$Y = Z^{-1} = \begin{bmatrix} \frac{Z_{22}}{\Delta Z} & \frac{-Z_{12}}{\Delta Z} \\ \frac{-Z_{21}}{\Delta Z} & \frac{Z_{11}}{\Delta Z} \end{bmatrix}$$



$$\Delta Z = 24 - 4 = 20$$

$$\therefore \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} 0.2 & -0.1 \\ -0.1 & 0.3 \end{bmatrix} \underline{v}$$

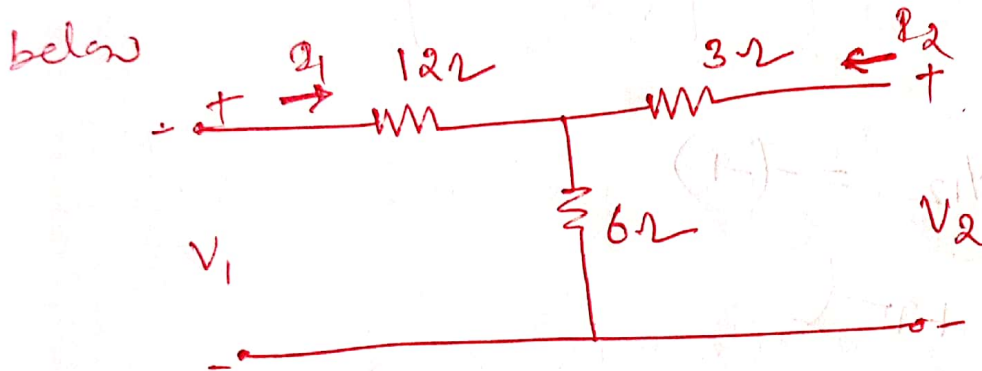15) Find the 2-parameters of the n/w shown



$$\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} 18 & 6 \\ 6 & 9 \end{bmatrix} \underline{v}$$

16) The port current of a two-port n/w are given by

$$I_1 = 2.5V_1 - V_2$$

$$I_2 = -V_1 + 5V_2$$

Find equivalent  $\pi$  n/w.

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} 2.5 & -1 \\ -1 & 5 \end{bmatrix} \underline{v}$$



The admittances of  $\pi$  n/w are,  $Y_A$ ,  $Y_B$  &  $Y_C$

$$Y_A = Y_{11} + Y_{12}$$

$$Y_{11} = Y_A + Y_C$$

$$Y_C = 2.5 - 1 = 1.5 \text{ S}$$

$$Y_{22} = Y_B + Y_C$$

$$Y_A = 1.5 \text{ S}$$

$$Y_{12} = Y_{21} = -Y_C$$

$$Y_B = Y$$

$$Y_C = -Y_{12} = -(-1)$$


$$Y_C = 1 \text{ S}$$

$$Y_A = Y_{11} - Y_C$$

$$Y_C = 2.5 - 1 = 1.5 \text{ S}$$

$$Y_B = Y_{22} - Y_C$$

$$Y_B = 5 - 1 = 4 \text{ S}$$

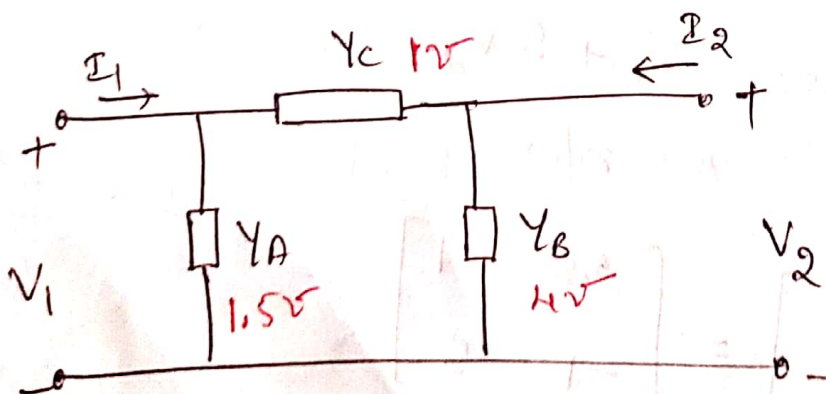

17) The Z-parameters of a two port n/w are

$$Z_{11} = 20\Omega, Z_{12} = 10\Omega, Z_{21} = 10\Omega \text{ \& } Z_{22} = 10\Omega.$$

find its Y & ABCD parameters.

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} \frac{Z_{22}}{\Delta Z} & -\frac{Z_{12}}{\Delta Z} \\ -\frac{Z_{21}}{\Delta Z} & \frac{Z_{11}}{\Delta Z} \end{bmatrix}$$


$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \frac{Z_{11}}{Z_{21}} & \frac{\Delta Z}{Z_{21}} \\ \frac{1}{Z_{21}} & \frac{Z_{22}}{Z_{21}} \end{bmatrix}$$

$$\Delta Z = Z_{11}Z_{22} - Z_{12}Z_{21}$$

Shun:

18) Find Z-parameters of the n/w shown.

June/July-19

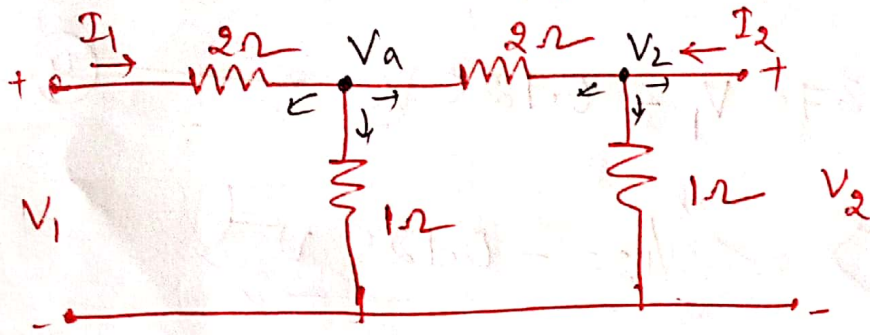

→ Apply KCL @ node a

$$\frac{V_a}{1} + \frac{V_a - V_2}{2} - I_1 = 0$$

$$I_1 = 1.5V_a - 0.5V_2 \quad \text{--- (1)}$$

→ KCL @ node 2

$$\frac{V_2 - V_a}{2} + \frac{V_2}{1} - I_2 = 0$$

$$I_2 = 1.5V_2 - 0.5V_a \quad \text{--- (2)}$$

from the figure.

$$I_1 = \frac{V_1 - V_a}{2} \Rightarrow 2I_1 = V_1 - V_a$$

$$\text{* or } V_a = V_1 - 2I_1 \quad \text{--- (3)}$$

Substituting (3) in (1)

$$I_1 = 1.5[V_1 - 2I_1] - 0.5V_2$$

$$I_1 = 1.5V_1 - 3I_1 - 0.5V_2$$



$$4I_1 = 1.5V_1 - 0.5V_2$$

$$I_1 = 0.375V_1 - 0.125V_2$$

(4)

$$Y_{11} = 0.375 \text{ S}$$

$$Y_{12} = -0.125 \text{ S}$$

Substituting (3) in (2)

$$I_2 = 1.5V_2 - 0.5[V_1 - 2I_1]$$

$$I_2 = 1.5V_2 - 0.5V_1 + I_1$$

$$I_2 = 1.5V_2 - 0.5V_1 + 0.375V_1 - 0.125V_2$$

$$I_2 = -0.125V_1 + 1.375V_2$$

$$Y_{21} = -0.125 \text{ S}$$

$$Y_{22} = 1.375 \text{ S}$$

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} 0.375 & -0.125 \\ -0.125 & 1.375 \end{bmatrix} \text{ S}$$

$$Z_{22} = Y^{-1} = \begin{bmatrix} \frac{Y_{22}}{\Delta Y} & -\frac{Y_{12}}{\Delta Y} \\ -\frac{Y_{21}}{\Delta Y} & \frac{Y_{11}}{\Delta Y} \end{bmatrix}$$




$$\Delta Y = Y_{11} Y_{22} - Y_{12} Y_{21}$$

$$= 0.375 \times 1.375 - (-0.125)(-0.125)$$

$$\rightarrow = 0.51 - 0.015 = \cancel{0.225} \quad 0.5$$

$$Z = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} 2.75 & 0.25 \\ 0.25 & 0.75 \end{bmatrix} \Omega$$

19) Determine  $Y$  &  $Z$  parameters.

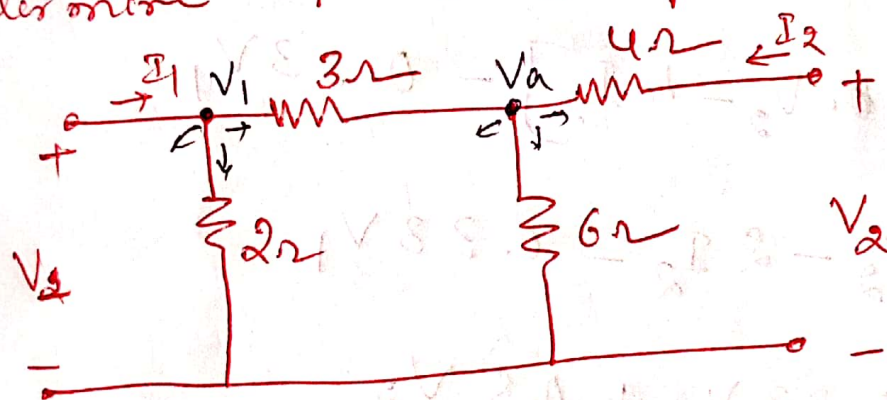

KCL @ node  $V_1$

$$-I_1 + \frac{V_1}{2} + \frac{V_1 - V_a}{3} = 0$$

$$0.5V_1 + 0.33V_1 - 0.33V_a - I_1 = 0$$

$$\therefore I_1 = 0.83V_1 - 0.33V_a \quad \text{--- (1)}$$

KCL @ node  $V_a$

$$\frac{V_a - V_1}{3} + \frac{V_a}{6} - I_2 = 0$$

$$\text{or } I_2 = 0.5 V_a - 0.33 V_1 \quad \text{--- (2)}$$

from the fig.

$$I_2 = \frac{V_2 - V_a}{4}$$

$$4I_2 = V_2 - V_a$$

$$\text{or } V_a = V_2 - 4I_2 \quad \text{--- (3)}$$

Substituting (3) in (2)

$$I_2 = 0.5 [0. V_2 - 4I_2] - 0.33 V_1$$

$$I_2 = 0.5 V_2 - 2I_2 - 0.33 V_1$$

$$3I_2 = -0.33 V_1 + 0.5 V_2$$

$$I_2 = -0.11 V_1 + 0.166 V_2 \quad \text{--- *}$$

Comparing with std eqn  $V_{21} = -0.11 V$

&  $V_{22} = 0.166 V$

Now (3) in (1) becomes.

$$I_1 = 0.83 V_1 - 0.33 [V_2 - 4I_2]$$



$$I_1 = 0.83 V_1 - 0.33 V_2 + 1.32 I_2$$

$$I_1 = 0.83 V_1 - 0.33 V_2 + 1.32 \left[ -0.11 V_1 + 0.166 V_2 \right]$$

I<sub>2</sub> eqn (\*)

$$I_1 = 0.83 V_1 - 0.33 V_2 - 0.145 V_1 + 0.219 V_2$$

$$I_1 = 0.685 V_1 - 0.111 V_2$$

Compare with std eqn  $I_1 = Y_{11} V_1 + Y_{12} V_2$

$$Y_{11} = 0.685 \Omega \quad Y_{12} = -0.111 \Omega$$

$$\therefore \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} 0.685 & -0.111 \\ -0.111 & 0.166 \end{bmatrix} \Omega$$


$$Z = Y^{-1} = \begin{bmatrix} \frac{Y_{22}}{\Delta Y} & -\frac{Y_{12}}{\Delta Y} \\ -\frac{Y_{21}}{\Delta Y} & \frac{Y_{11}}{\Delta Y} \end{bmatrix}$$

$$\Delta Y = Y_{11} Y_{22} - Y_{12} Y_{21} = 0.113 - [0.0123]$$

$$\Delta Y = \underline{\underline{0.1}}$$

$$\therefore \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} 1.662 & 1.1 \\ 1.1 & 6.8 \end{bmatrix} \Omega$$

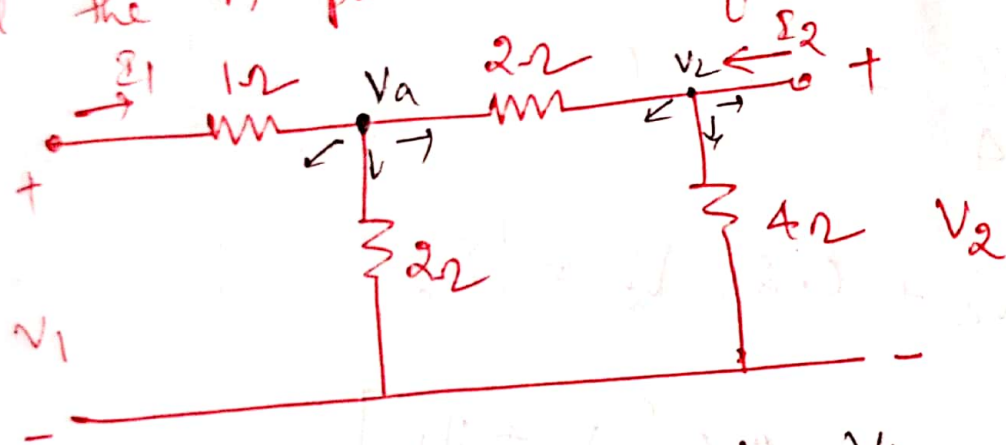28) Find the h-parameters of the ckt shown. Sharma  
Nov-2020 (ACU)



KCL method

Apply KCL at node  $V_a$

~~$$-I_1 + \frac{V_a}{2} + \frac{V_a - V_2}{2} = 0$$~~

$$\frac{V_a - V_2}{2} + \frac{V_a}{2} - I_1 = 0$$

$$I_1 = V_a - \frac{V_2}{2} \quad \text{--- (1)}$$

from the big  $I_1 = \frac{V_1 - V_a}{1}$

$$V_a = V_1 - I_1 \quad \text{--- (2)}$$



Assume (2) in (1)

$$I_1 = V_1 - I_1 - \frac{V_2}{2}$$

$$2I_1 = V_1 - \frac{V_2}{2}$$

~~$$I_1 = 0.5V_1 - 0.25V_2$$~~

$$I_1 = 0.5V_1 - 0.25V_2 \quad \text{--- (3)}$$

$$Y_{11} = 0.5 \text{ S} \quad Y_{12} = -0.25 \text{ S}$$

KCL @ node 2

$$\frac{V_2 - V_a}{2} + \frac{V_2}{4} - I_2 = 0$$

$$0.5V_2 - 0.5V_a + 0.25V_2 = I_2$$

$$\text{or } I_2 = 0.75V_2 - 0.5[V_1 - I_1]$$

$$I_2 = 0.75V_2 - 0.5V_1 + 0.5 \underbrace{[0.5V_1 - 0.25V_2]}_{\text{eqn (3) } I_1}$$

$$I_2 = 0.75V_2 - 0.5V_1 + 0.25V_1 - 0.125V_2$$

$$I_2 = -0.25V_1 + 0.625V_2 \quad \text{--- (4)}$$

$$Y_{21} = -0.25 \text{ v}$$

$$Y_{22} = 0.625 \text{ v}$$

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} 0.5 & -0.25 \\ -0.25 & 0.625 \end{bmatrix} \text{ v}$$

WKT, 
$$\begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} = \begin{bmatrix} \frac{1}{Y_{11}} & -\frac{Y_{12}}{Y_{11}} \\ \frac{Y_{21}}{Y_{11}} & \frac{\Delta Y}{Y_{11}} \end{bmatrix}$$


$$\Delta Y = Y_{11} Y_{22} - Y_{12} Y_{21}$$

$$\Delta Y = 0.25$$

$$\begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} = \begin{bmatrix} \frac{1}{0.5} & -\frac{(-0.25)}{0.5} \\ \frac{-0.25}{0.5} & \frac{0.25}{0.5} \end{bmatrix}$$

$$\begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} = \begin{bmatrix} 2 & 0.5 \\ -0.5 & 0.5 \end{bmatrix}$$

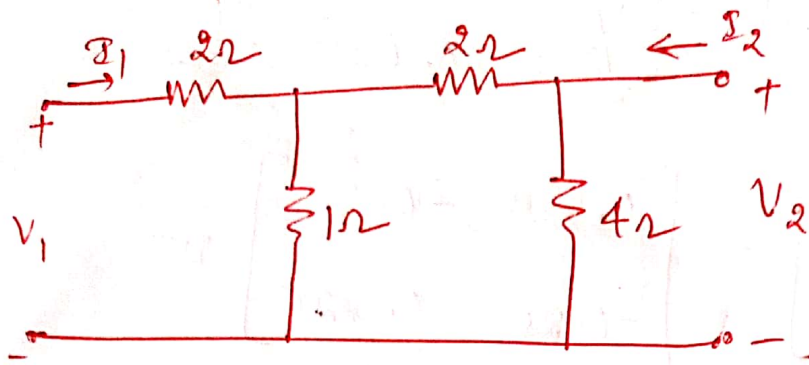2) S.T the n/w is reciprocal but not symmetrical by finding h parameters.



$$\text{Ans :- } \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} = \begin{bmatrix} 2.66 & 0.33 \\ -0.33 & 0.59 \end{bmatrix}$$

Since  $h_{12} = -h_{21}$

$$0.33 = -(-0.33)$$

$$0.33 = 0.33$$

$\therefore$  the n/w is reciprocal.



$$\Delta h = \begin{vmatrix} 2.66 & 0.33 \\ -0.33 & 0.59 \end{vmatrix}$$

$$\Delta h = 1.67$$

Since  $\Delta h \neq 1$   $\therefore$  the n/w is not symmetrical.

method.

22) Find the Y-parameters

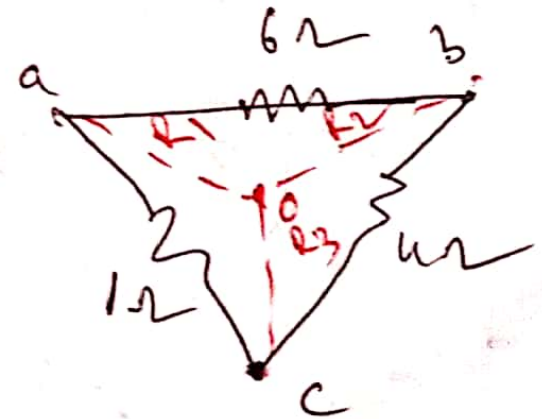
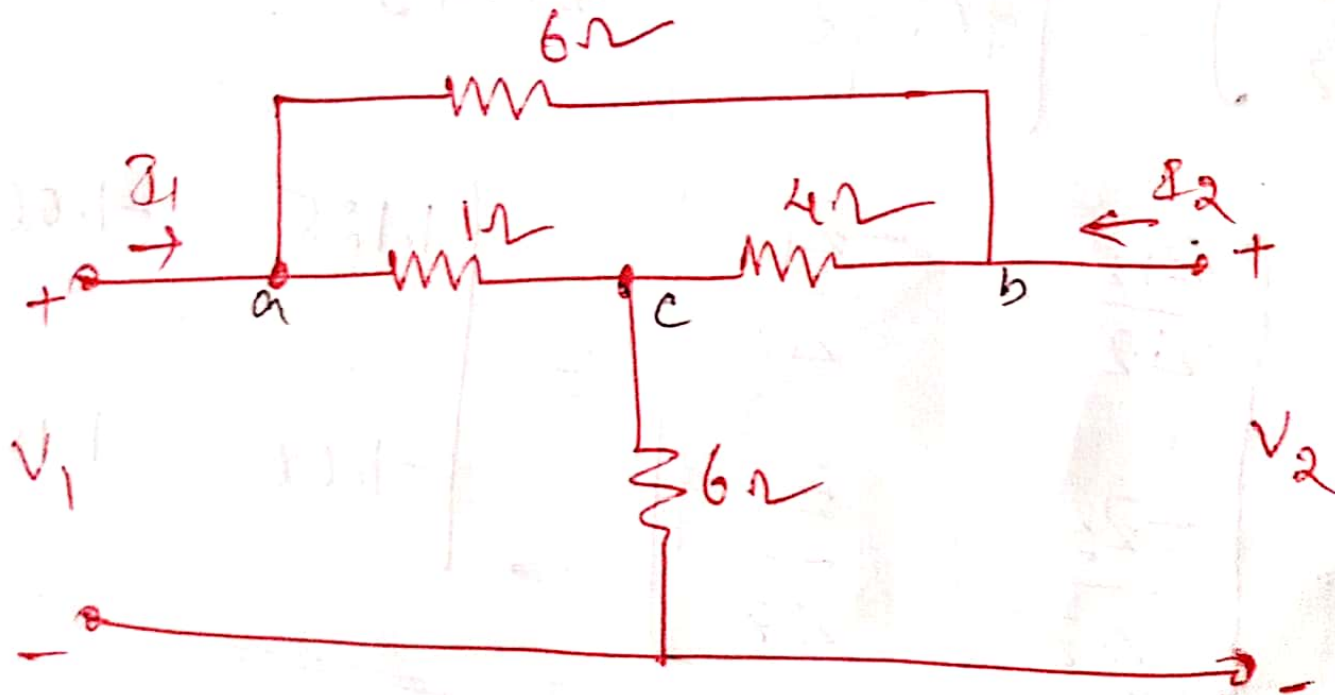


$$R_1 = 0.545 \Omega$$

$$R_2 = 2.18 \Omega$$

$$R_3 = 0.363 \Omega$$



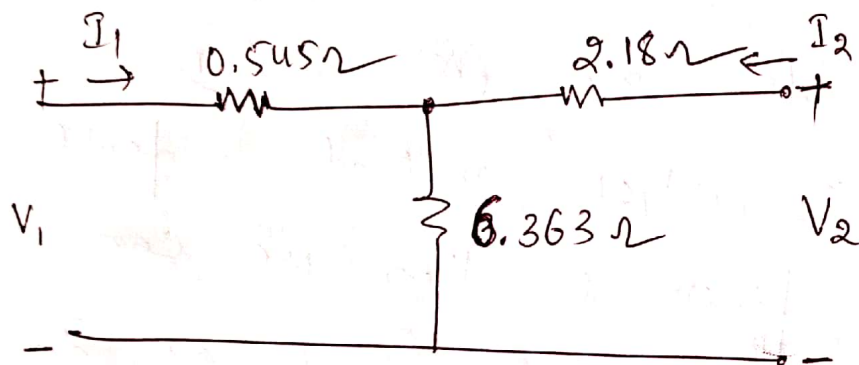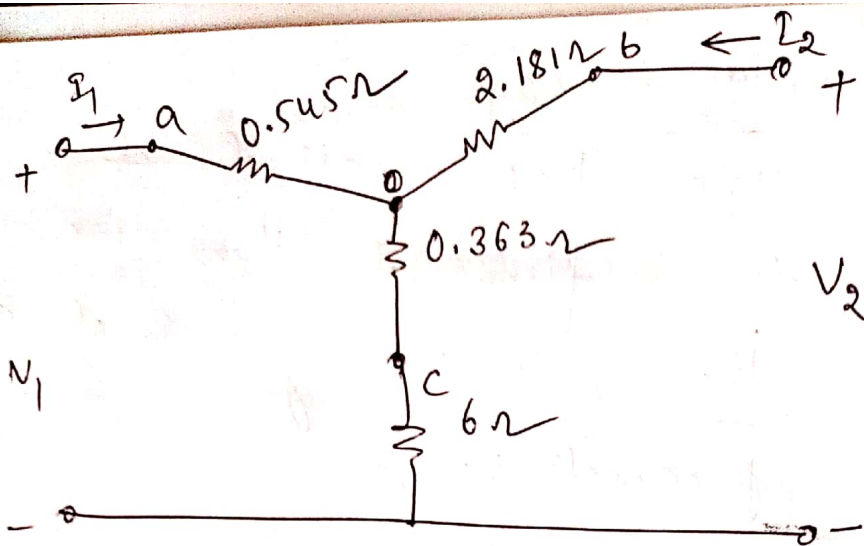

Since  $T = \omega / \omega_1$

$$Z_{11} = 6.908 \Omega \quad Z_{12} = Z_{21} = 6.363 \Omega$$

$$Z_{22} = 8.54 \Omega$$


$$\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} 6.908 & 6.363 \\ 6.363 & 8.54 \end{bmatrix} \Omega$$

$$Y = Z^{-1} = \begin{bmatrix} \frac{Z_{22}}{\Delta Z} & -\frac{Z_{12}}{\Delta Z} \\ -\frac{Z_{21}}{\Delta Z} & \frac{Z_{11}}{\Delta Z} \end{bmatrix} = \begin{bmatrix} 1.125 & -1.06 \\ -1.06 & 1.15 \end{bmatrix} \Omega^{-1}$$

$$\Delta Z = 5.97 \Omega$$

23) Determine the transmission parameters for the given circuit - 2019

n/w show below

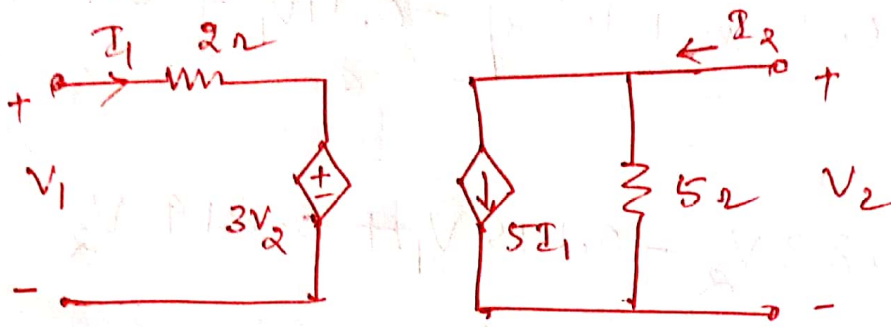

WKT Transmission parameters

$$V_1 = AV_2 - BI_2 \quad \text{--- (1)}$$

$$I_1 = CV_2 - DI_2 \quad \text{--- (2)}$$

\* By KVL (to the LHS side)

$$+V_1 - 2I_1 - 3V_2 = 0$$

$$\text{or } V_1 = 2I_1 + 3V_2 \quad \text{--- (3)}$$

By KCL (to the RHS side)

$$I_2 = \frac{V_2}{5} + 5I_1$$

$$5I_1 = I_2 - 0.2V_2$$

$$I_1 = -\frac{0.2}{5}V_2 + \frac{I_2}{5}$$

$$I_1 = -0.04V_2 + 0.2I_2 \quad \text{--- (4)}$$

Compare (4) & (2)

$$C = -0.04$$

$$D = -0.2$$

Substituting (4) in (3)

$$V_1 = 2[-0.04V_2 + 0.2I_2] + 3V_2$$

$$V_1 = -0.08V_2 + 0.4I_2 + 3V_2$$


$$V_1 = 2.92V_2 + 0.4I_2 \quad \text{--- (5)}$$

Compare (5) & (1)


$$A = 2.92 \quad B = -0.4$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 2.92 & -0.4 \\ -0.04 & -0.2 \end{bmatrix}$$



24) Determine Z-parameters

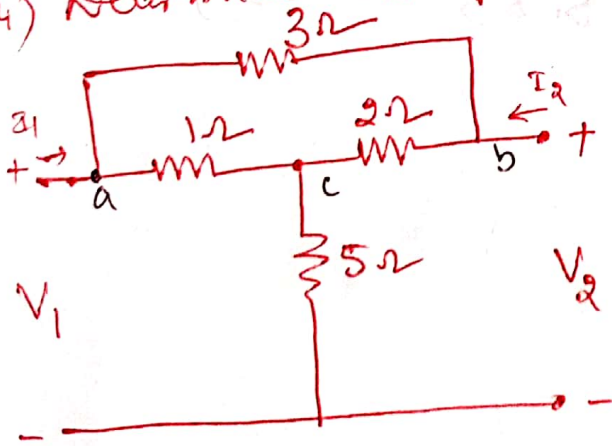

for the o/w. June/July -18

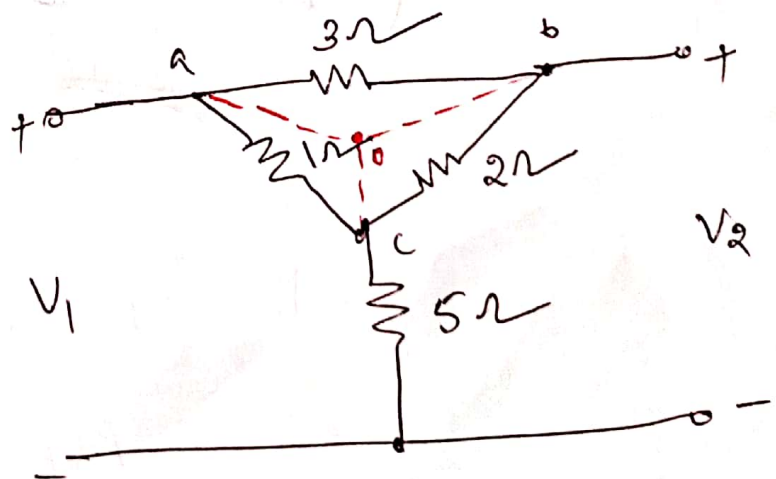



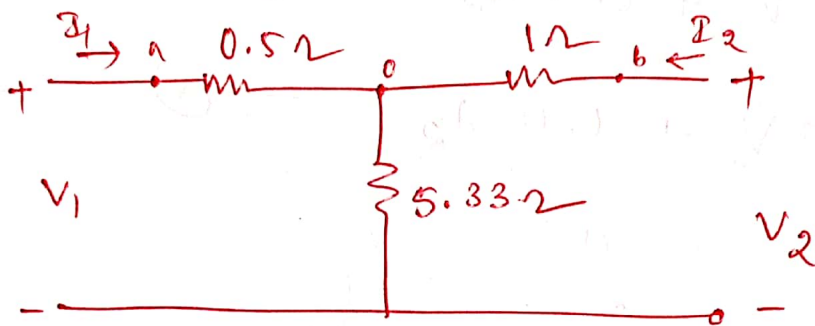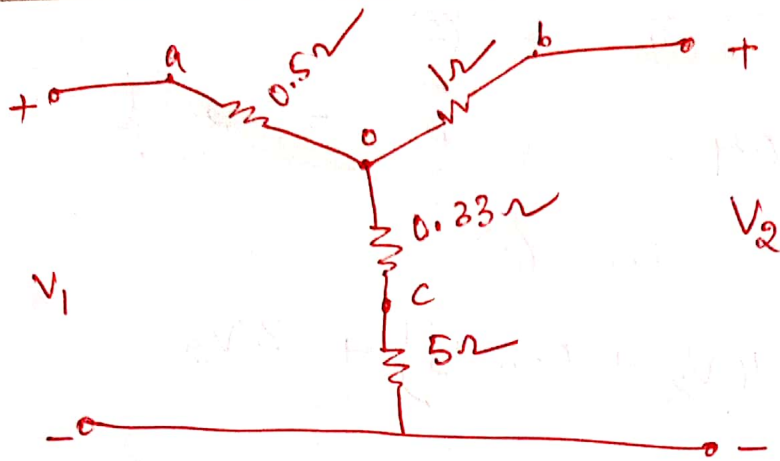

Since T-n/w,

$$Z_{11} = 5.83\Omega \quad Z_{22} = 6.33\Omega$$

$$Z_{12} = Z_{21} = 5.33\Omega$$

$$\therefore \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} 5.83 & 5.33 \\ 5.33 & 6.33 \end{bmatrix} \Omega$$



# CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

15EC34

## Third Semester B.E. Degree Examination, June/July 2018 Network Analysis

Time: 3 hrs.

Max. Marks: 80

**Note: Answer any FIVE full questions, choosing ONE full question from each module.**

### Module-1

- 1 a. Determine the equivalent resistance across XY shown in Fig.Q1(a) (05 Marks)

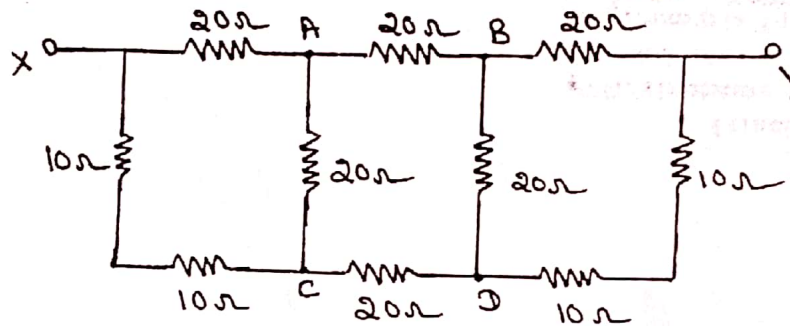


Fig.Q1(a)

- b. Calculate the voltage across the  $6\Omega$  resistor using source shifting and transformation technique shown in Fig.Q1(b). (05 Marks)

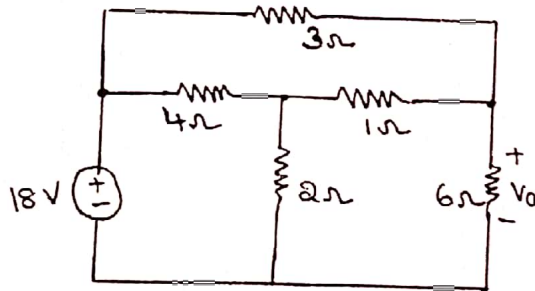


Fig.Q1(b)

- c. Determine the power supplied by the dependent source of Fig.Q1(c) shown. (06 Marks)

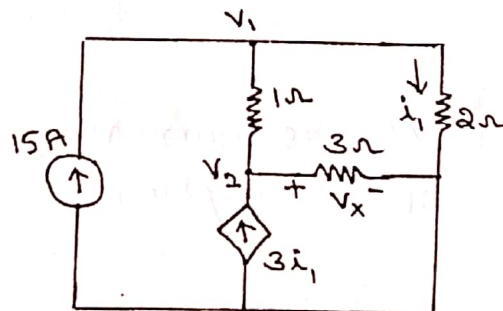


Fig.Q1(c)  
1 of 5

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.

OR

- 4 a. Using Millman's theorem, find  $I_L$  through  $R_L$  for the network shown in Fig.Q4(a). (06 Marks)

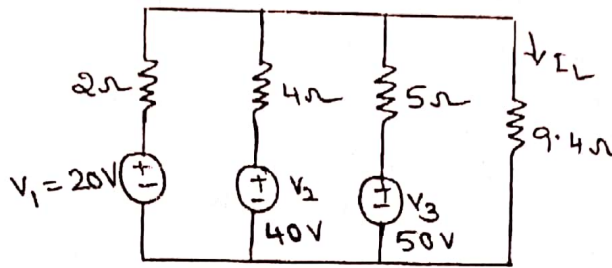


Fig.Q4(a)

- b. Verify reciprocity theorem for the circuit shown in Fig.Q4(b). (06 Marks)

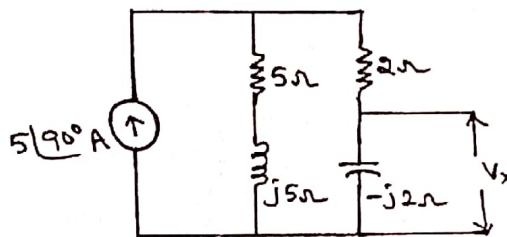


Fig.Q4(b)

- c. State and explain maximum power transfer theorem. (04 Marks)

**Module-3**

- 5 a. In the circuit shown in Fig.Q5(a), the switch K is changed from position 1 to position 2 at  $t = 0$ , the steady state has been reached before switching. Find the values of  $i$ ,  $\frac{di}{dt}$  and  $\frac{di^2}{dt^2}$  at  $t=0$ . (08 Marks)

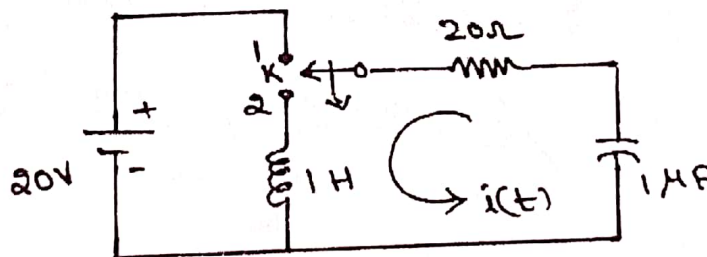


Fig.Q5(a)

- b. The switch in the network shown in Fig.Q5(b) is closed at  $t = 0$ . Determine the voltage across the capacitor. Use Laplace transform. (08 Marks)

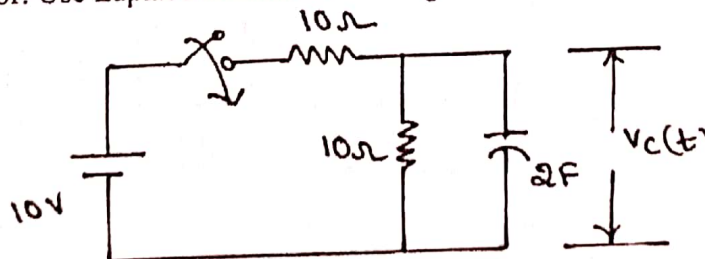


Fig.Q5(b)

OR

- 6 a. In the network shown in Fig.6(a), the switch K is opened at  $t = 0$ . At  $t = 0^+$ , solve for the values of  $v$ ,  $\frac{dv}{dt}$  and  $\frac{d^2v}{dt^2}$  if  $I = 2A$ ,  $R = 200\Omega$  and  $L = 1H$ . (08 Marks)

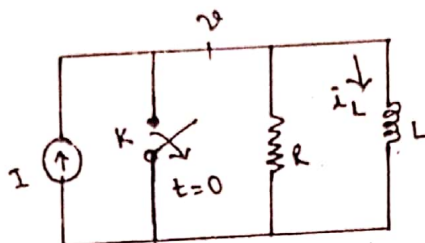


Fig.Q6(a)

- b. Determine the Laplace transform of the periodic saw tooth waveform of Fig.Q6(b). Use gate function. (08 Marks)

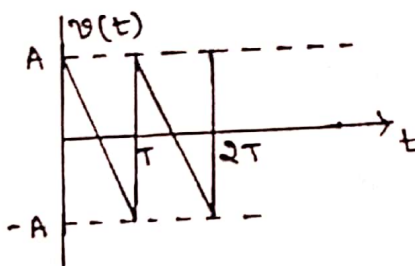


Fig.Q6(b)

**Module-4**

- 7 a. Derive for a resonant circuit, the resonant frequency  $f_0 = \sqrt{f_1 f_2}$ , where  $f_1$  and  $f_2$  are the two half power frequencies. (07 Marks)
- b. Find the value of L for which the circuit shown in Fig.Q7(b) is resonant at a frequency of  $\omega = 5000$  rad/sec. (06 Marks)

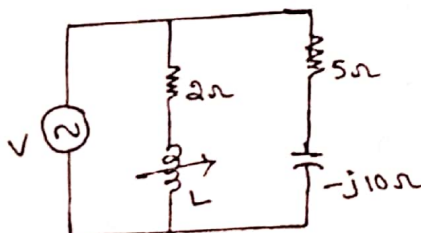


Fig.Q7(b)

- c. A series RLC circuit has  $R = 10\Omega$ ,  $L = 0.01H$  and  $c = 0.01\mu F$  and it is connected across 10mV supply. Calculate : i)  $f_0$  ii)  $Q_0$  iii) B.w. (03 Marks)

OR

- 8 a. A series RLC circuit has a resistance of  $10\Omega$ , an inductance of  $0.3H$  and a capacitance of  $100\mu F$ . The applied voltage is  $230V$ . Find : i) Resonant frequency ii) Quality factor iii) Lower and upper cut off frequencies iv) Bandwidth v) Current at resonance vi) currents at  $f_1$  and  $f_2$  vii) voltage across inductance at resonance. (08 Marks)
- b. Derive an expression for the resonant frequency of a parallel resonant circuit. Also show that the circuit is resonant at all frequencies if  $R_L = R_C = \sqrt{\frac{L}{C}}$  where  $R_L =$  Resistance in the inductor branch,  $R_C =$  resistance in the capacitor branch. (08 Marks)

**Module-5**

9 a. Find Y parameters and Z parameters for the circuit show in Fig.Q9(a).

(08 Marks)

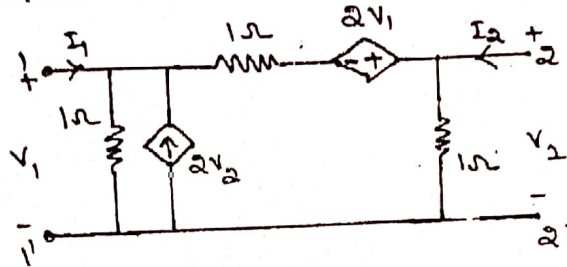


Fig.Q9(a)

b. Express ABCD parameters interms of Y-parameters and h-parameters.

(08 Marks)

**OR**

10 a. Determine z parameters for the network shown in Fig.Q10(a).

(08 Marks)

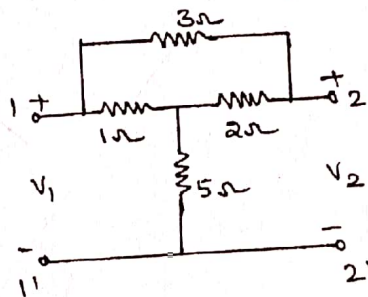


Fig.Q10(a)


b. Express h-parameters interms of Y-parameters.

(08 Marks)

\*\*\*\*\*



# CBCS SCHEME

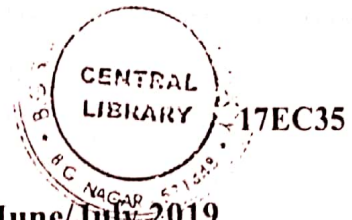

USN

--	--	--	--	--	--	--	--	--	--

## Third Semester B.E. Degree Examination, June/July 2019 Network Analysis

Time: 3 hrs.

Max. Marks: 100

*Note: Answer any FIVE full questions, choosing ONE full question from each module.*

### Module-1

- 1 a. Define the following terms with examples:
  - i) Active elements
  - ii) Passive elements
  - iii) Linear and non linear elements
  - iv) Lumped node
  - v) Unilateral and bilateral elements. (10 Marks)
- b. Use the node analysis and find the value of  $V_x$  in the circuit shown in below Fig.Q.1(b). Such that the current through the impedance  $(2 + j3)\Omega$  is zero.

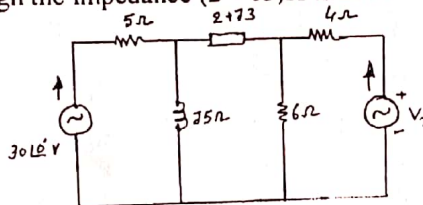


Fig.Q.1(b)

(10 Marks)

OR

- 2 a. Derive an expression for i)  $\Delta$  to Y transformation ii) Y to  $\Delta$  transformation. (10 Marks)
- b. Find the voltage across  $20\Omega$  resistor in the network shown in Fig.Q.2(b) below by using Mesh analysis method. (10 Marks)

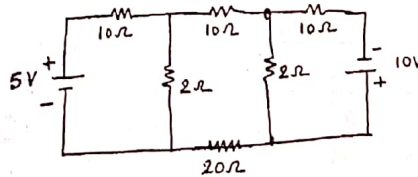


Fig.Q.2(b)

### Module-2

- 3 a. State and prove Millman's theorem with an example. (10 Marks)
- b. Find the Thevenin's equivalent circuit of Fig.Q.3(b) shown below: (10 Marks)

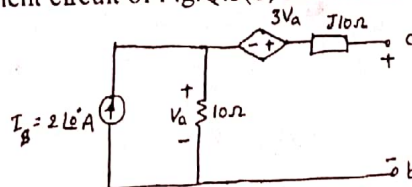


Fig.Q.3(b)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.

OR

4 a. Prove that the maximum power transferred from source to load when,

- i)  $R_L = R_o$     ii)  $R_L = |Z_o|$     iii)  $Z_L = \dot{Z}_o$  (10 Marks)

b. Find the value of  $i_b$  using Norton's equivalent circuit when  $R = 667\Omega$ , refer Fig.Q.4(b). (10 Marks)

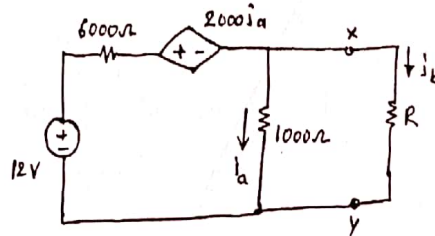


Fig.Q.4(b)

Module-3

5 a. Determine  $i$ ,  $\frac{di}{dt}$ ,  $\frac{d^2i}{dt^2}$  at  $t = 0^+$ , when the switch is closed at  $t = 0$ , from the Fig.Q.5(a) shown below. (10 Marks)

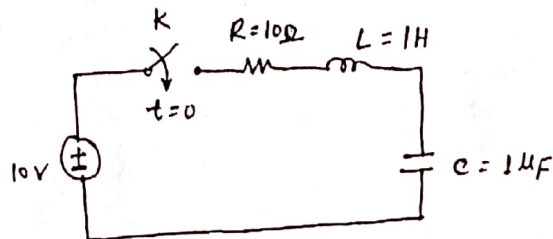


Fig.Q.5(a)

b. Find :

- i)  $i(0^+)$  and  $v(0^+)$   
 ii)  $\frac{di(0^+)}{dt}$  and  $\frac{dv(0^+)}{dt}$   
 iii)  $I(\infty)$  and  $v(\infty)$

from the circuit shown in Fig.Q.5(b) below. (10 Marks)

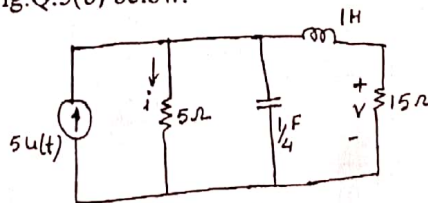



Fig.Q.5(b)

OR

6 a. Deduce the Laplace transform of the following:

- i)  $\sin^2 t$     ii)  $\cos^2 t$     iii)  $\sin \omega t$     iv)  $\int_0^t i(t) dt$  (10 Marks)

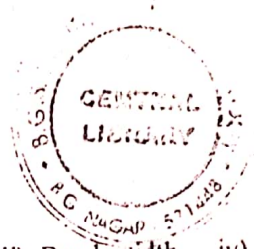b. State and prove Initial and Final value theorems. (10 Marks)



**Module-4**

- 7 a. Demonstrate the terms: i) Resonance ii) Q-factor iii) Band width iv) Selectivity v) Half power frequency pertaining to a R-L-C series circuit. (10 Marks)  
 b. Prove that the Resonating frequency in a R-L-C series circuit is geometrical mean of half power frequencies i.e.  $f_0 = \sqrt{f_1 f_2}$ . (10 Marks)

OR

- 8 a. Evaluate  $\omega_0$ , Q, BW and half power frequencies and the output voltage V at  $\omega_0$ . refer Fig.Q.8(a). (10 Marks)

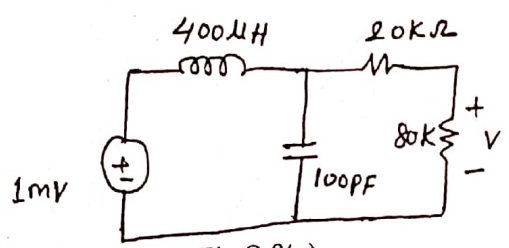


Fig.Q.8(a)

- b. Derive an expression for resonance by varying  $R_L$  in parallel RLC circuit. (10 Marks)

**Module-5**

- 9 a. Express Z parameters in terms h parameters and what are hybrid parameters. (10 Marks)  
 b. Determine the transmission parameters for the network shown Fig.Q.9(b) below. (10 Marks)

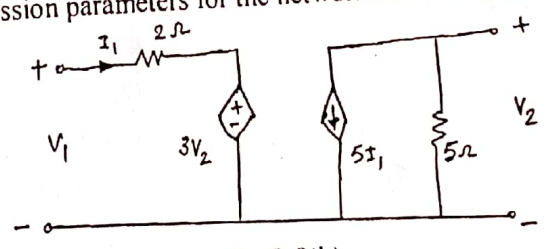


Fig.Q.9(b)

OR

- 10 a. Obtain the condition of transmission parameters for two networks connected in cascade. (10 Marks)  
 b. Determine the Z-parameters for the circuit shown in Fig.Q.10(b) below. (10 Marks)

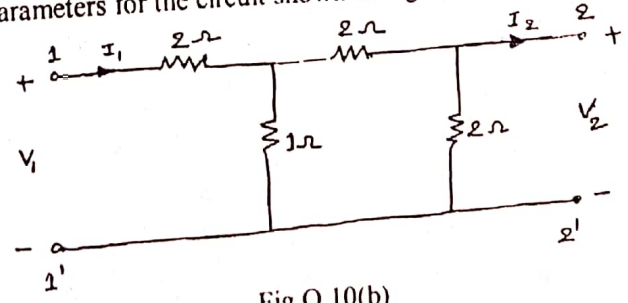


Fig.Q.10(b)

\*\*\*\*\*



USN 

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

## Third Semester B.E. Degree Examination, Dec.2019/Jan.2020 Network Analysis

Time: 3 hrs.

Max. Marks: 100

*Note: Answer any FIVE full questions, choosing ONE full question from each module.*

### Module-1

- 1 a. Derive the expression for: (i)  $\Delta$  to Y transformation (ii) Y to  $\Delta$  transformation (10 Marks)
- b. Calculate the voltage across the  $6\Omega$  resistor in the network of Fig.Q1(b) using source shifting technique.

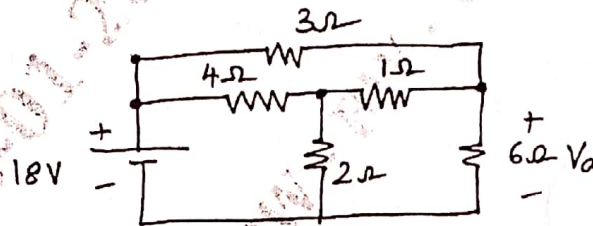


Fig.Q1(b)

(10 Marks)

OR

- 2 a. Determine the resistance between the terminals A and B of the network shown in Fig.Q2(a).

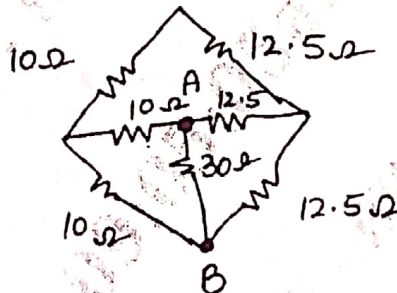


Fig.Q2(a)

(10 Marks)

- b. Find currents in all the branches of the network shown in Fig.Q2(b) using mesh analysis.

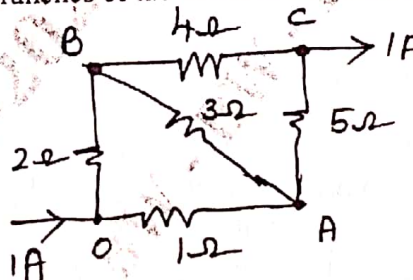


Fig.Q2(b)

(05 Marks)

- c. Find voltages  $V_1$  and  $V_2$  in the network shown in Fig.Q2(c) using node analysis method.

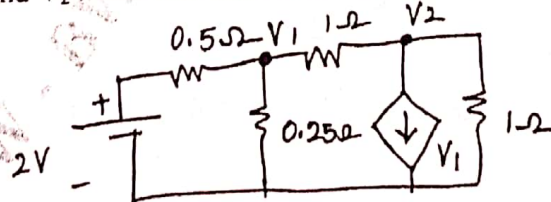


Fig.Q2(c)

(05 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
 2. Any revealing of identification, appeal to evaluator and/or equations written e.g. 12.8 50, will be treated as malpractice.



**Module-2**

- 3 a. Obtain Thevenin's equivalent network for Fig.Q3(a).

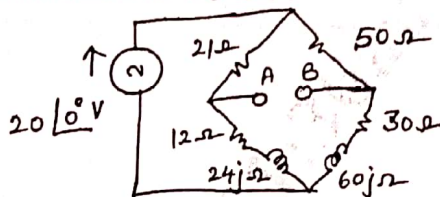


Fig.Q3(a)

(08 Marks)

- b. State and prove Millman's theorem.

(06 Marks)

- c. For the circuit shown in Fig.Q3(c), find the voltage  $V_x$  and verify reciprocity theorem.

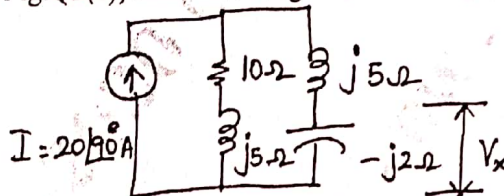


Fig.Q3(c)

(06 Marks)

**OR**

- 4 a. State and prove maximum power transfer theorem for AC circuits (when  $R_L$  and  $X_L$  are varying)

(10 Marks)

- b. Find 'V' in the circuit shown in Fig.Q4(b) using super position theorem.

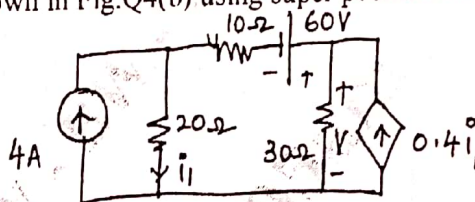


Fig.Q4(b)

(10 Marks)

**Module-3**

- 5 a. What is the significance of initial conditions? Write a note on initial and final conditions for basic circuit elements.

(05 Marks)

- b. In the network shown in Fig.Q5(b) switch 'S' is changed from A to B at  $t = 0$  having already established a steady state in position A shown that at  $t = 0^+$ ,  $i_1 = i_2 = \frac{-V}{R_1 + R_2 + R_3}$  and

$i_3 = 0.$

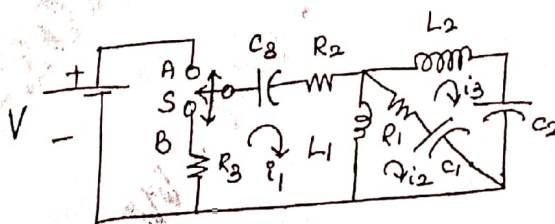


Fig.Q5(b)

(10 Marks)

- c. In the network of Fig.Q5(c) switch 'S' is closed at  $t = 0$  with zero initial current in the inductor. Find  $i$ ,  $\frac{di}{dt}$  and  $\frac{d^2i}{dt^2}$  at  $t = 0^+$  if  $R = 10 \Omega$ ,  $L = 1 \text{ H}$  and  $V = 10 \text{ Volts}$ .


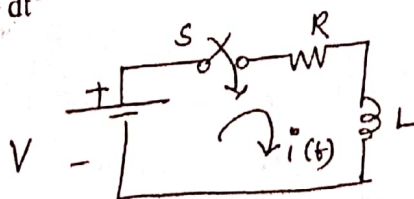


Fig.Q5(c)

2 of 4

(05 Marks)

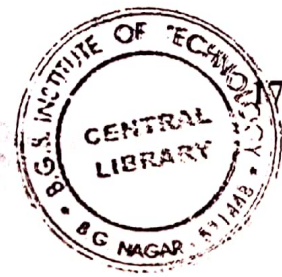

OR

- 6 a. Obtain Laplace transform of:  
 (i) Step function  
 (ii) Ramp function  
 (iii) Impulse function

(10 Marks)

- b. Find the Laplace transform of the waveform shown in Fig.Q6(b).

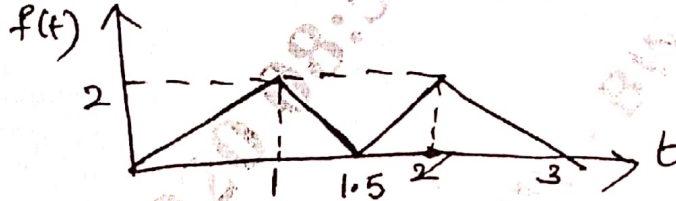


Fig.Q6(b)

(10 Marks)

**Module-4**

- 7 a. Derive the relation between bandwidth and quality factor  $B.W = f_0/Q$ . (10 Marks)  
 b. Show that the value of capacitance for max voltage across the capacitor in case of capacitor tuning series resonance is given by  $C = \frac{L}{R^2 + X_L^2}$ .

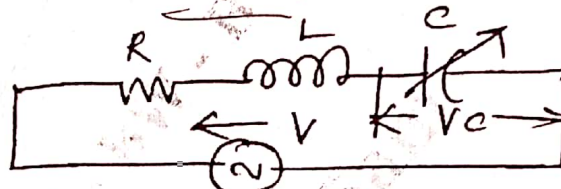


Fig.Q7(b)

(10 Marks)

OR

- 8 a. Derive for  $f_0$  for parallel resonance circuit when the resistance of the capacitance is considered.

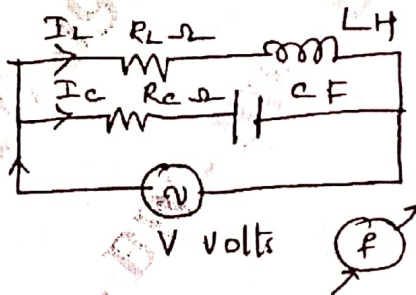


Fig.Q8(a)

(10 Marks)

- b. Find the value of L for which the circuit in Fig.Q8(b) resonates at  $\omega = 5000$  rad/sec.

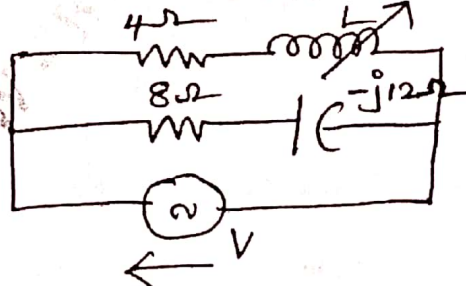


Fig.Q8(b)

(10 Marks)

**Module-5**

- 9 a. Derive the expression of Z parameters in terms of Y parameters.  
 b. Determine Y and Z parameters for the network shown in Fig.Q9(b).

(10 Marks)

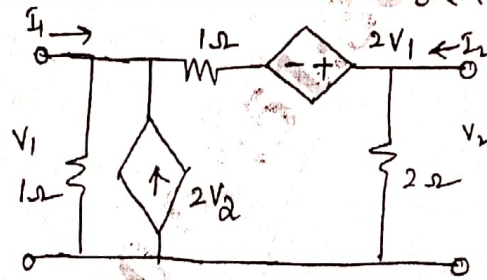


Fig.Q9(b)

(10 Marks)

**OR**

- 10 a. Derive the expression of h parameters in terms of ABCD parameters.  
 b. Find ABCD constants and show that  $AD - BC = 1$  for the network shown in Fig.Q10(b).

(10 Marks)

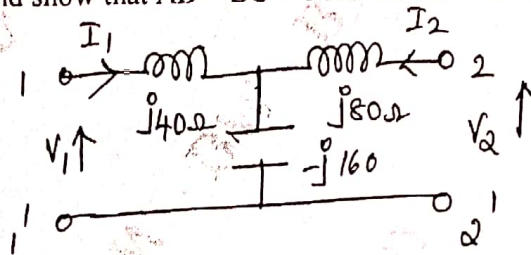


Fig.Q10(b)

(10 Marks)

\*\*\*\*\*



Third Semester BE Degree Examination November 2020  
(CBCS Scheme)

Time: 3 Hours

Max Marks: 100 marks


## Sub: Network Analysis

Q P Code: 62305

- Instructions: 1. Answer five full questions.  
2. Choose one full question from each module.  
3. Your answer should be specific to the questions asked.  
4. write the same question numbers as they appear in this question paper.  
5. Write Legibly

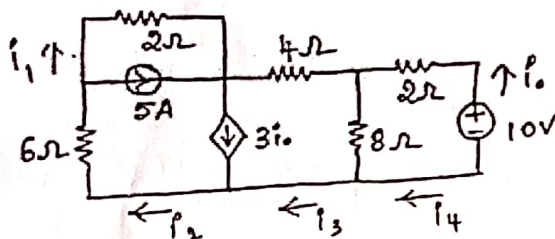
## Module - 1

- 1 a Find the currents  $i_1$ ,  $i_2$ ,  $i_3$  and  $i_4$  using mesh analysis for the circuit shown in figure Q1(a). 07 marks




Fig, Q1(a)

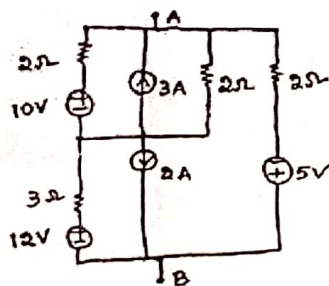- b Reduce the network shown in figure Q1(b) to a single voltage source in series with a resistance between terminals A and B. 07 marks



Fig, Q1(b)

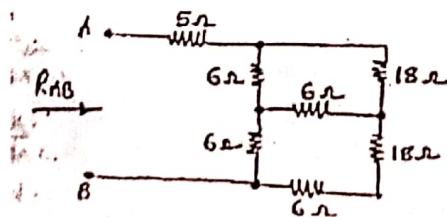- c Determine  $R_{AB}$  in the network shown in figure Q1(c). 06 marks




Fig, Q1(c)

PTO



Or

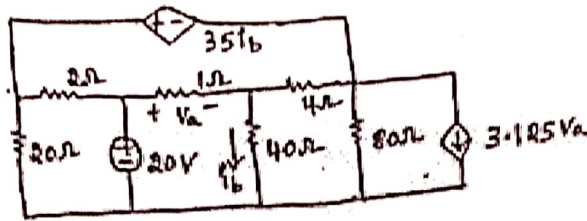- 2 a Determine the power supplied by the 20V voltage source to the circuit shown in figure Q2(a) using nodal analysis. 10 marks



Fig, Q2(a)

- b Distinguish between the following with suitable examples 10 marks
- i) Linear and non-linear elements.
  - ii) Dependent and independent sources.
  - iii) Supernode and supermesh.
  - iv) Ideal and practical current sources.
  - v) Unilateral and bilateral elements.

Module - 2

- 3 a State and prove Thevenin's theorem. 10 marks
- b Using superposition theorem, obtain the response I for the network shown in figure Q3(b). 10 marks

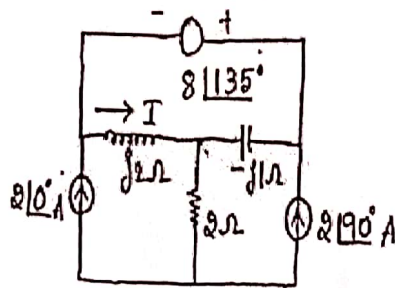


Fig. Q3(b)

Or

- 4 a State and prove maximum power transfer theorem for an AC circuit with an impedance as the load with variable  $R_L$  and fixed load reactance. 10 marks
- b For the circuit shown in figure Q4(b), find Thevenin's equivalent circuit across the terminals ab. 10 marks

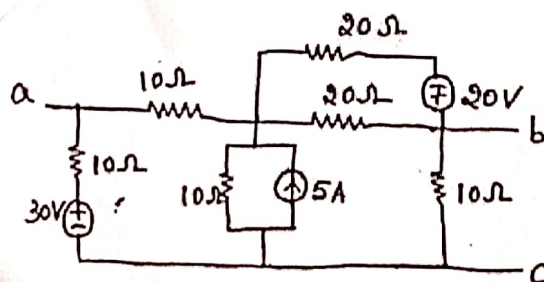


Fig. Q4(b)

Module - 3

- a The network shown in figure Q5(a), has two independent node pairs. Switch K is opened at  $t=0$ , find the following quantities at  $t=0^+$ . 10 marks  
 i)  $V_1$  ii)  $V_2$  iii)  $dV_1/dt$  iv)  $dV_2/dt$  v)  $di_L/dt$

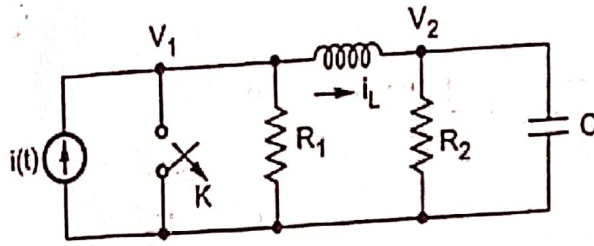


Fig. Q5(a)

- b In the network shown in figure Q5(b), K is changed from position 1 to 2 at  $t=0$ . Solve for  $i$ ,  $di/dt$  and  $d^2i/dt^2$  at  $t=0^+$ . 10 marks

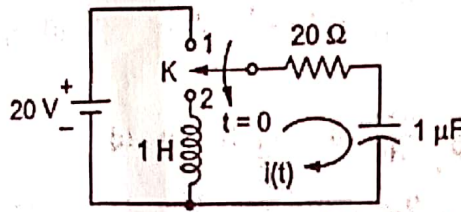


Fig. Q5(b)

Or

- 6 a Obtain the Laplace transform of saw tooth waveform shown in figure Q6(a). 06 marks

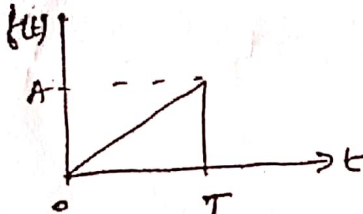


Fig. Q6(a)

- b Find the Laplace transform of i)  $\delta(t)$  ii)  $t$  iii)  $e^{-at}$  06 marks  
 c Find initial and final value theorem for the function given below. 08 marks  
 $F(s) = (s^3 + 7s^2 + 5) / (s^3 + 3s^2 + 4s + 2)$

Module - 4

- 7 a Two coils one of  $R_1=0.51\Omega$ ,  $L_1=32\text{mH}$ , the other of  $R_2=1.3\Omega$  and  $L_2=15\text{mH}$  and two capacitors of  $25\mu\text{F}$  and  $62\mu\text{F}$  are all in series with a resistance of  $0.24\Omega$ . Determine the following of this circuit. 10 marks  
 i) Resonance frequency ii) Q of each coil iii) Q of the circuit  
 iv) Cut-off frequencies v) Power dissipated of resonance if  $E=10\text{V}$ .
- b In a two RL-RC parallel resonant circuit  $L=0.4\text{H}$  and  $C=40\mu\text{F}$ , obtain resonant frequency 10 marks for the following values of  $R_L$  and  $R_C$ .  
 i)  $R_L=120\Omega$ ,  $R_C=80\Omega$  ii)  $R_L=R_C=80\Omega$  iii)  $R_L=80\Omega$ ,  $R_C=0\Omega$   
 iv)  $R_L=R_C=100\Omega$  v)  $R_L=R_C=120\Omega$

PTO



Or

- a A RLC series circuit consists of  $50\ \Omega$  resistance,  $0.2\text{H}$  inductance and  $10\ \mu\text{F}$  capacitance with an applied voltage of  $20\text{V}$ . Determine i) Resonant frequency ii) Q factor iii) Lower and upper frequency limits iv) Bandwidth. 10 marks
- b Define the following terms with reference to resonant circuit 04 marks  
i) Resonance ii) Q-factor iii) Half-power frequency iv) Selectivity
- c Derive the expression for resonant frequency of a parallel resonant circuit with lossless capacitor in parallel with a coil of resistance  $R$  and inductance  $L$ . 06 marks

Module - 5

- a Define Y parameters. Determine the Y parameters for the network shown in figure Q9(a). 08 marks

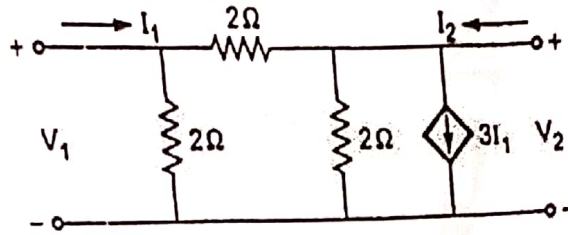


Fig. Q9(a)

- b The Z parameters of a two port network are  $Z_{11}=20\ \Omega$ ,  $Z_{12}=10\ \Omega$ ,  $Z_{21}=10\ \Omega$  and  $Z_{22}=10\ \Omega$ . Find its Y and ABCD parameters. 06 marks
- c Define h-parameters. Represent h-parameters in terms of ABCD parameters. 06 marks

Or

- 10 a Define transmission parameters and Z parameters. Express transmission parameters in terms of impedance parameters. 10 marks
- b Find the h parameters of the network shown in figure Q10(b). Also draw its equivalent circuit. 10 marks

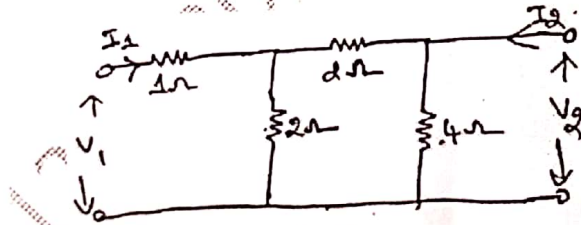


Fig. Q10(b)

\*\*\*\*\*

# ADICHUNCHANAGIRI UNIVERSITY

18EC35

Third Semester BE Degree Examination January 2020  
(CBCS Scheme)

Time: 3 Hours


Max Marks: 100 Marks

## Sub: Network Analysis

- Instructions:**
1. Answer five full questions
  2. Choose one full question from each module
  3. Your answer should be specific to the questions asked
  4. Write the same question numbers as they appear in this question paper
  5. Write Legibly.

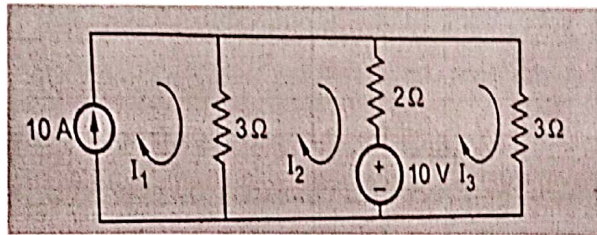
### Module -1

- 1 a. Derive expressions for i) Star to Delta conversion (10 marks)  
ii) Delta to Star conversion
- b. Write the mesh equation for the circuit shown below and determine mesh currents using mesh analysis. (10 marks)



OR

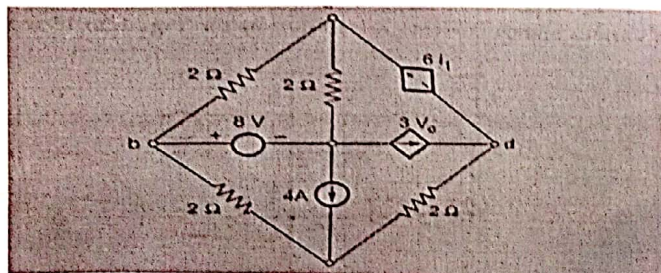- 2 a. Explain the classification of Networks. (10 marks)
- b. For the network shown below, find the node voltages  $V_d$  and  $V_e$ . (10 marks)




### Module -2

- 3 a. State and prove Maximum power transfer theorem for AC circuits. (10 marks)



b. Find the Thevenin's equivalent of the network shown below.

(10 marks)

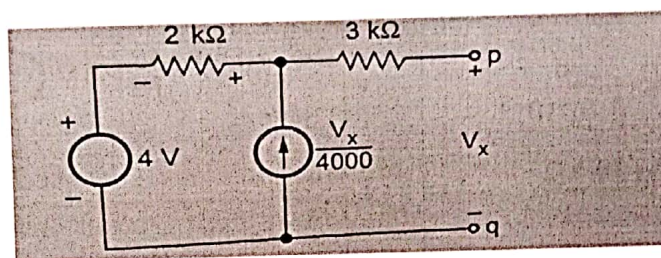


OR

4 a. State and prove Millman's Theorem.

(10 marks)

b. Find the voltage  $V_x$  and verify the reciprocity theorem for the network shown below.

(10 marks)

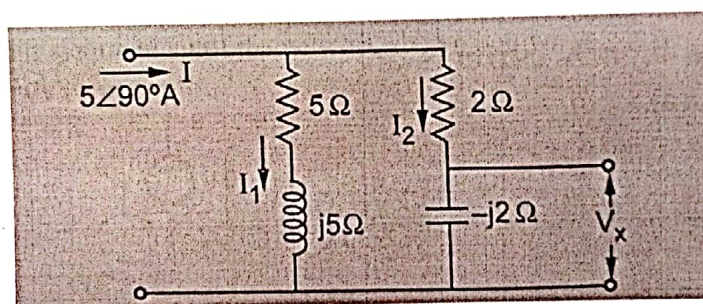


Module -3

5 a. Write a note on initial conditions in basic circuit elements.

(10 marks)

b. In the network shown below, a steady state is reached with the switch K open. At  $t=0$ , the switch is closed. For the element values given, determine the values of  $V_a(0^-)$  and  $V_a(0^+)$ .

(10 marks)

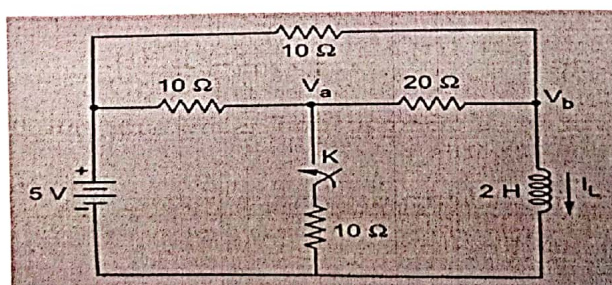

OR

6 a. State and prove i) Initial value theorem and ii) Final value theorem.

(10 marks)

b. Find the Laplace transform of the following: i)  $\sin^2 t$  and ii)  $\cos^2 t$  (10 marks)

Module -4


7 a. Show that resonant frequency of series resonance circuit is equal to the geometric mean of two half power frequencies. (10 marks)

b. A series RLC circuit has  $R = 4 \Omega$ ,  $L = 1 \text{ mH}$  and  $C = 10 \mu\text{F}$ , calculate Q-factor, bandwidth, resonant frequency and the half power frequencies  $f_1$  and  $f_2$ . (10 marks)

OR

8 a. Derive the expression for resonant frequency for parallel circuit containing resistance in both the branches. (10 marks)

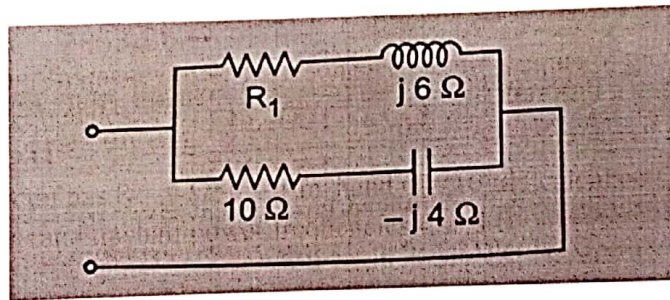
b. Find the value of  $R_1$  such that the circuit given below is resonant. (10 marks)



Module -5

9 a. Define Y parameters and derive Y parameters in terms of h parameters. (10 marks)

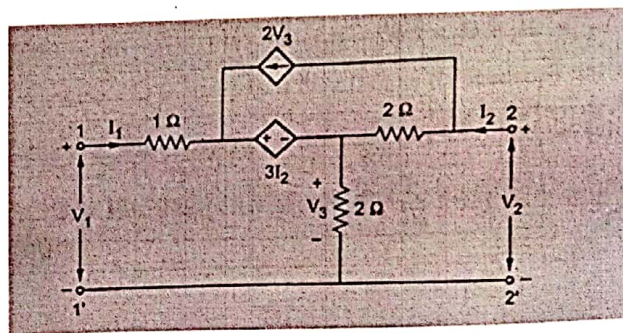b. Find Z parameters for the circuit shown below. (10 marks)



OR

10 a. Define Z parameters and derive Z parameters in terms of y parameters. (10 marks)



b. Determine Y parameters for the circuit shown below.

(10 marks)

